

# How to Deliver Oodles and Oodles of Current to HEP Detectors in High Radiation and Magnetic Fields?

Satish K Dhawan  
Yale University



1 Oodle = 10,000 amps

## Collaborators:

Yale University: Keith Baker

Brookhaven National Laboratory: Hucheng Chen, James Kierstead, Francesco Lanni, David Lynn, Sergio Rescia,

2010 Linear Collider Workshop (LCWS10) and International Linear Collider meeting (ILC2010)  
Session: LCWS: Tracking/Vertex: Silicon tracking R&D

March 27, 2010

## CMS ECAL: 5 Oodles (50 Kamps) .

Power Supply output = 315 KW  
Power loss in Leads to SM = 100 KW  
Power loss in Regulator Card = 90 KW  
Power Delivered @ 2.5 V = 125 KW

# of Power Supplies ~ 700

# of ST LDO Chips = 35 K LHC Radiation Hard made by ST Microelectronics

# of LVR Cards = 3.1 K.

**Yale: Designed, built, burn-in and Tested.**

Power Supply  
6.3 V

64 Amps

30 m

Vdrop = 2V  
Pd = 128 W

50 mm<sup>2</sup> (AWG 00)

2x16 mm<sup>2</sup> (AWG 6)

1 to 3 m

SM: Super Module

4.3 V

Junction Box

2.5V  
64 amps  
160 W

4 LVR Boards




**Power Delivery Efficiency = 40%  
NOT INCLUDED**

1. Power Supply efficiency
2. Water cooling
3. Removal of Waste heat
4. Air Conditioning

# What can we do?

- Is there a better way to distribute power ?
- High Radiation
- Magnetic Field 4 T
- Load ~1 V Oodles of current
- Feed High Voltage and Convert - *like AC power transmission*
- Commercial Technologies — *No Custom ASIC Chips*
- Learn from Semiconductor Industry
- Use Company Evaluation Boards for
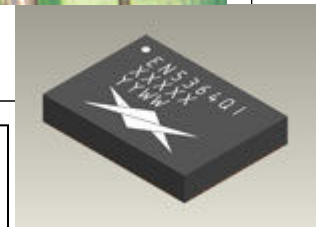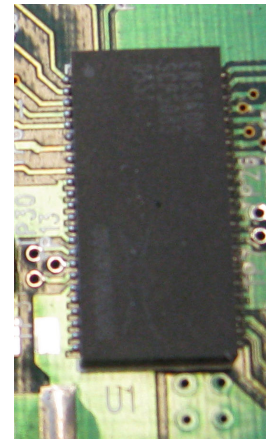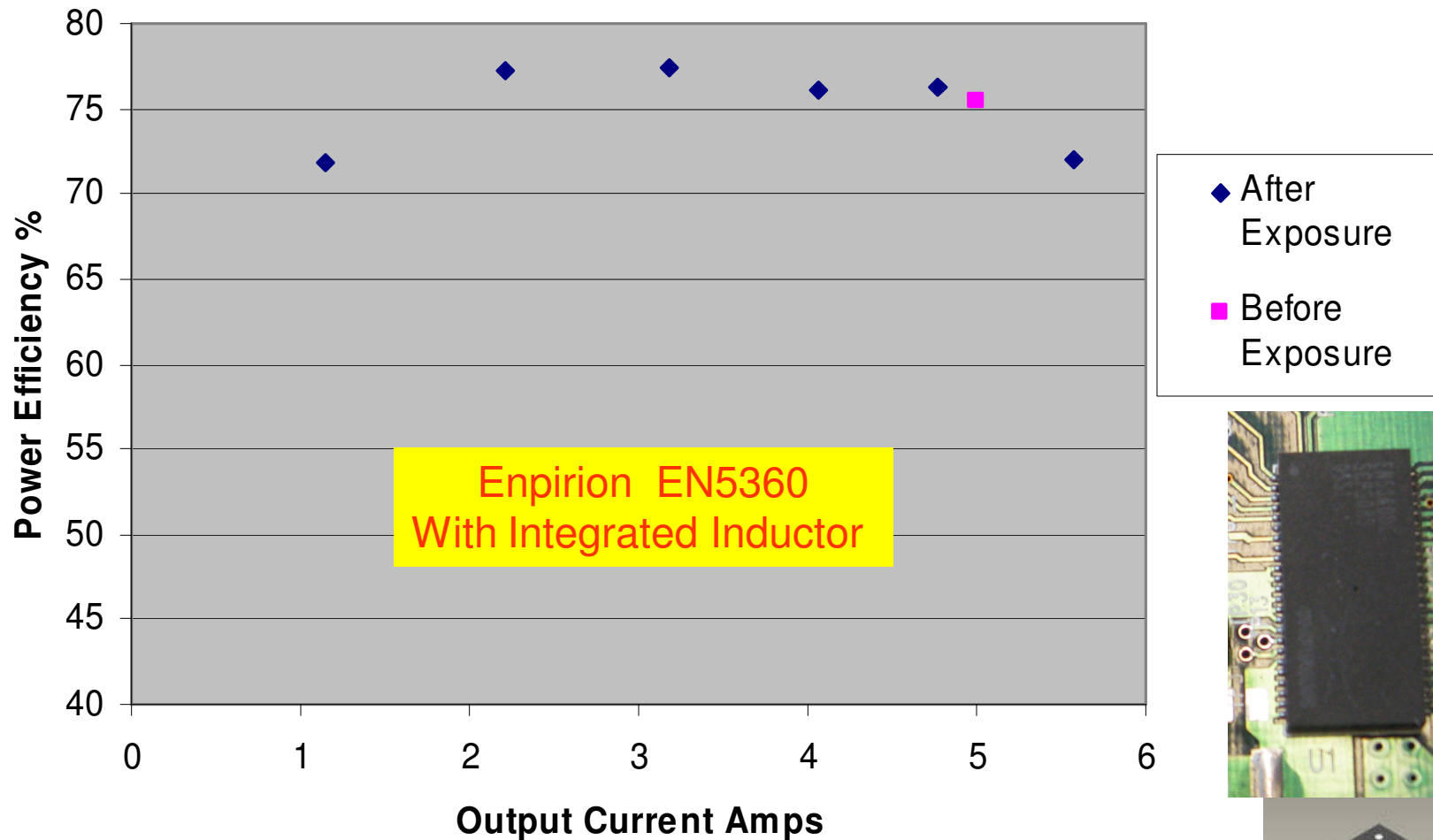
## Buck Regulator Efficiency after 100 Mrad dosage



Found out at Power Technology conference 0.25  $\mu$ m Lithography


- Irradiated Stopped on St. Valentines Day 2007
- We reported @ TWEPP 2008 - IHP was foundry for EN5360

## Length of Power Cables = 140 Meters


### LHC Solution



### sLHC Solution

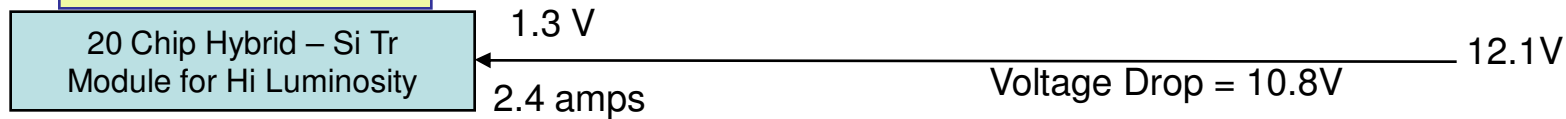


### 2 Step Solution

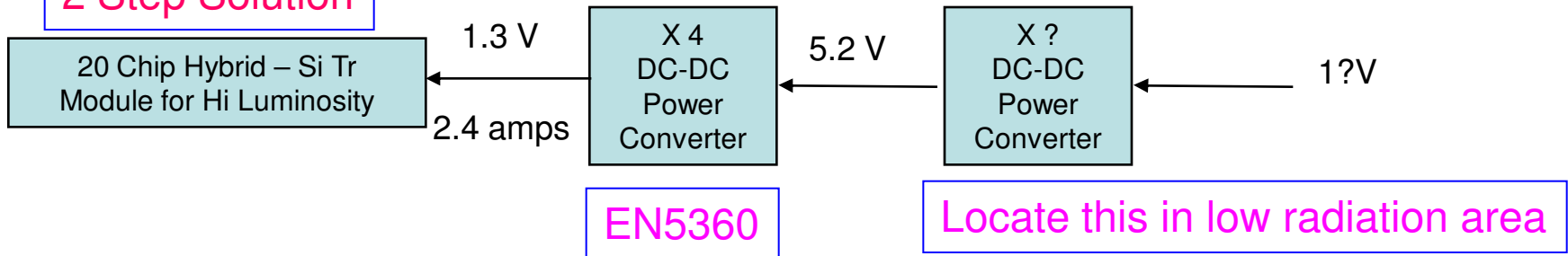

Overall Efficiency is product of 2 efficiencies

### 1 Step Solution Desired

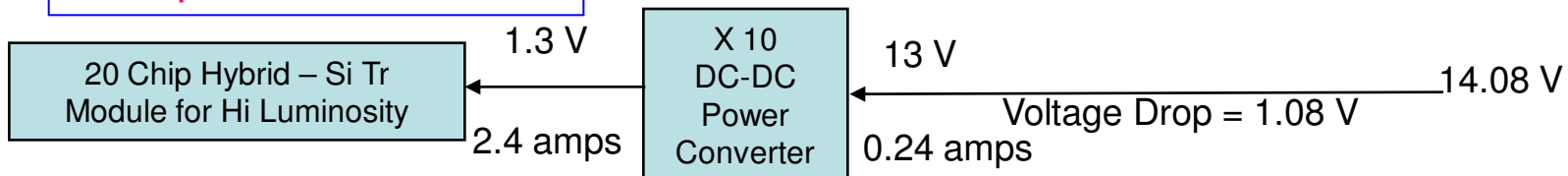

# Type of High to Low Voltage Converters without transformers


## ❖ Charge pumps

- Normally limited to integral fractions of input voltage
- Losses proportional to switch losses
- Can provide negative voltage

## ❖ Buck Converter – Used in consumer & Industrial Electronics


- Needs an ASIC, Inductor and Capacitors
- Cannot provide a negative voltage
- Topology allows for more flexibility in output voltage than charge pump
- Much more common use in commercial applications

# Synchronous Buck Converter

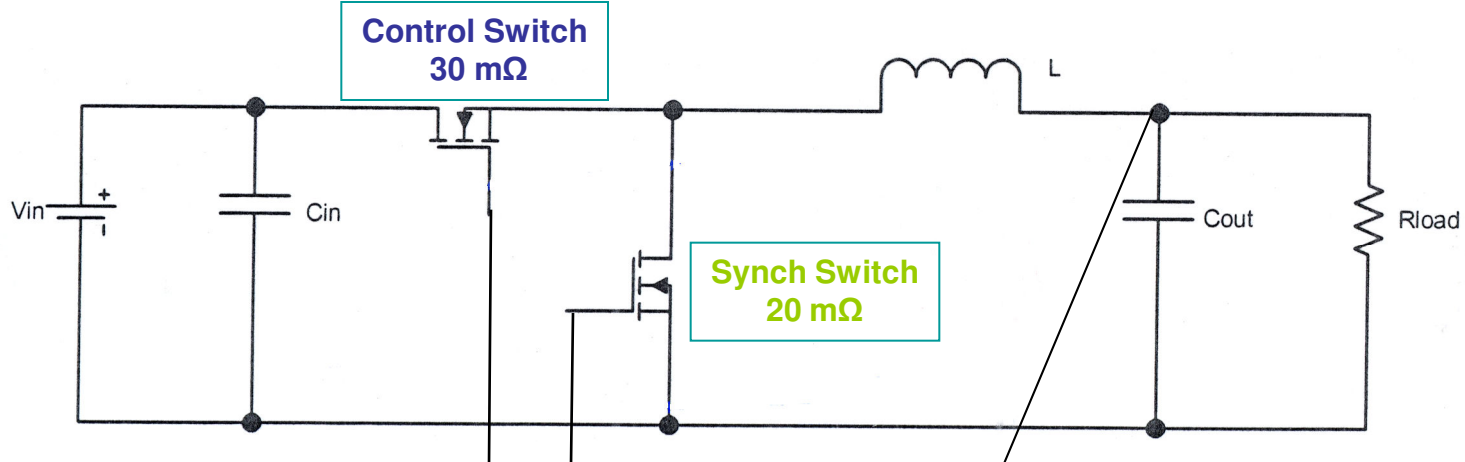


Power Stage  
- High Volts

Controller  
Low Voltage

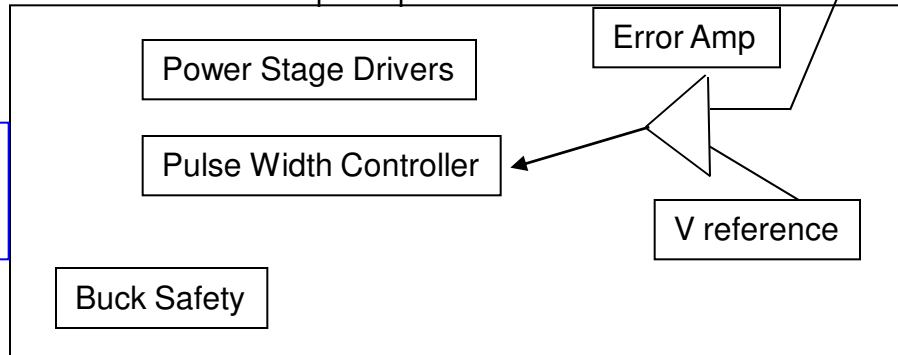

Minimum Switch ON Time  
Limits Max Frequency  
10 nsec @ 10 MHz

Vout = 11%

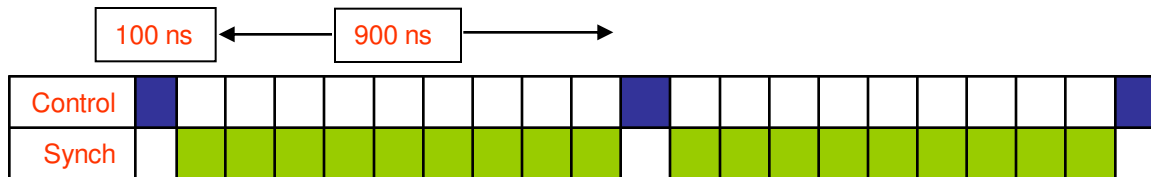

Control Switch: Switching Loss >  $I^2$   
Synch Switch:  $R_{ds}$  Loss Significant



Vout = 50%




# Proximity Effect

2 oz copper for coils


2 coils in series for larger L

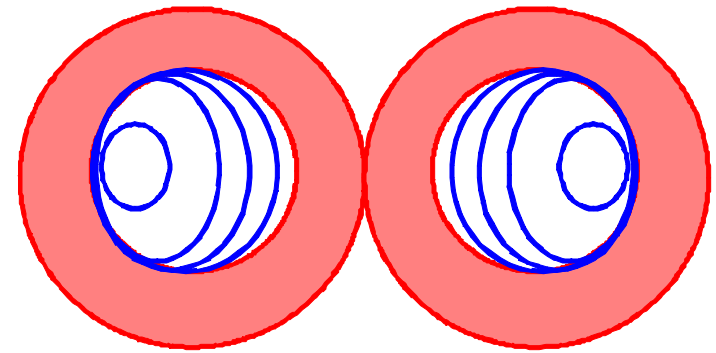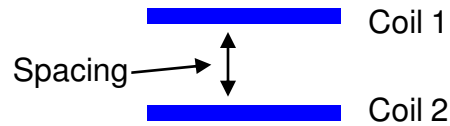

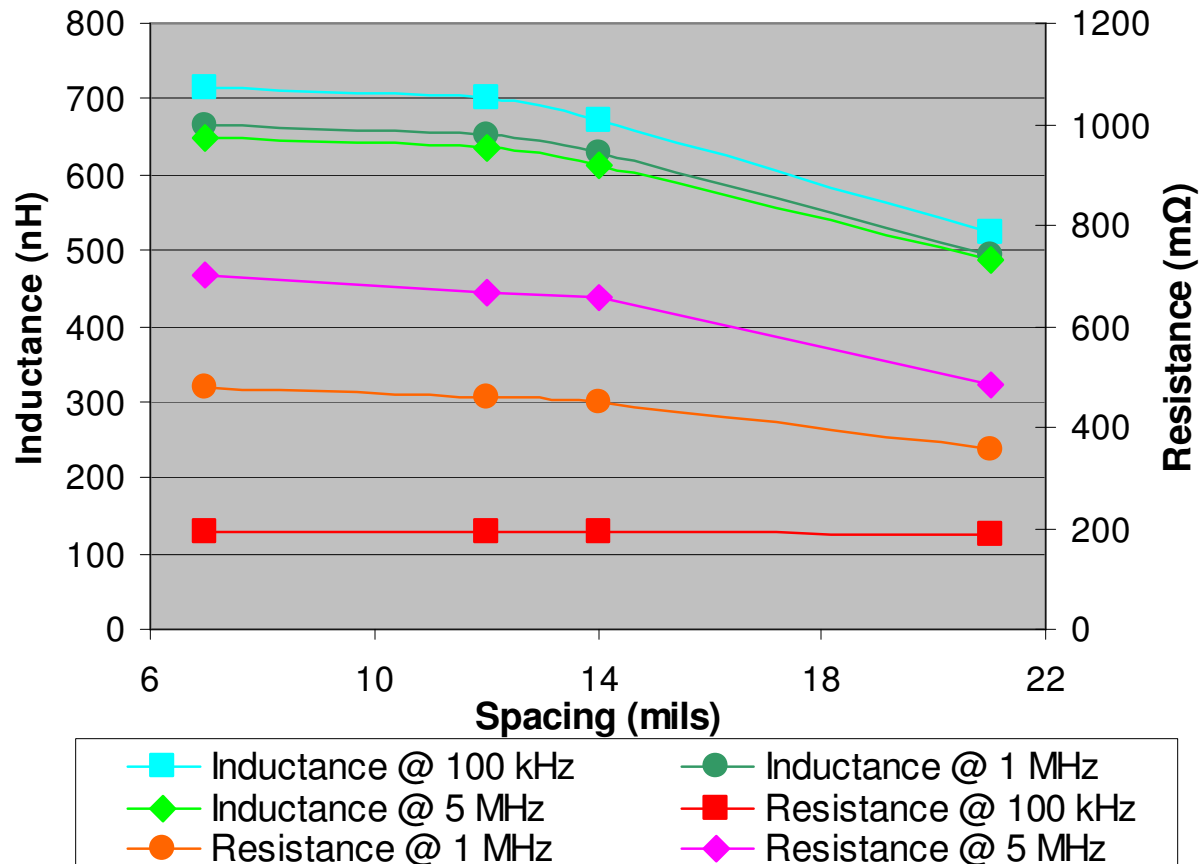
## Inductance and Resistance vs Coil Spacing


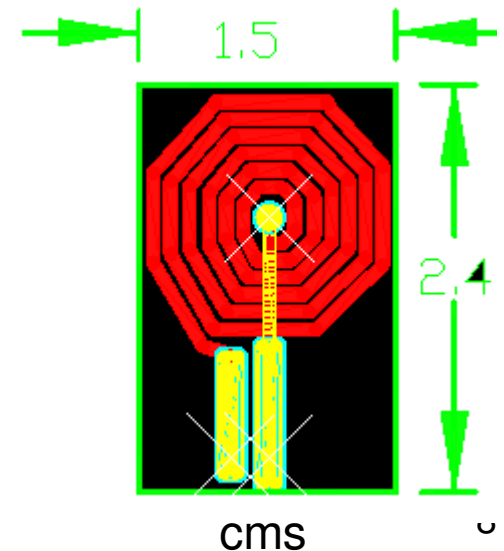
## Current Distribution in Neighboring Conductors




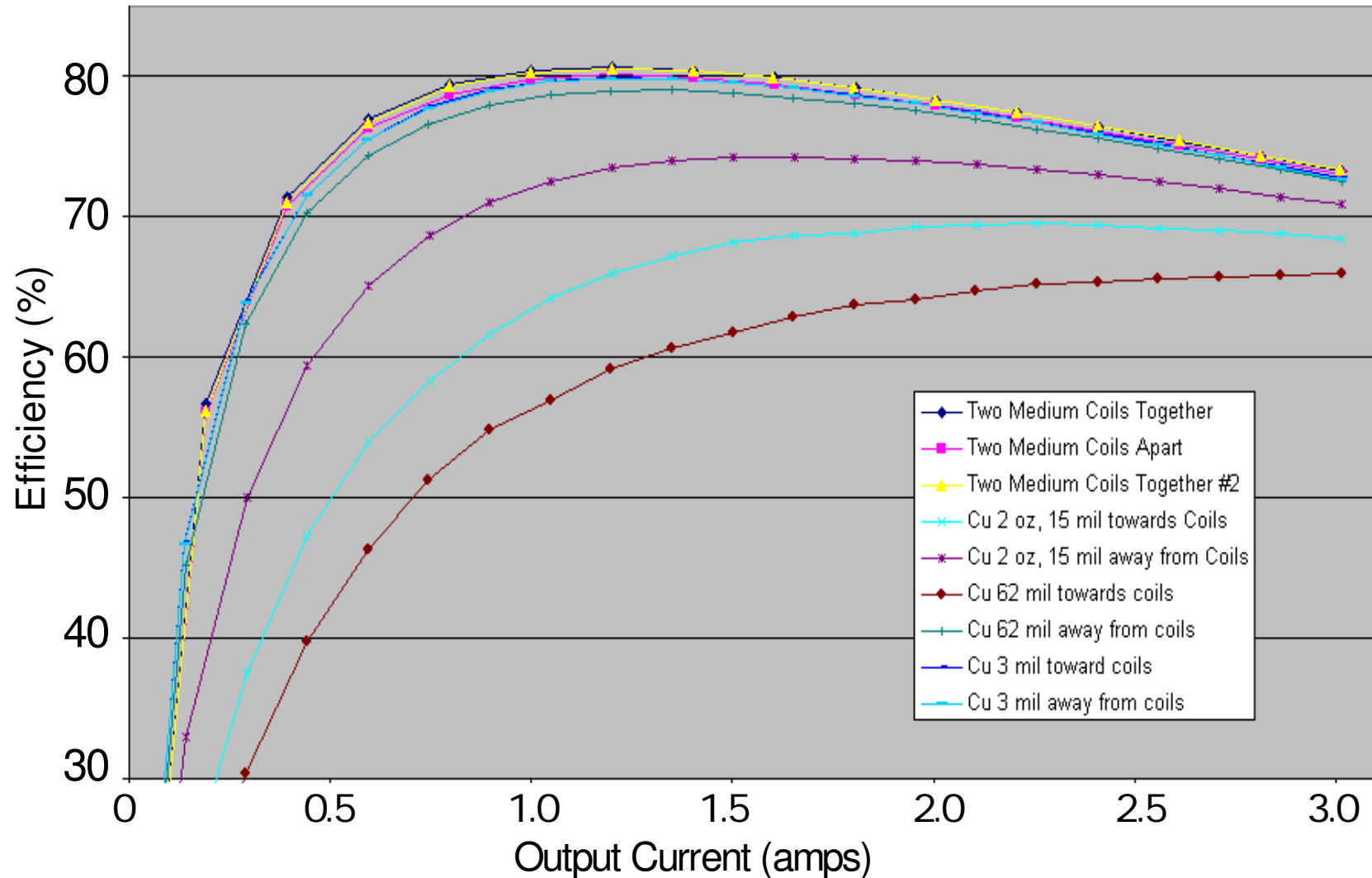A proximity effect is seen in the spiral coils



2 spiral Coils in series- Squeezing together lowers efficiency !


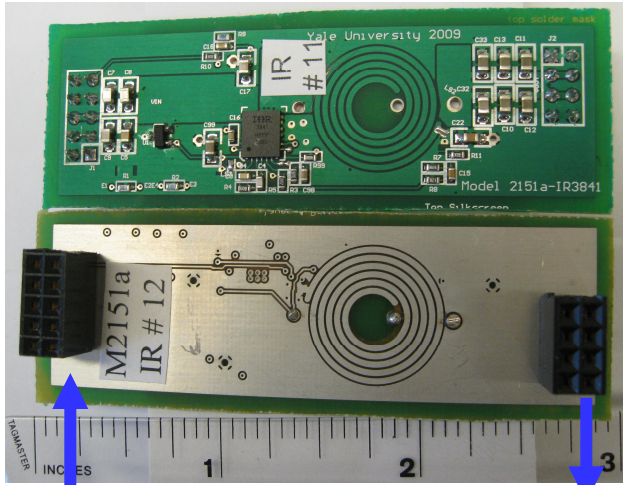
# Plug In Card with Shielded Buck Inductor



12 V

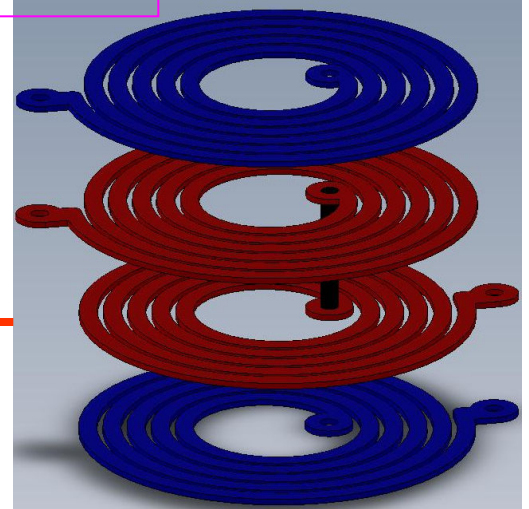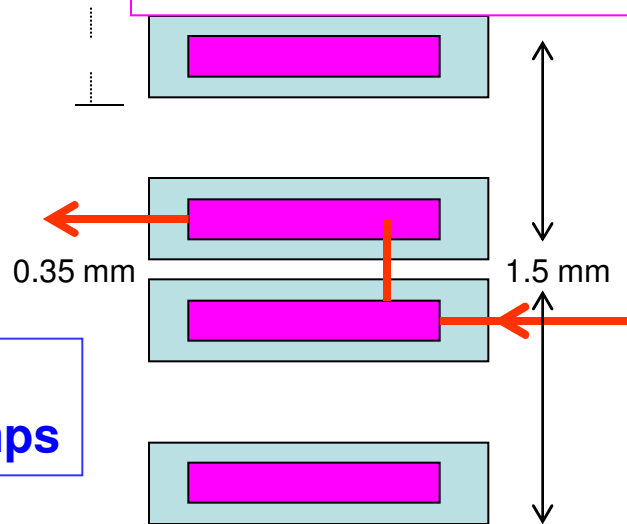2.5 V  
@ 6 amps

Coupled Air Core Inductor  
Connected in Series



Spiral Coils Resistance in mΩ

	Top	Bottom
3 Oz PCB	57	46
0.25 mm Cu Foil	19.4	17

## Different Versions


### ❖ Converter Chips

Max8654 monolithic  
IR8341 3 die MCM
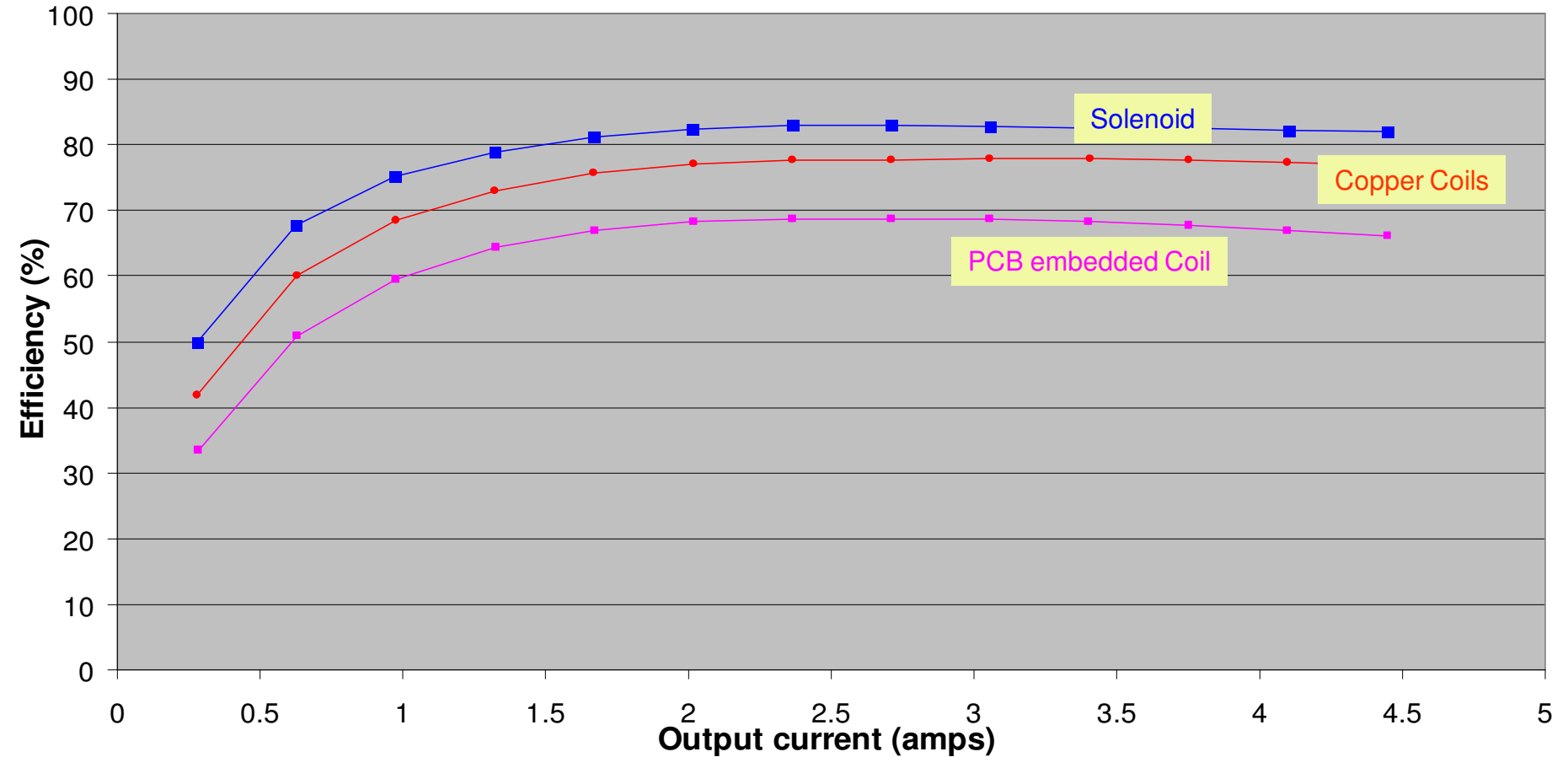
### ❖ Coils

Embedded 3oz cu  
Solenoid 15 mΩ  
Spiral Etched 0.25mm


**MAX8654 with embedded coils (#12), external coils (#17) or Renco Solenoid (#2)**  
**V<sub>out</sub>=2.5 V**




—■— MAX #12, V<sub>in</sub> = 11.9 V —●— MAX #17, V<sub>in</sub> = 11.8 V —■— MAX #2, V<sub>in</sub> = 12.0 V

Test @ BNL


Only One Chip Bonded

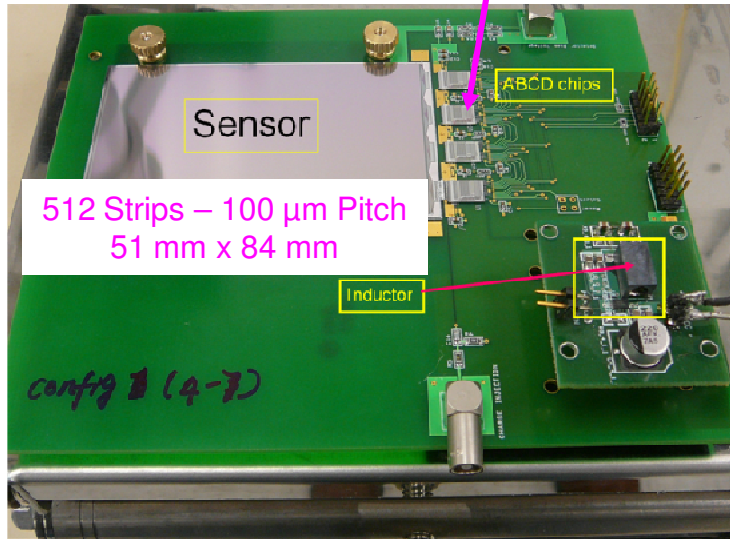

# Noise Tests with Silicon Sensors

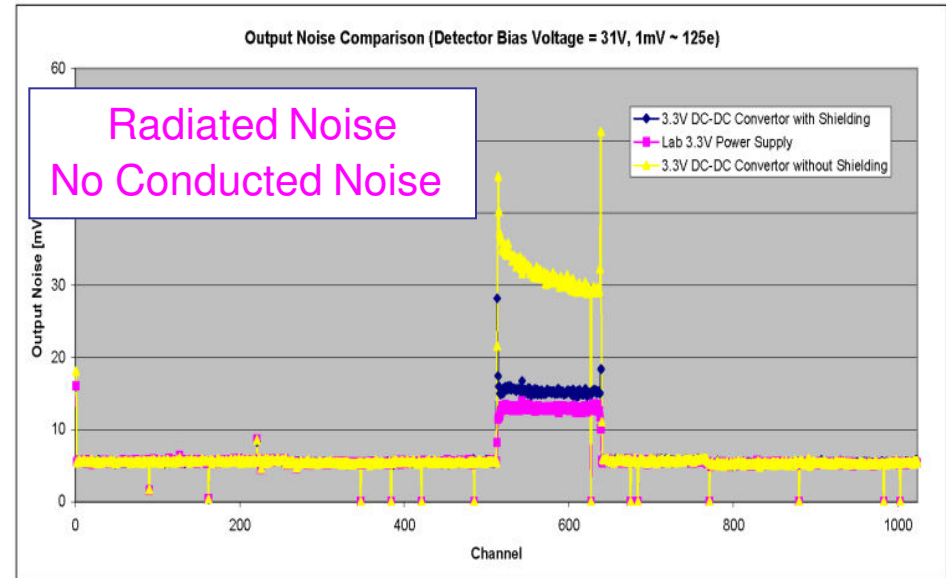

Test @ Liverpool

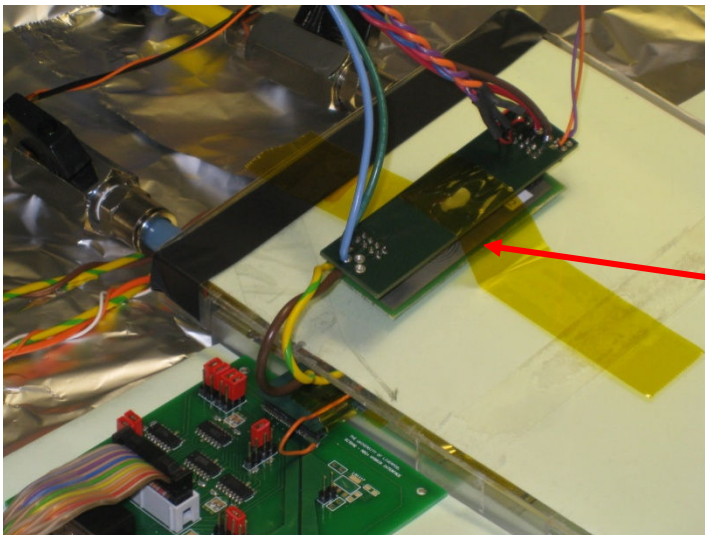

Plug in Card  
1 cm from Coil  
facing Sensor

20  $\mu$ m Al foil  
shielding

Coil Type	Power	Input Noise electrons rms
Solenoid	DC - DC	881
Solenoid	Linear	885
Solenoid	DC - DC	666
Solenoid	Linear	664

## Magnetic Field Effect

7 Tesla Field Chemistry Department  
Super Conducting Magnet in  
Persistence Mode


Effect:

Vout = 3.545 Outside

Vout = 3.546 Edge of magnet

Vout = 3.549 Center of magnet

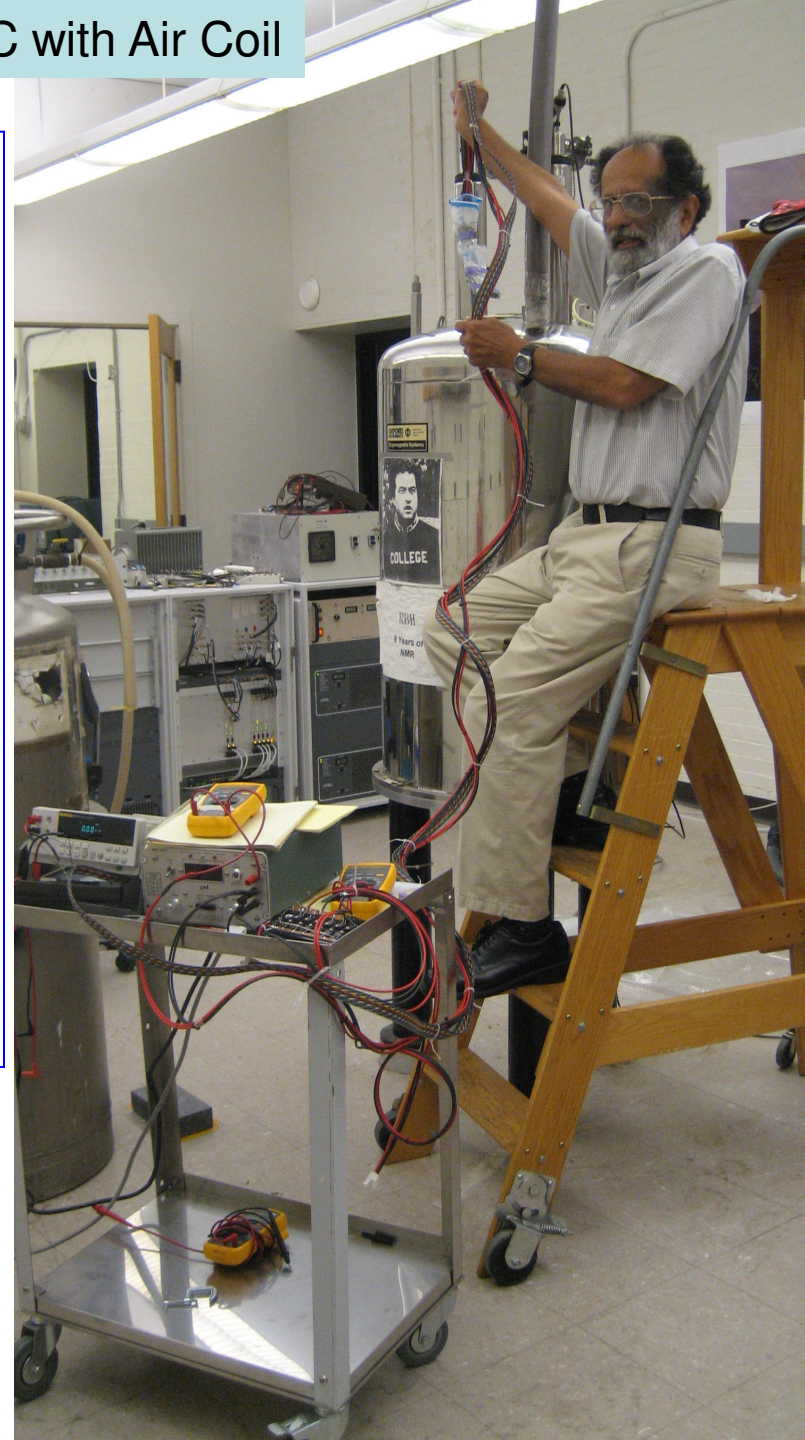Change= Increased Vout 1 part in 900 at 7T



## Ionizing Radiation Results – Commercial Converters



Dose rate= 0.2 Mrad/hr

Device	Time in Seconds	Dose before Damage Seen (krads)	Observations Damage Mode
TPS 62110	720	40	Increasing input current
ISL 8502	730	40.6	Increasing input current
MAX 8654	850	47.2	Loss of output voltage regulation
ADP 21xx	1000	55.6	Loss of output voltage regulation
ST1510	2250	125	Loss of output voltage regulation
IR3822	2500	139	Increasing input current
EN5382	2000	111	Loss of output voltage regulation
EN5360 #3	864000 Tested in 2008	48000	MINIMAL DAMAGE
EN5360 #2	Tested in 2007	100000	MINIMAL DAMAGE

5 nm Oxide DC-DC



Many more tested but similar failure-  
Thin oxide converters survive > 200 Krads
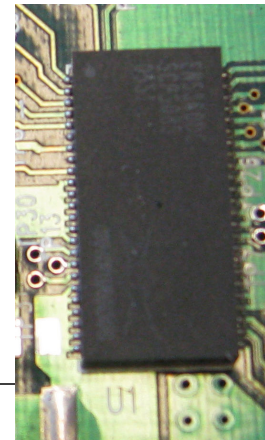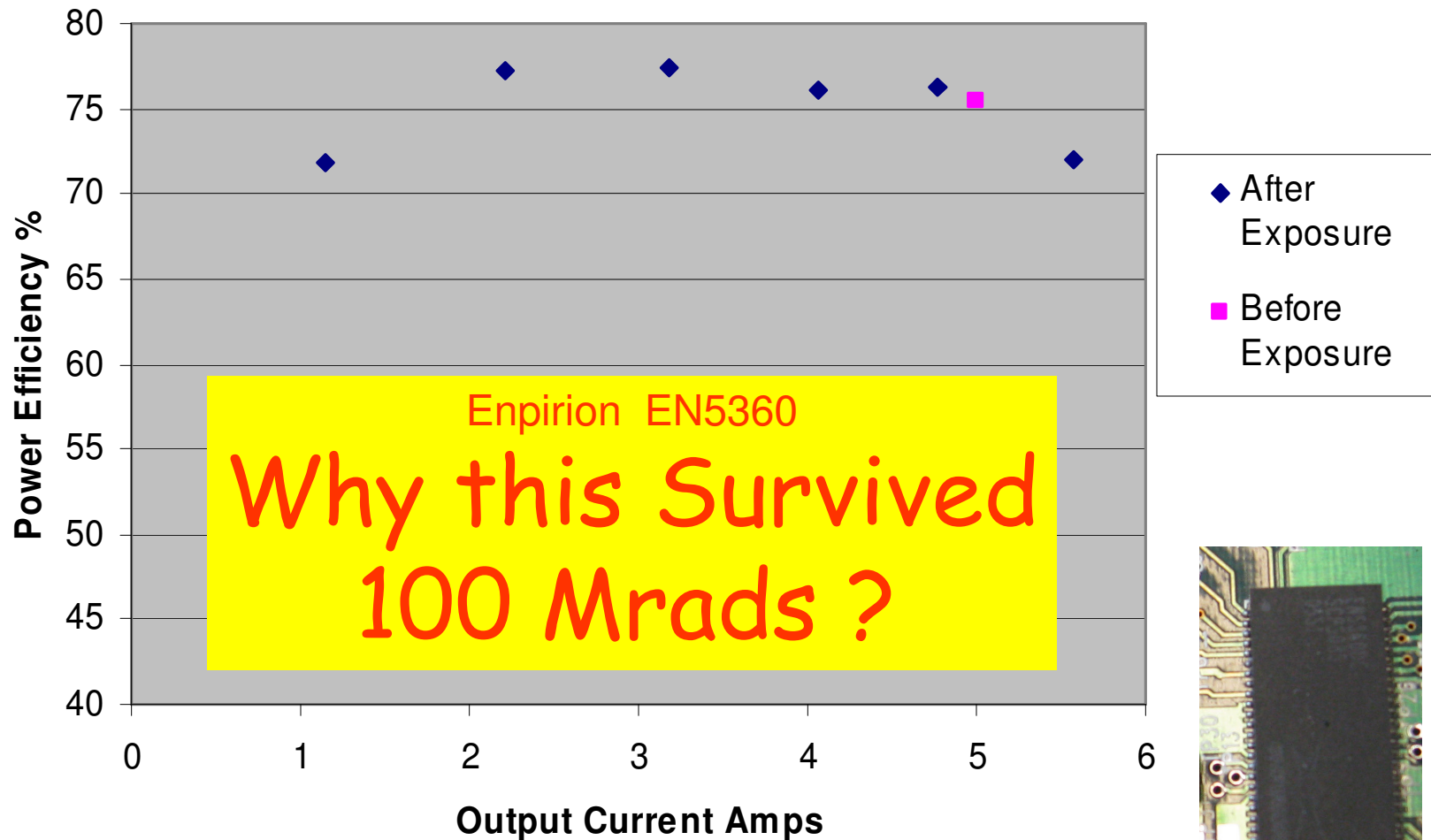
## Buck Regulator Efficiency after 100 Mrad dosage


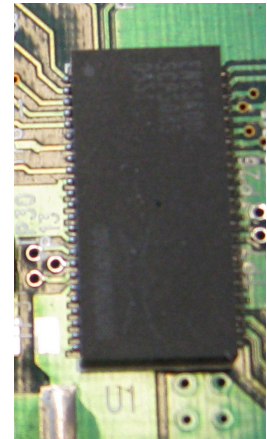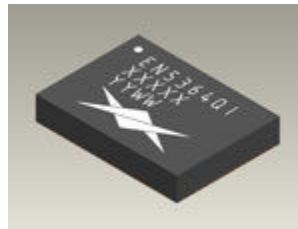
# What Makes it Rad Resistant ?


Empirical Evidence: Deep submicron  
But what why?




# What Makes it Rad Resistant ?

We say thin Gate Oxide is a  
necessary Condition

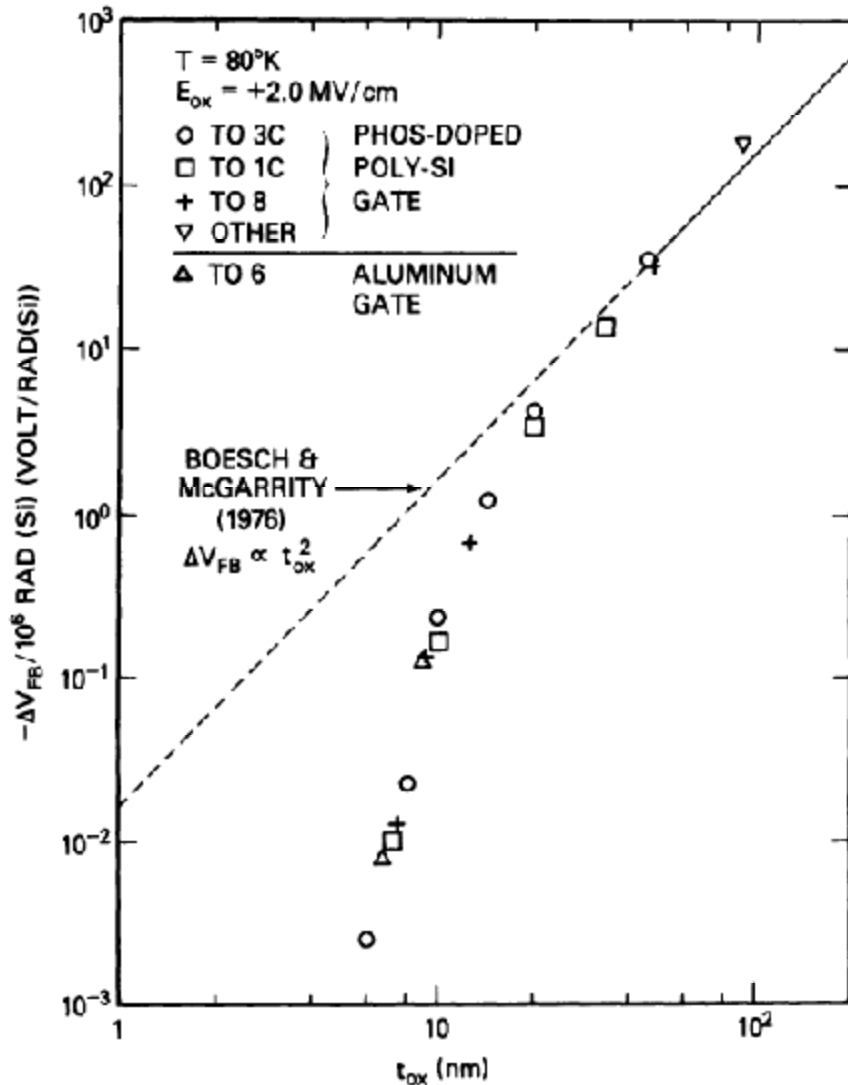
# Threshold Shift vs Gate Oxide Thickness



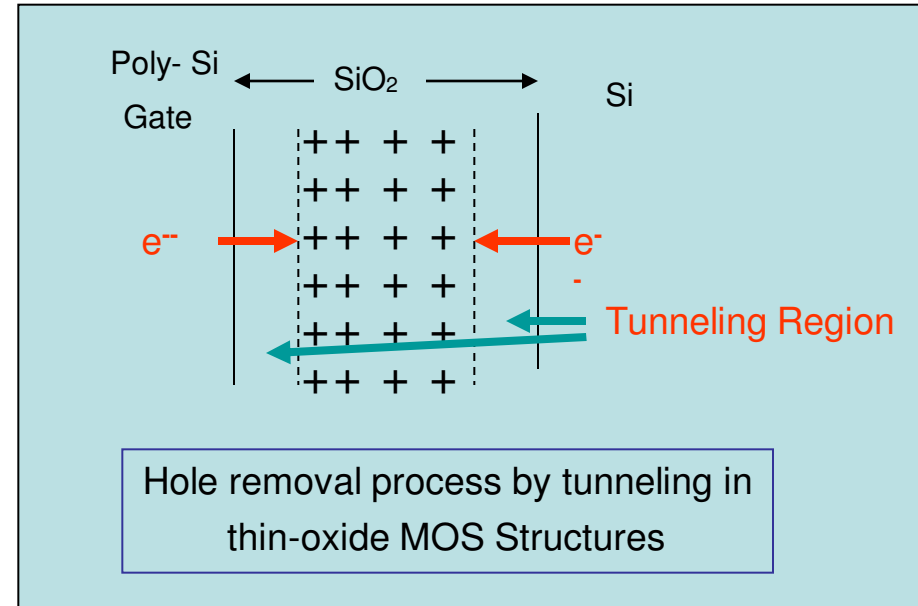Sachs et. al. IEEE Trans. Nuclear Science NS-31, 1249 (1984)



## Shifting $V_t$ of MOSFET With Gammas

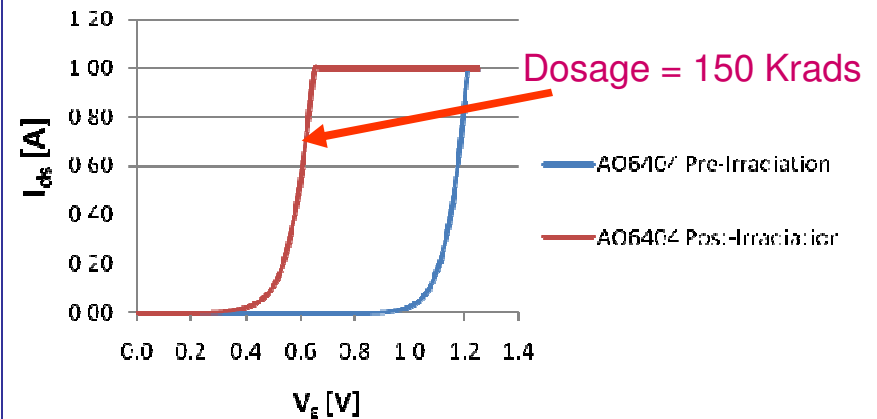


## Can We Have High Radiation Tolerance & Higher Voltage Together ???

Controller : Low Voltage

High Voltage: Switches –

LDMOS, Drain Extension, Deep Diffusion etc
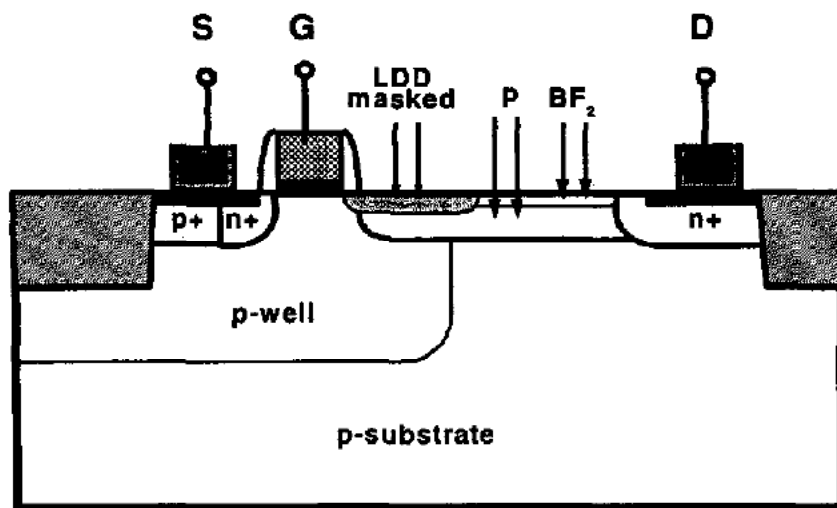
>> 20 Volts HEMT GaN on Silicon, Silicon Carbide, Sapphire



## LDMOS Structure

Laterally Diffused  
Drain Extension

High Voltage / high Frequency  
Main market. Cellular base stations

Fig.1: Schematic cross-section of the RF-LDMOS transistor.

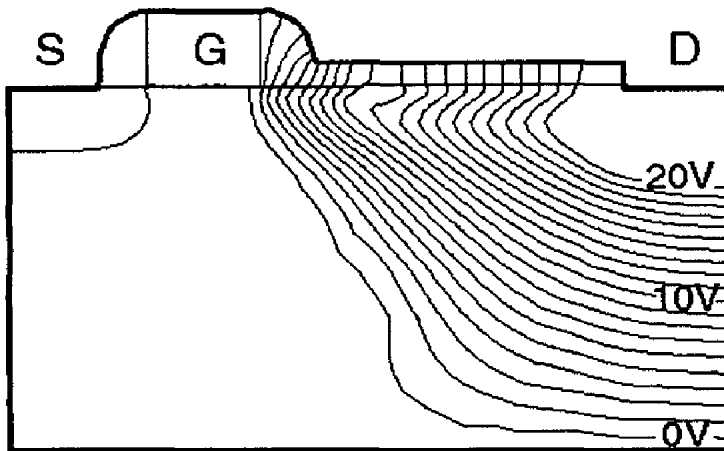


Fig.3a: Potential distribution at the highest operating voltage (20V) with  $V_G = 0V$  (LDMOS 3 from Table 1).

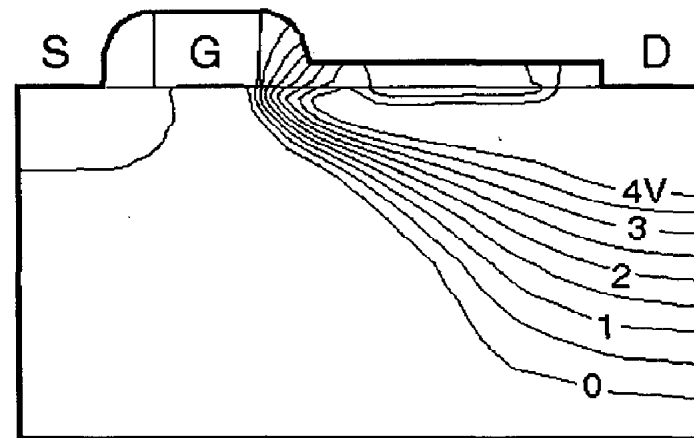


Fig.3b: Potential distribution at the lowest operating voltage (4V) with  $V_G = 0V$  (LDMOS 3 from Table 1).

High performance RF LDMOS transistors with 5 nm gate oxide in a 0.25  $\mu m$  SiGe:C  
BiCMOS technology: IHP Microelectronics  
[Electron Devices Meeting, 2001. IEDM Technical Digest. International](#)  
2-5 Dec. 2001 Page(s):40.4.1 - 40.4.4

## Thin Oxide Devices (non IBM)

Company	Device	Process	Foundry	Oxide	Dose before	Observation
		Name/ Number	Name	nm	Damage seen	Damage Mode
IHP	ASIC custom	SG25V GOD <b>12 V</b>	IHP, Germany	5		Minimal Damage
XySemi	FET 2 amps	HVMOS20080720 <b>12 V</b>	China	7		Minimal Damage
XySemi	XP2201	HVMOS20080720 <b>20 V</b>	China	7		1Q2010
Enpirion	EN5365	CMOS 0.25 $\mu$ m	Dongbu HiTek, Korea	5	64 Krads	
Enpirion	EN5382	CMOS 0.25 $\mu$ m	Dongbu HiTek, Korea	5	111 Krads	
Enpirion	EN5360 #2	SG25V (IHP)	IHP, Germany	5	100 Mrads	Minimal Damage
Enpirion	EN5360 #3	SG25V (IHP)	IHP, Germany	5	48 Mrads	Minimal Damage


Necessary condition for Radiation Hardness - **Thin Gate Oxide**

***But not sufficient***


IHP: Epi free, High resistivity substrate, Higher voltage, lower noise devices

Dongbu: Epi process on substrate, lower voltage due to hot carriers in gate oxide

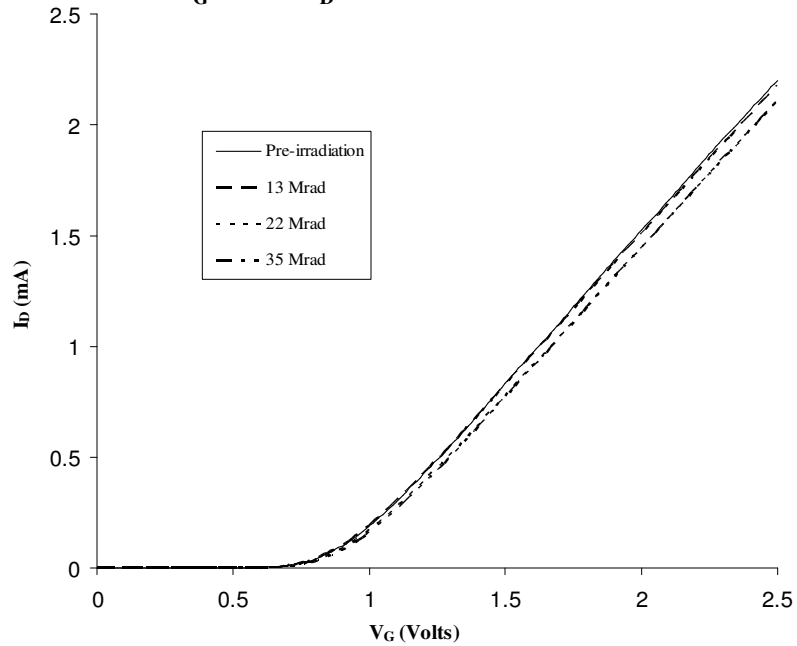
**IHP NMOS Transistor**  
 **$V_G$  versus  $I_D$  at Selected Gamma Doses**



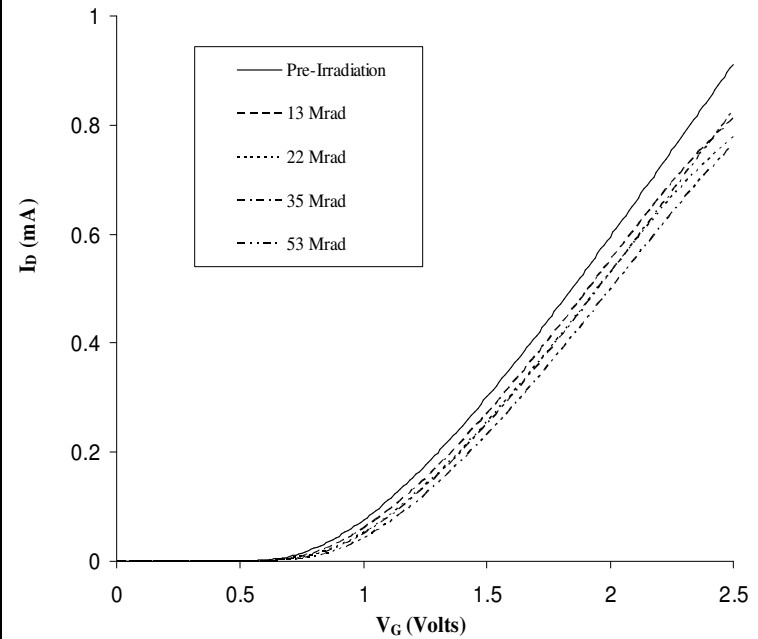**IHP PMOS Transistor**  
 **$V_G$  versus  $I_D$  at selected Gamma Doses**



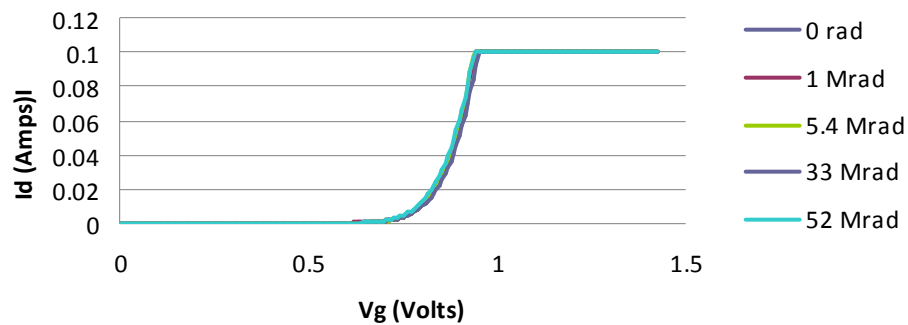
**XY Semi ( $V_D = 12V$ )**  
**2 Amp FET- HVMOS20080720 Process**



## XP2201 - 20V 2A STEP-DOWN DC to DC CONVERTER

### General Description

Non- Synchronous

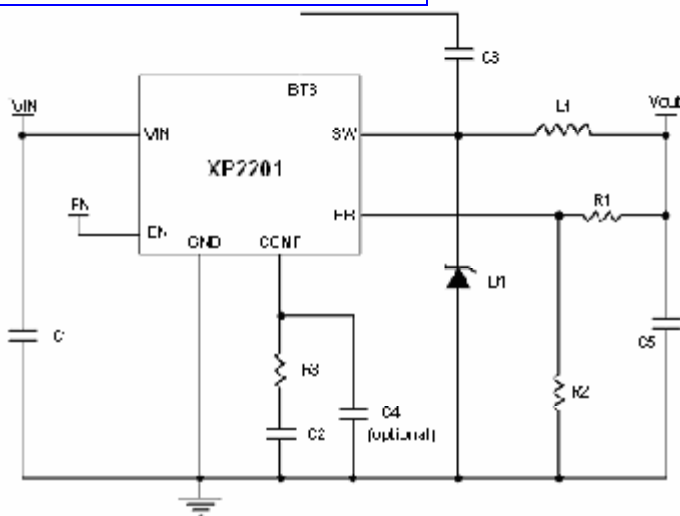


Replacement for LHC4913:

LHC Radiation Hard LDO  
Made by ST Microelectronics

Use with Ferrite Coil
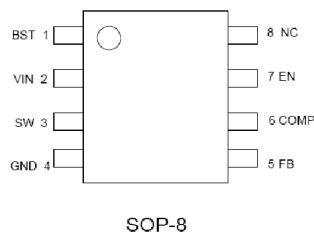
### Features

- 2A Output Current
- Up to 95% Efficiency
- 4.5V to 20V Input Range
- Adjustable Output Voltage
- Fixed 400KHz Frequency
- Integrated 0.2Ω Switch
- 20uA Shutdown Supply Current
- Internal Soft Start
- Cycle-by-Cycle Over Current Protection
- Thermal Shutdown
- Programmable Under Voltage Lockout
- Operating Temperature: -40°C to +85°C
- Available in an 8-Pin SO Package



Engineering Samples  
1Q2010

# GaN HEMTs Why of Interest?

- High voltage and current rating
- Very high switching frequency ( $> 1$  GHz range)
- Depletion mode are radiation Hard (details follow), Enhancement mode devices not yet available

# Gallium Nitride Devices under Tests

## **RF GaN** 20 Volts & 0.1 amp

❖ 8 pieces: Nitronex NPT 25015: [GaN on Silicon](#)

✓ Done Gamma, Proton & Neutrons

✓ 65 volts Oct 2009

❖ 2 pieces: CREE CGH40010F: [GaN on siC](#)

❖ 6 pieces: Eudyna EGNB010MK: [GaN on siC](#)

✓ Done Neutrons

## **Switch GaN**

❖ International Rectifier [GaN on Silicon](#)

[Under NDA](#)

Gamma: @ BNL


Protons: @ Lansce

Neutrons: @ U of Mass Lowell

Plan to Expose same device to  
Gamma, Protons & Neutrons  
Online Monitoring

# Nitronex 25015


Serial # 1

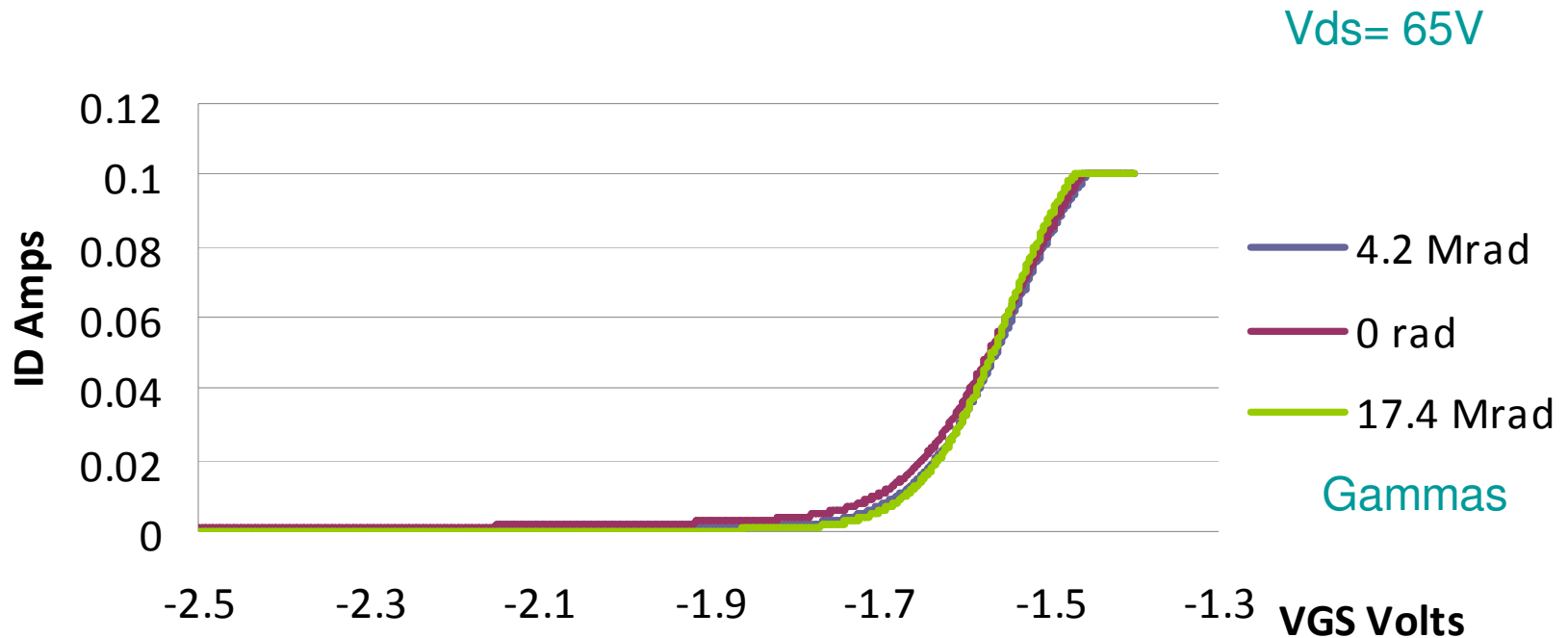




200 Mrads of Protons had no effect – switching 20 V 0.1 Amp  
Parts still activated after 7 months
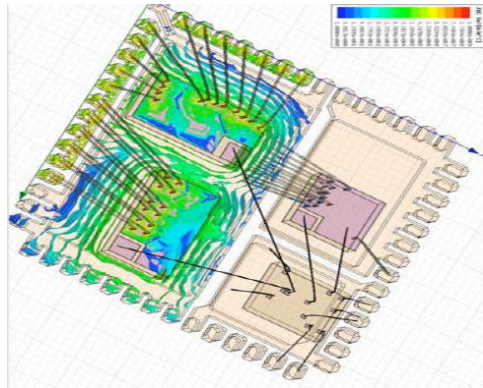
# PSOC: Power Supply On a Chip

National: LMZ Package 10 x14 x5 mm 20/42 V > 1.2V 5 A




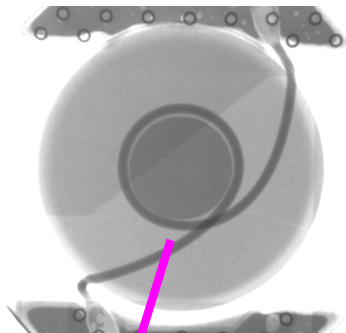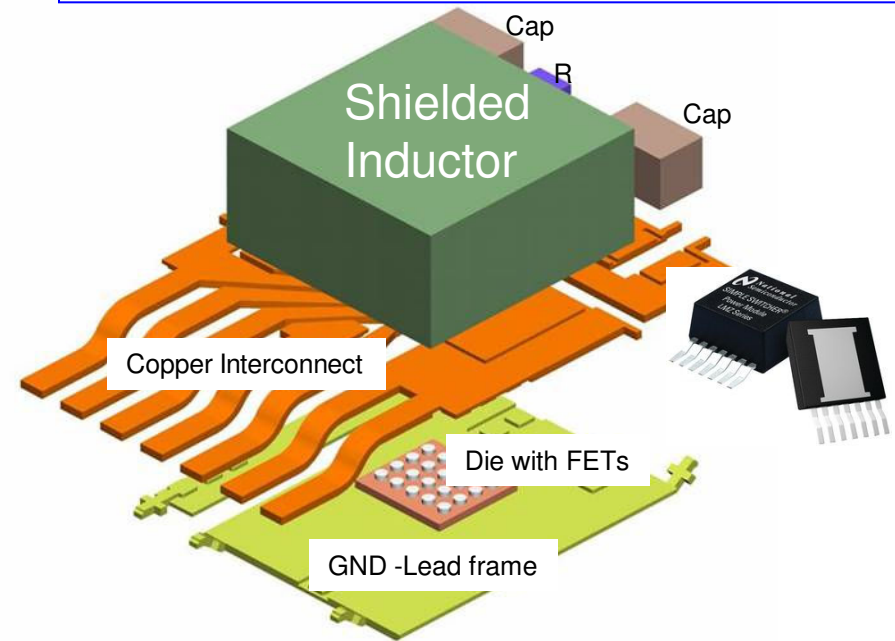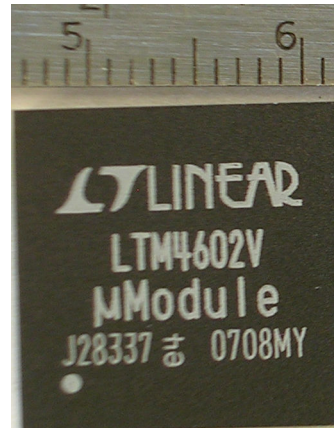FAN5009 8 x 8 mm MCM  
12 V > 1.2 V = 88.5% @ 30 A




1 turn around slug



5 MHz

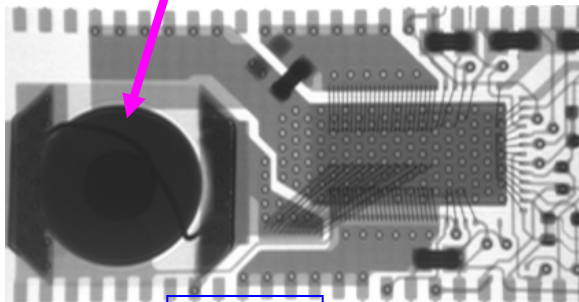


EN5360

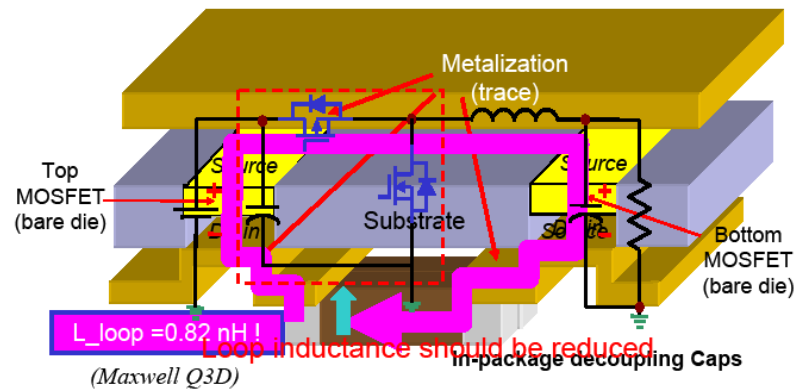

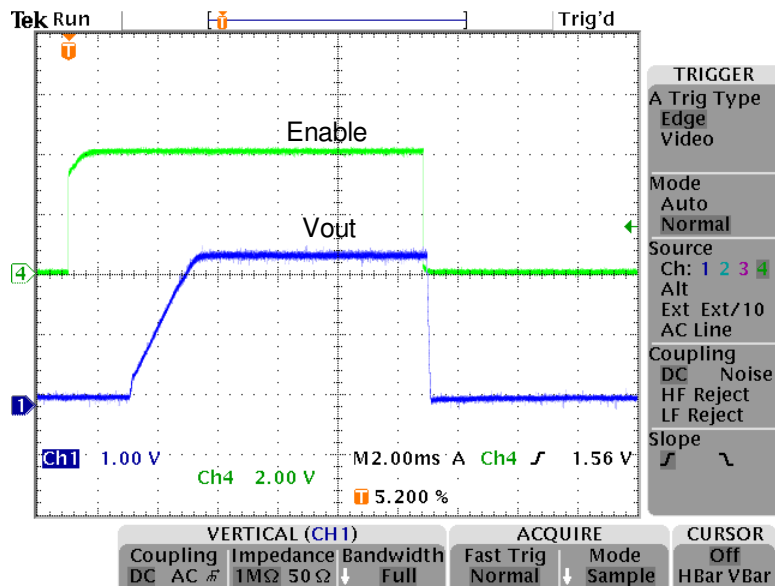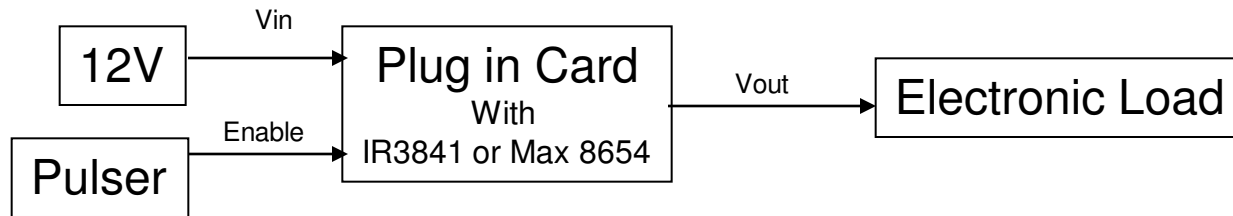
❖ Embedding the flipped devices allows for smallest loop inductance and for layering of components on top and bottom



IR8431 with 3 amp Load  
 $V_{in} = 12\text{ V}$   
 $V_{out} = 2.5\text{ V}$   
 Load = 3 amps (Electronic)

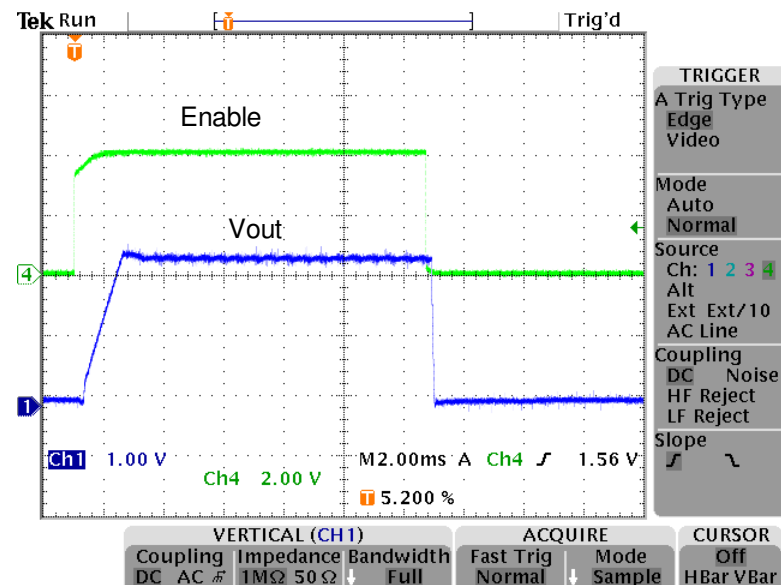

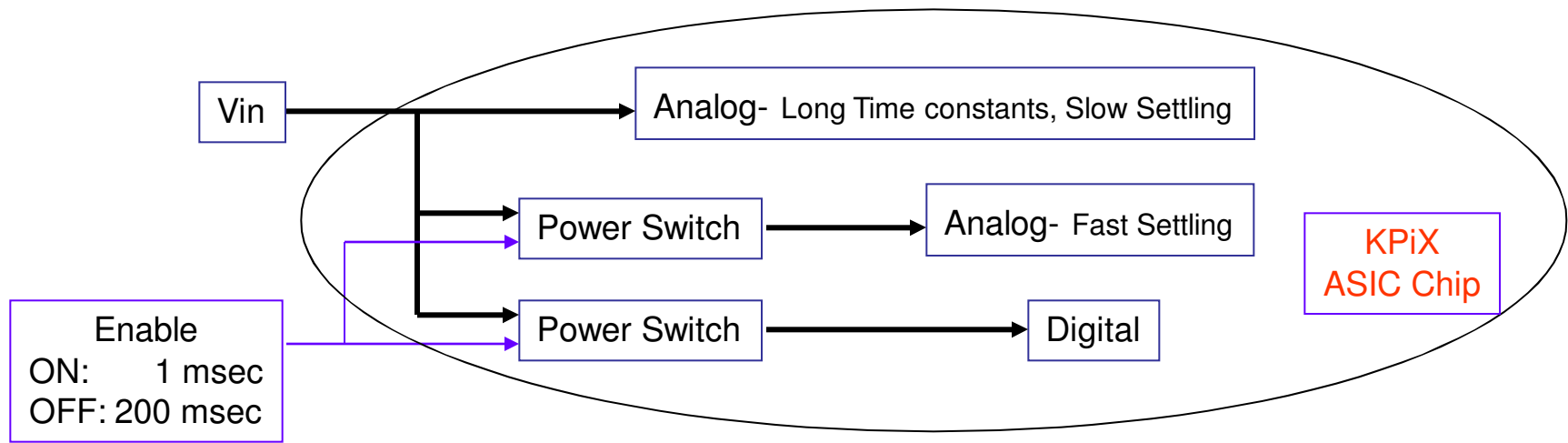MAX8654  
 $V_{in} = 12\text{ V}$   
 $V_{out} = 2.5\text{ V}$   
 Load = 3 amps (Electronic)



### Simulation with a National Semiconductor Buck Converter

- ~ 1 MHz
- Load 3 amps Type R, Electronic, CMOS ASIC
- $V_{in} > 12\text{ V}$
- $V_{out} = 1.2 / 2.5\text{ V}$
- Settling Time on/off, Voltage/ Current Loop?, Caps, Stability, Ripple/Noise

Circuit for simulation of converter settling times

## Some Random Remarks

- Learned from commercial devices, companies & power conferences
- Can get high radiation tolerance & higher voltage simultaneously
- High frequency > smaller air coil > less material
- Goal: ~20 MHz buck, MEM on Chip *size 9 mm x 9mm*
- Power SOC: MEMs air core inductor on chip
- Will study feasibility of 48 / 300V converters
- Irradiations:
  - Important to run @ max operating V & I.
  - Limit power dissipation by switching duty cycle
  - Use online monitoring during irradiation for faster results
- Yale Plug Cards can be loaned for evaluation
- Collaborators are Welcome

# Conclusions

- The power distribution needs of HEP detectors require new solutions/technologies to meet power and environmental requirements.
- DC/DC (Buck) Converters are potential solutions for these needs.
- The environment requires that these converters operate in high radiation environments and high magnetic fields at high switching frequencies in a small size/mass package.
- Target technologies for the switches are radiation hard GaN and 0.25  $\mu\text{m}$  LDMOS. High frequency controllers driving small sized nonmagnetic/air core inductors are also required.
- Many of these components have been tested and now need integration to produce a working prototype. This is the next step in our R&D program.