

WASA: A Low power consumption ASIC for TPC

Wei Liu^{1,2}, Canwen Liu^{1,2}, **Zhi Deng**^{1,2}, Fule Li³, Yulan Li^{1,2}, Huirong Qi⁴

¹ Department of Engineering Physics, Tsinghua University, Beijing, China

²Key Laboratory of Particle & Radiation Imaging, Ministry of Education, Beijing, China

³Institute of Microelectronics, Tsinghua University, Beijing, China

⁴Institute of High Energy Physics, Chinese Academy of Science, Beijing, China


Joint Workshop of the CEPC Physics, Software and New Detector Concept
Beijing, 2022-5-23



Outline

- Introduction
- The Progress of WASA V1
- The Progress of WASA V2
- Summary & Future Plan

Introduction

 


Momentum resolution (B=3.5T)	$\delta(1/p_t \approx 10^{-4}/\text{GeV}/c)$
δ_{point} in $r\Phi$	<100 μm
δ_{point} in rZ	0.4-1.4 mm
Inner radius	329 mm
Outer radius	1800 mm
Drift length	2350 mm
TPC material budget	$\approx 0.05X_0$ incl. field cage $< 0.25X_0$ for readout endcap
Pad pitch/no. padrows	$\approx 1 \text{ mm} \times (4\sim 10\text{mm}) / \approx 200$
2-hit resolution	$\approx 2 \text{ mm}$
Efficiency	$>97\%$ for TPC only ($p_t > 1\text{GeV}$) $>99\%$ all tracking ($p_t > 1\text{GeV}$)

- TPC can provide large-volume high-precision 3D track measurement with stringent material budget
- In order to achieve high spatial resolution, small pads (e.g. 1 mm x 6mm) are needed, resulting **~ 1 million** channel of readout electronics
- Need low power consumption readout electronics **working at continuous mode**





Chip Architecture

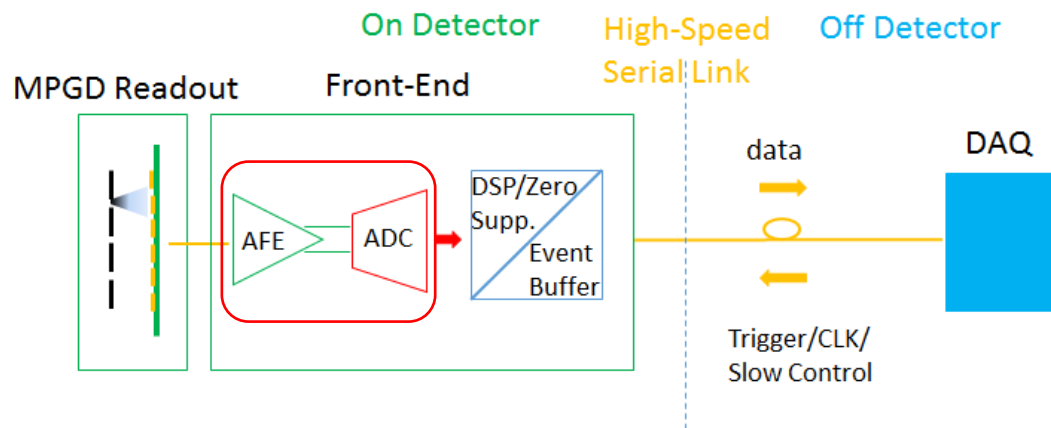- In order to reduce the power consumption:
 - Using more advanced 65 nm CMOS process favoring digital logics
 - Reducing analog circuits:
 - $CR-(RC)^n \rightarrow CR-RC$, moving high order shaping to digital domain
 - ADC structure : pipeline \rightarrow SAR (Successive Approximation Register)




WASA: WAVEform SAMPLING FE ASIC for TPC

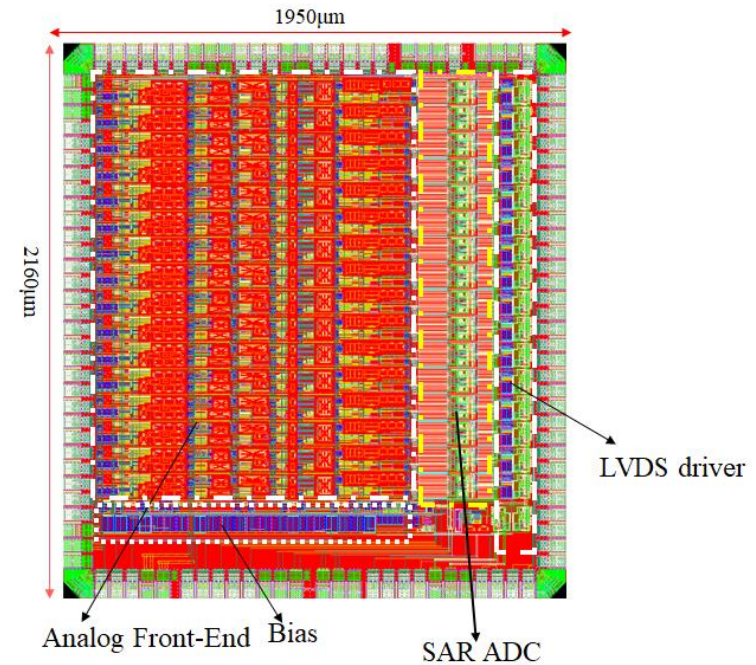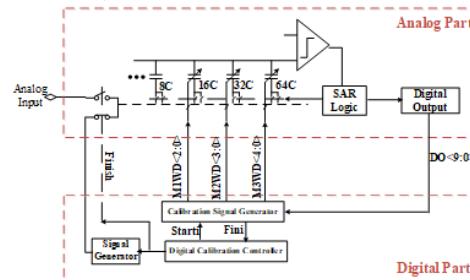  - WASA V1 :
 - 16 channel AFE+ADC+LVDS data output
 - The Power consumption: AFE in 1.4 mW/ch and ADC in 1 mW/ch
 - Die size in 1950 μm x 2160 μm
 - Submitted in Dec, 2019




Test Setup

- Test Setup

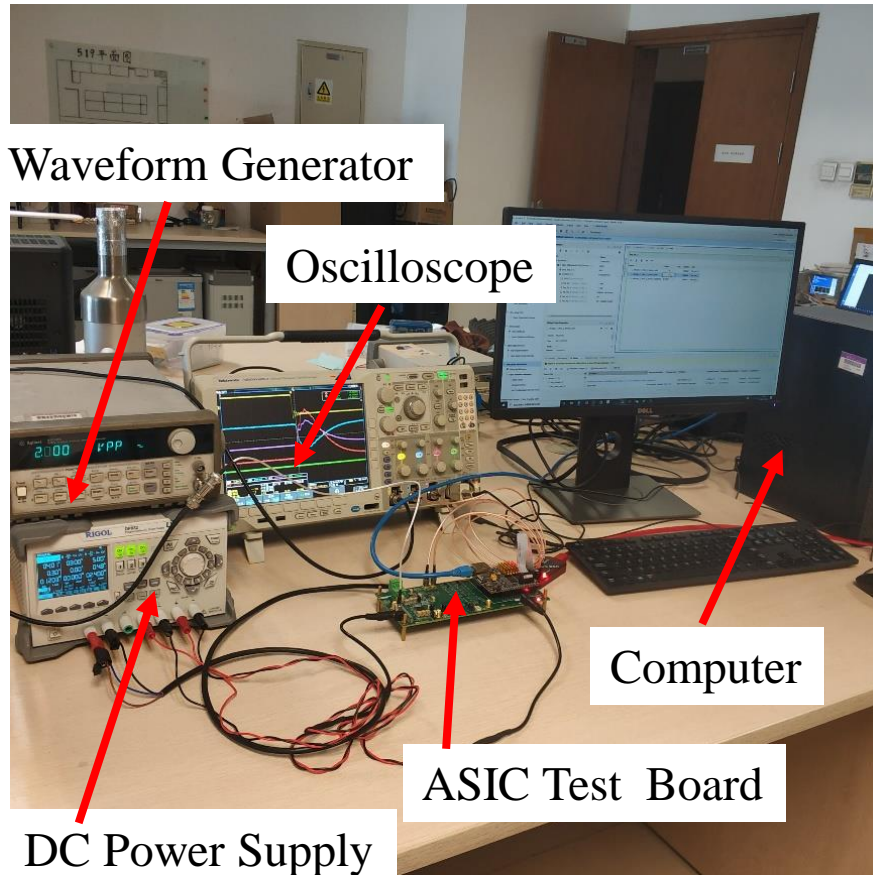


- ASIC Test Board

 

Test Results: Power Consumption

 
- The power consumption of the AFE: **1.43 mW/ch** (1.40 mW/ch sim.)
- The power consumption of the ADC increases as the sampling rate




	AFE (mW/ch)	ADC (mW/ch)	Total (mW/ch)
WASA_V0 (simulation)	1.93	1.0	2.93
WASA_V0(measured)	2.02	1.0	3.02
WASA_V1 (simulation)	1.40	1.0	2.40
WASA_V1 (measured)	1.43	1.06 @40MS/s	2.49

Test Results: Transient waveforms

 - Transient outputs
 - Differential baseline can be externally adjusted




ADC Transient outputs @ 30MSPS

 


Test Results: Non-Linearity

- Transient outputs

 


- The linearity @ gain = 10 mV/fC

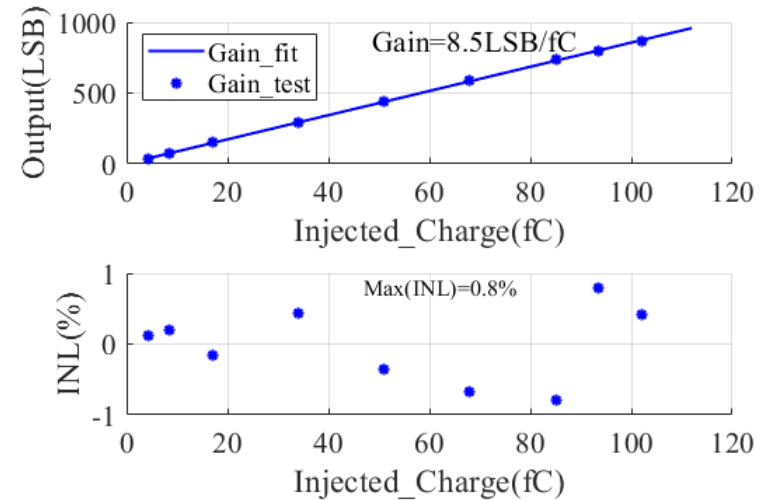

$$\text{Gain} = 8.5 \text{ LSB/fC} = 8.5 \times 1.3 \text{ mV/fC} = 11.05 \text{ mV/fC}$$


Test Results: Noise

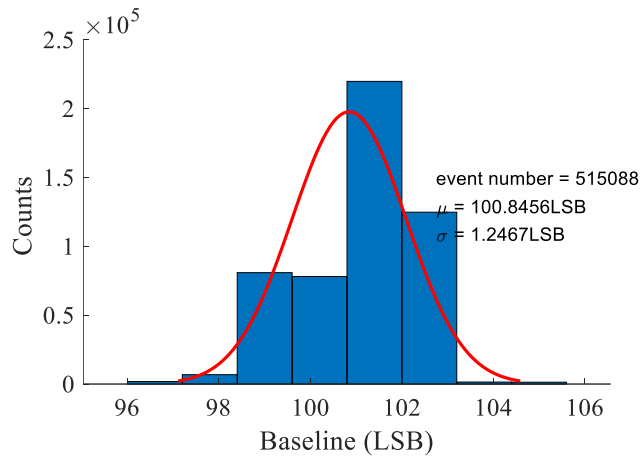- Baseline distribution @8.5 LSB/fC, $C_{in}=15.2$ pF





$$\text{ENC}: 1.24/8.5 * 6250 = 911.76 \text{ e}$$

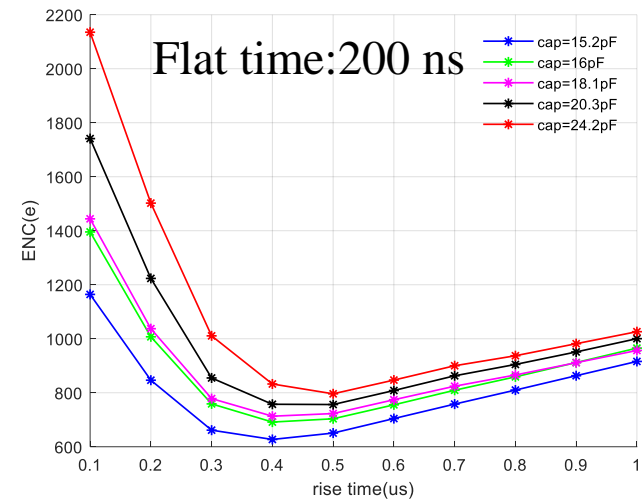- ENC after digital trapezoidal filter in MATLAB




Test Results: Timing @ 30 MS/s

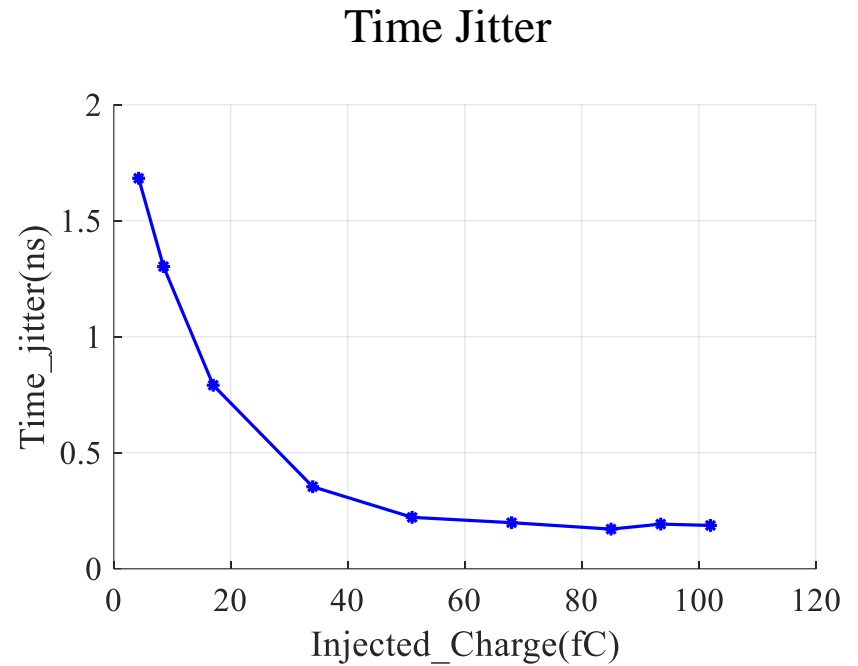 - Constant fraction time distribution @ $Q_{in}=100$ fC, 10 mV/fC




Test Results: Fe-55

 


TPC Work Conditions:

 
- GEM: 280 V
- Drift Field: 323 V/cm
- Gas: Ar/CF₄/iC₄H₁₀ 95/3/2 (T2K)




Transient Waveforms After Digital Filter

 

Fe-55 Energy Spectrum

 


Test Results: Laser Tracks

 


TPC Work Conditions :

 - GEM: 280 V
- Drift Field: $9000 \text{ V}/50 \text{ cm} = 180 \text{ V/cm}$
- Gas: $\text{Ar}/\text{CF}_4/\text{iC}_4\text{H}_{10} \text{ 95/3/2 (T2K)}$
- Laser: 7.2 mJ @20 Hz
- Sampling Rate: 30 MS/s




Track & Position Resolution (Preliminary)

- Laser Tracks

 


- Position Resolution

 


WASA V2

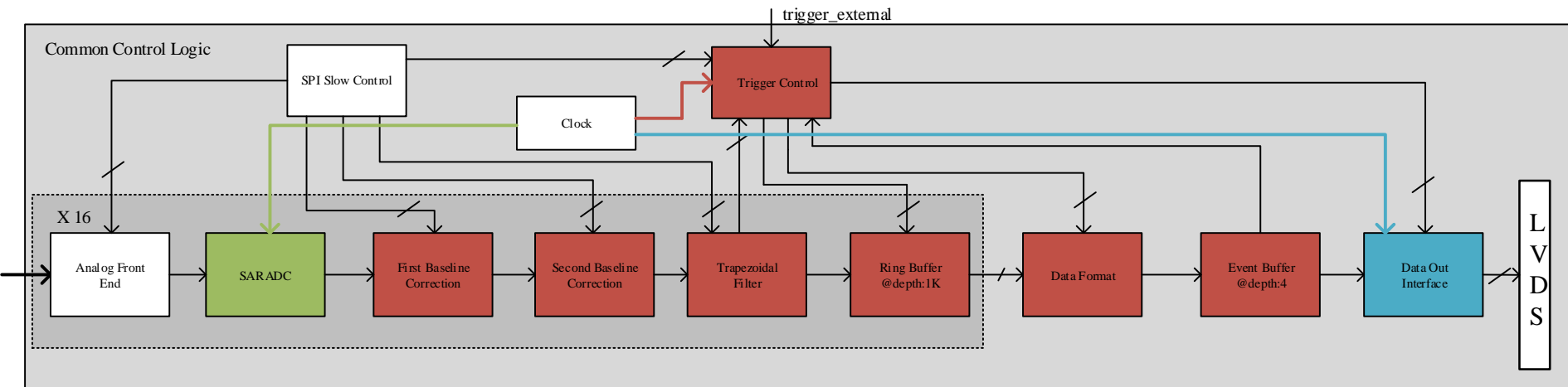- Digital signal processing:
 - Two stage baseline corrections, learnt from SAMPA
 - Digital trapezoidal filter, to make pulse shape symmetric and shorter
- Trigger logics with two stage data buffer (ring buffer and event buffer)




Integrated Digital Trapezoid Filter

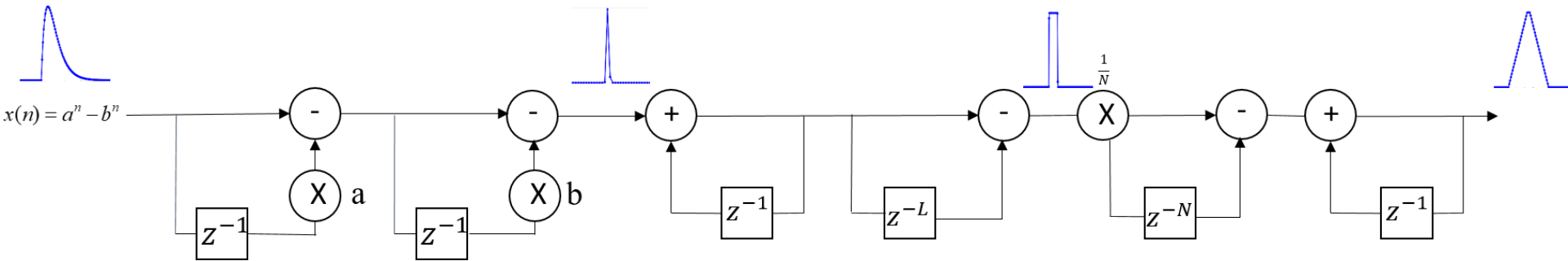


Valentin T. Jordanov, Unfolding-synthesis technique for digital pulse processing. Part 1: Unfolding, NIMA Vol 805, 2016, 63-71

- Transient Outputs

 



- Linearity

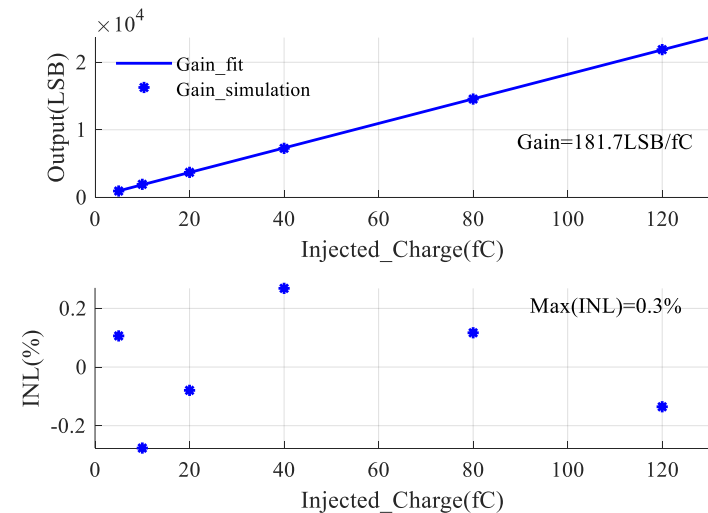


Power Consumption Estimation

- The simulation settings of digital logics @ 1.2 V, tt, 25 C, switch activity = 10% (**Conservatively**)
- The power consumption: $3.36 \text{ mW} + 0.078 \text{ mW/MHz} \times \text{sampling rate in MHz}$

Sampling Rate MS/s	10	20	30	40	50	60	70	80	90	100
Digital logics: mW/ch	2.03	2.69	3.34	4.0	4.62	5.28	5.90	6.55	7.20	7.85
ADC: mW/ch	0.69	0.81	0.94	1.06	1.19	1.31	1.44	--	--	--

  

The Layout of WASA V2

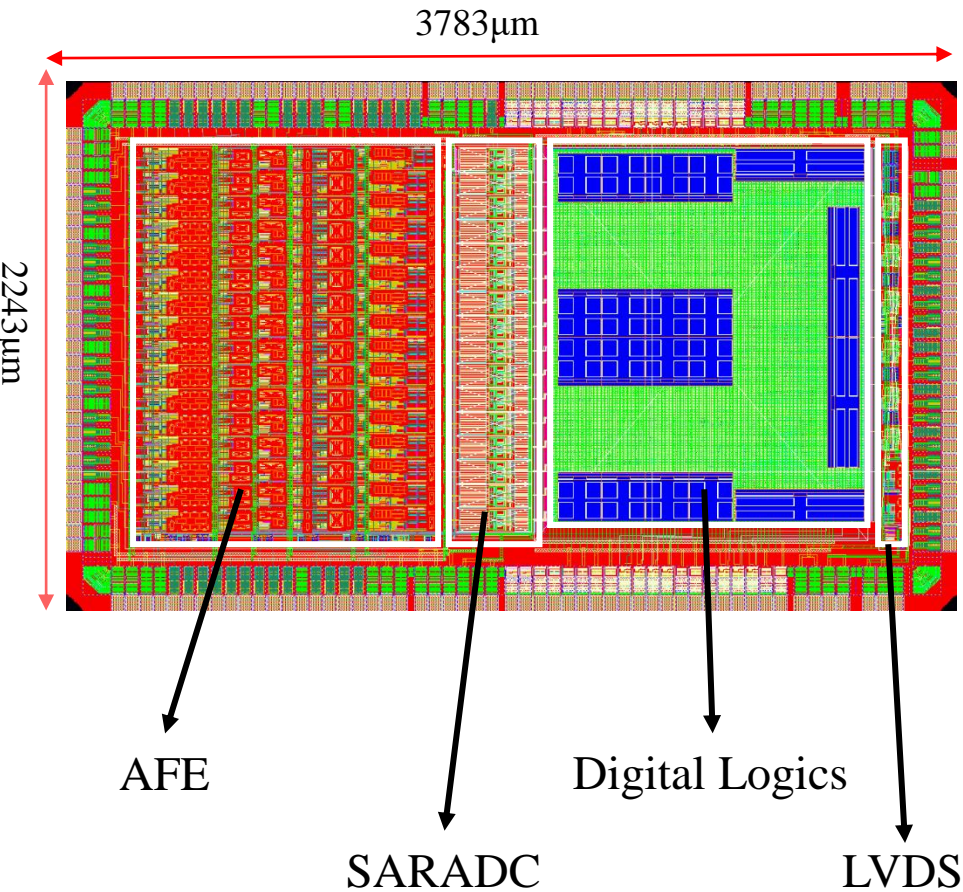


- The floor plan in layout:
 - The die size : 3783 μm x 2243 μm
 - Analog Front-End, SAR ADC, Digital Logics, LVDS driver are supplied by separate power
 - Analog Front-End, SAR ADC, Digital logics, LVDS driver are separated by guarding ring
- The ASIC have been taped out in Jan 12 ,2022 and is being evaluated.

The Layout of WASA V2

- ASIC Test Board

WASA_V1

ZYNQ Core Board


 


Summary

- A 16 channel low power readout ASIC WASA V1 has been developed and evaluated
 - The power consumption is **2.49 mW/channel**
 - $P_{AFE}=1.43$ mW/channel
 - $P_{ADC} = 1.06$ mW/channel @ 40MS/s
 - ENC = **911.7 e** @ $C_{in}=15.2$ pF, gain=10 mV/fC and can be reduced to **627 e** using digital trapezoidal filter
 - Tested with TPC detector at IHEP: OK, more tests with more readout channels
- The second iteration of WASA V2 has also been designed
 - Two stage BC, digital trapezoidal filter, and trigger logics with two stage data buffer are implemented on chip
 - The ASIC have been taped out and is being evaluated.

Future Plan

  - Large Pixel Readout
 - $1\text{mm} \times 6\text{mm} \rightarrow 0.3\sim 0.5\text{mm}$ pixel
 - Higher precision, higher rate
 - Potential for dN/dx
- Concept Design
 - ROIC + Interposer PCB as RDL
 - High metal coverage, 4-side buttable
 - Low power Energy/Timing measurement ASIC
 - $\sim 100\text{e}$ noise
 - 5ns drift time resolution
 - $< 100\text{mW/cm}^2$



Thank You