

# ASIC R&D Progress for ATLAS Silicon Pixel Detector Upgrade

**CPPM & IHEP**

W WEI (IHEP)

N Wang (IHEP) JP Luo (IHEP) Z WANG (IHEP)

RC Fei (CPPM) P Panguad (CPPM)

JC Clemens (CPPM) A Rozanov (CPPM)

9 April 2011


# Details of Collaborations of 2010~2011

---




- **FEC4\_P3C pulse generator (W. WEI)**
  - Design
  - Single chip measurement result
  - FEC4\_P3C associated with FEC4\_P1 measurement
- **Other Designs and simulation:**
  - Design of power saving blocks for pixel unit (W. WEI)
  - Full chip functional evaluation of FEC4\_P3 (W. WEI)
  - Power-on-reset block (N. WANG)
  - Modification of the SEU latch (N. WANG)

# FEC4\_P3C pulse generator

 


 - Provide a very fast and precise pulse to the pixel matrix
- Up to 30k pixels (FE\_I4 case), parasitic capacitive load of 40pF~80pF
- A falling edge faster than 10ns to avoid ballistic deficit
- Rising time of hundreds of  $\mu$ s to avoid baseline shift
- Capable of pulse phase tuning and rising time tuning



Dynamic range	0~1.5V (rail-to-rail)	Input DAC range	0~30 $\mu$ A
Pixel matrix	53760 pixels	Load capacitance	53pF
EoDC switches	82	Falling time	< 2.5ns
Rising time	20 $\mu$ s~500 $\mu$ s	Rising time tuning	3 bits
Delay span	50ns	Delay tuning	6 bits
Output DC linearity (Full isolation)	< 1%	Output DC linearity (Shrunk isolation)	< 0.5%
Process corner endurance	all	Temperature corner endurance	-20~50
PSRR	40dB	Offset	< 9mV
Noise	<200 $\mu$ V rms	Power down	Yes


# Design of the pulse generator

 



- Reference design: FEI4
- Current-to-voltage rail-to-rail DC output
- Very fast falling: End-of-Double Column Switches,
- Very slow rising: very weak PMOS and big resistor
- I2v amp: reuse the buffer in FEC4-P3 (designed by Jiangping)

Weak stage: modification on FEC4\_P3 buffer


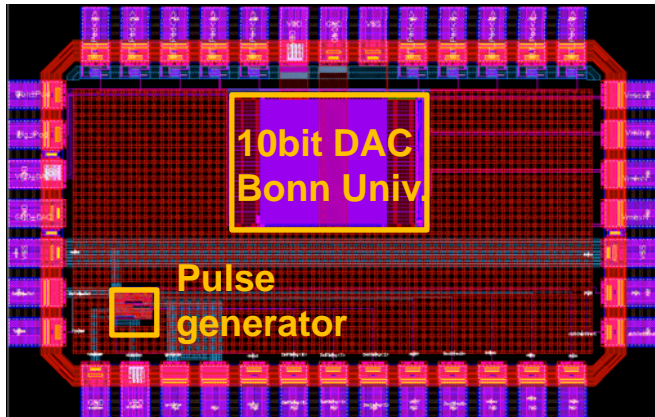
- Building blocks chip FEC4\_P3C
- Tapeout: Nov. 2010, measurement: March, 2011
- Size of chip:  $2.5 \times 1.5 \text{ mm}^2$
- Area of block:  $150 \times 150 \text{ } \mu\text{m}^2$
- 20 pads (maximum sets)





# Measurement for single block

  

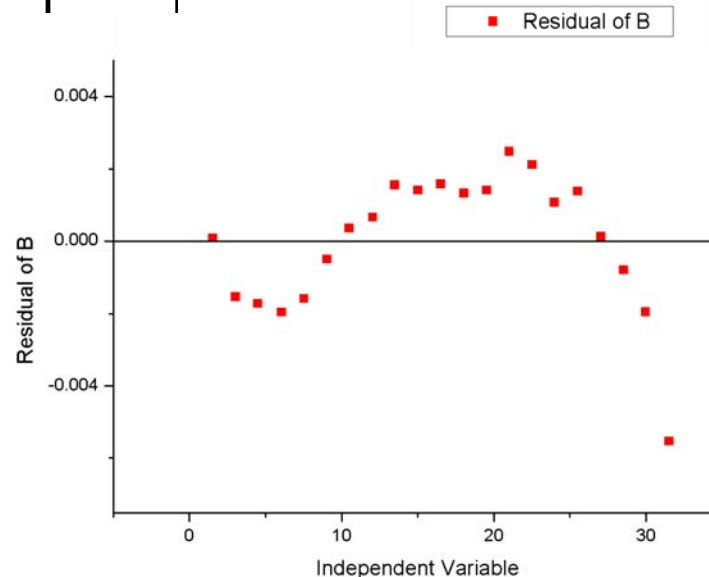 
- Falling time for charge injection:  $< 4\text{ns}$  @ 2ns stimuli pulse
- Rising time tuning:
  - Overlapped snapshots from four measured outputs with different tuning bits configuration( 001/011/101/111)
  - Showing rising time is tunable 20~400  $\mu\text{s}$
- Dynamic range: Better than 1.4V
- Linearity:  $< \pm 0.5\%$
- Similar results as in simulation




# FEC4 P3C & P1 combined system

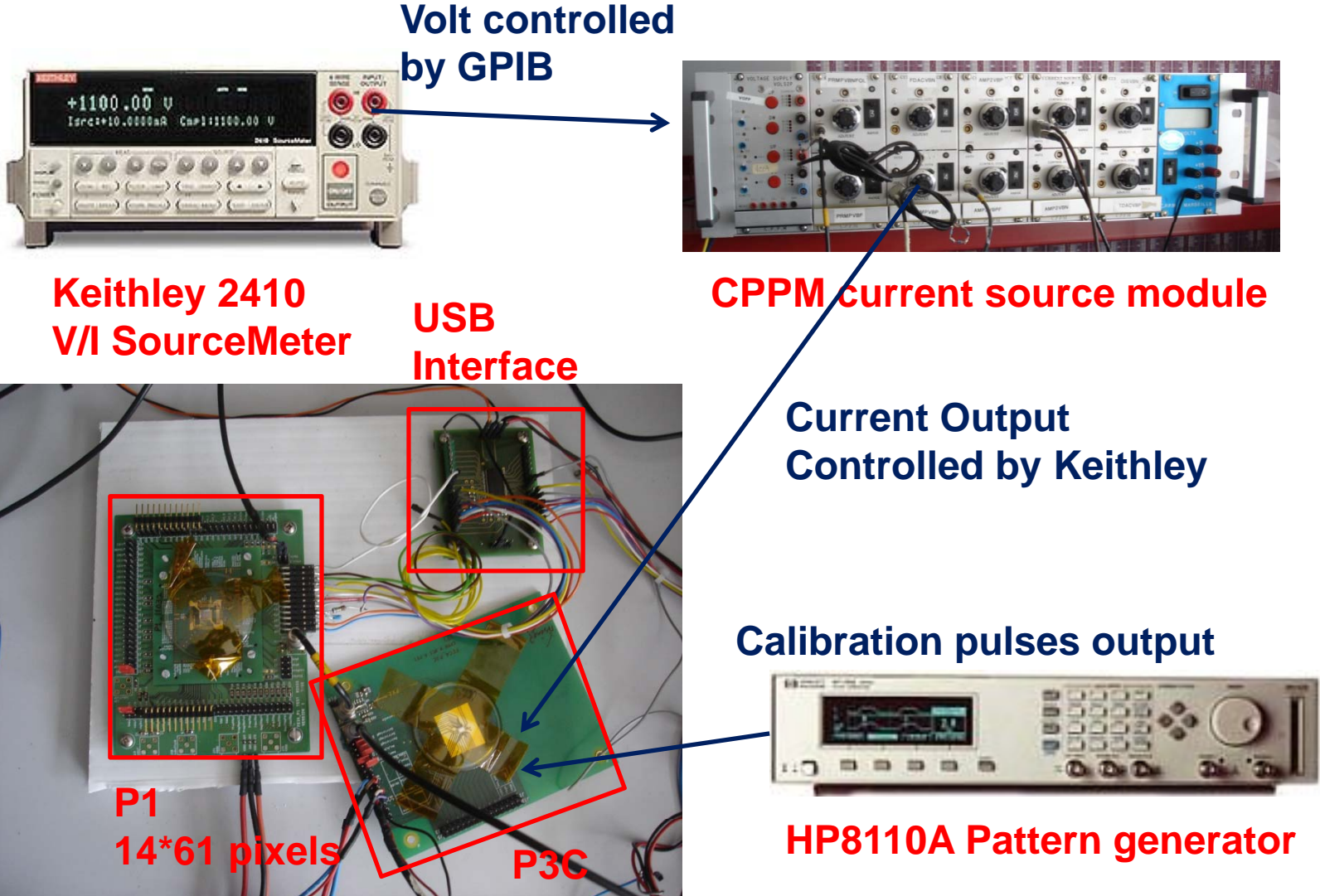 


# S-curve measurement

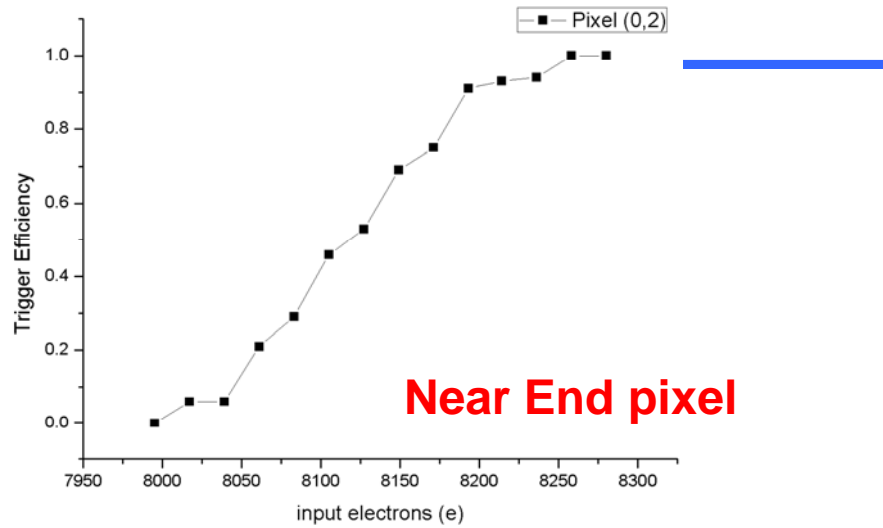

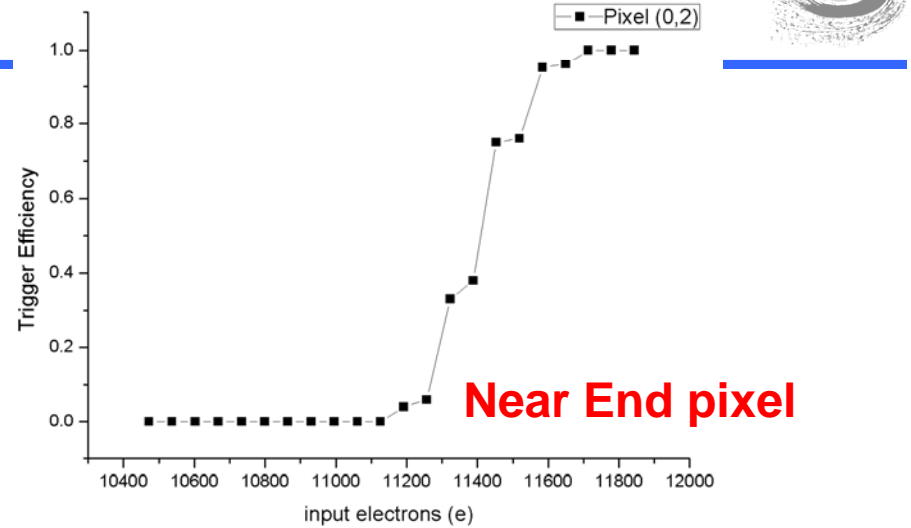
**Pixel (0,2) HP generator + P1**  
**Rms = 50e, 50% threshold = 8117e**



 **Pixel (0,2) P3C generator + P1**  
**Rms = 104e, 50% threshold = 11409e**





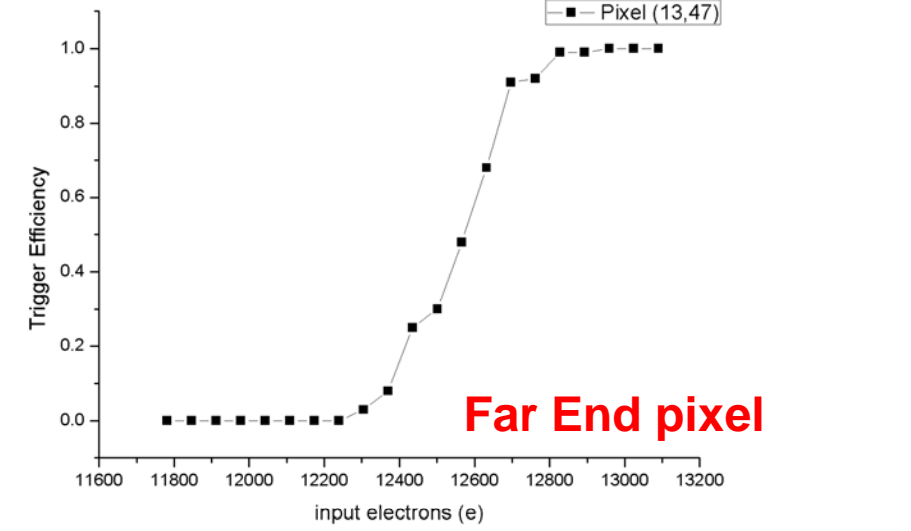**Pixel (13,47) HP generator + P1**  
**Rms = 95e, 50% threshold = 9454e**





**Pixel (13,47) P3C generator + P1**  
**Rms = 109e, 50% threshold = 12572e**

# Full chip scan image

  

HP generator + P1, **threshold** distribution

  P3C generator + P1, **threshold** distribution




HP generator + P1, **noise** distribution


P3C generator + P1, **noise** distribution




# Dispersion comparison

 

 
HP generator + P1, **threshold** histogram



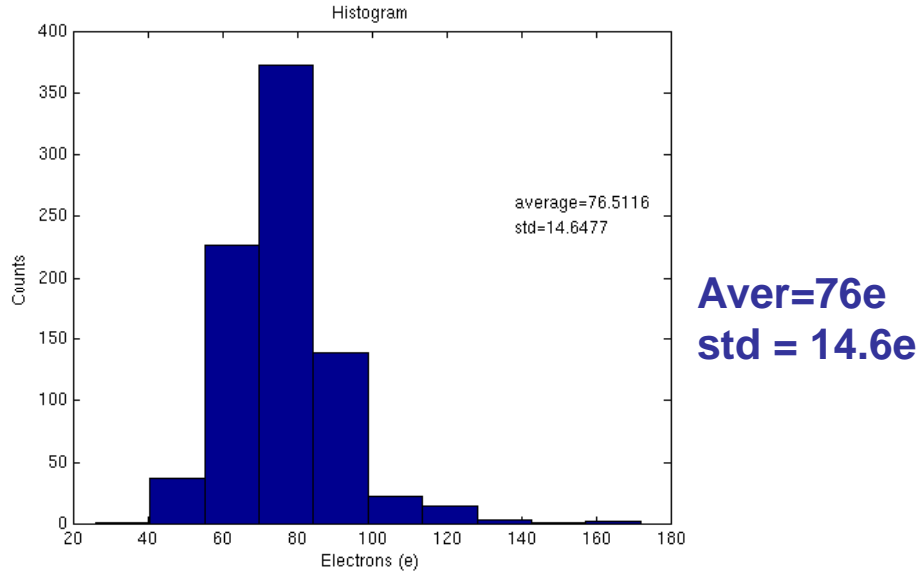P3C generator + P1, **threshold** histogram




HP generator + P1, **noise** histogram

 

P3C generator + P1, **noise** histogram

# Summary of the measurement

---

 

- **Single block**
  - **Functionality is good: fast falling, slow and tunable rising edge**
  - **Performance: linearity  $< \pm 0.5\%$ , dynamic range:  $> 0\sim 1.45$  V**
  - **Unterminated problem because of the very high output impedance, expected to be solved in the final internal version**
- **Combined with P1 pixel matrix load**
  - **P3C pulse generator is compatible with P1 load**
  - **No growing of threshold/noise dispersion was found**
  - **PCB connections a issue: reflections are hard to be eliminated – rms noise slightly increased**
  - **Expecting a better performance in final version if the generator is dwelled inside the chip**


# Details of Collaborations of 2010~2011

---




- **FEC4\_P3C pulse generator (W. WEI)**
  - Design
  - Single chip measurement result
  - FEC4\_P3C associated with FEC4\_P1 measurement
- **Other Designs and simulation:**
  - Design of power saving blocks for pixel unit (W. WEI)
  - Full chip functional evaluation of FEC4\_P3 (W. WEI)
  - Power-on-reset block (N. WANG)
  - Modification of the SEU latch (N. WANG)

# Design of the power saving blocks

 


- **Power consumption of Pixel: Analog 10  $\mu$ A, Digital 10  $\mu$ A**
- **FEC4\_P3 pixel: half size of FEI4, 2X amount – 2X power**
- **To save power:**
  - Design optimization (static)
  - Sleep – low power standby – wakeup – working – sleep (dynamic)
- **A most power consuming block: discriminator (4  $\mu$ A)**
- **Preamp output monitoring  $\rightarrow$  Wakeup pulse for Discri**
- **Design issue:**
  - Very large gain: Preamp output  $\rightarrow$  Digital level
  - Speed: Wakeup pulse to be faster than TOT output
  - Area: very limited space in the existing FEC4\_P3 design

 


# Full chip overall simulation and evaluation

---

 


- **Full chip overall simulation**
  - **Common simulation: configuration of pixels are preset, configuration phase ignored**
  - **Real case of operation: configuration → normal operation time consuming in simulation**
  - **Overall simulation by FastSpice (Ultrasim):**
    - **Work as in the real case**
    - **Evaluate all the bias settling**
    - **Evaluate the configuration process and compatiability with PUC**
  - **Debug: Problems of HitEn, ClrGlobal, LdEn... were solved**
- **Full chip power network layout evaluation**
  - **Power distributed as a non-ideal grid with para. R**
  - **IR Drop: Bias condition may vary from near end to far end**
  - **FastSpice (Ultrasim Power Network Solver) with estimated R from layout extraction, to evaluate IR Drop and bias of all pixels**

# Power-on-reset block

 


Designed by N. WANG

 
- **Reset signals generated on both of the rising and falling edge of power supply**
- **Hysteresis of 100mV**
- **Implanted to Chrt 0.13  $\mu\text{m}$**
- **Compatiable with both 1.5V and 1.2V supply**
- **Layout is ready, to be embedded in the next tapeout**




# Modification of DICE latch for SEU

 

by N. WANG

 

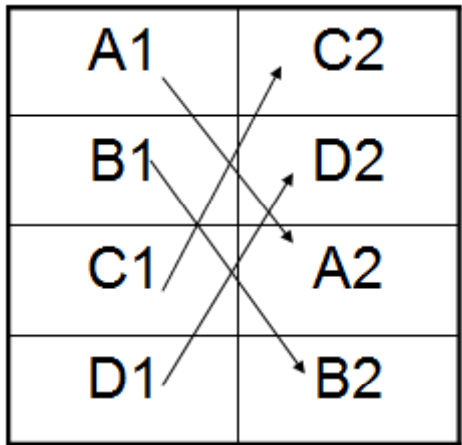
- Included two latches in each cell
- SEU is restricted in one latch, the other one remains unchanged
- Capable of anti-SEU
- **Modification:**
  - Based on the 4-latch cell
  - Further separate the complementary node, enhance the anti-SEU capability
  - Layout size shrunk
- Expected to be evaluated in the next tapeout



4-latch cell

## Summary and future

---


 


- **Collaboration between CPPM and IHEP was successful and fruitful in the past few years and will continue**
- **IHEP would like to contribute more on the coming ATLAS silicon pixel upgrades especially on the front-end readout chips**



**Thank you !**


# Functionality

  


## Output specification:

 1. Very fast falling edge -> charge injection (less than 2.5ns @ 0.5ns input rising edge)
2. Very slowing rising edge -> baseline restoration (3-bits tuning, 20  $\mu$ s ~ 500  $\mu$ s)

Ringings detected due to the unterminated cable  
Expected to be eliminated if dwelled inside the chip




 falling edge ~ 4ns @ 2ns input rising edge





Rising edge ~500  $\mu$ s @ 25uA input current





# Performance

 

- **Rising time tuning:**
  - Overlapped snapshots from four measured outputs with different tuning bits configuration( 001/011/101/111)
  - Same input current 20  $\mu$ A, output 1 V
  - Same time scale 40  $\mu$ s/div
  - Showing rising time is tunable 20~400  $\mu$ s
  
- **Dynamic range:**
  - Best case: fastest rising: 1.45 V
  - Worst case: slowest rising: 1.3 V
  - Same result as in simulation

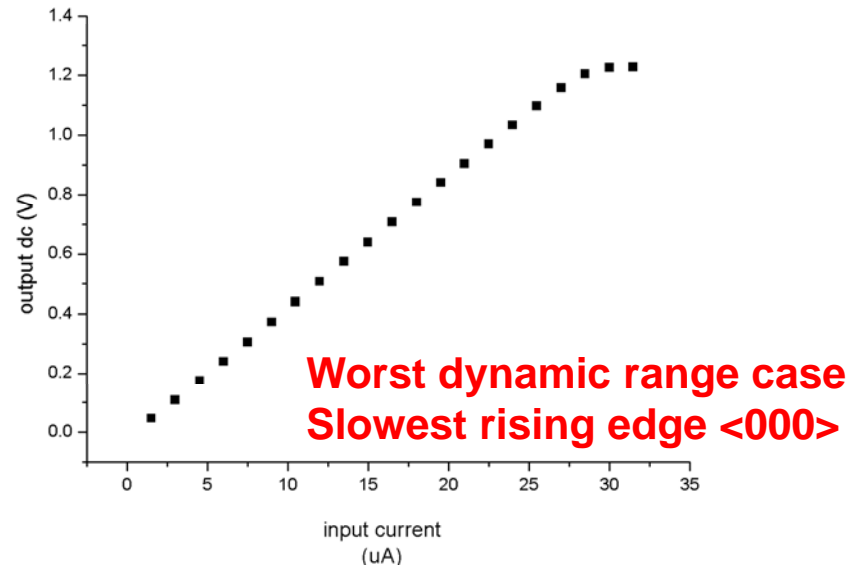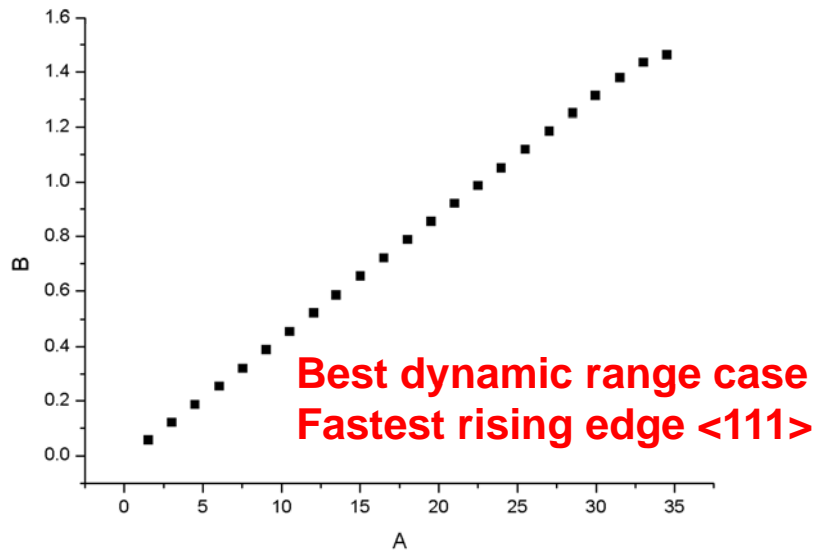


# Linear fit result

 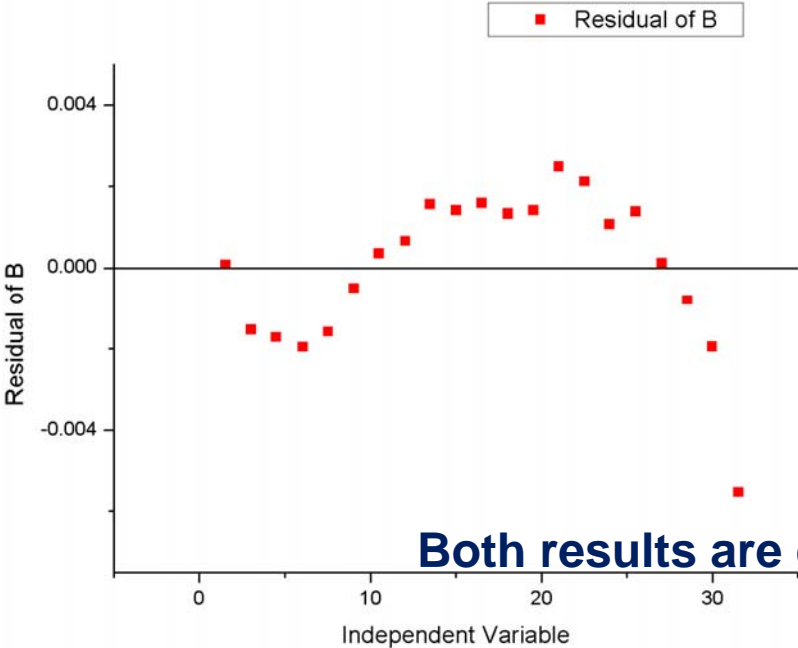  

Both results are quite similar to simulation

# Design and simulation

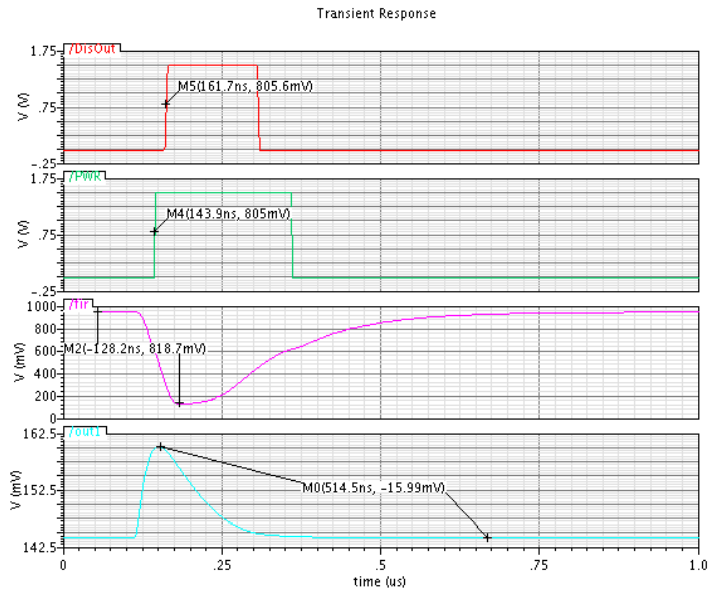

- **Transimpedance**
- **Equivalent:**
  - DC close loop (operating pt.)
  - AC open loop (large gain)
- **Optimization: para. & corner**
- **Discriminator: modified for fast wakeup and settling**
- **M.C. sim: explore the full corner range**

