 


CEPCPix1: A HVCMOS pixel sensor for CEPC experiment

Hui. Zhang, Ruoshi Dong, Ivan. Peric




55nm High Voltage CMOS Technology

- We have submitted the dedicated CEPC design in August with 55nm HVCMOS technology
- An area of 1.25 x 1.25 mm is reserved for our design
- The 55nm logic technology combines improved performance and reduced power consumption with increased design possibilities and cost efficiencies.
- The maximum voltage for HV transistors is 32V
- Low voltage power supply is 1.2V
- Deep n-well to p-substrate should have higher breakdown
- Metal layers 1 – 5 can be used for fine pitch routing
- There are three more thick metal layers, suitable for power


HVCMOS introduction

- Sensor and readout electronics could be produced in one chip.
- High reverse bias accelerate the charge collection by drift.
- High reverse bias creates thick depletion region between deep n/well and p substrate
- N-well/p sub diode works as sensor. Electronics embeded in deep n-well.
- Substrates from $300\Omega\text{cm}$ to $\sim 20\text{k}\Omega\text{cm}$
- Could be produced in standard technology, eg. 180nm, 65nm, 55nm.
- Radiation tolerance.

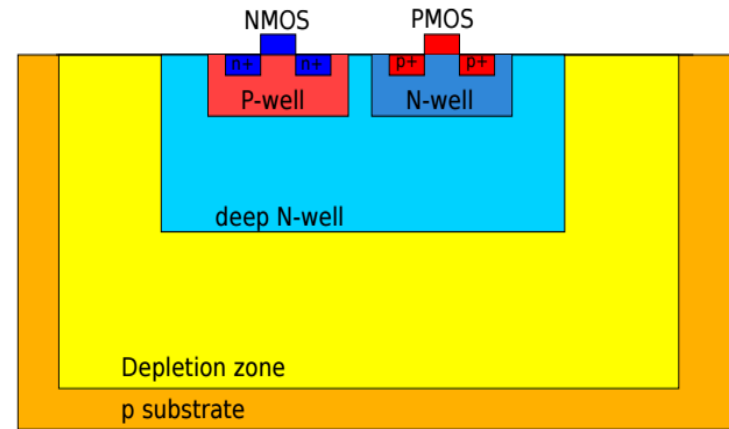


CPECPix1: Overview

- Timestamp measurement:
 - Two columns use digital encoding of pixel address and 24 columns use analog encoding of addresses
 - leading & trailing edge timestamp
 - Address double check for hit consistency
- Digital Readout FSM:
 - Polling readout of 4 hit channels
 - Compatible with test mode
- Digital Interface
 - Synchronous serialized slow output
 - Asynchronous serializer
 - SPI configuration

 


CPECPix1: Pixel Electronics

- Pixel electronics contains
 - Sensor diode
 - Charge Sensitive Amplifier (CSA)
 - CR filter
 - Comparator
 - RAM and tune DAC
 - Output stages

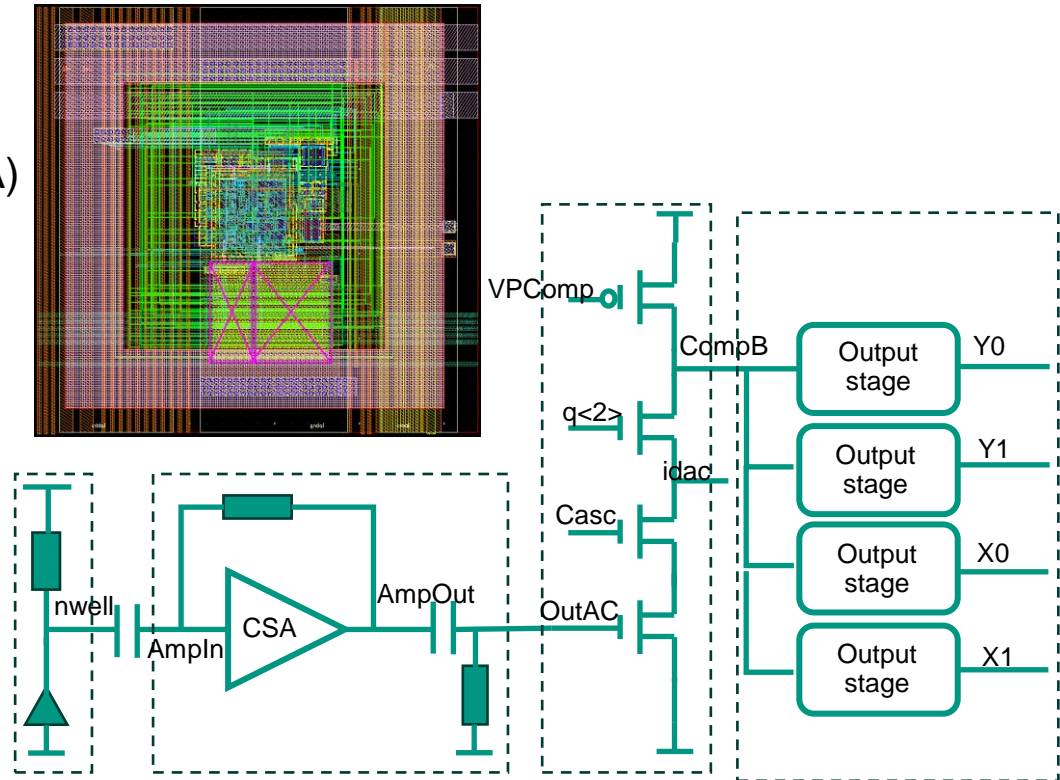


CPECPix1: Pixel Electronics

- Work principle
 - Charge collected by pixel n-well
 - Converted to voltage signal by Charge Sensitive Amplifier
 - Analog voltage pulse shaped and converted to digital signal by comparator
 - Output stage generates current
 - Current is sent via address line to the transimpedance amplifier outside matrix
 - Address lines have constant potential – no cross talk

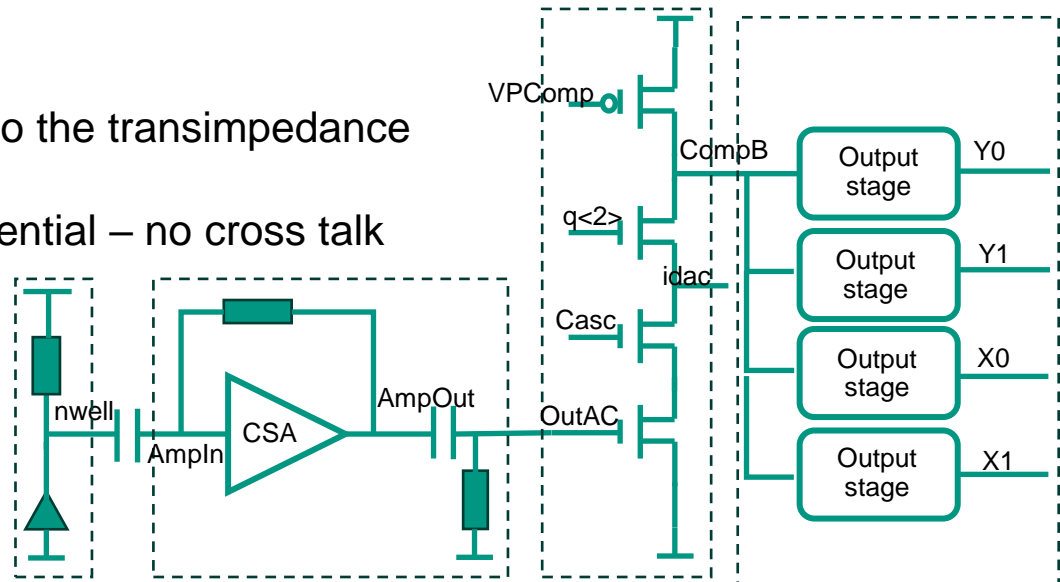


CPECPix1: Address bus

- Compare different address buses.
 - Less address buses as before version
 - Number of address buses \ll number of pixels

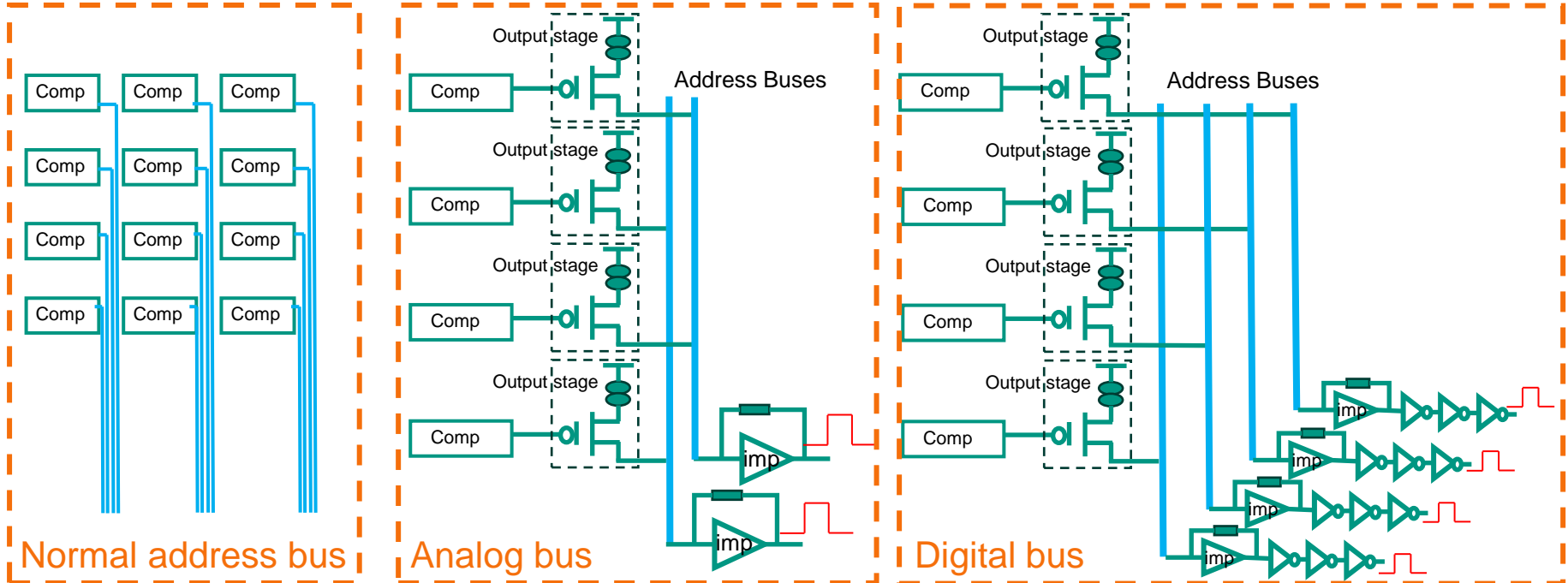


CPECPix1: Address group (Analog Part)

- Since the pixels are small, we expect 4-pixel clusters
- If we had just one hit bus line, we could not measure the amplitude of 4 pixels of a cluster
- Now I explain analog encoding
- To allow amplitude measurement of 4 pixels in a cluster, we foresee 8 address lines for whole matrix (2 per group for x and y) – AY, AX, BY, BX, CY, CX, DY, DX
- Addresses are encoded as amplitudes
- The pixel output stages are connected alternately to A, B or C, D

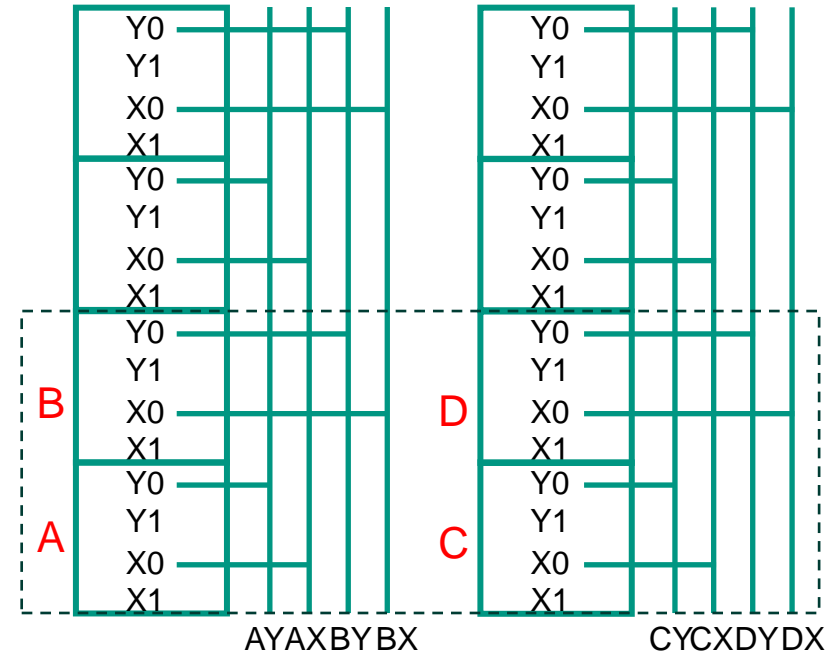



CPECPix1: Address group (Analog Part)

- For example: four columns of pixel
- In different columns the pixel A_x has different amplitudes and in different row A_y has different amplitudes.
- The address encoding is done in the way, that if 4 neighbour pixels are hit, the received code corresponds one of the pixels
- In the case of 4-pixel clusters, by examining the A, B, C, D address signals we can obtain pixel row and column by measuring amplitudes and signal amplitudes by measuring pulse width.

 

CPECPix1: Address hit bus to pad connection



- Analog hit address lines go to top of the chip and then connect directly to rightside pads.
- Now I explain digital encoding.
- We use 4 bit digital signal (address bus) to encode pixel address. We have 4 groups of pixels A B C D and every group has own 4 bit address bus.
- Digital address lines are connected to voltage level shifter and then to the synthesized digital part.

  

CEPCPix1: Digital Readout

- Timestamp measurement
 - Timestamp bin size 5 ns
 - Make an OR logic on 4 address bit input
 - Hit pulse width ~ 1 μ s
 - Set a detect max length parameter
 - Ignore too long pulse
 - Set an address check position parameter
 - Double check address at leading edge
 - Error bit for overlapped or too short pulse
- Submerge FSM until detect max length
 - Shield spurs hit, control data rate
- Output fifo for each timestamp channel
 - 37 bits fifo bit width

| | | | | |
|-----------|-----------|-------------|---------------|----------------|
| error_bit | addr[3:0] | hit_id[7:0] | lead_ts[11:0] | trail_ts[11:0] |
|-----------|-----------|-------------|---------------|----------------|

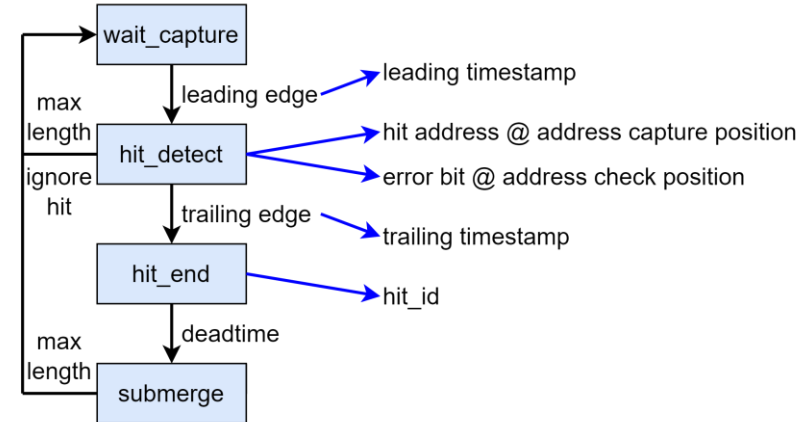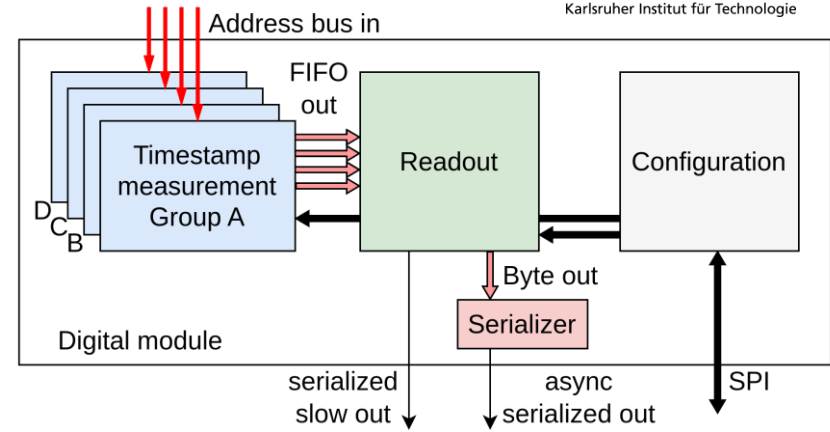


CEPCPix1: Digital Readout

Data readout

- Polling readout from 4 timestamp fifo
- Mode select
 - Hit data
 - Test pattern: fixed or counter
- 48 bits data package to readout interface

Readout interface

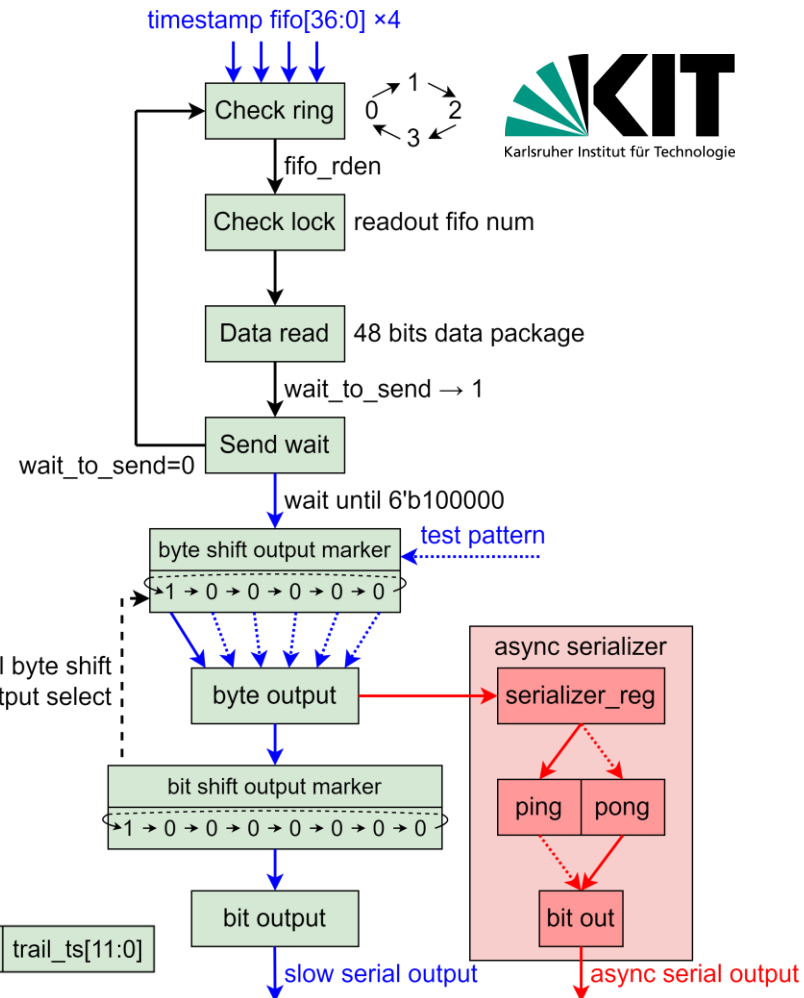- Mutual exclusive output selection
- Slow serial output
 - 48 to 8 to 1
- Asynchronous serializer output
 - 8 to 1 serializer
 - Ping-pong register to cross clock domain




| | | | | | | | | |
|-------------|------------------|--------------|------|-----------|-----------|-------------|---------------|----------------|
| Header[5:0] | pack_marker[1:0] | chn_num[1:0] | 1'b0 | error_bit | addr[3:0] | hit_id[7:0] | lead_ts[11:0] | trail_ts[11:0] |
|-------------|------------------|--------------|------|-----------|-----------|-------------|---------------|----------------|

Simulation results

Transient Response

| Name | Vis |
|-----------------------|-----|
| VT("/*IO/*-0>/net11") | ☉ |
| VT("/*IO/*-0>/net13") | ☉ |

 

← AmpOut

← OutAC

← CompOut

← Address Bus

← Level shift Output

Conclusion

- HVCMOS introduction and 55nm HVCMOS technology
- CEPCPix1: Analog Part
 - 4 output stages in each pixel electronics
 - Address lines have constant potential → no cross talk
 - Special design in pixel to reduce analog and digital buses
 - Group 4-pixel cluster and use different amplitudes of pixel A in each group to cope with charge sharing
- CEPCPix1: Digital Readout Part
 - Hit pulse from address bus capture rising and falling edge of time stamp
 - Several design to solve overlap problem
 - Two mutually exclusive interface (asynchronous interface is 8 times faster than main clock)

Thank you!