


Considerations for Serial Powering

Mitch Newcomer

University of Pennsylvania

Notional Serial Power system

SP Advantage = recycle Module Current 8X

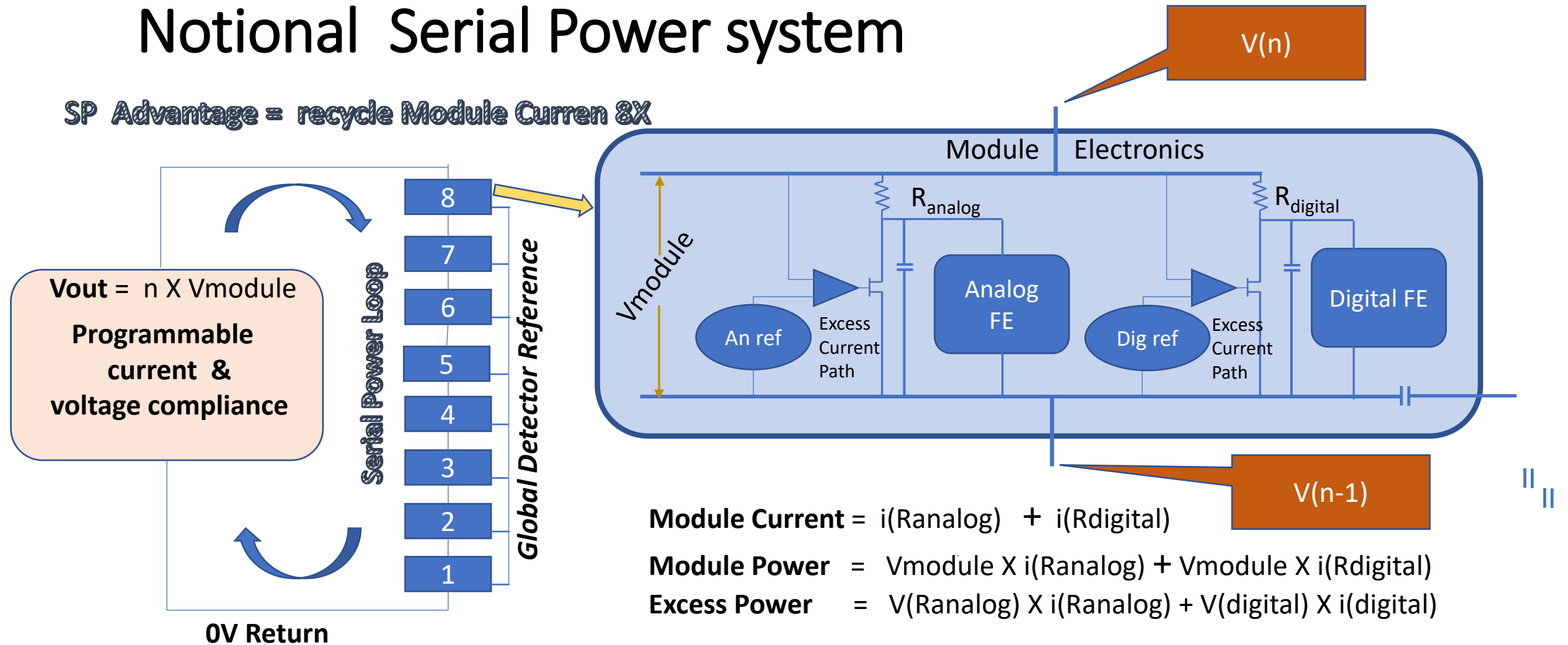

$$\text{Module Current} = i(R_{analog}) + i(R_{digital})$$

$$\text{Module Power} = V_{module} \times i(R_{analog}) + V_{module} \times i(R_{digital})$$

$$\text{Excess Power} = V(R_{analog}) \times i(R_{analog}) + V(digital) \times i(digital)$$


Minimum Loop Current -> **Set by Highest Consumption SP Element** + variations within the loop. (Modules in a loop may have widely varying occupancy eg. along a barrel stave for instance.

Serial Power Implementation Details to consider


- **Number of parallel devices in a voltage Step**
- **Uniformity of Occupancy** along Serial power step especially important for digital logic where power consumption is a $f(\text{activity})$
- **Real time local monitoring** within a step
 - *Can the LDO within the ASIC be externally addressed / controlled?*
- **Realistic Operational Modes:**
 - power up / while powered / power down
 - Ramp UP/Down Speed
 - One of several ASICs powered down ...at startup?during a run?
 - Architecture for control / data signals within a step

Module organization within a Serial Step


Single

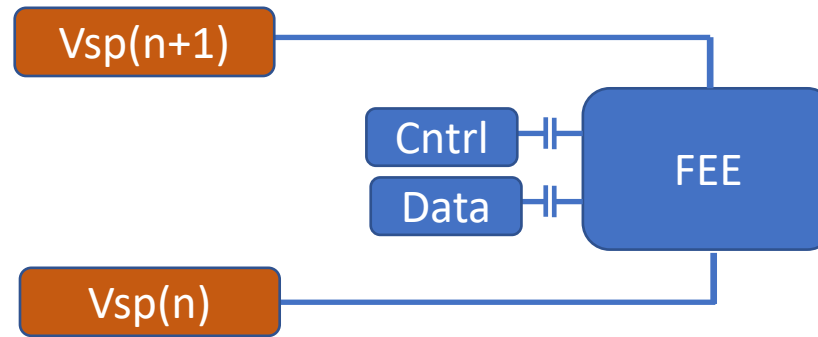

Parallel Identical

 

Function Specific

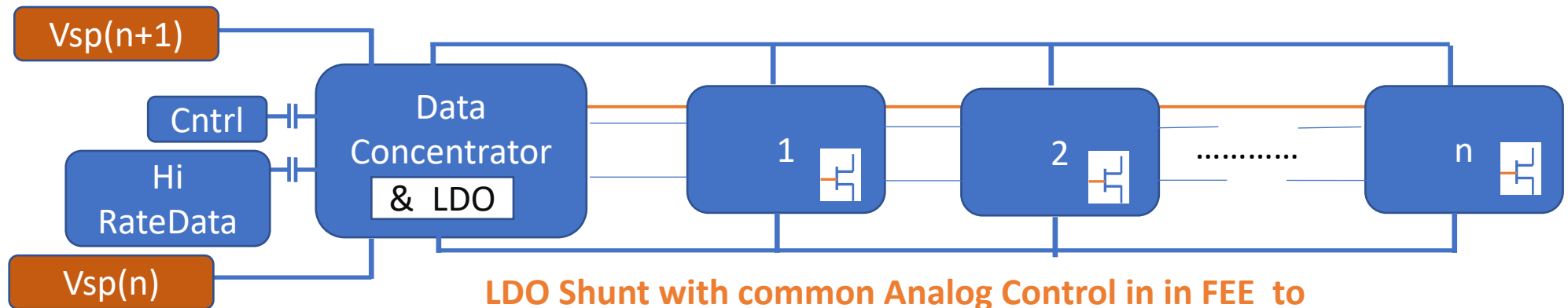

LDO Shunt with common Analog Control in in FEE to ensure even heat distribution.

Advantages of a Serial Powered System

The **ADVANTAGE** → **Material Burden benefit realized by reduced gauge supply & return cables sufficient to provide a single module with power a SP loop of 'n' modules by increasing the loop voltage 'n' times instead of the current.**

→ **Simplicity of a nearly DC control structure..** LDO for each voltage with consideration for Maximum power excursions capacitive filtering for instantaneous current deviations eg clocked logic or trigger response

→ **No clocked switching circuits** to generate pattern noise Or Switching Rate related heat.

→ **Possibility of aggregating many module consumers in parallel** where detector topology permits.

- **Evens out SP voltage step current loading.** Allows the SP voltage step to take advantage of security in numbers when single units have deviations or may need to be turned off ..
- But this is not magic, simply parallel powering so there is no wire gauge material reduction advantage.

Serial Power Disadvantages

Serial power is an *unfamiliar* approach to module powering



- **Serial power Loop Supply** is **crucial** for fault free operation. Requires a somewhat novel, programmable constant current, programmable voltage compliant approach. An Accelerator driven feed forward control could be advantageous here.
- Communications need to be capacitively coupled **requiring balanced code or receivers with hysteresis and startup procedures.**
- To maintain high levels of operability Module failure modes need to be addressed. Current flow in the SP loop must be maintained. A serial step can be taken out of the loop by shorting the Module with a current bypass element. The time frame is important.
 - **Slow changes in voltage steps can result in overheating & damage to current shunt elements.**
 - **Fast changes can cause cascade communication failures in the Serial Loop**

Engineering A stable power efficient Serial Power System


Current Uniformity in the Loop Maximizes Efficiency

- Start with the ASIC. ***Minimize data taking power variations.*** For system stability it may be best to shunt unavoidable trigger related readout current in quiescent operational states to avoid data taking spikes.
- Choose loops with common occupancy levels where possible.
- Design with care the reference potential system for proximal read out loops.
- Isolate Communication in Serial Loops with capacitive or optical communication schemes if TID and SEU effects are manageable.
- Co-design a SP Supply with FB from the serial loop and potentially spigots for Feed Forward from the Accelerator control room to provide tuneable increased current during predictable data taking spikes.
- Design in connection redundancy & provision for controlled failure behavior.
- Make sure powered down modules don't present low impedances on bussed communication lines.

ATLAS Pixel Experience with SP systems

Power Requirements



Preliminary	L0		L1		L2-L4	
power parameter for 1 chip	Simulation (L0)	Measurement	Simulation (L4)	Measurement	Simulation (L4)	Measurement
Analog Periphery [mA]	143	110	107	110	107	110
Analog Matrix [mA]	614	640	461	538	461	430
Digital Periphery [mA]	225	220	225	220	225	220
Digital Periphery Activity [mA]	25	50	5	20	5	10
Digital Matrix (Idle) [mA]	403	460	403	460	403	460
Digital Matrix Activity [mA]	113	120	39	80	39	40
Analog Total [mA]	757	750	568	648	568	540
Digital Total [mA]	766	850	672	780	672	730
Total	1523	1600	1523	1428	1523	1270
Total + Overhead (20/10%)	1751.9	1845	1431.2	1648.8	1431.2	1470
Module Current		5535		6595.2		5880

*measurement at room temp.
 ** in yellow, conservative estimates

- This table represents an upper boundary
 - Maxes out power envelope of detector
- Difference in layers due to digital activity and analog preamplifier current
- Power requirements drive BOM choice for Flex hybrid
- Estimates can be updated (lowered) after Module pre-production

Timon Heim
4
FE Chip PRR

Serial Powered Modules with Multiple Parallelpowered ASICs





Powering

Serial powering:


- Chips in modules are powered in parallel
- Modules are connected serially and powered with a constant current
- Shunt in regulator will burn excess current not consumed by the chip core to have each chip act like a resistor

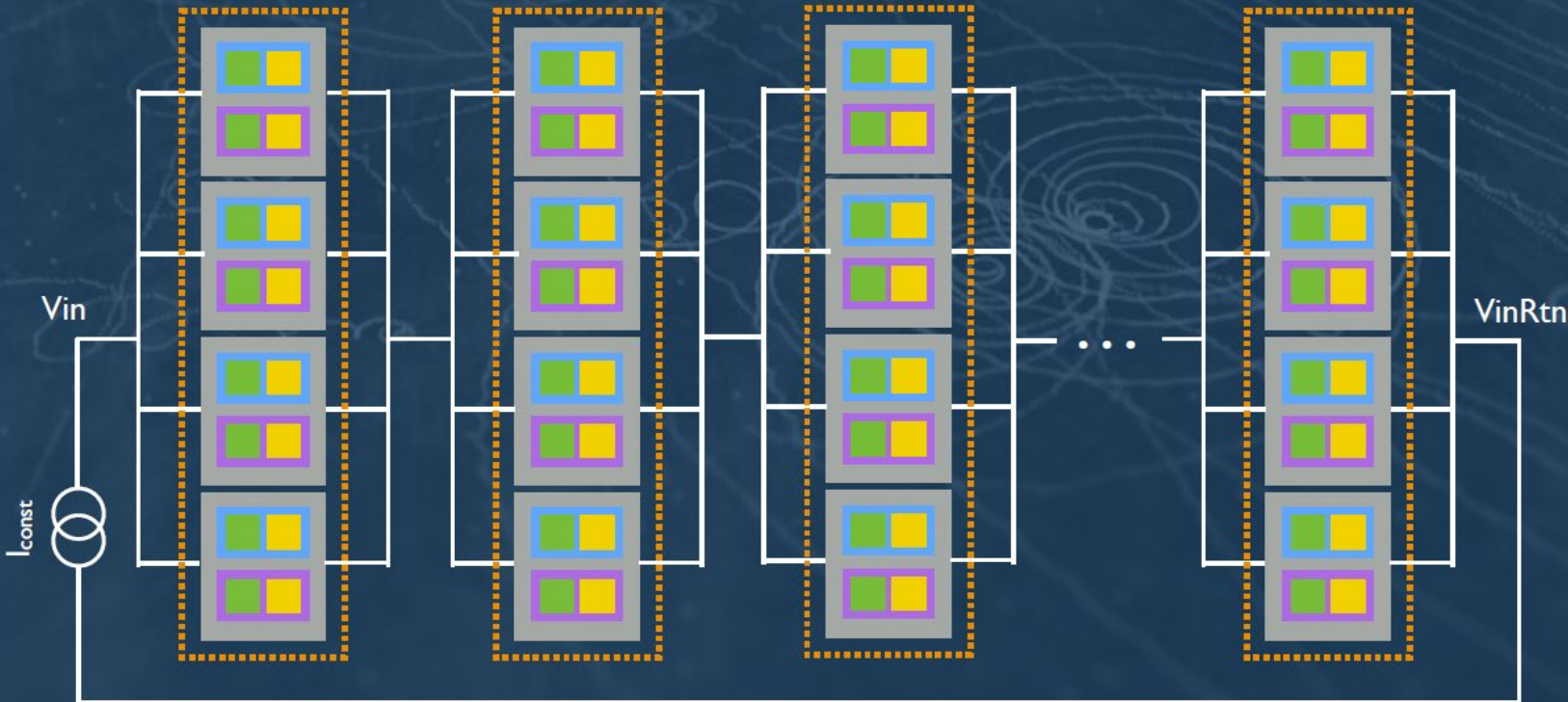 - Shunt
- Core
- Analog regulator
- Digital regulator
- ITkPix chip
- Quad Module




Each ATLAS Pixel Chip has a Analog & Digital Shunt LDO

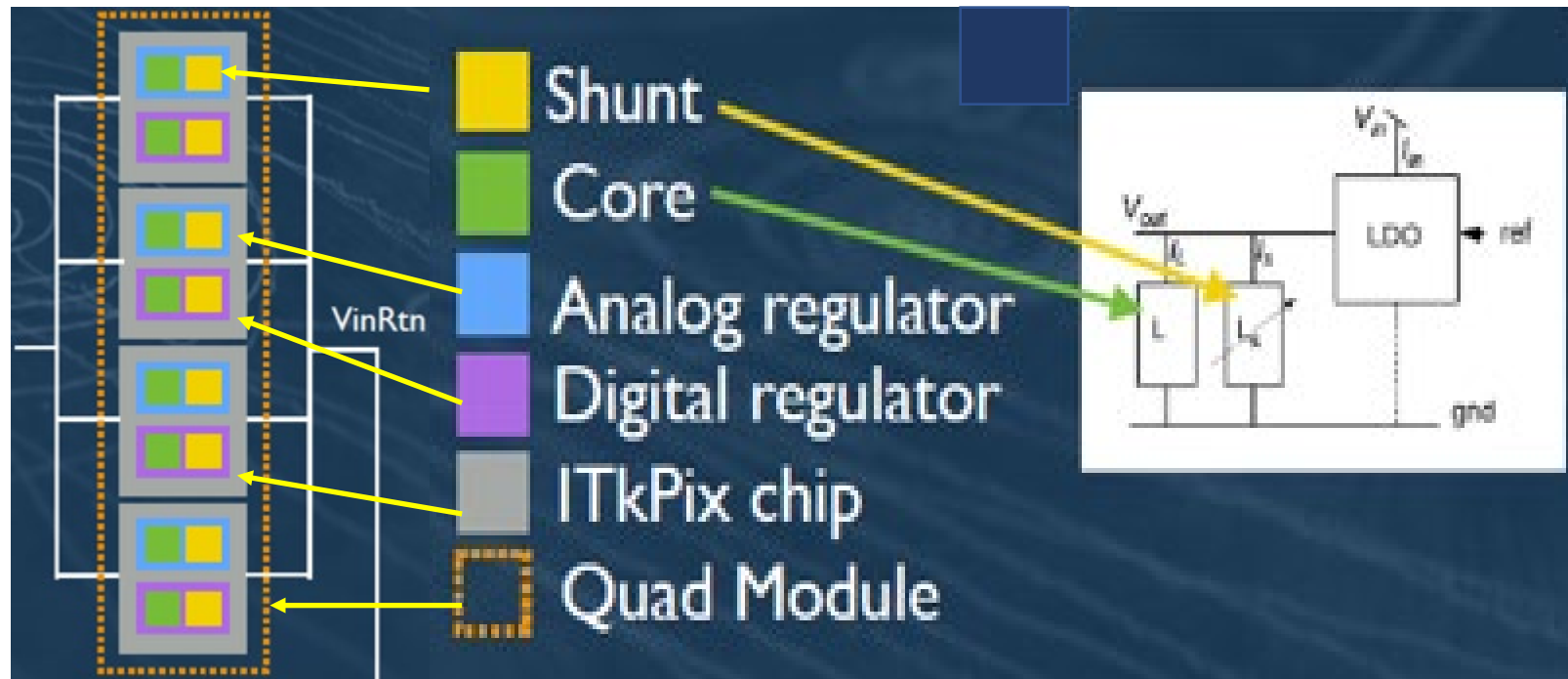A Shunt is required to equalize current in each serial step



Powerup Characteristics

SLDO Parameters

 

Variables:

- Voffset: voltage offset controlled by voltage drop through **external resistor** from the **current reference**
- Reff: given by current through **external resistor** from **Vin** to **local GND** multiplied by **current mirror**

Important aspects for Modules:

- Module through current is split over all chips within
- Current split is given by the equivalent impedance of the chip
- Goal: **chip impedances supposed to be as equal as possible to ensure equal current sharing**
- Unequal current sharing could lead to a chip not having enough current

Methods to ensure equal Current split:

- Voffset sharing (Voffset connected between all chips in module)
- Equalize resistance on Vin and VinRtn nodes to avoid unequal voltage drops
- High precision resistors (0.1%)
- Main uncertainty on current sharing is current mirror multiplication factor (k-factor) -> have sufficient cut during wafer probing

IV curves show the operating current Stability/Efficiency




RD53A PLANAR SERIAL POWERING CHAIN – MODULE IV CURVES

- Example: Module SPQ14
- $V_{IN_A,D}$ tied together on flex
- $> V_{IN}$ nearly same for all SLDOs
- **Good agreement with expectation**

Vin controlled by SP
Loop supply

Spice	Full SPQ14
Slope	0.15 V/A

 

Efficiency of Serial Power Depends on current Overburden




RD53A PLANAR SERIAL POWERING CHAIN – MODULE IV CURVES

- Example: Module SPQ14
- $V_{IN_A,D}$ tied together on flex
- $> V_{IN}$ nearly same for all SLDOs
- Good agreement with expectation

Loop Supply Current
Determines Efficiency

Spice	Full SPQ14
Slope	0.15 V/A

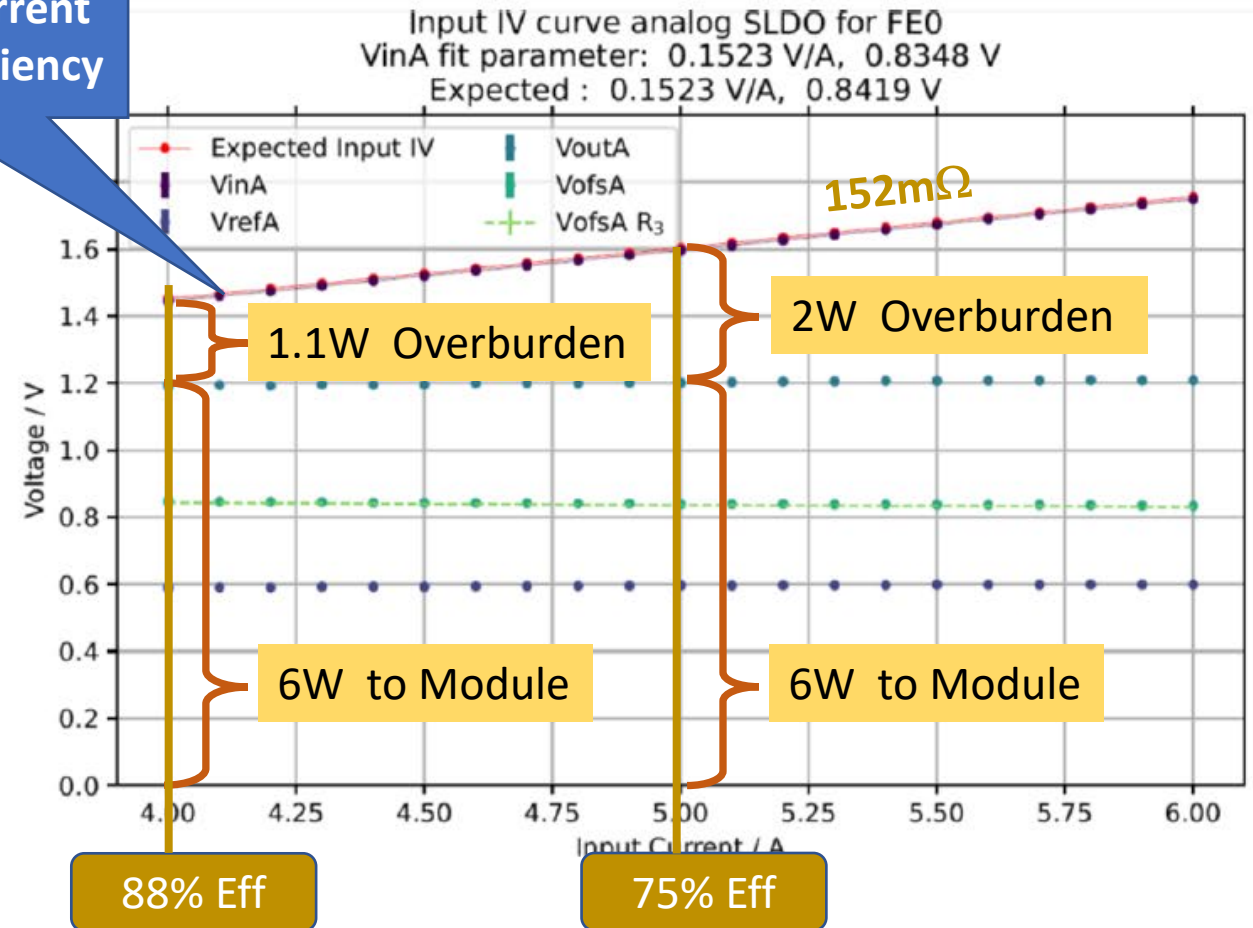


CMS pixel Readout Chip * CROC

- Part of the RD53 joint CMS and ATLAS collaboration to design the pixel electronics of the experiment upgrades for the HL-LHC.
- Designed in 65nm CMOS technology, features 1.5×10^5 pixel channels and
- Consumes about 8 – 10 μA per channel.
- Current per chip is ~ 1.5 A, with a supply voltage of 1.2V.
- Shunt-LDO (SLDO) constant current drain in time, independently of the chip power consumption
- Hit rates of 3Ghz/cm² and TID of 500MRad
- Serial powering scheme to provide the ~ 60 kW required by ~ 4000 modular units.


Total current at 1.2V = 50kA

* Jinst 2024 JINST 19 C01056 **Rudy Ceccarelli**, 16th Topical Seminar on Innovative Particle and Radiation Detectors

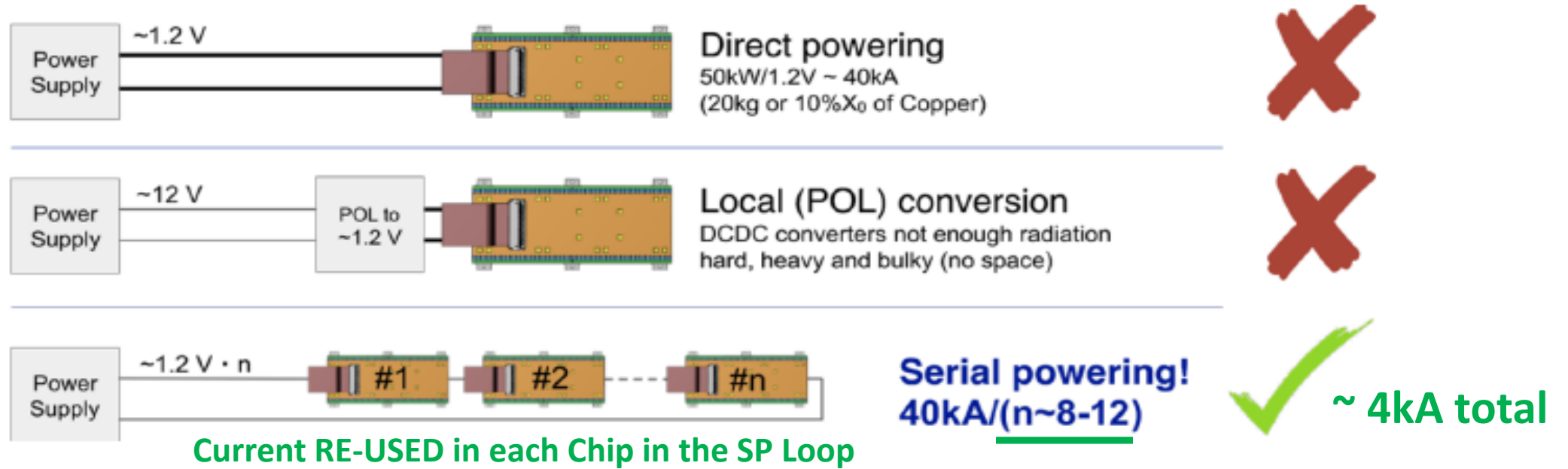Evaluating the Powering scheme for the CMS Inner tracker



 10 Step CMS CROC Serial Powering Test Setup with a Mix of 3D and Planar Pixel Sensors



Pixel Performance comparison under Serial Power

Serial power step Position 1, 6, 10 of 10 total


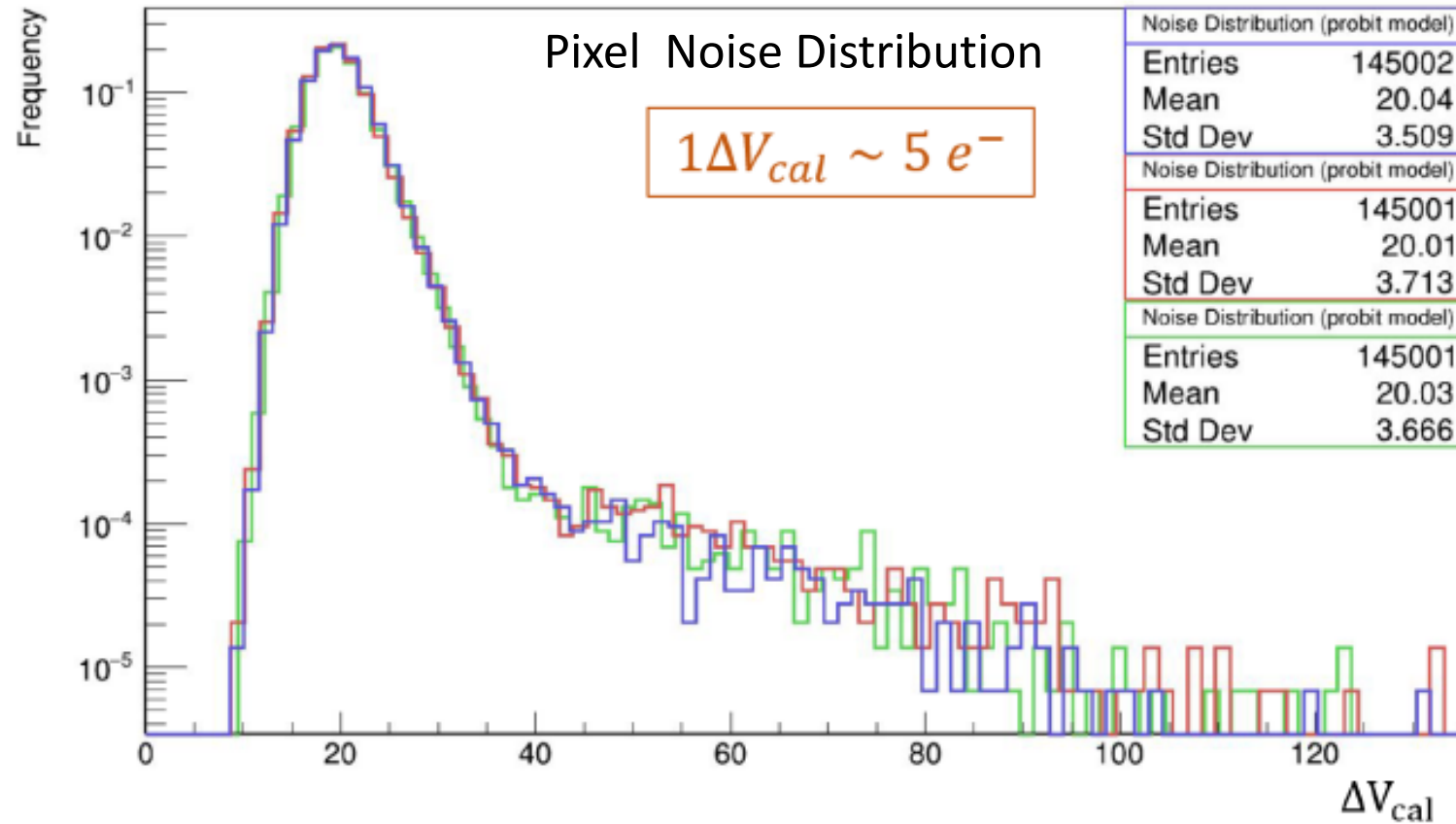


Figure 8. Pixel noise distribution in ΔV_{cal} units (where 1 ΔV_{cal} corresponds to approximately 5 electrons) of the 3D CROC module under test in three different positions of the serial powering chain: blue is the first position, red is the sixth position and green is the tenth position. No significant differences can be observed.

Other tests performed in CROC prototype SP Chain



- Powering up and data taking with some parallel powered ASICs disabled. Demonstrated stable operation with shunts taking up the load of unpowered ASICs.
- **Missing discussion about live time failure modes.**

Work in Serial Powering in DRD 7.1b

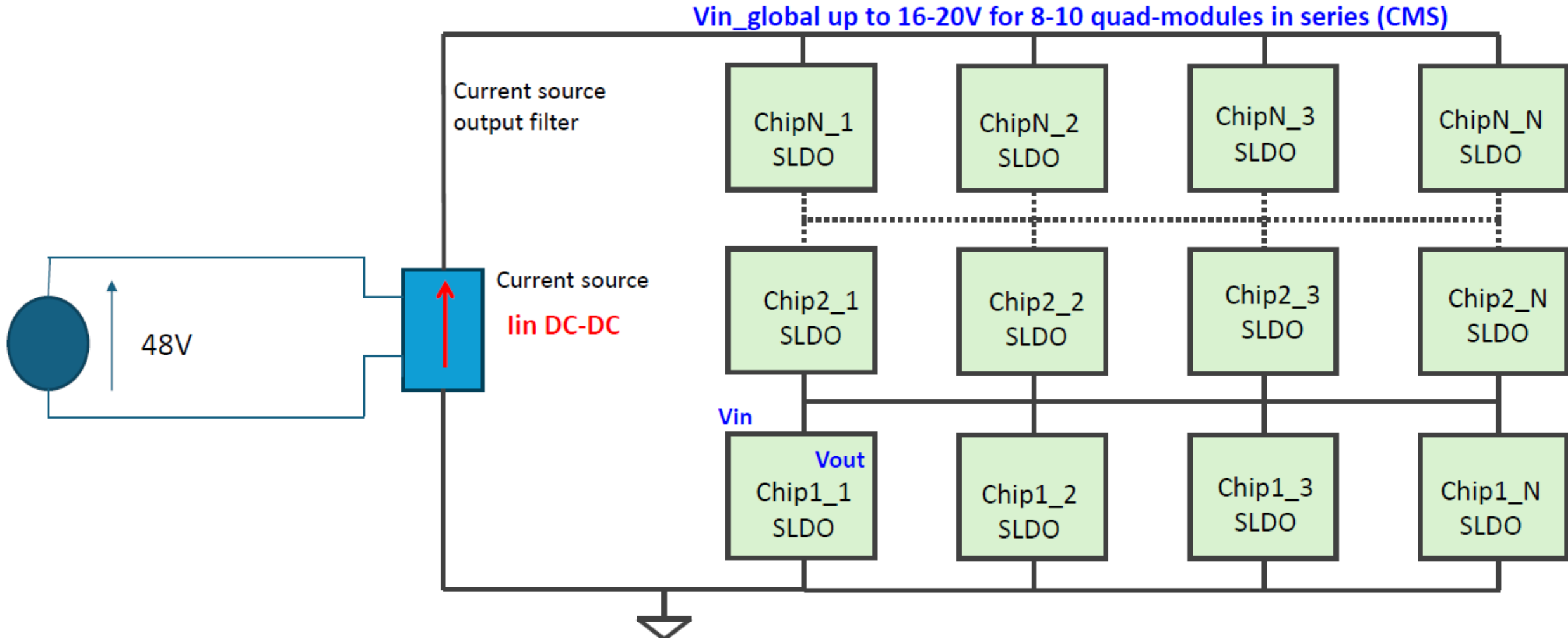

First SP Designs in 28nm process..

Shunt-LDO Design in 28nm

 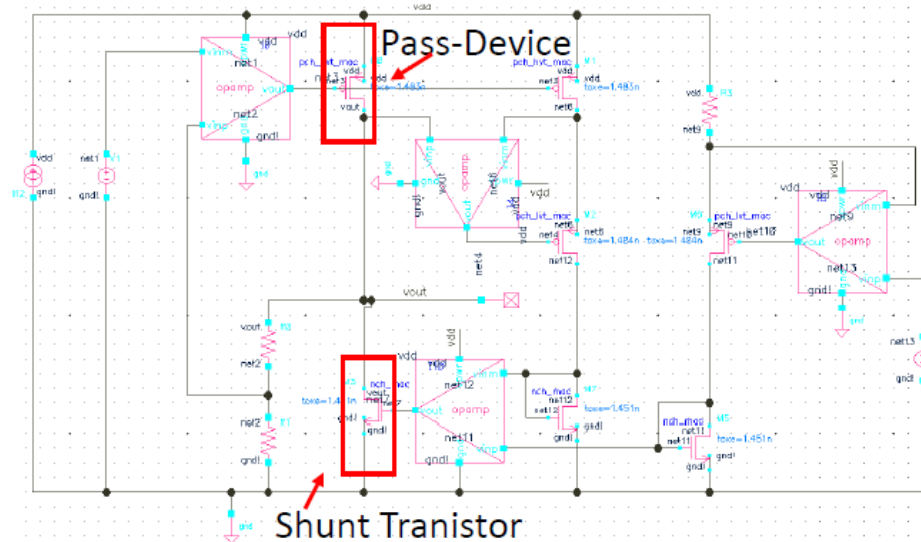



- First simulation studies performed in 28nm based on Verilog-A amplifier models
- Devices types and dimensions studied for shunt and pass-device
- Studies show SLDO thin-gate oxide core transistor implementation feasible in 28nm
- Technology limits maximum input voltage to 1.8V with overvoltage tolerant design (2V @ 65nm)
- Full transistor level implementation ongoing

GaN based power converter for Serial Powering


- The main goal of this task is to assess the feasibility of utilizing GaN- based DC-DC converters (current source) for serial powering applications.
- Several critical issues have been identified to optimized the design of these units
 - Design implications associated to GaN switching
 - High frequency (MHz) and short transition times (ns)
 - Precise Duty Control & deadtimes (High Resolution PWM modulator)
 - EMI filter design : Filter embedded in the PCB & magnetic components
 - Radiation hardness
 - Modular /Multiphase concept
- Several activities focused on the development of 200W / 2MHz GaN-based DC-DC have been carried out
 - **Design & Develop a preliminary prototype, which includes (2023)**
 - **Perform a performance evaluation, encompassing efficiency and EMI testing (2024)**
 - This evaluation will also involve combined EMI testing in radiation environments (on going)
 - Design printed circuit boards (PCBs) that incorporate embedded filters and magnetic components.
 - Design & develop a new prototype based on a modular concept, incorporating identified improvements.(2025)

GaN based power converter for Serial Powering

 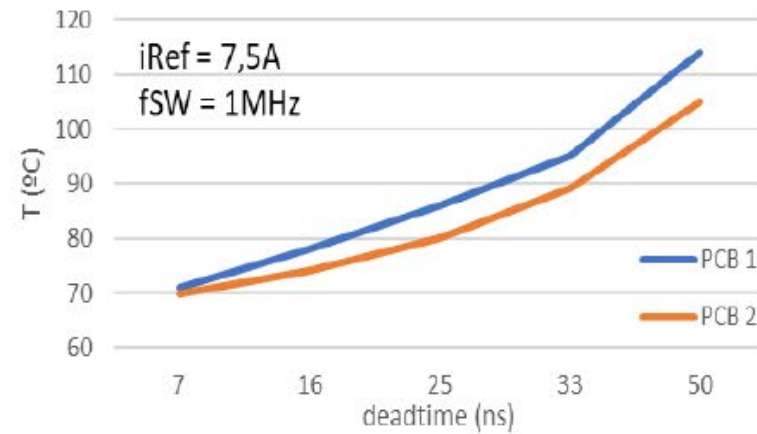- The performance assessment of the preliminary prototype is almost finalized.





 - The preliminary prototype was also tested on a real serial power chain during the noise Transfer Function characterization of 1x2 RD53A modules equipped with 3D sensors (IMB-CNM Barcelona) – CMS IT – Phase II



GaN based power converter for Serial Powering

- The EMI evaluation of the prototype was conducted using a specialized setup developed under the AIDAINNOVA project.
 - The setup is portable and fully automated, allowing both time and frequency domain measurements.
 - It is highly effective for measuring transients related to power supplies (PS)
 - The system can also perform noise measurements during radiation campaigns (Measurements are planned at IPHC-Strasbourg).

  


- Measurements of the noise emission of the DC-DC has been already performed

19

ATLASPIX3.1 Serial Powering

- ATLASPIX3 is a full reticle size monolithic pixel sensor
 - I. Peric (KIT) main designer
- Version ATLASPix3.1 has possibility for serial powering through two shunt/low dropout regulators
 - digital and analog (VDDD/A)
 - 3 bits to tune threshold of shunt regulator
 - 3 bits to tune VDD
 - gatenmos, outref, gatepmos are for monitoring
 - regresetoutb can be used as power on reset
- Possibility to use a single power supply line for all the 6 biases needed to operate the chip

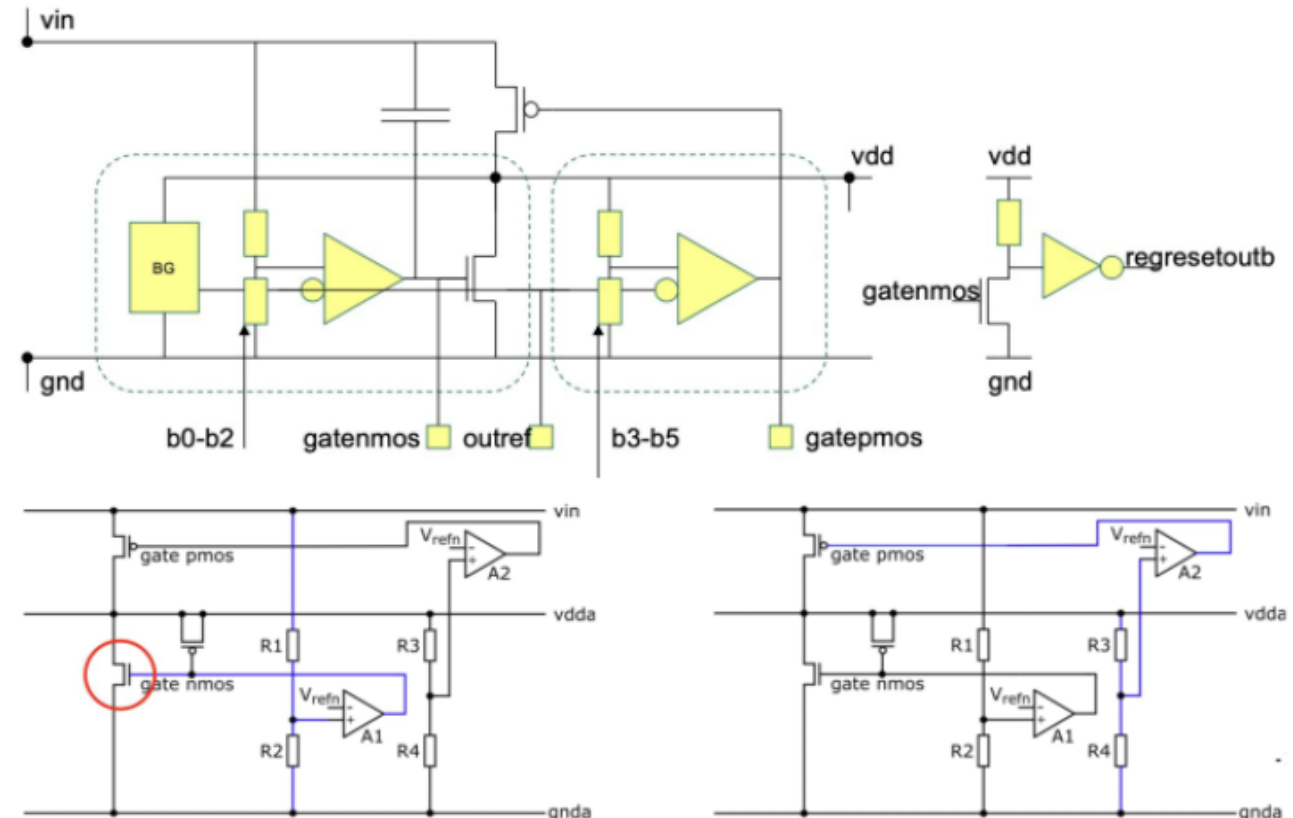

• First loop defines shut regulators

• Second loop regulates VDDD/As

**180nm HV CMOS process Active Pixel Sensor
Compatible with Serial Powering.**

Summary

- Serial Power is a serious candidate for delivering power with low mass cabling without adding the overhead of high frequency conversion process that may affect near by sensitive electronics.
- It can be configured in a variety of way to suit detector implementations.
- Efficiency is maximized by tight control of the module to module current differences.
 - These may include part to part quiescent power differences
 - Minimizing/understanding the occupancy differences during data taking
- Communications must be capacitively coupled and will likely require utilizing balanced code transmissions.
- Early Implementation in the design cycle is essential although the same FEE parts complatible with Serial Powering can be used with parallel powering.