
 


2026.9.24组会

郝宝书

 



- 电阻
图1.rnwfox_633ohm_2个39K
串联
串联电阻电流不一致——漏电


图2.rppolywo_455ohm_80k

- layout_长150u_宽45u

Cell Name	rppolywo	value
View Name	symbol	off
Instance Name	R98	off

Add
Delete
Modify

CDF Parameter	Value	Display
Model name	rppolywo	off
Description	P+ POLY Resistor	off
Segments	4	off
Segment Connection	Series	off
Calculated Parameter	Length	off
Resistance	80.004K Ohms	off
Segment Width	1u M	off
Segment Length	42.228u M	off
Effective Width	1u M	off
Effective Length	819.876m M	off
Temp rise from ambient	0	off
Mismatch Flag	1	off
Sheet Resistivity	455.87 Ohms	off
End Resistance	124.56u Ohms	off
Delta Width	31.297n M	off

 

layout_长150u_宽45u


 
 


图 3-3 传输门结构

 


D1=1.2V

$$V_{gs} = 1.2V - 0.9V = 0.3V$$


$V_{gs} < V_{th}$, 截止, 无法将900mv建立到电阻处

vref1=900mv; vref2=600mv

 - 当D1=1时, PMOS栅极接0, $V_{gs}=0.9V > V_{th}$, 线性导通, $v_{out}=900mv$
- 当D1=0时, NMOS栅极接1.2v, $V_{gs}=0.6V > V_{th}$, 线性导通, $v_{out}=600mv$
- 开关电阻: 线性电阻约为200~350欧, 相对占比小




调节前_


 


调节后_

DAC—buffer

 

1. 负载大小_目前600f
2. 驱动电流_目前34u
3. 增益要求_目前57dB

  

 


图 4-2 CML 预驱动结构图

 


图 3.8 发送端预加重技术

接下来的工作

- 调节buffer/bias
- 给CML发送端结构加预驱动/预加重