



中國科學院高能物理研究所
Institute of High Energy Physics
Chinese Academy of Sciences

DRX-II chip for the optical links upgrade of the ATLAS Pixel Detector


Ying ZHANG, Hongbo ZHU

CLHCP workshop, 22-24 December, 2017



ATLAS Pixel Detector optical links

 Elements and path of the optical link from the MCC to the Pixel DAQ



Rx plugin (optical receiver)

- Receiving signals from optical fiber
- Converting optical signal to electrical signal
- Recovering the electrical signal


- Optical readout of the L1/L2 will suffer from bandwidth limitation after LS1
- A wider range of threshold setting will help operations
- Option is to use new BOC for pixel operation
- Commercial optical receivers can NOT cope with NRZ signal
- Old Rx design has different connector, and old DRX chip is NOT available anymore

New Rx plugins needed

Link occupancy at 75 kHz L1 Trigger						
	μ	B-Layer	Layer 1	Layer 2	Disks	
50 ns	37	39%	34%	52%	30%	
25 ns; 13 TeV	25	35%	31%	48%	27%	
	51	53%	59%	66%	39%	
	76	71%	73%	111%	64%	


Link occupancy at 100 kHz L1 Trigger						
	μ	B-Layer	Layer 1	Layer 2	Disks	
50 ns	37	51%	45%	69%	40%	
25 ns; 13 TeV	25	47%	42%	65%	37%	
	51	71%	67%	88%	52%	
	76	95%	97%	148%	75%	




 

Project requirements





- Should **operate with NRZ signals** (as in Pixel operations) at 80Mbps, high stability for low frequency is needed
- Have stable **operation over a wide range** of light power received/input current: from 10 μ A up to few mA
- Have independent thresholds for all **12 channels**
- Have a **BER < 10⁻¹¹** after aging
- Should be able to perform a measurement of the input current/light power in order to monitor the stability of the on-detector VCSELS

 

 


Rx plugin designs

- Two alternative designs developed: sharing the same optical package, mechanical package and dimensions, but with different data receiver solutions
- **Discrete solution (P. Lutz, BERN)**
 - ↪ Commercial discrete components
 - ↪ Using a pull-up resistor and a discriminator
 - ↪ No amplification applied
- **ASIC solution (Y. ZHANG, IHEP)**
 - ↪ Full custom design integrated circuit
 - ↪ Two amplification chains
 - ↪ Optimized at 80 MHz

    




DRX-II chip



 



Rx prototype


**Optopackage:
provided by OSU**

   


PCB + connector
Designed, loaded, and
tested in Bern

  Readout electronics:
DRX-II chip (IHEP) or
Discrete components (BERN)



 


DRX-II chip design (1)

 


- A single channel consists of two transimpedance amplifiers (TIAs), a voltage-control-currents block (VCCS), a comparator, a limiting amplifier (LA), and an LVDS output driver.
- One TIA amplifies the photocurrent produced by the PIN diode. The other TIA is to offer a reference voltage. Two identical TIAs are used to minimize the difference on the baseline due to the process mismatch and variations.
- A two-gain TIA is proposed to extend the effective dynamic range → good linearity over the complete input current range of 10 μA to 2.4 mA.




 


DRX-II chip design (2)

 

- Gain selection is made by measuring “input signals”. The individual threshold for each channel, normally half of the signal current, indicating the input current amplitude. By comparing the threshold current with a reference voltage, which defines the range of the high gain of the TIA, the comparator decides if the TIA needs to reduce its gain.
- The gain of the TIAs is chosen during the calibration phase and will be fixed during the operation phase. Forward system free from stability problem.
- The chip is designed in AMS 0.35 μm CMOS process.


 


 

DRX-II chip design (3)

■ TIA with two gain modes

  - ↪ TIA core: RGC (Regulated-Cascode) topology, featuring low input impedance
- ↪ Two alternative transimpedance gain controlled by switched



High gain $R_H = R_D$


Low gain $R_L = R_D \parallel R_{D1}$

For stable operation in each gain mode, the load resistance linked with the transimpedance gain is also changed.

High gain $R_{LOAD} = R_L$

 
Low gain $R_{LOAD} = R_L \parallel R_{L1}$






DRX-II chip design (4)

 ■ Transient response in two gain modes: good linearity & sufficient dynamic range




Good linearity ($\pm 1\%$) for lin < 600 μ A

 
400 μ A was chose as the gain change point in simulations



Good linearity ($\pm 1\%$) in the range of 400 μ A to 2.4 mA

 
The gain change point is defined by an external reference voltage, which is adjustable



 


DRX-II chip design (5)

 ■ Simulated performance of a single channel:




Symbol	Parameters	Typical value	Unit
VDDA/VDD	Power supply	3.3 ± 10%	V
I _p	Supply current	154 to 178	mA/Chip
R _{LOAD}	Output loading	50	Ω
V _{thr}	Individual threshold voltage	0 to 2.5	V
V _{GS}	TIA gain transition reference voltage	0.45	V
R _T	TIA transimpedance gain	2.5/0.5	kΩ
I _{in}	Linear dynamic input range	10 to 2400	μA
	Data rate	80	Mbps
J _p	Output jitter peak-to-peak	340	ps

 

 Designed in 2014, using the AMS 0.35 μm CMOS process







Test results (1)

- **Synchronization test:** the BOC over samples the received signals in order to be able to synch its clock with the incoming signal
- Keep on sending an idle word and trying to synchronize on it, scanning thresholds of the prototype and the optical power of the optoboard
- **synchronization efficiency = No. of synchronized channel/No. of total ch.**

Discrete

 


ASIC Synch

 

 Range of the ASIC significantly broader than the discrete design







Test results (2)

- **Data integrity test:** in the region where the BOC synchronized, scan sending 10 bytes 8b/10b encoded, including start and end of frame words, 200 times for a total of 2000 bytes
- **Data integrity efficiency = No. of working channel/No. of total ch.**

Discrete

 


ASIC

 

 Range of the ASIC significantly broader than the discrete design





Test results (3)

- BER test of the Rx plugins with ASIC :


- ↪ Input current of 1.2 mA

- ↪ Transmitting 8b/10b encoding data at 80 Mbps

RX channel	Transmitted Bits	Errors
9	1,036,438,631,340	0
10	1,026,958,157,490	0
11	1,026,956,151,805	0
12	1,026,958,190,122	0
13	1,026,957,957,358	0
14	1,026,953,952,342	0
TOT	6,171,223,040,457	0 4

 BER of the Rx plugins with ASIC less than 10^{-12}






DRX-II chip for L1/L2 upgrade


- Due to the better performance, **DRX-II chip has been selected as the baseline design for the L1/L2 upgrade**

NUMBER OF LAYER 1 RX PLUGINS:	152
NUMBER OF LAYER 2 RX PLUGINS:	104
MINIMUM AMOUNT OF SPARES:	24

TOTAL WORKING RX PLUGINS:	280

 - **Chip characterization performed by OSU, Rx plugin mass production made by OSU and BERN**
- **Layer2/ Layer1 has been upgraded during Dec. 2015/2016**
- **Running status ?**



 

Summary

- IHEP designed a ASIC chip (DRX-II) for the optical links upgrade of the ATLAS Pixel Detector (L1/L2)
- DRX-II meets the requirement well, and offers better performance than the alternative solution.
- DRX-II chip has been used in the new Rx plugins, which have been installed in the Pixel Detector upgraded readout during 2015 to 2016

