

Front-End Electronics for Timing Detectors

A. Rivetti


INFN -Sezione di Torino

[*rivetti@to.infn.it*](mailto:rivetti@to.infn.it)

August 22th, 2018

- 1 Applications of timing systems
- 2 Time digitizers
- 3 Jitter
- 4 Input stages
- 5 Time walk
- 6 Discriminators
- 7 ASICs for timing: some examples

 - Traditionally, **high resolution** timing detectors are used in HEP to **identify** particles



- Measure the time to fly between two points to obtain **velocity**
- Combine with **momentum** information to derive the **mass**

$$t = \frac{L}{v} = \frac{LE}{pc^2}$$

$$t = \frac{L\sqrt{(pc)^2 + (m_0c^2)^2}}{pc^2}$$

$$t = \frac{L}{c} \sqrt{1 + \frac{(m_0c^2)^2}{(pc^2)^2}}$$

- Take two particles with **same** momentum

$$\Delta t = L \left(\frac{1}{v_1} - \frac{1}{v_2} \right) = \frac{L}{pc^2} (E_1 - E_2)$$


$$\Delta t = \frac{L}{pc^2} \left(\sqrt{p^2c^2 + m_{01}^2c^4} - \sqrt{p^2c^2 + m_{02}^2c^4} \right)$$

$$\sqrt{p^2c^2 + m_{01}^2c^4} = pc \sqrt{1 + \frac{m_{01}^2c^4}{p^2c^2}} \approx pc \left(1 + \frac{m_{01}^2c^4}{2p^2c^2} \right)$$


$$\Delta t \approx \frac{L}{pc^2} \left[\left(pc + \frac{m_{01}^2c^4}{2pc} \right) - \left(pc + \frac{m_{02}^2c^4}{2pc} \right) \right] = \frac{Lc}{2p^2} (m_{01}^2 - m_{02}^2)$$

- For Kaon (500 MeV), pion (140 MeV) with $p=1$ GeV, $L=2$ m, $\Delta t=$ **800 ps**

 - Large area: 160 m^2
- Channel counts: about 160.000
- Time resolution: $O(50 \text{ ps})$



 
- Sensors: Multi-gap Resistive Plate Chambers (MRPC)



- For more info: http://aliceinfo.cern.ch/Public/en/Chapter2/Chap2_TOF.html

Application 2: Time of flight mass spectrometry

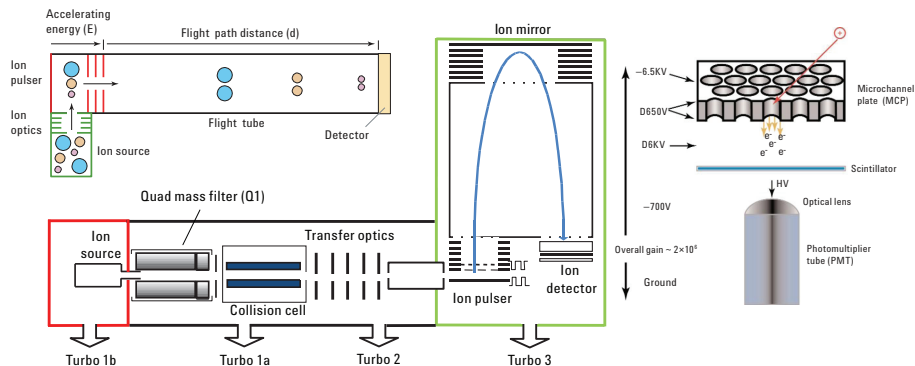- Sorting chemical species on the basis of their **mass-to-charge** ratio
- Powerful **analysis** technique applicable both to **pure samples** and **mixtures**
- ToF is just **one** among **many** possible technique



- Non-relativistic regime!

$$E = \frac{1}{2}mv^2 \rightarrow v^2 = \frac{2E}{m}$$

$$v = \frac{d}{t} \rightarrow m = \frac{2Et^2}{d^2}$$

$$m = A(t_m - t_0)^2$$

- Non-relativistic regime!

$$E = \frac{1}{2}mv^2 \rightarrow v^2 = \frac{2E}{m}$$

$$v = \frac{d}{t} \rightarrow m = \frac{2Et^2}{d^2}$$

$$m = A(t_m - t_0)^2$$

- Fastest mass spectrometry analyzer
- Well suited for pulse ionization techniques
- Highest practical mass range

- Non-relativistic regime!


$$E = \frac{1}{2}mv^2 \rightarrow v^2 = \frac{2E}{m}$$

$$v = \frac{d}{t} \rightarrow m = \frac{2Et^2}{d^2}$$

$$m = A(t_m - t_0)^2$$

- Fastest mass spectrometry analyzer
- Well suited for pulse ionization techniques
- Highest practical mass range
- Require pulse ionization methods
- Dynamic range of fast digitizers


 
- ▶ Anticipated 50 years ago, but still evolving




- More weight to photons coming from the **ROI**
- Stronger benefit on **larger patients**
- Commercial instruments offering better than **300 ps** arriving on the market
- The holy Grail:
10 ps → **3 mm** → **direct imaging**

S. Surti, *Journal of Nucl. Med.*


$$\Delta x = \Delta t \frac{c}{2}$$

  

 


- The peak luminosity of the HL-LHC will increase up to $\approx 10^{35}$
- This will produce 140 to 200 collisions per bunch crossing
 - ▶ Disentangling interesting events from background only with tracking and vertexing becomes challenging
 - ▶ The average collision distance in time is $100 \div 170$ ps

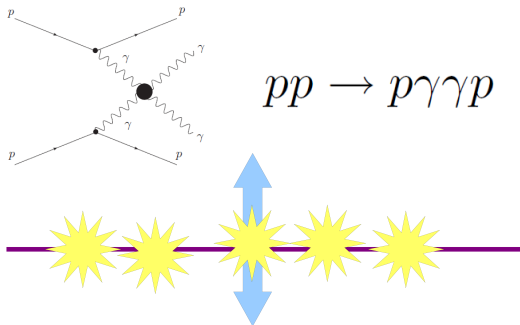- ▶ Collision survivors can be used to probe new physics





- $pp \rightarrow p\gamma\gamma p$ sensitive to **extra-dimensions**
- Intact protons detected **250 m** far from the **collision point**
- Need of **10 ps** timing to suppress **pile-up**

 - ▶ Particle identification through Cherenkov radiation: $\cos \theta_c = \frac{1}{\beta n(\lambda)}$





- Red photons give smaller angles than blue photons
- Red photons propagate faster in the medium
- Time of propagation used for chromatic corrections
- Improvement by 0.7 mrad reported
- Time resolution $O(100 \text{ ps})$

  - LIDAR expected to become a **key component** in future cars





S. Gnechi, C. Jackson, "A 16 SiPM Array for Automotive 3D Imaging LiDAR Systems" <http://imagesensors.org/2017-papers/>

- Ring oscillators

  


- VCOs and (analogue) PLL

  


- ▶ A precise timing system is in (almost) every pocket...

Analog PLL

 


- Feedback signal generated by **charge pump** and **filters**
- VCO controlled by an **analog** voltage


All Digital PLL

 

 - Phase difference measured with a **TDC**
- VCO programmed by **digital** signals



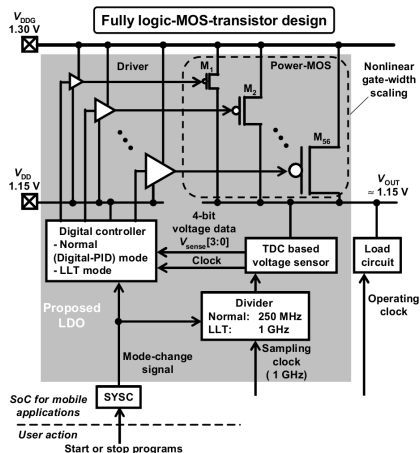- Low Dropout-Regulators (LDO)
- They usually use **analog** loops
- ...but the loop can also be **digital**
- A **TDC** measures a known **time interval**
- V_{out} **reduced** → **less** counts
- V_{out} **increased** → **more** counts
- The loop keeps counts **constant** counts




K. Otsuga et al,

IEEE International SoC Conference, 2012


- Time resolution of **100 ps or better** already achieved in the sixties of last century
- Typical ToF systems have low **channel density**
- Electronics either discrete or based on front-end ASICs with **few channels**

 - Improve time resolution well below 100 ps (target **10 ps**)
- Extend timing to **densely packed** detector systems.
- Need of **highly integrated** ASICs for timing



- The sensor signal is usually amplified and shaped
- A **comparator** generates a digital pulse
- The **threshold crossing** time is captured and digitized by a TDC
- TDC can be **embedded** on the front-end chip or **external**

 ▶ Timing is derived from a **single** sample



- The sensor signal is usually amplified and shaped
- The full waveform is **sampled** and **digitized** at high speed
- In many systems, sampling and digitization are **decoupled**
- Timing is extracted with **DSP** algorithms from the **digitized** waveform samples


► Timing is derived from **multiple** samples

- Different **algorithms** are used to compute the timing from the digitized samples
- There is nothing such an **optimal method**
- Some techniques can be **more suited** than others for real time execution on **FPGA**


- Some examples of digital algorithm:
 - Digital leading edge
 - Digital constant fraction
 - Interpolation
 - Initial slope approximation
 - Reference pulse
 - ...

To learn more: E. Delagnes, [Precise Pulse Timing based on Ultra-Fast Waveform Digitizers](#),
Lecture given at the IEEE NSS Symposium, Valencia, 2011

 
- 1 Applications of timing systems
- 2 Time digitizers**
- 3 Jitter
- 4 Input stages
- 5 Time walk
- 6 Discriminators
- 7 ASICs for timing: some examples



 
- Count the transitions of a periodic signal (clock)



 
- **Count** the transitions of a **periodic signal** (clock)
- When the **event** of interest **arrives**, **store** the counter value into registers



 - **Count** the transitions of a **periodic signal** (clock)
- When the **event** of interest **arrives**, **store** the counter value into registers
- Problem: **100 ps** bin requires **10 GHz** clock



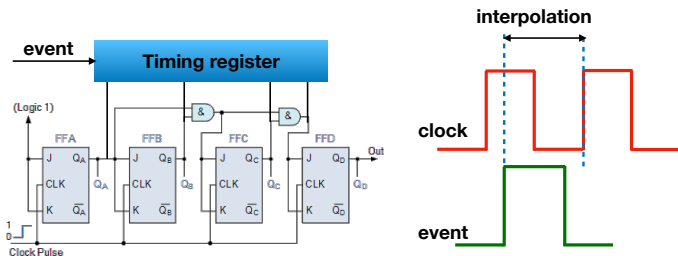- **Count** the transitions of a **periodic signal** (clock)
- When the **event** of interest **arrives**, **store** the counter value into registers
- Problem: **100 ps** bin requires **10 GHz** clock
- Then: **count** the transitions of a **slower** clock and **interpolate**



- **Count** the transitions of a **periodic signal** (clock)
- When the **event** of interest **arrives**, **store** the counter value into registers
- Problem: **100 ps** bin requires **10 GHz** clock
- Then: **count** the transitions of a **slower** clock and **interpolate**
- **Interpolating**= Measuring the time elapsing between the **event** and the **next clock** transition with an **additional** and **dedicated** circuit (interpolator)

What is a TDC

- **mixed-mode or fully-digital circuit**
 - input: trigger signals, typ CMOS
 - output is a **time stamp**: **N-bit digital word** corresponding to a **time difference between two events**
- **Full scale range** T_{ref} : maximum time difference that can be measured
- **Time Binning**: smallest time step (LSB): $T_{ref}/2^N$

Performance dictated by:

- **Conversion Rate** (samples/sec)
- **Linearity** - i.e. Proportionality of digital code to input time difference
- **Quantization error**: rms is $LSB/\sqrt{12}$
- **Single-shot accuracy** (precision in measuring an individual hit)
- **Power**

- **Asynchronous**
 - measures the time difference between two pulses
 - no need for an external reference signal

- **Asynchronous**


- measures the time difference between two pulses
- no need for an external reference signal

- **Synchronous**


- use of a clock to **extend dynamic range**
 - clock provides a coarse time stamp
 - measure the phase between the trigger signal and the clock
 - clock jitter must be below the *rms* quantization error

- **Asynchronous**
 - measures the time difference between two pulses
 - no need for an external reference signal
- **Synchronous**
 - use of a clock to **extend dynamic range**
 - clock provides a coarse time stamp
 - measure the phase between the trigger signal and the clock
 - clock jitter must be below the *rms* quantization error
- **Common in particle detector instrumentation:**
 - **Analog Interpolators**
 - **Digital delay line**
 - **Pulse shrinking**


- **Asynchronous**
 - measures the time difference between two pulses
 - no need for an external reference signal
- **Synchronous**
 - use of a clock to **extend dynamic range**
 - clock provides a coarse time stamp
 - measure the phase between the trigger signal and the clock
 - clock jitter must be below the *rms* quantization error
- **Common in particle detector instrumentation:**
 - **Analog Interpolators**
 - **Digital delay line**
 - **Pulse shrinking**

 


 
- Oldest method to measure time intervals: charge a capacitor with a constant current source and digitize the resulting voltage
 - $V_{out} = \frac{I_1}{C_1}(t_{start} - t_{stop})$



 - Oldest method to measure time intervals: **charge a capacitor with a constant current source and digitize the resulting voltage**
 - $V_{out} = \frac{I_1}{C_1}(t_{start} - t_{stop})$
- If t_{stop} is the edge of a reference clock: becomes a **Synchronous TDC**



- Oldest method to measure time intervals: **charge a capacitor with a constant current source and digitize the resulting voltage**
 - $V_{out} = \frac{I_1}{C_1}(t_{start} - t_{stop})$
- If t_{stop} is the edge of a reference clock: becomes a **Synchronous TDC**
- ADC is frequently Wilkinson (determines the NBITs of the TDC)
 - little circuitry, simple to implement
 - low power, good linearity
 - **Problem: conversion time!**

  


A. Rivetti et al, [IEEE NSS-MIC Conference Records, 2009](#)

ISSCC 2016 / SESSION 19 / DIGITAL PLLs / 19.7


19.7 A 65nm CMOS ADPLL with 360 μ W 1.6ps-INL SS-ADC-Based Period-Detection-Free TDC

Akhide Sai, Satoshi Kondo, Tuan Thanh Ta, Hidenori Okuni, Masanori Furuta, Tetsuro Itakura

Toshiba, Kawasaki, Japan


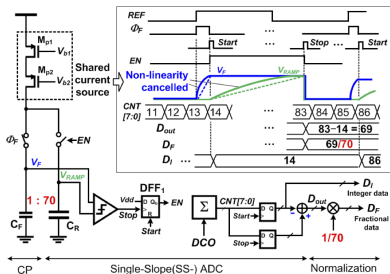


	[3] ISSCC'10	[4] JSSC'15	[5] CICC'13	[6] ISSCC'15	This work	
Architecture	VDL+DTC	TA+TDC	CP+SAR-ADC	Stochastic	CP+SS-ADC	
Supply Voltage	1.2V	1.0V	1.0V	1.2V	1.2V	
Technology	65 nm CMOS	65 nm CMOS	65 nm CMOS	14 nm FinFET	65 nm CMOS	
Cal. Needed? (Time)	Yes (120ms)	Yes (3Bus)	Yes (-)	Yes (-)	No	
Measurement Type	-	-	Static	Static	Dynamic	
w/ ADPLL?	Yes	Yes	No	No	Yes	
TDC	Sample Rate	35MS/s	50MS/s	40MS/s	100MS/s	40MS/s
	State Resolution	6.8ps	0.9ps	0.84ps	1.17ps	6.0ps
	Effective Resolution	5.4bit	4bit	8bit	10bit	6.1bit
	INL	-	1.25ps (sim)	2.3ps	2.7ps	1.6ps
	Power	-	0.2mW (Except DTC)	2.7mW	0.78mW	0.36mW (Except CNT)
ADPLL	In-band Worst Frac. Spur	-52dBc @3kHz	-51.5dBc @392kHz	-	-	-52.6~-43dBc 2.4k~40MHz
	Ref. Spur	-	-69dBc	-	-	-65dBc
	In-band P _{1dB} @2.4G	-105dBc/Hz	-112dBc/Hz	-	-	-106dBc/Hz


 


- Exploits the **intrinsic delay of digital gates** to measure time intervals

  - Exploits the **intrinsic delay of digital gates** to measure time intervals





  - Exploits the **intrinsic delay of digital gates** to measure time intervals





- Start Signal** fed to the buffer chain

 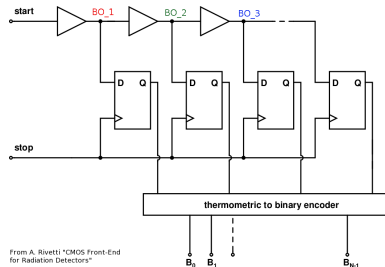- Exploits the **intrinsic delay of digital gates** to measure time intervals




- Start Signal** fed to the buffer chain
- Stop Signal** samples the of the buffer outputs into the register

 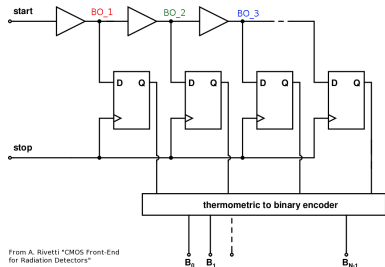- Exploits the **intrinsic delay of digital gates** to measure time intervals




- Start Signal** fed to the buffer chain
- Stop Signal** samples the of the buffer outputs into the register
- bit pattern processed by a thermometric to binary encoder

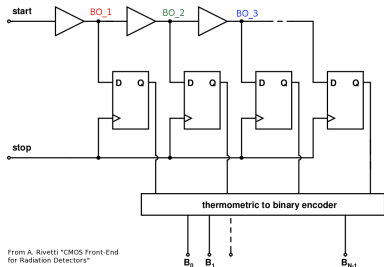- Exploits the **intrinsic delay of digital gates** to measure time intervals



 From A. Rivetti "CMOS Front-End for Radiation Detectors"




- Start Signal** fed to the buffer chain
- Stop Signal** samples the of the buffer outputs into the register
- bit pattern processed by a thermometric to binary encoder

- Maximum time interval measured:** T
- Delay of single cell:** τ_1
- Required $N = \frac{T}{\tau_1}$ cells**


- Resolution set by the delay of a single cell (typ 20-30 ps for a DSM CMOS)

 - Resolution set by the delay of a single cell (typ 20-30 ps for a DSM CMOS)
- **Vernier topology**: approach to increase the resolution of the delay-line TDC




From: A. Rivetti "CMOS Front-End for Radiation Detectors"

 - Resolution set by the delay of a single cell (typ 20-30 ps for a DSM CMOS)
- Vernier topology**: approach to increase the resolution of the delay-line TDC



- Start and Stop Signal** propagate through delay lines with cell delay τ_1 and τ_2
- The LSB is given by $\tau_1 - \tau_2$
- Required $N = \frac{T}{\tau_1 - \tau_2}$ cells

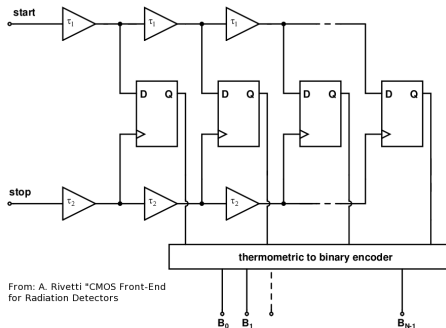- Resolution set by the delay of a single cell (typ 20-30 ps for a DSM CMOS)
- Vernier topology**: approach to increase the resolution of the delay-line TDC




- Start and Stop Signal** propagate through delay lines with cell delay τ_1 and τ_2
- The LSB is given by $\tau_1 - \tau_2$
- Required $N = \frac{T}{\tau_1 - \tau_2}$ cells

Large dynamic range are require many cells

↪ **area becomes prohibitive!**

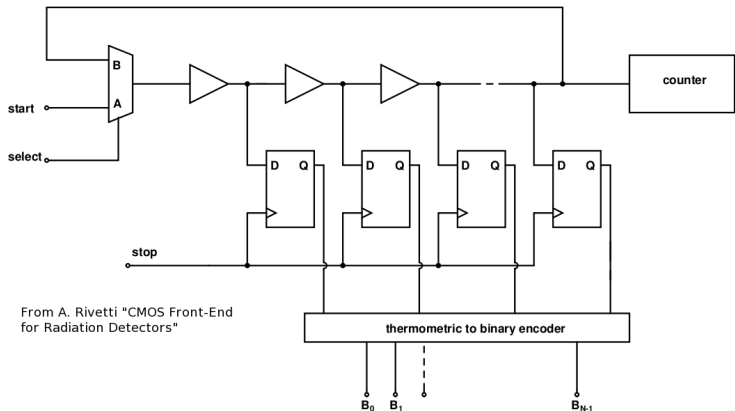Implementation example of a looped delay line:



- Re-use the same cells: **pulse folded-back** to the input of the delay line
- Count how many times the pulse edge has circulated:
 - ↳ **Counter provides coarse time information**

- The use of these techniques require good knowledge on the effects of process, voltage and temperature (PVT) variation


- The use of these techniques require good knowledge on the effects of process, voltage and temperature (PVT) variation
 - global process drifts affect all cells similarly - systematic gain/offset errors
 - ↳ in radiation detectors, solved with calibration

- The use of these techniques require good knowledge on the effects of process, voltage and temperature (PVT) variation
 - **global process drifts** affect all cells similarly - **systematic gain/offset errors**
 - ↳ in radiation detectors, solved with calibration
 - **local random process variations** can induce non-linearities or missing codes


- The use of these techniques require good knowledge on the effects of process, voltage and temperature (PVT) variation
 - **global process drifts** affect all cells similarly - **systematic gain/offset errors**
 - ↳ in radiation detectors, solved with calibration
 - **local random process variations** can induce non-linearities or missing codes
 - **hotspots or IR drops** can induce similar errors

- The use of these techniques require good knowledge on the effects of process, voltage and temperature (PVT) variation
 - **global process drifts** affect all cells similarly - **systematic gain/offset errors**
 - ↳ in radiation detectors, solved with calibration
 - **local random process variations** can induce non-linearities or missing codes
 - **hotspots or IR drops** can induce similar errors

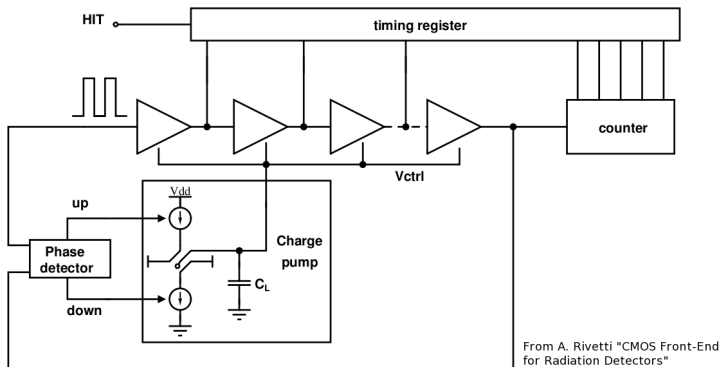
↳ **Good use of statistical simulation tools and proper layout is fundamental**



 
- Delay of the buffer chain is forced by the feedback loop



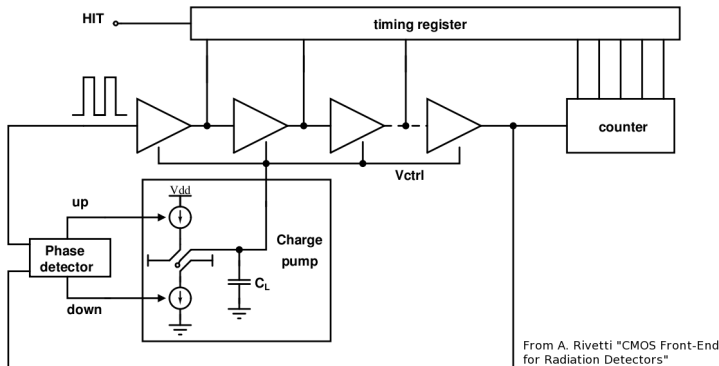- Delay of the buffer chain is forced by the feedback loop
 - Phase detector compares the phase of the delay line output signal and a reference clock



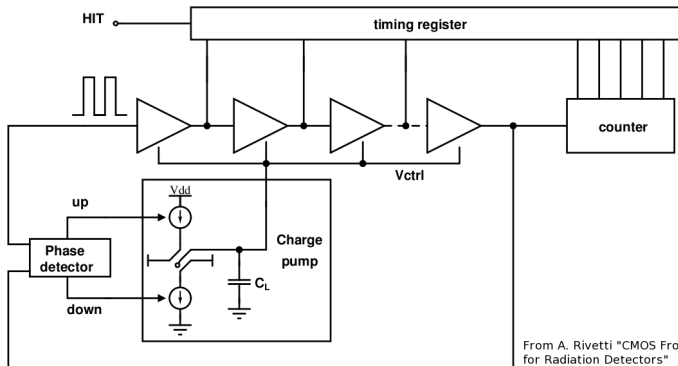- Delay of the buffer chain is **forced by the feedback loop**
 - **Phase detector** compares the phase of the delay line output signal and **a reference clock**
- Output signal increments a counter and provides **coarse information**



- Delay of the buffer chain is **forced by the feedback loop**
 - **Phase detector** compares the phase of the delay line output signal and **a reference clock**
- Output signal increments a counter and provides **coarse information**
- Status of DLL is latched to registers and allows **fine interpolation**

Pros and Cons

Pros and Cons

- **Conversion Speed!**

Pros and Cons

- **Conversion Speed!**

- The hit signal triggers the storage of the DLL and Coarse counter status

Pros and Cons

- **Conversion Speed!**

- The hit signal triggers the storage of the DLL and Coarse counter status
- Conversion result is **immediately available**

Pros and Cons

- **Conversion Speed!**

- The hit signal triggers the storage of the DLL and Coarse counter status
- Conversion result is **immediately available**

↳ **Sampling rate can be very high**

Pros and Cons

- **Conversion Speed!**
 - The hit signal triggers the storage of the DLL and Coarse counter status
 - Conversion result is **immediately available**
 - ↳ **Sampling rate can be very high**
- **very high power consumption**

Pros and Cons

- **Conversion Speed!**

- The hit signal triggers the storage of the DLL and Coarse counter status
- Conversion result is **immediately available**

↳ **Sampling rate can be very high**

- **very high power consumption**

- use of differential delay line (current steering) to minimize noise (victim/agressor)

Pros and Cons

- **Conversion Speed!**

- The hit signal triggers the storage of the DLL and Coarse counter status
- Conversion result is **immediately available**

↳ **Sampling rate can be very high**

- **very high power consumption**

- use of differential delay line (current steering) to minimize noise (victim/agressor)
- reference clock running at high speed

Pros and Cons

- **Conversion Speed!**

- The hit signal triggers the storage of the DLL and Coarse counter status
- Conversion result is **immediately available**

↳ **Sampling rate can be very high**

- **very high power consumption**

- use of differential delay line (current steering) to minimize noise (victim/agressor)
- reference clock running at high speed

↳ $LSB = \frac{T_{clk}}{n_{cells}} \Rightarrow$ **50 ps with 640 MHz and 32 delay cells**

Pros and Cons

- **Conversion Speed!**

- The hit signal triggers the storage of the DLL and Coarse counter status
- Conversion result is **immediately available**

↳ **Sampling rate can be very high**


- **very high power consumption**

- use of differential delay line (current steering) to minimize noise (victim/agressor)
- reference clock running at high speed

↳ $LSB = \frac{T_{clk}}{n_{cells}} \Rightarrow$ **50 ps with 640 MHz and 32 delay cells**




- Tackle: share a global DLL among several channels - **robust buffer scheme to control skew**





DLL-based TDC: a practical example

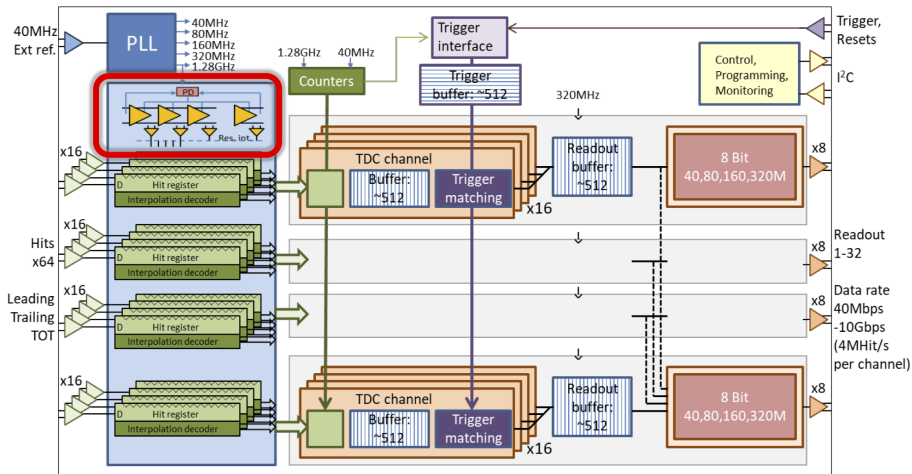



● M. Horstmann (CERN): <https://indico.cern.ch/event/688153/sessions/261017/#20180521>

DLL-based TDC: a practical example

   

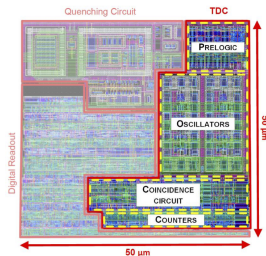   

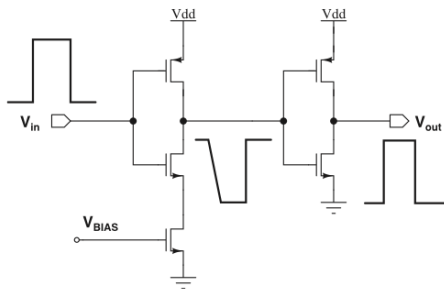 - N. Roy (Sherbrooke): <https://indico.cern.ch/event/688153/sessions/261017/#20180521>



A 14-Bit, 1-ps Resolution, Two-Step Ring and 2D Vernier TDC in 130nm CMOS Technology

Hechen Wang and Fa Foster Dai

Dept. of Electrical and Computer Eng., Auburn University, Auburn, AL 36849

TABLE I. TDCs PERFORMANCE COMPARISON

	VLSI 14 [7]	ISSCC 15 [8]	ISSCC 16 [9]	CICC 17 [2]	ISSCC 17 [1]	This work
Topology	Cyclic	Stochastic	SS-ADC	2D Vernier	SAR-ADC	Ring+2D Vernier
Process	28nm	14nm	65nm	45nm	14nm	130nm
NoB	12	10	6.1	8	7	14
ENoB ⁽¹⁾	9.74	8.28	5.76	7.58	3.68	13.2
Resolution	0.63ps	1.17ps	6ps	1.25ps	0.2ps	1.0ps
ER ⁽²⁾	3.15ps	3.85ps	7.60ps	1.67ps	2ps ⁽⁴⁾	1.74ps
Speed [MHz]	10	100	40	80	26	10
DNL [LSB]/[ps]	0.5/0.32	0.8/0.94	---/---	0.25/0.31	---/---	0.41/0.41
INL [LSB]/[ps]	3.8/2.39	2.3/2.7	0.27/1.6	0.34/0.4	9/1.8	0.79/0.79
Power [mW]	0.82	0.78	0.36	0.33	---	2.4
FoM ⁽³⁾	0.02	0.01	0.13	0.02	---	0.02

1. $ENoB = NoB - \log_2(INL+1)$.


2. Effective Resolution (ER) = Resolution $\times 2^{(NoB - ENoB)}$.

3. $FoM = Power / (2^{NoB} \times F_s)$ [pJ / conv-step].


4. calculated based on in-band phase noise. $PN = 10\log(N^2(2\pi f)^2\tau_{res}^2/12/f_r)$.

A 128-Channel, 710 M Samples/Second, and Less Than 10 ps RMS Resolution Time-to-Digital Converter Implemented in a Kintex-7 FPGA

Chong Liu and Yonggang Wang

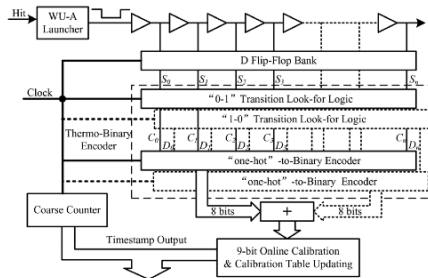

(a)

 

(c)

- 1 Applications of timing systems
- 2 Time digitizers
- 3 Jitter**
- 4 Input stages
- 5 Time walk
- 6 Discriminators
- 7 ASICs for timing: some examples

- Several factors challenge the timing accuracy of a system:
 - Random noise **internal** to the front-end electronics (can be traded with **power**)
 - Random noise from **external** sources (e.g. clock distribution system)
 - Signal **integrity** (substrate noise, PSSR, etc..)
 - Pulse **amplitude** variations
 - Pulse **shape** variations
- ▶ Timing below **100 ps** rms is not trivial
- ▶ Research is now geared towards sub 10 ps **system** resolution

$$\sigma_t = \frac{\sigma_V}{\frac{dV}{dt}} \quad \frac{dV}{dt} \approx \frac{V}{t_r} \rightarrow \sigma_t = \frac{t_r}{SNR}$$

Checks:

$$t_r = 1 \text{ ns}, SNR = 10 \rightarrow \sigma_t = 100 \text{ ps}$$


$$t_r = 40 \text{ ns}, SNR = 500 \rightarrow \sigma_t = 80 \text{ ps}$$

$$t_r \propto \frac{1}{BW} \quad SNR \propto \frac{1}{\sqrt{BW}} \rightarrow \sigma_t \propto \frac{1}{\sqrt{BW}}$$

► Match the front-end rise time with the sensor rise/collection time

► Calorimeters can profit from **large signals** to make timing is **easier!**

 - Calorimeters already achieve **quite good** time resolution
- System resolution now saturates at around **100 ps**
- Exact values depends on the situation considered
- Interaction region ≈ 6 cm
- With **30 ps** resolution event origin confined to **1 cm**.
- Need a **4-5x** improvement with respect to today standard



From D. Del Re, *J. of Physics: Conference Series 587* (2015),
doi:10.1088/1742-6596/587/1/012003

Timing jitter: multiple sampling

- Sample the input signal **beyond** Nyquist
- Assume **first-order** system relationship

$$\sigma_t = \frac{t_r}{SNR} \frac{1}{\sqrt{N}} \quad N = \frac{t_r}{t_s}$$


$$\sigma_t = \frac{1}{SNR} \sqrt{\frac{0.35}{BW \cdot f_s}} = \frac{1}{SNR} \frac{1}{\sqrt{3f_{-3dB} f_s}}$$

SNR	f_s	f_{-3dB}	σ_t
10	1 Gs/s	150 MHz	150 ps
10	10 Gs/s	1.5 GHz	15 ps
100	1 Gs/s	150 MHz	15 ps
1000	10 Gs/s	1.5 GHz	0.15 ps


- Redundancy is **advantageous** only if noise is **uncorrelated**

► Unfortunately, jitter is not the full story...

 
- 1 Applications of timing systems
- 2 Time digitizers
- 3 Jitter
- 4 Input stages**
- 5 Time walk
- 6 Discriminators
- 7 ASICs for timing: some examples




Charge sensitive

 

Transimpedance

 

Common base (gate)

 

Voltage amplifier

- Take a simple voltage amplifier
- Step at the input is Q_{in}/C_d
- Assume single pole response with time constant $\tau = RC$
- Amplifier rise time is: $t_a = 2.2\tau$
- Amplifier cut-off frequency is $f_T = \frac{1}{2\pi\tau}$
- Total rise time at the output is $\sqrt{t_d^2 + t_a^2}$
- Output voltage squared is $v_n^2 \frac{\pi}{2} f_T$
- Now put everything together...



$$\sigma_t = \frac{\sigma_n}{\frac{dV}{dt}} \approx \frac{v_n}{\sqrt{2t_a}} \frac{C_d}{Q_{in}} \sqrt{t_a^2 + t_d^2} = \frac{v_n C_d}{Q_{in}} \sqrt{t_d}$$

See also C. de la Taille lecture

- Consider the following parameters: $t_d = 1 \text{ ns}$, $C_d = 300 \text{ pF}$,
 $Q_{in} = 1 \cdot 10^6 e^-$
- If we want $\sigma_t = 10 \text{ ps}$, we need $v_n \approx 1.7 \cdot 10^{-10} \text{ V}/\sqrt{\text{Hz}}$
- Assume MOS input transistor in weak inversion: $v_n = \sqrt{\frac{2\alpha kT}{g_m}}$
- Combining all parameters (take $\alpha = 1$), we get $g_m = 0.291 \text{ S}$
- The transconductance in w.i. is $g_m = \frac{I_{DS}}{n\phi_T}$
($n \approx 1.3$, $\phi_T = kT/q = 26\text{mV}$)
- The bias current needed in the input transistor is $\approx 10 \text{ mA}$

TIA or CSA topology

  - $f_{in} < 1/2\pi R_f C_f \rightarrow$ TIA
- $f_{in} > 1/2\pi R_f C_f \rightarrow$ CSA




Rise time calculation


TIA or CSA topology

- $f_{in} < 1/2\pi R_f C_f \rightarrow$ **TIA**
- $f_{in} > 1/2\pi R_f C_f \rightarrow$ **CSA**

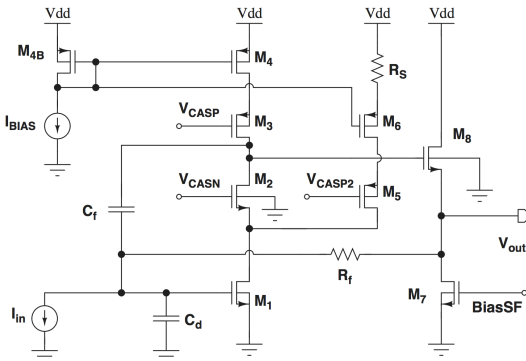Equations and figures from A. Rivetti, CMOS Front-End for Radiation Sensors, CRC Press, 2015



Step1: small signal model

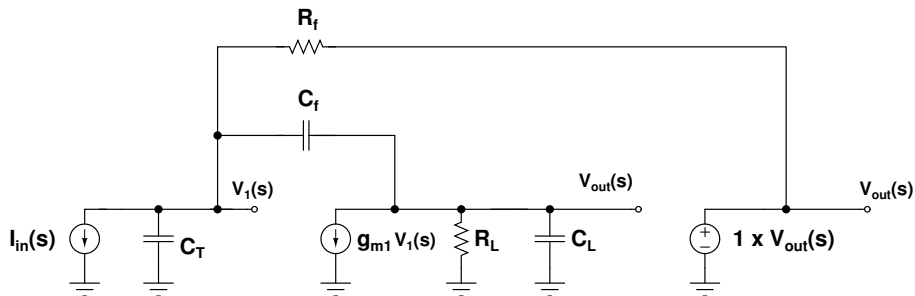

$$T(s) = \frac{(g_{m1} - sC_f) R_f R_L}{s^2 \zeta R_f R_L + s [R_L C_L + R_f C_T + (1 + g_{m1} R_L) C_f R_f] + 1 + g_{m1} R_L}$$

$$R_f C_f > \frac{4(C_T C_L + C_T C_f + C_f C_L)}{g_{m1} C_f}$$

$$\tau_f = R_f C_f$$


$$\tau_r = \frac{C_T C_L + C_T C_f + C_L C_f}{g_{m1} C_f}$$


- **Impulse** response of a system with **two real** poles

$$V_{out}(t) = Q_{in} \frac{R_f}{\tau_r - \tau_f} \left(e^{-\frac{t}{\tau_r}} - e^{-\frac{t}{\tau_f}} \right) = \frac{Q_{in}}{C_f} \frac{\tau_f}{\tau_r - \tau_f} \left(e^{-\frac{t}{\tau_r}} - e^{-\frac{t}{\tau_f}} \right)$$

$$V_{out,peak} = \frac{Q_{in}}{C_f} \left(\frac{\tau_f}{\tau_r} \right)^{\frac{\tau_r}{\tau_r - \tau_f}}$$

 
$$\tau_r \approx \frac{C_T (C_L + C_f)}{g_{m1} C_f}$$



 

$$\frac{V_{out}}{I_{in}} = \frac{R_L}{\left[1 + s \frac{(C_T + AC_{gs})}{g_{m1}A}\right] (1 + sR_L C_L)}$$

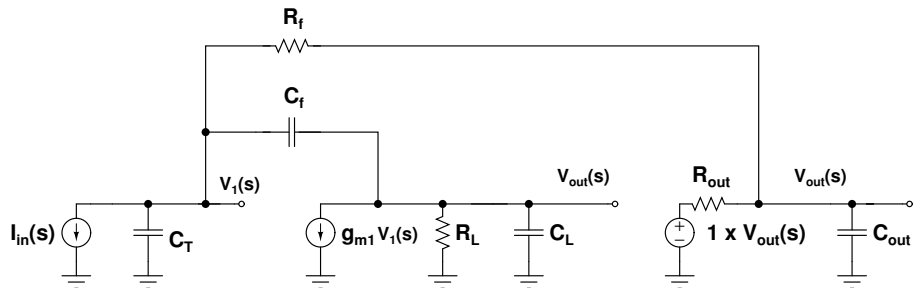
$$\frac{V_{out}}{I_{in}} = \frac{R_L}{\left(1 + s \frac{C_T}{g_{m1}A}\right) (1 + sC_L R_L)}$$




- Front-end transfer function **analysis** essential to gain **intuition**
- Unfortunately it needs many **approximations** to be manageable
- Transistors **models** in deep submicron technologies are **very complex**
- Mathematical modeling helpful for a **first-cut design**
- Constraint-driven **CAD optimization**

- 1 Applications of timing systems
- 2 Time digitizers
- 3 Jitter
- 4 Input stages
- 5 Time walk**
- 6 Discriminators
- 7 ASICs for timing: some examples

 - Pulses of **same** shape and **different** amplitude crosses the threshold at **different** times
- Even worse if also the **shape** changes
- This is a **problem** for accurate timing



 
- Pulses of **same** shape and **different** amplitude crosses the threshold at **different** times
- Even worse if also the **shape** changes
- This is a **problem** for accurate timing



Common solutions

- **Correct** using the pulse amplitude
- Correction usually done **off-line**
- Time-over-threshold often used
- Zero-crossing timing
- **Track** in real-time the pulse with the **threshold**

 - Pulses of **same** shape and **different** amplitude crosses the threshold at **different** times
- Even worse if also the **shape** changes
- This is a **problem** for accurate timing







Common solutions


- **Correct** using the pulse amplitude
- Correction usually done **off-line**
- Time-over-threshold often used
- Zero-crossing timing
- **Track** in real-time the pulse with the **threshold**

► Constant Fraction Timing

   
- All signals reach the **peak** at the **same time**
- Differentiate and take the **zero crossing** time
- Jitter is **increased**



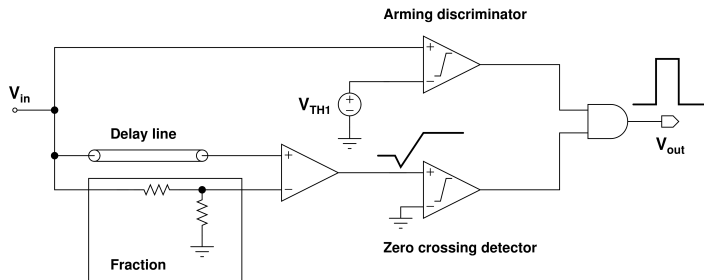


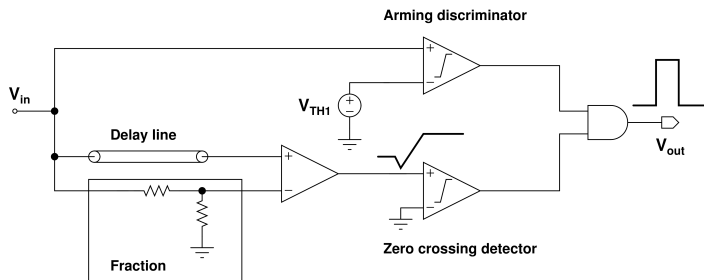

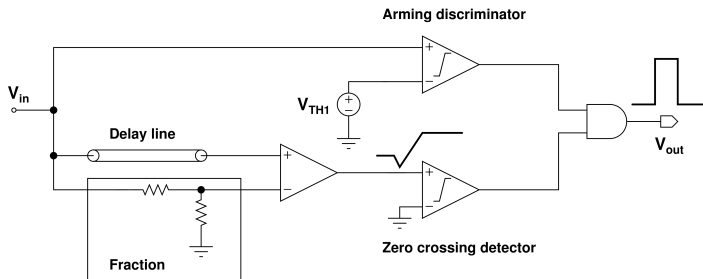- The input signal is both **delayed** and **attenuated**



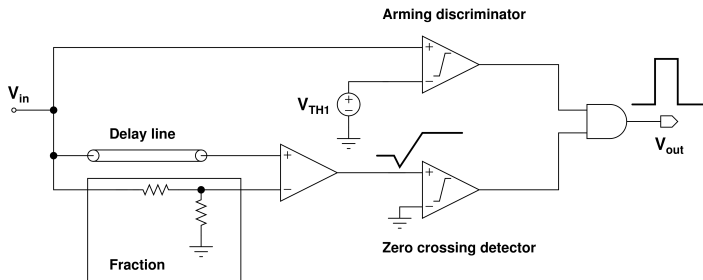
- The input signal is both **delayed** and **attenuated**
- The delayed and attenuated signals are **combined** to yield a **bipolar** waveform



- The input signal is both **delayed** and **attenuated**
- The delayed and attenuated signals are **combined** to yield a **bipolar** waveform
- The **zero crossing** of the bipolar waveform is used for **timing**

Assume a **step** input signal:
 
$$V(t) = \begin{cases} 0 & \text{for } t < 0 \\ \frac{t}{t_r} V_0 & \text{for } 0 < t < t_r \\ V_0 & \text{for } t > t_r \end{cases}$$



$t_d > t_r$, amplitude compensation

$$fV_0 = \frac{t-t_d}{t_r} V_0 \quad t_{zc} = ft_r + t_d$$

$t_d < t_r$, ARC compensation


$$f \frac{t}{t_r} V_0 = \frac{t-t_d}{t_r} V_0 \quad t_{zc} = \frac{t_d}{1-f}$$

Take now simple $CR - RC$ shaping and an **ideal** delay line:

$$\frac{t - t_d}{\tau} e^{-\frac{t-t_d}{\tau}} - f \frac{t}{t_d} e^{-\frac{t}{\tau_d}} = 0 \rightarrow t_{zc} = \frac{t_d e^{\frac{t_d}{\tau}}}{e^{\frac{t_d}{\tau}} - f}$$

- Jitter optimization: $\tau = t_{coll} \rightarrow$ sensitivity to **pulse shape fluctuations!**
- Can be reduced by reducing t_d , f , or both...
- CFDs rely of **fully linear** signal processing
- Not trivial to implement in modern CMOS technologies due to the reduced voltage headroom, but it can be done.

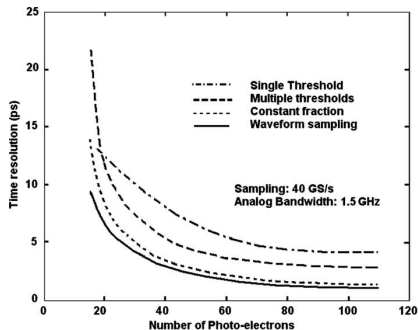J. F. Genat et al. [Signal processing for picosecond resolution timing measurements](#), NIM A 607 (2009) 387-393



- Simulations based on **MCP** signal
- No sampling jitter added
- The barrier of **10 ps** broken around **20 pe**
- Practical equivalency between **WS** and **CFD**



ELSEVIER

Nuclear Instruments and Methods in Physics Research A 457 (2001) 347–355

**NUCLEAR
INSTRUMENTS
& METHODS
IN PHYSICS
RESEARCH**

Section A

www.elsevier.nl/locate/nima

Timing of pulses of any shape with arbitrary constraints and noises: optimum filters synthesis method

E. Gatti*, A. Geraci, G. Ripamonti

Dipartimento di Elettronica e Informazione, Politecnico di Milano, Piazza Leonardo da Vinci 32, Milano 20133, Italy

Received 9 June 2000; accepted 15 June 2000

Abstract

In this paper the optimum filtering for the precise measurement of the occurrence time of any kind of time-limited signal is dealt with. We find the time-limited optimum weighting function (WF) in the presence of any kind of uncorrelated, stationary, additional noises and we allow the introduction of arbitrary assigned time domain constraints in the WF. The method can be easily translated into computer programs and it can be used as a tool for optimising a digital signal processing spectroscopy set-up in its digital filter section. An application of the method to signals at the output of large volume HPGe γ -ray detectors is finally presented. © 2001 Elsevier Science B.V. All rights reserved.


 


Fig. 1. Comparison between the approximated optimum synthesised WF $w(t)$ (a) and the analytical one (b) in the test case (see text): the two curves almost coincide and the maximum divergence is in correspondence with the cusp peak. This is to be expected, since our representation of $w(t)$ involves an analytical function expressed with a finite number of harmonics. The number of harmonics is 200. The difference in time resolution is just 2%.


- Generate a set of charges from the Landau distribution covering the dynamic range
- Send the charges in different part of the sensing element
- Collect the resulting current waveforms in the form of time-amplitude lists
- Input them in SPICE with the timing chain (transistor level)
- Important to consider also the discriminators
- Analyze the SPICE outputs and extract the timing
- A lot of scripting...

Courtesy L. Pancheri, Trento

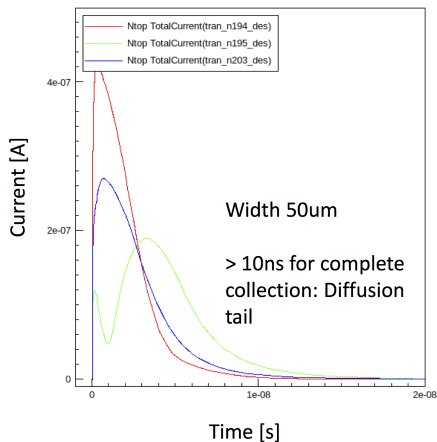



- The ideal timing detector should provide:
 - very **fast** signals → short **flight path** of the charge carriers in the sensor
 - shape stability
 - low pulse **amplitude spread**
 - small capacitance
 - sustain **high** counting **rates**
 - be **radiation tolerant**
 - be easily **scalable** to large **large** areas
 - cheap
- ▶ No sensor fulfills all the above specs


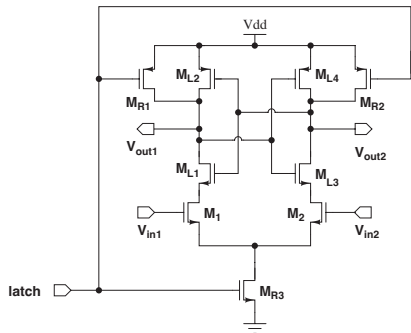
- 1 Applications of timing systems
- 2 Time digitizers
- 3 Jitter
- 4 Input stages
- 5 Time walk
- 6 Discriminators**
- 7 ASICs for timing: some examples




- Latched (**synchronous** comparators) have many **advantages**
- Only **dynamic** power
- Very **fast** thanks to positive **feedback**
- **Are they good as timing discriminator?**

  
- Comparator can contribute significantly to time-walk
- Fast comparators means power



  

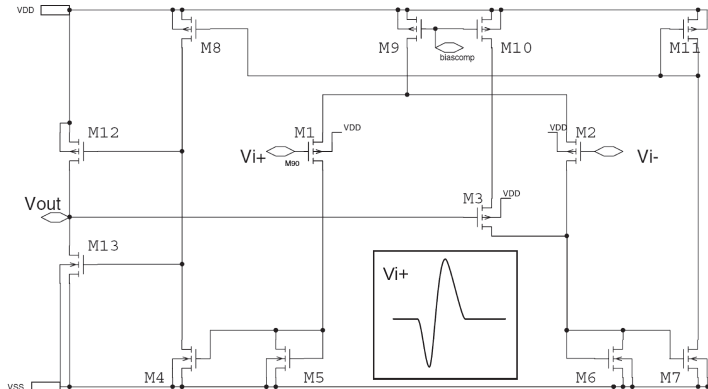- Assume $g_{m1} = g_{m2}$, $g_{m3} = g_{m6}$
- **Differential** gain dominated by transistor **output conductance**
- **Common mode** gain dominated by **diode-connected** transistors







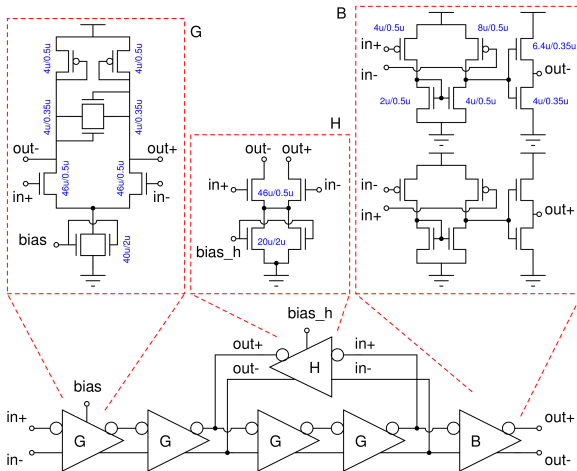




- 1 Applications of timing systems
- 2 Time digitizers
- 3 Jitter
- 4 Input stages
- 5 Time walk
- 6 Discriminators
- 7 ASICs for timing: some examples**

A 64-Gb/s 1.4-pJ/b NRZ Optical Receiver Data-Path in 14-nm CMOS FinFET


Ilter Ozkaya, *Student Member, IEEE*, Alessandro Cevrero, *Member, IEEE*,
Pier Andrea Francese, *Senior Member, IEEE*, Christian Menolfi, *Member, IEEE*,
Thomas Morf, *Senior Member, IEEE*, Matthias Brändli, Daniel M. Kuchta, *Senior Member, IEEE*,
Lukas Kull, *Senior Member, IEEE*, Christian W. Baks, Jonathan E. Proesel, *Senior Member, IEEE*,
Marcel Kossel, *Senior Member, IEEE*, Danny Luu, *Student Member, IEEE*,
Benjamin G. Lee, *Senior Member, IEEE*, Fuad E. Doany, Mounir Meghelli, *Member, IEEE*,
Yusuf Leblebici, *Fellow, IEEE*, and Thomas Toifl, *Senior Member, IEEE*

   

  


  

 ...or “how many things you can do with an inverter”!





 Why transistors are used in feedback?
What is the purpose of the inductor?





What we study here?

  
$$\frac{C_{i1}}{C_{i2}} = \frac{g_{m_p}}{g_{m_n}} = \frac{C_{o1}}{C_{o2}}$$



ISSCC 2018 / SESSION 5 / IMAGE SENSORS / 5.1

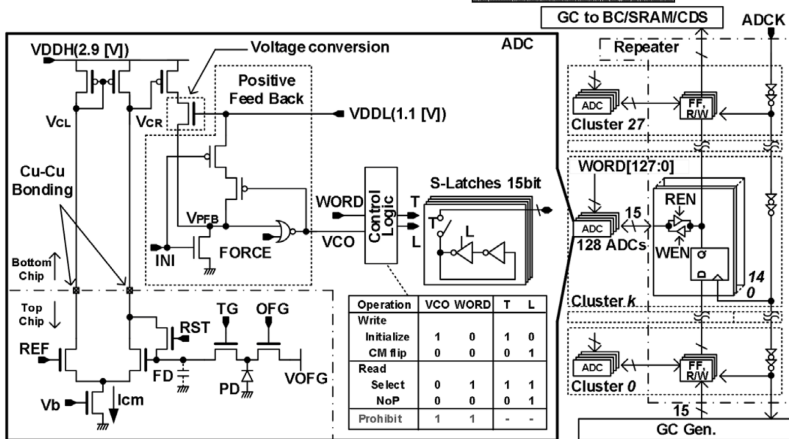
 
5.1 A Back-Illuminated Global-Shutter CMOS Image Sensor with Pixel-Parallel 14b Subthreshold ADC




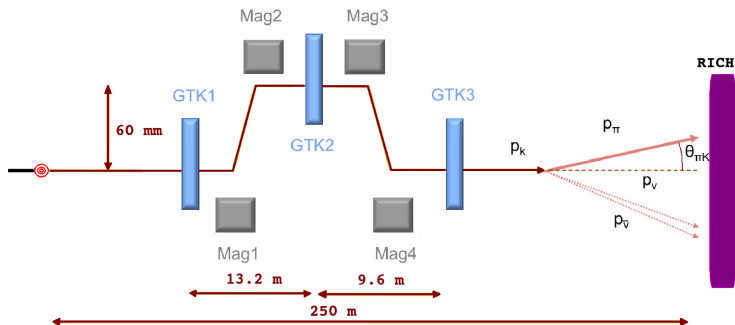


- Study of **very rare** Kaon decay: $K^+ \rightarrow \pi^+ \nu \bar{\nu}$
- Time tag the K^+ tracks to match the π^+ track in the RICH
- GTK: three stations of **hybrid silicon pixels** with ≤ 200 ps rms resolution per station
- Sensor area: **60 mm x 27 mm** readout by 10 TDCpix chips

The TDCpix chip at a glance

  


  - Timing method: LED + offline ToT compensation
- Pixel area: $300 \mu\text{m} \times 300 \mu\text{m}$
- DLL-based TDC in the periphery
- 360 equivalent TDC per chip
- 210 Mhit/s/chip
- 4×3.2 Gbit/s serializers
- CMOS 130 nm, designed at CERN




- **Transimpedance** amplifier followed by **leading edge** discriminator
- Peaking time ≈ 5 ns
- Only analog electronics and quite configuration registers in the pixel
- Discriminator signal sent to the EoC TDC with **integrated t-lines**

 ► Achieve **65 ps rms** electronic resolution at **2.4 fC** on 1800 pixels!




 - TDC based on **DLL** approach
- **320 MHz** clock and **32 delay taps**
- **Differential** delay buffers for low noise
- One DLL share among two columns
- One timing register shared among 5 pixels




RMS time resolution obtained with the TDCPix demonstrator

With **laser** in the **lab**...

 

 
...and with **particles** in the **beam**



M. Fiorini

Where is the difference?...

In the sensor! (and in the physics...)

 


G. Aglieri Rinella

- **Weighting field** different at the **center** and at the **pixel border**
- Particles hitting in **different points** produce **different signal shapes**
- This effect has been estimated to contribute about **85 ps**
- Charge straggling also contributes **> 60 ps**


TDCpix references:

 - M. Noy, TDCPix: **A High Time Precision Pixel Chip for the NA62 GigaTracker**, CERN-PH-ESE Seminar, <https://indico.cern.ch/event/302077/>
- M. Noy et al.: **The TDCPix ASIC: Tracking for the NA62 GigaTracker**, TIPP 2014, Proceeding of Science, <http://pos.sissa.it/>



- Timing front-end ASIC: 1024 channels, 4096 TDC, 20 Gbit/s output bandwidth
- Technology 110 nm CMOS
- Pixel size 400 $\mu\text{m} \times 400 \mu\text{m}$
- TDC binning 20 \div 100 ps, DNL %
- Overall system jitter \approx 30 ps r.m.s.

 - ▶ Anticipated 50 years ago, but still evolving



- More weight to photons coming from the ROI
- Stronger benefit on **larger patients**
- Commercial instruments **400 - 500 ps**, 300 ps expected soon


$$\Delta x = \Delta t \frac{c}{2}$$

S. Surti, [Update on time-of-flight PET imaging](#),
J. Nucl. Med. Jan. 2015; 56 (1); 98-105


- Chip developed in the framework of the **EndoToF-US** project
- Sensors: **analog SiPM** with capacitance in the **75 to 300 pF** range

Parameter	Value
Number of channels	64
Clock frequency	80 – 160 MHz
Dynamic range of input charge	300 pC
SNR ($Q_{in} = 100$ fC)	> 20-25 dB
Amplifier noise (in total jitter)	< 25 ps (FWHM)
TDC time binning	50 ps
Coarse gain	$G_0, G_0/2, G_0/4$
Max. channel hit rate	100 kHz
Max. output data rate	320 Mb/s (640 w/ DDR)
Channel masking	programmable
SiPM fine gain adjustment	500 mV (5 bits)
SiPM	up to 320pF term. cap., 2MHz DCR
Calibration BIST	internal gen. pulse, 6-bit prog. amplitude
Power	< 10 mW per channel


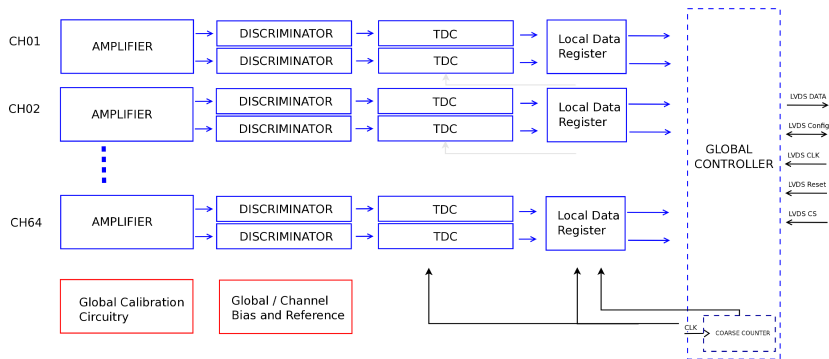
- Charge encoding with **Time over Threshold**
- Dual threshold system




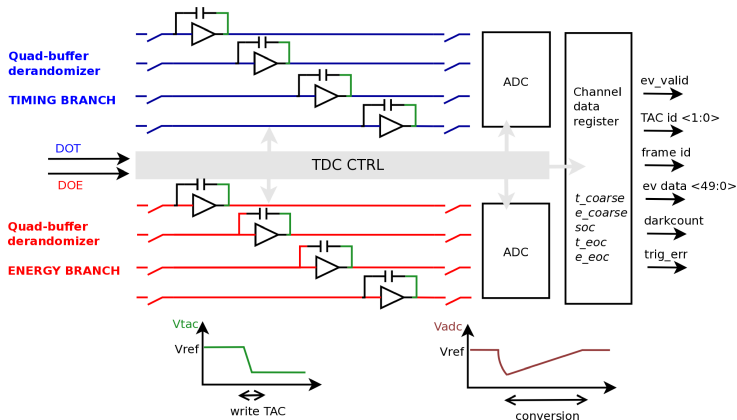- TDC based on Time to Amplitude Converters
- **Four TACs** per TDC for **derandomization**
- Rate capacitance > **300 kHz** per channel




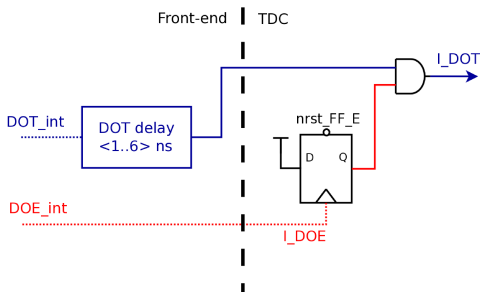 - Important **not to trigger** TACs with **dark counts**
- **Timing pulse** is delayed and **confirmed** by energy pulse (**higher threshold**)





 




a)

 

b)

   - Two chips can be put side-by-side to get a compact 128 channel system



  



TDC resolution ≈ 20 ps rms
(with 50 ps bin size)

Resolution with crystals and SiPM

TOF-PET references:

M.D. Rolo et al., [TOF-PET ASIC for PET applications](#), JINST, Vol. 8, Feb. 2013

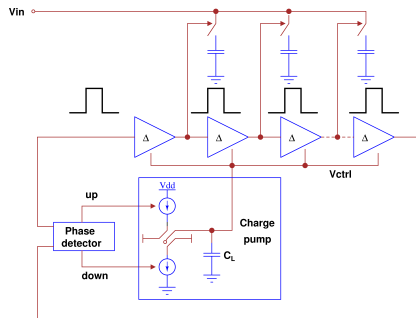 M.D. Rolo. , [Integrated Circuit Design for Time of Flight PET](#), PhD thesis, Univ. of Torino, 2014




- ▶ In a **TDC**, the **delayed pulses** are captured into **registers** when the hit arrives
- ▶ In a **WS**, the **delayed pulses** are used to control the **analog storage cells**
- ▶ Sampling frequency is $1/\Delta$ and can be well above **10 GHz** in modern technologies
- ▶ In earlier implementations **open loop** buffers were employed. Today the use of **DLL** and **PLL** prevalent (jitter and sampling time uniformity)

ASIC	Year	Node	Time res.	Max sample/ch.	Channels
LABRADOR3	2005	250 nm	16 ps	260	8
BLAB	2009	250 nm	< 5 ps	65536	1
DRS4	2014	250 nm	≈ 1 ps	1024	8
PSEC4	2014	130 nm	≈ 1 ps	256	6
SamPic	2014	180 nm	≈ 3ps	64	16

- Typical small channel count per ASIC
- Resolution: **same pulse split** and sent to different channels and **time difference** measured


E. Oberla et al., A 15 GSa/s, 1.5 GHz bandwidth waveform digitizing ASIC

NIM A 735 (2014) 452-461

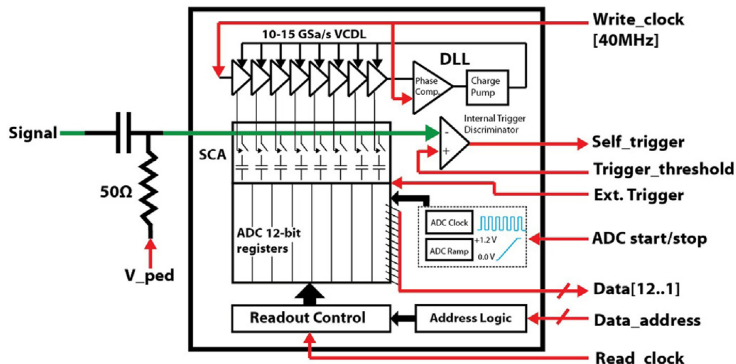



- Input signal AC coupled (terminations external)
- On chip RF microstrip lines at the input
- DLL with 256 taps fed by a 40 MHz clock

 E. Oberla et al., *NIM A* 735 (2014) 452-461



- Small sampling capacitance (**20 fF**) to guarantee **1.5 GHz** analog bandwidth
- A Wilkinson **ADC** integrated in **each** cell
- Common ADC ramp generated externally to the cell

  E. Oberla et al., [NIM A 735 \(2014\) 452-461](#)




Example of digitized pulse


Timing performance

- Time resolution better than **5 ps rms** obtained after time-base calibration

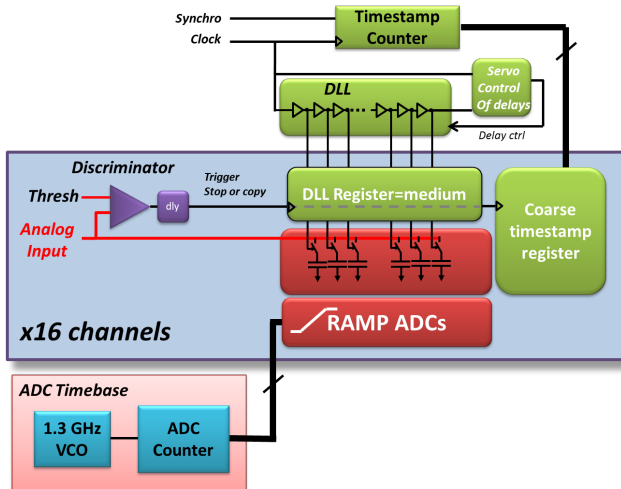E. Delagnes et al., [Reaching a few picosecond timing precision with the 16-channel digitizer and timestamper SAMPIC ASIC NIM A 787 \(2015\) 245-249](#)



 
E. Delagnes et al., *NIM A 787* (2015) 245-249



- Time resolution:


- < 20 ps without time-base correction
- < 5 ps with time based correction
- 10 ps TDR achieved over 10 μ s difference between pulses

- SoC for mobile



 


- Different functions implemented in **selected** areas

 
- ASIC for hybrid pixel detectors (RD53A prototype for ATLAS/CMS upgrades)



   - About **80.000** pixels of $50 \mu\text{m} \times 50 \mu\text{m}$ in 65 nm







 
- Analog islands surrounded by digital gates






- Most of a typical front-end ASIC is digital
- Low-noise analog and high speed digital can coexist
- Several isolation features offered by modern technologies
- ...but one has to be very careful!

  - Chip size $\approx 1.2 \text{ cm} \times 1.8 \text{ cm}$







   

   - **Uniform bias** among channels is a critical issue in large chips
- One of the most common **failure** reason in large IC
- Must be taken into consideration in **early** design phase



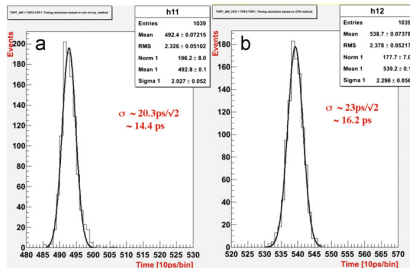   D. Breton et al., NIM A 629 (2011) 123-132



- Increasing number of **applications** for **timing** detectors
- **Comparable** performance with **TDC** and **waveform sampling**
- Trends:
 - **Higher** integration **density**
 - Better time resolution (targeting **10 ps and below**)
- **TDC** already achieve **1 ps** resolution
- **Electronics** resolution of waveform samplers comparable
- The key is at the **interplay** between the **sensor** and the **very front-end**
- ...but it's **not only** the front-end!
- State-of-the-art ASIC for timing are fairly complex **SoCs**
- Beware of **systems aspects**
- **Take your time** to design them!

Thank you!