



Introduction fo Front-End Electronics in Particle Physics

FEDSS 2018 Weihai 威海

Christophe de LA TAILLE

Director of OMEGA microelectronics group
Ecole Polytechnique & CNRS IN2P3
<http://omega.in2p3.fr>

Organization for **M**icro-**E**lectronics desi**G**n and **A**pplications

1. Low noise charge preamps : pixel readout
2. Large dynamic range/high speed designs : calorimeters
3. Trends and future

Lectures for physicists, not electronics engineers => will concentrate on front-end and performance of detector, not on detailed engineering






Many more slides than allocated time : don't be afraid !

I will skip many details : they are for further reference

Many thanks to the organizers for their kind invitation : 谢谢



Electronics in experiments

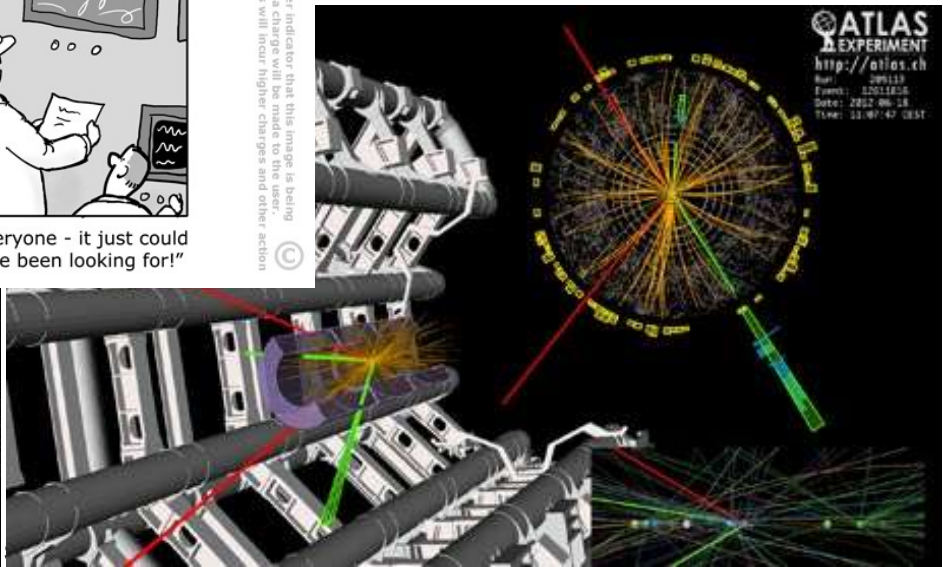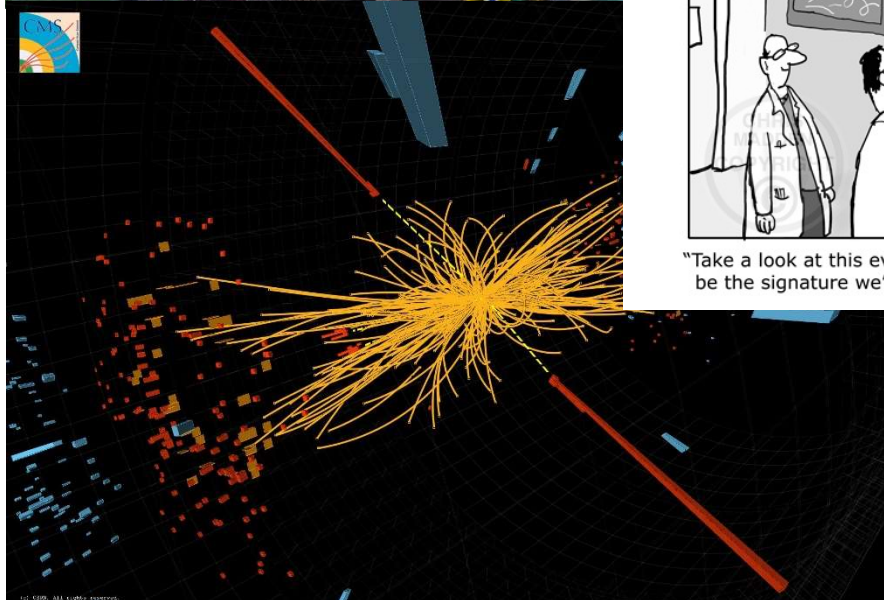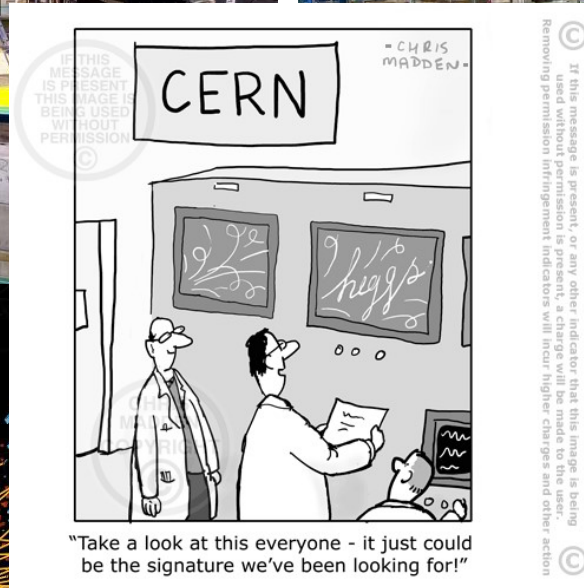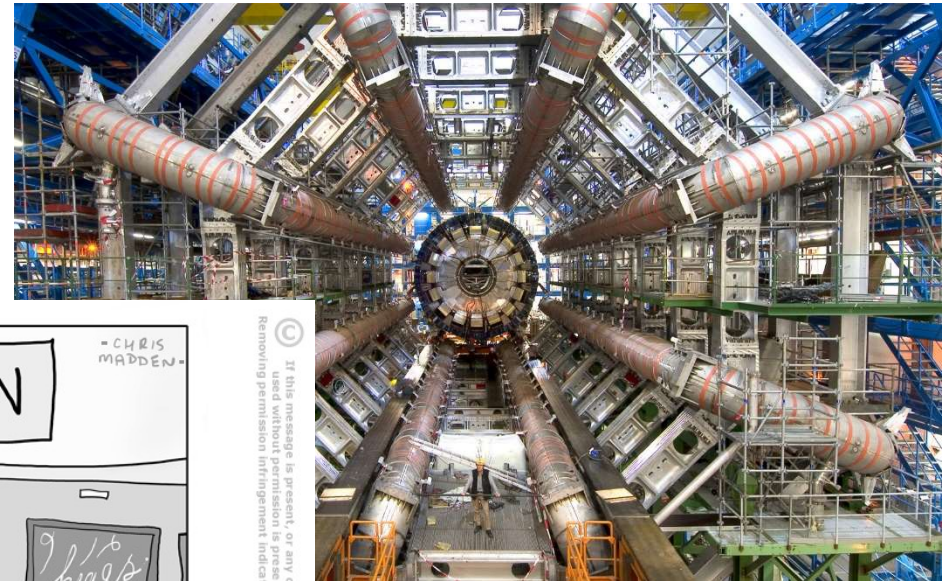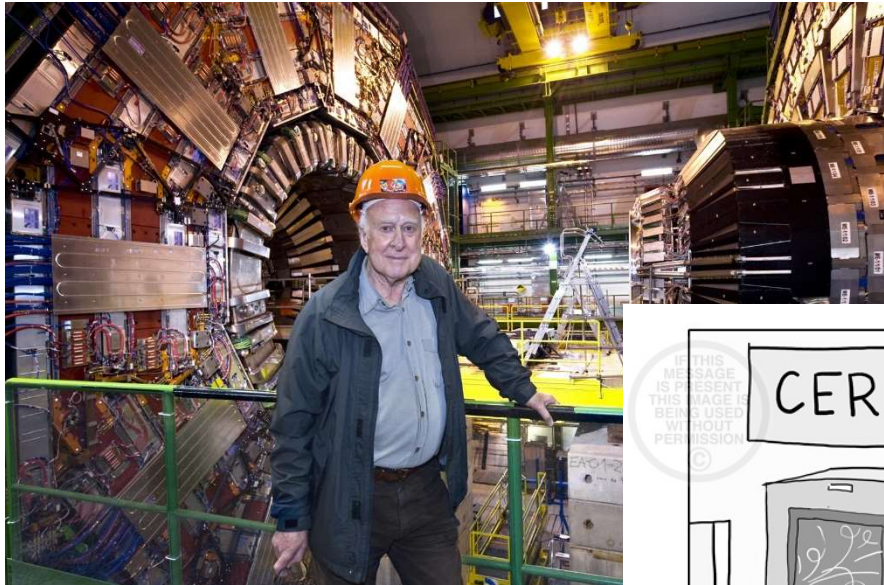- A lot of electronics in the experiments...which impacts the detectors




Electronics enabling new detectors : trackers

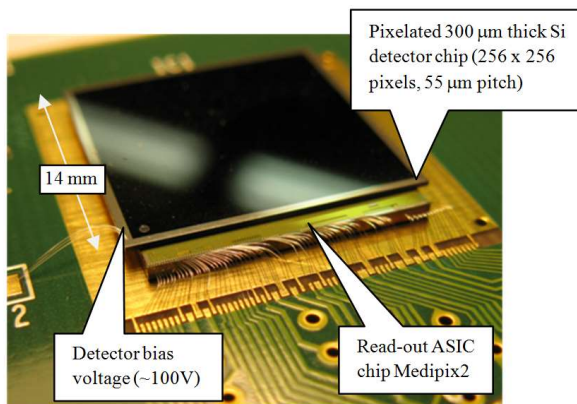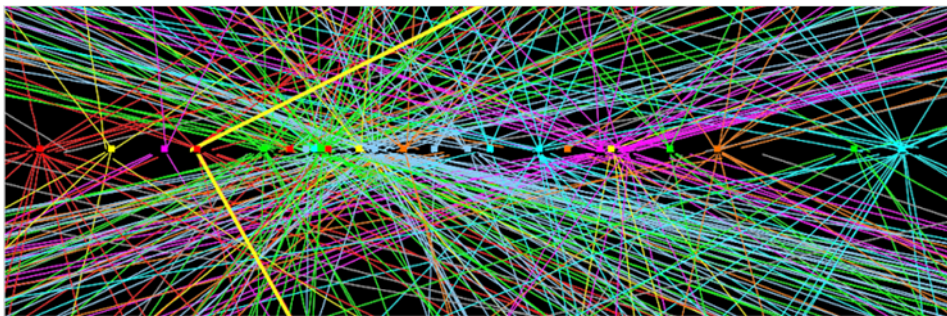
- Measurement of (charged) particle tracks
 - millions of pixels ($\sim 100 \mu\text{m}$)
 - binary readout at 40 MHz
 - High radiation levels
 - Made possible by ASICs



C. de l

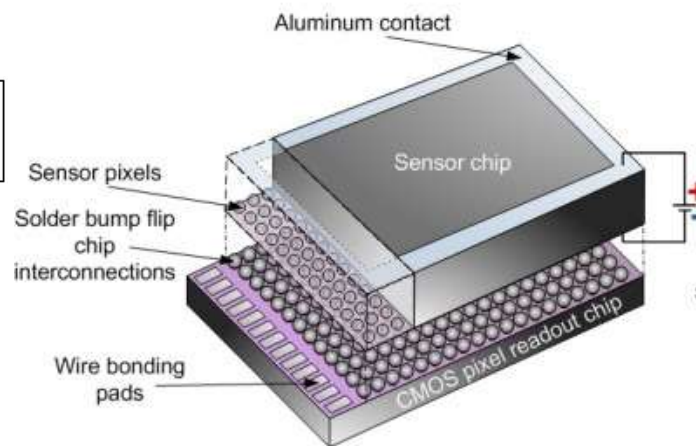

Generic pixel detector


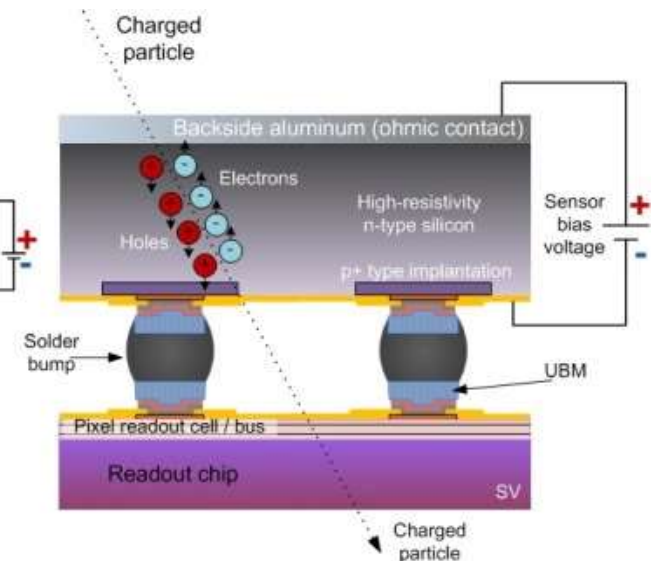


Cross-sectional cut

Importance of electronics : calorimeters








- Large dynamic range (10^4 - 10^5)
- High Precision $\sim 1\%$
 - Importance of low noise, uniformity, linearity...
 - Importance of calibration

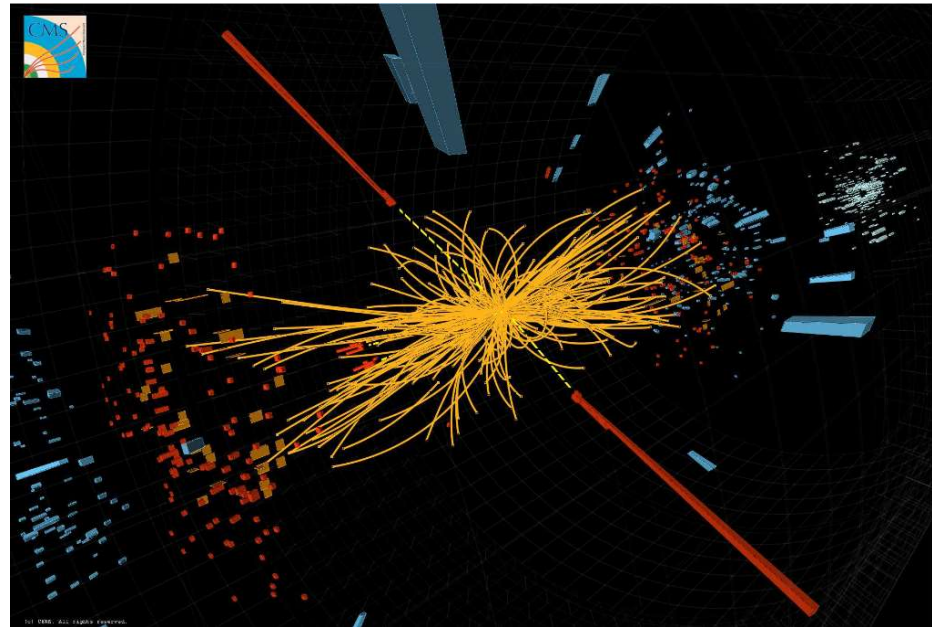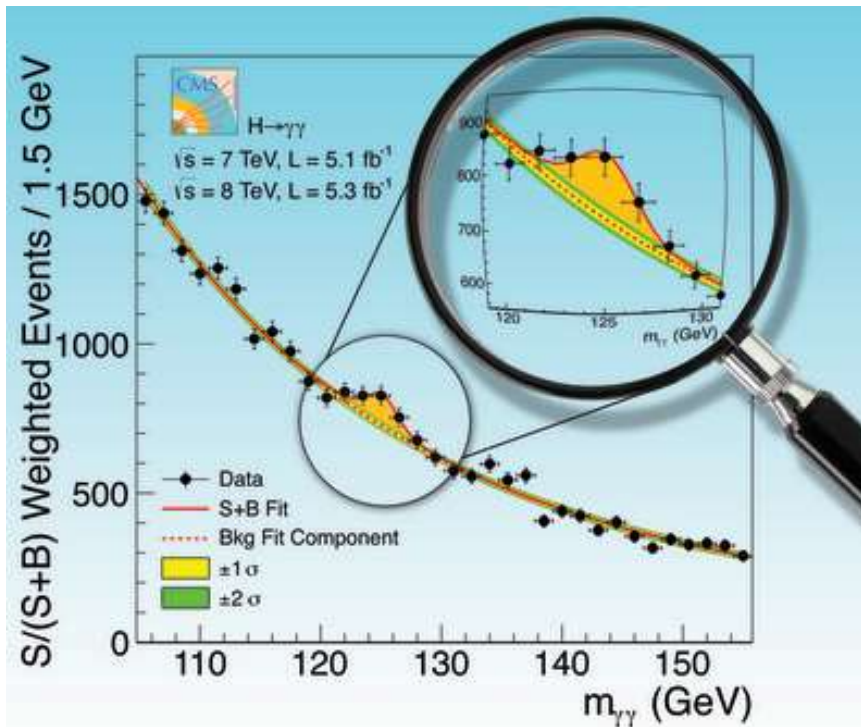H \rightarrow $\gamma\gamma$ in CMS calorimeter



Single photon sensors & timing information

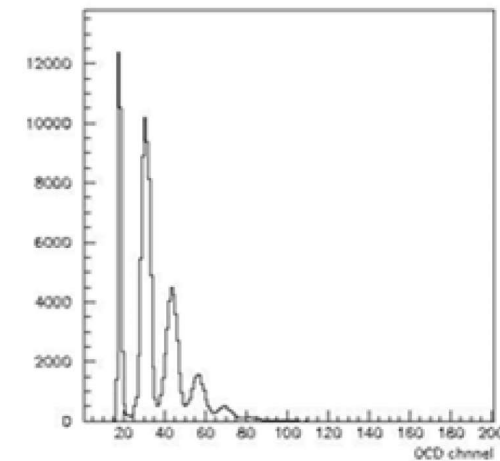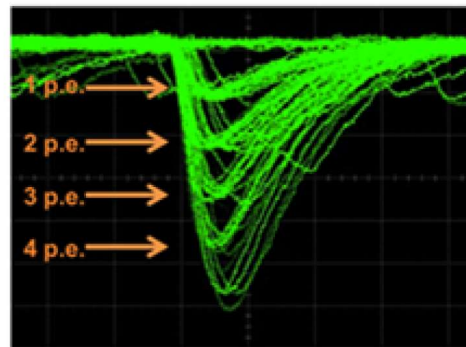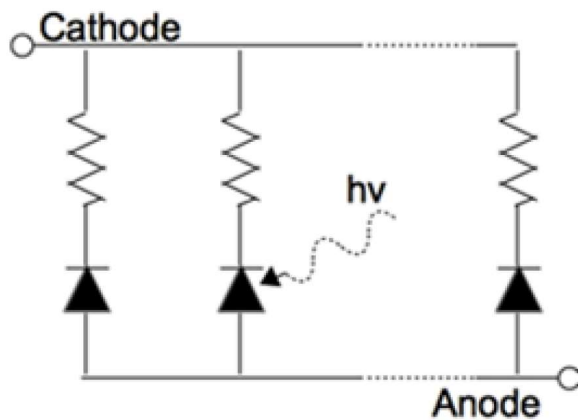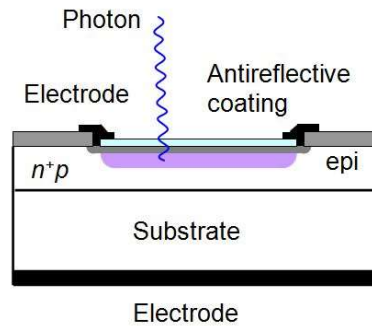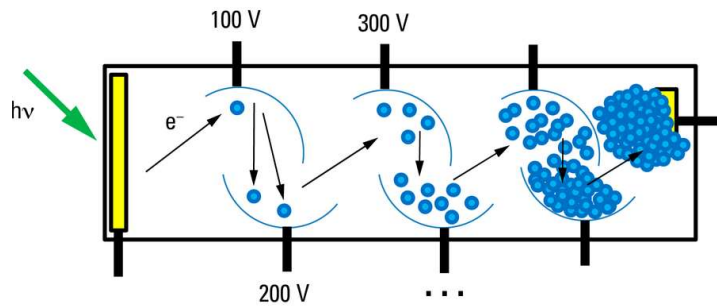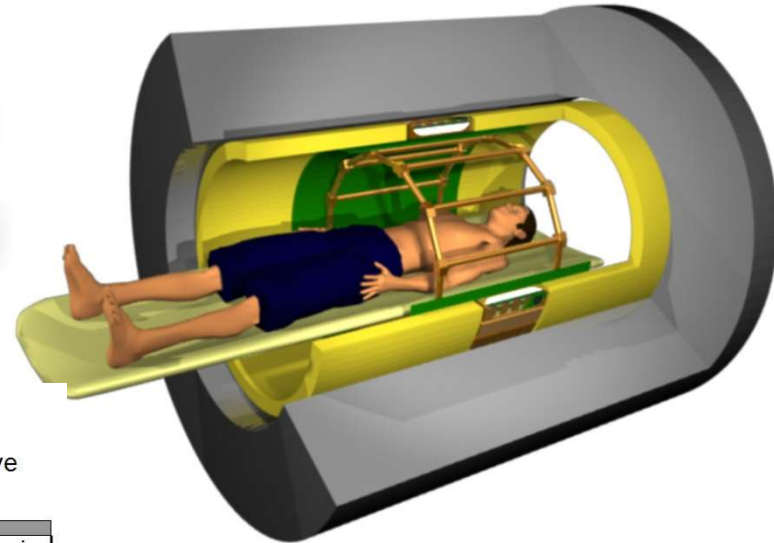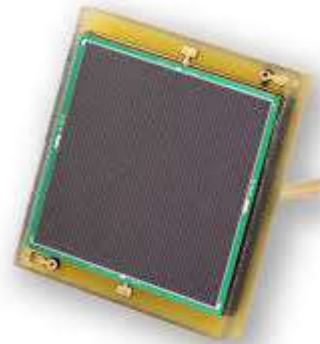- Photomultipliers, silicon photomultipliers




C. de La Taille


FEDSS Weihai Summer school 2018

Overview of readout electronics

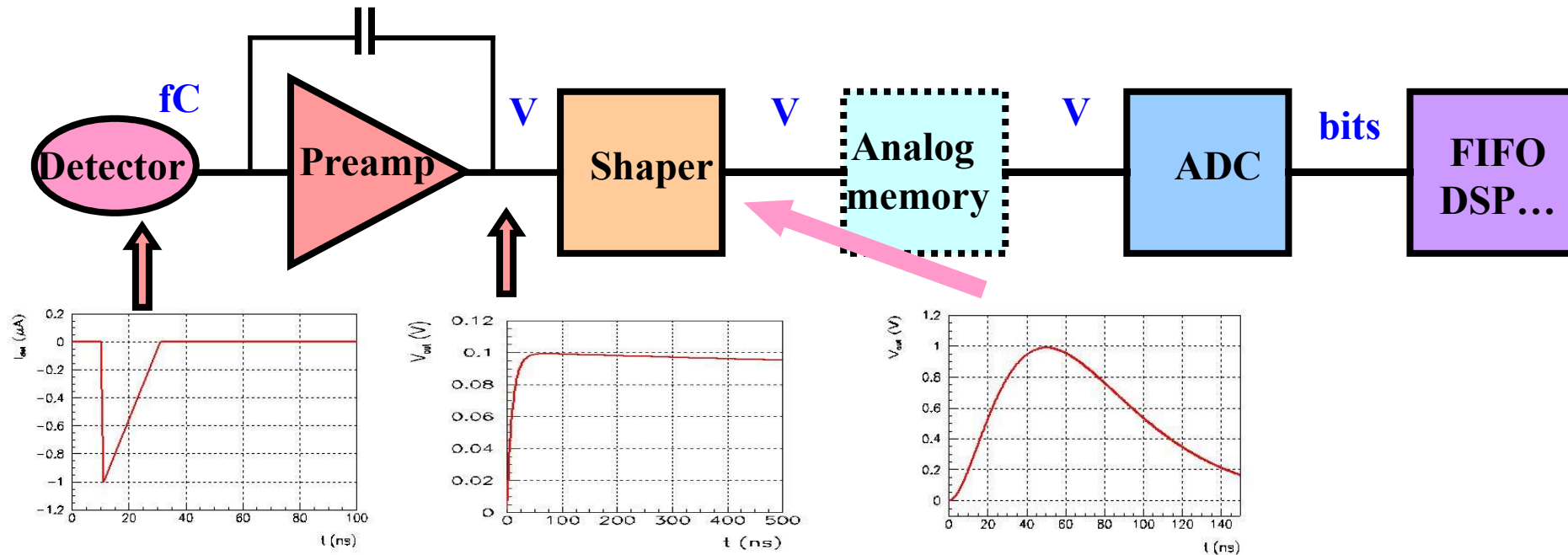- Most front-ends follow a similar architecture



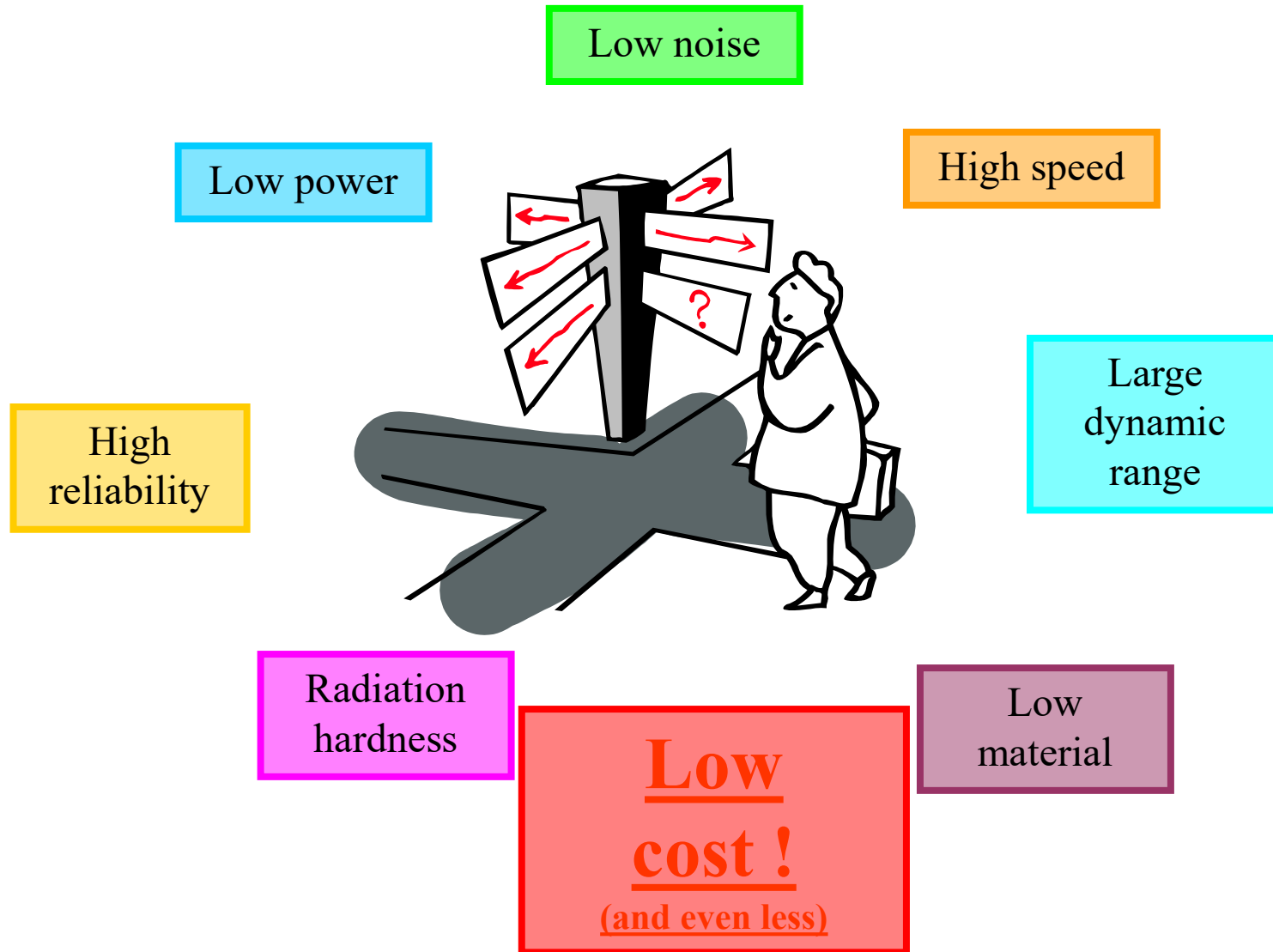- n Very small signals (fC) -> need **amplification**
- n Measurement of **amplitude** and/or **time** (ADCs, discris, TDCs)
- n Several thousands to millions of channels
- n **Trends** : high speed, low power




Detector modelization

- Detector = capacitance C_d
 - Pixels/strips : 0.1-10 pF
 - PMs/SiPMs : 3-300 pF
 - Ionization chambers 10-1000 pF
 - Sometimes effect of transmission line

- Signal : current source
 - Pixels : $\sim 100e^-/\mu m$
 - PMs : 1 photoelectron $\rightarrow 10^5-10^7 e^-$
 - Modelized as an impulse (Dirac) :
 $i(t) = Q_0 \delta(t)$

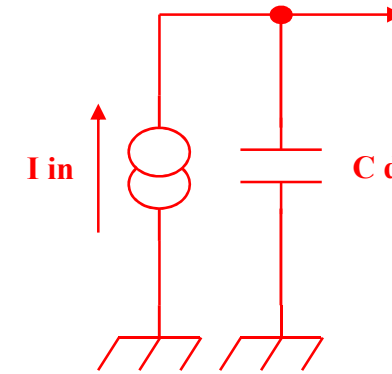
- Missing :
 - High Voltage bias
 - Connections, grounding
 - Neighbours
 - Calibration...



Detector modelization



CMS pixel module

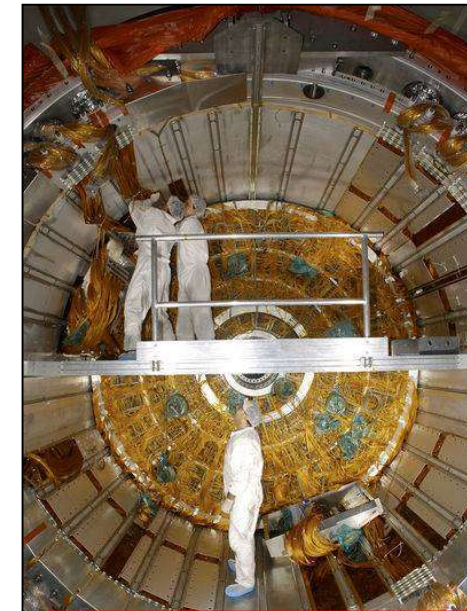

ATLAS LAr calorimeter

Signal & Source modelization (cf part 2)

Vacuum Photomultipliers

$$G = 10^5 - 10^7$$

$$C_d \sim 10 \text{ pF}$$

$$L \sim 10 \text{ nH}$$






Silicon Photomultipliers

$$G = 10^5 - 10^7$$

$$C = 10 - 400 \text{ pF}$$

$$L = 1 - 10 \text{ nH}$$

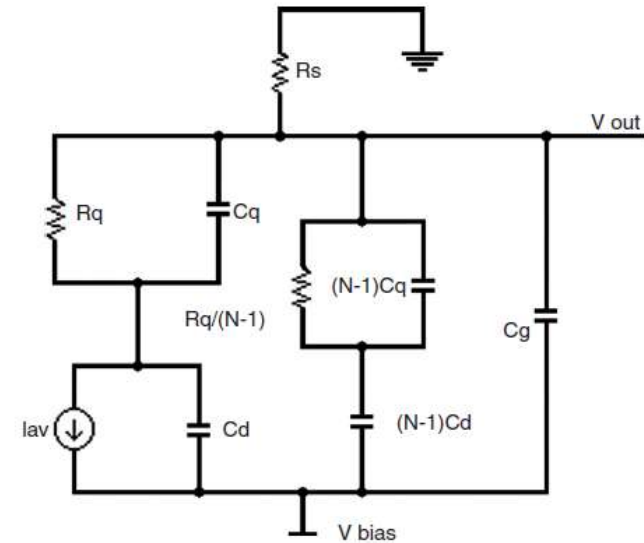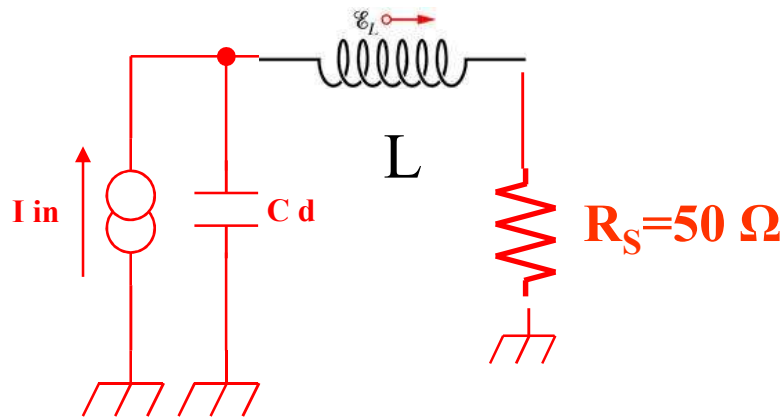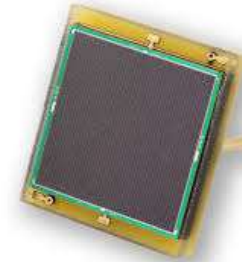

Optimizing signal shape for timing


Collazuol
2012

Single cell model $\rightarrow (R_d || C_d) + (R_q || C_q)$

SiPM + load $\rightarrow (||Z_{cell}) || C_{grid} + Z_{load}$


Signal = **slow** pulse ($\tau_{d (rise)}, \tau_{q-slow (fall)}$) + **fast** pulse ($\tau_{d (rise)}, \tau_{q-fast (fall)}$)

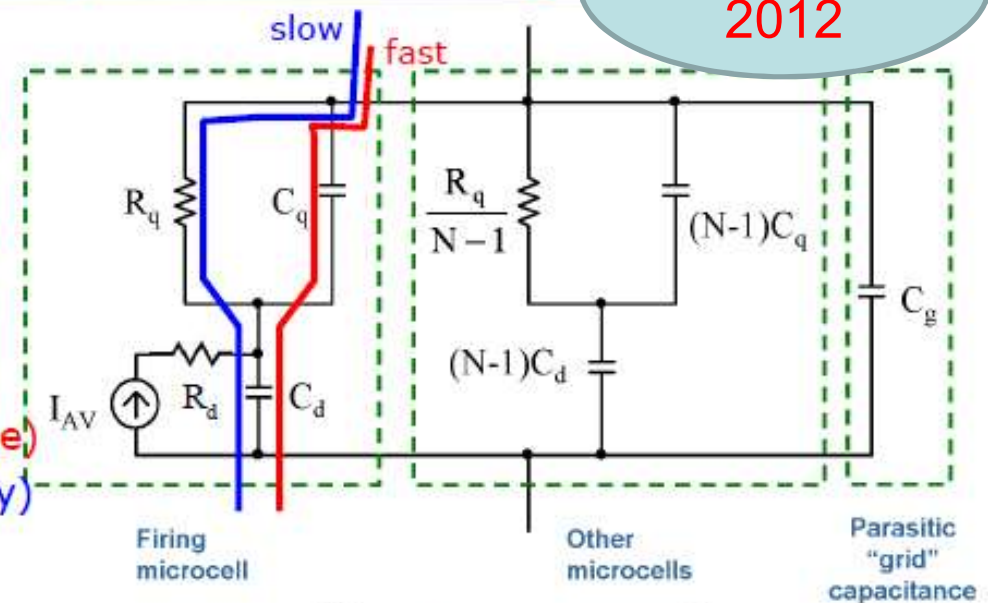- $\tau_{d (rise)} \sim R_d (C_q + C_d)$
- $\tau_{q-fast (fall)} = R_{load} C_{tot}$ (fast; parasitic spike)
- $\tau_{q-slow (fall)} = R_q (C_q + C_d)$ (slow; cell recovery)



Pulse shape
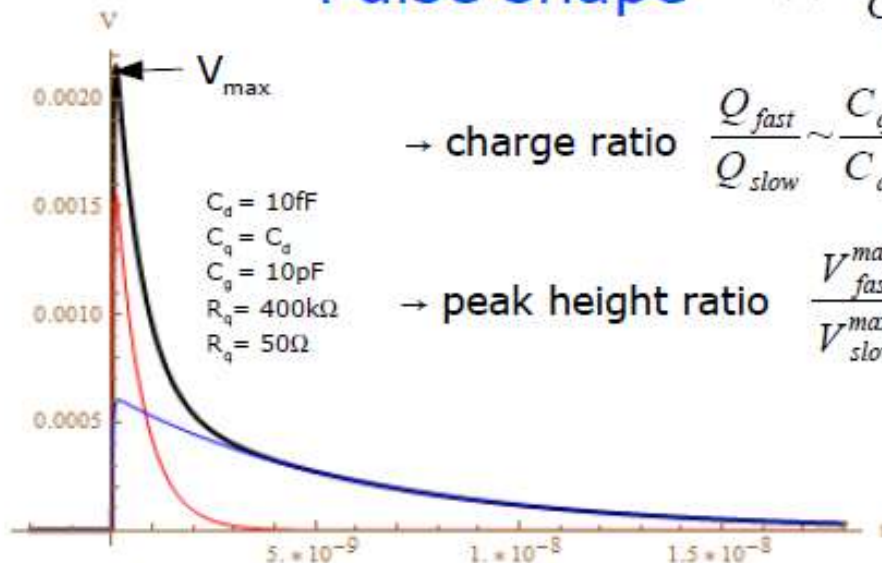
$$V(t) \simeq \frac{Q}{C_q + C_d} \left(\frac{C_q}{C_{tot}} e^{-\frac{t}{\tau_{FAST}}} + \frac{R_{load}}{R_q} \frac{C_d}{C_q + C_d} e^{-\frac{t}{\tau_{SLOW}}} \right)$$



→ charge ratio $\frac{Q_{fast}}{Q_{slow}} \sim \frac{C_q}{C_d}$


→ peak height ratio $\frac{V_{fast}^{max}}{V_{slow}^{max}} \sim \frac{C_q^2 R_q}{C_d C_{tot} R_{load}}$ increasing with R_q and $1/R_{load}$ (and C_q of course)

Increasing C_q/C_d or/and R_q/R_{load}
 → spike enhancement
 → better timing


Reading the signal

- Signal
 - Signal = current source
 - Detector = capacitance C_d
 - Quantity to measure
 - Charge => integrator needed
 - Time => discriminator + TDC

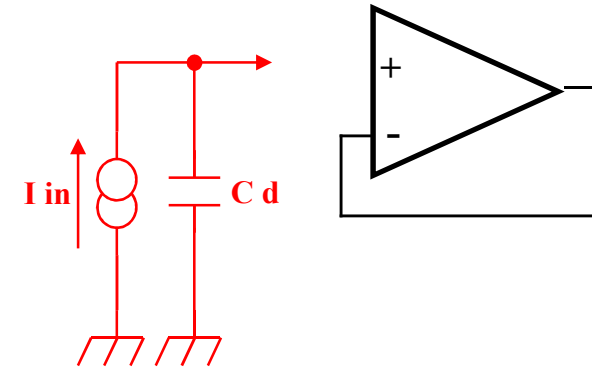- Integrating on C_d
 - Simple : $V = Q/C_d$
 - « Gain » : $1/C_d$: 1 pF -> 1 mV/fC
 - Need a follower to buffer the voltage... => parasitic capacitance
 - Gain loss, possible non-linearities
 - crosstalk
 - Need to empty C_d ...





Voltage readout

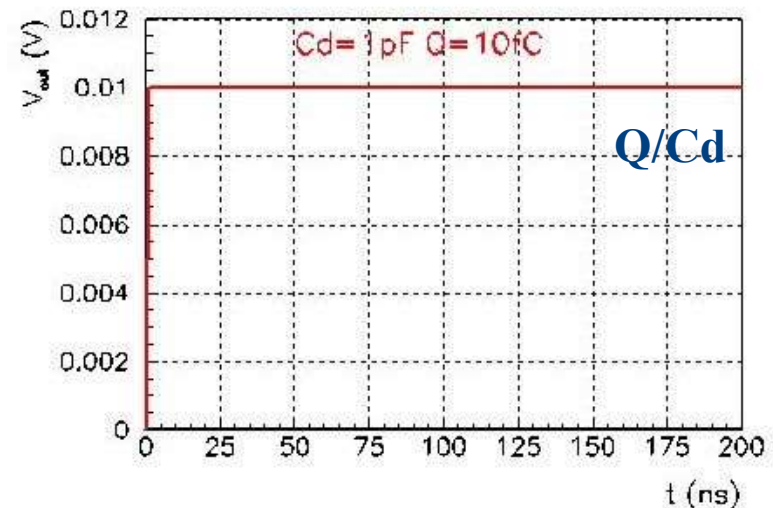

Impulse response


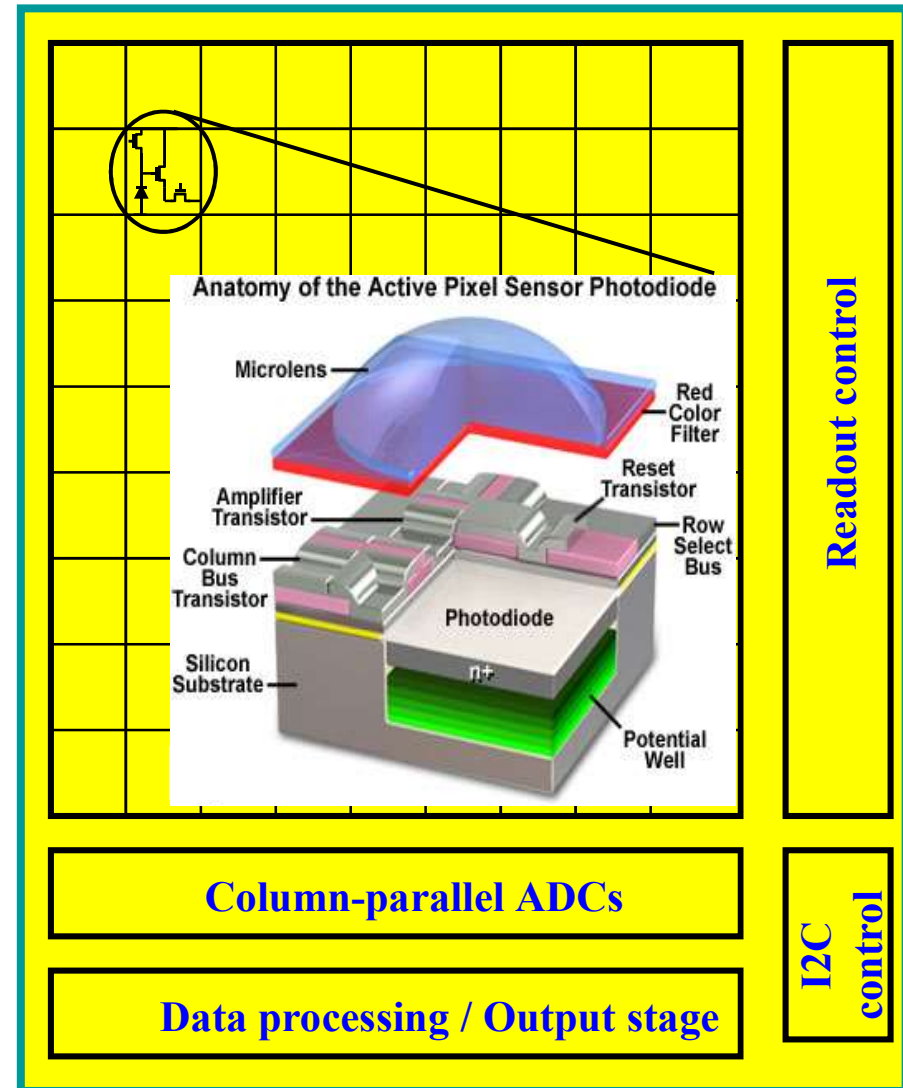
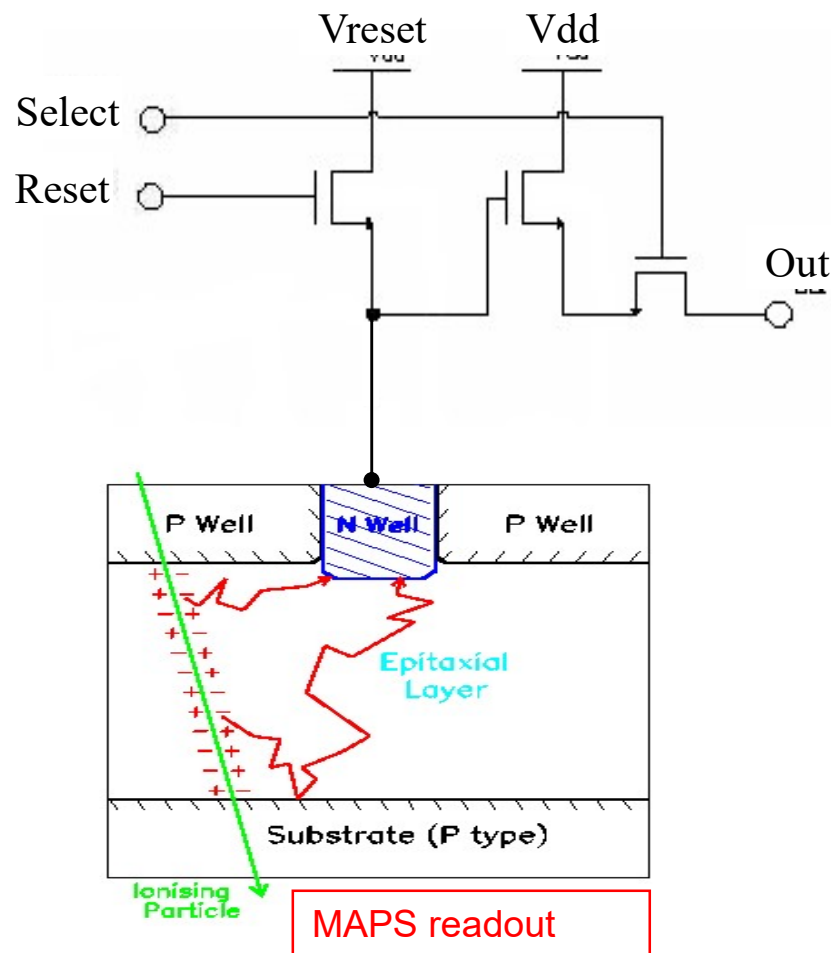
Example : Monolithic active pixels

- Epitaxial layer forms sensitive volume (2-20 μm)
- Charge collection by diffusion
- Read $\sim 100\text{ e}^-$ on $C_d \sim 10\text{fF}$ = few mV



MAPS in HEP : see talk by C. Hu

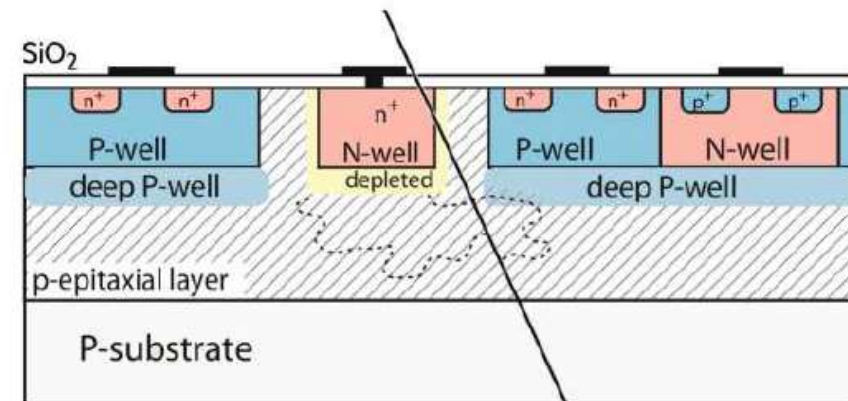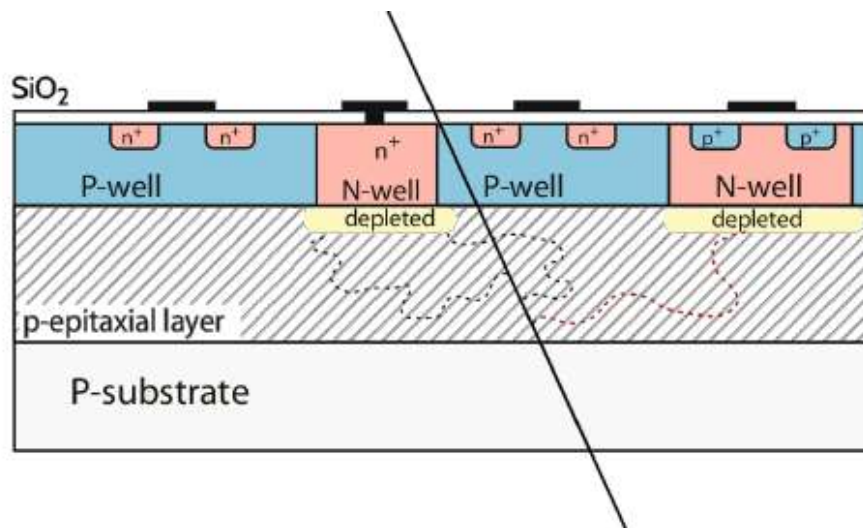
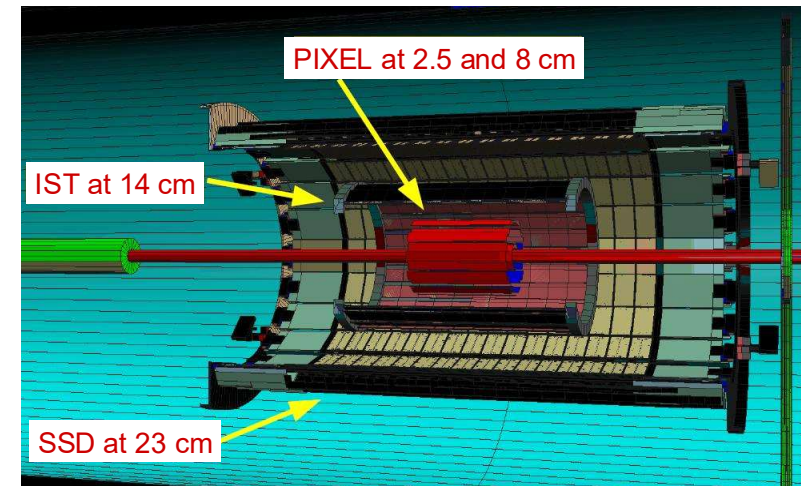
- MIMOSTAR [IPHC strasbourg et al.]
 - First use in HEP : STAR detector 2014
 - 2 cm² ASIC with 21x21 um pixels
- ALPIDE for ALICE upgrade [CERN et al.]
 - Several process and design improvements
 - Deep pwell to allow CMOS
 - In-pixel preamp and comparator
 - P = 40 nW/pixel (5 mW/cm²)



© C. Sauer Heidelberg


ALPIDE preamplifier

- Far from the 3T design...

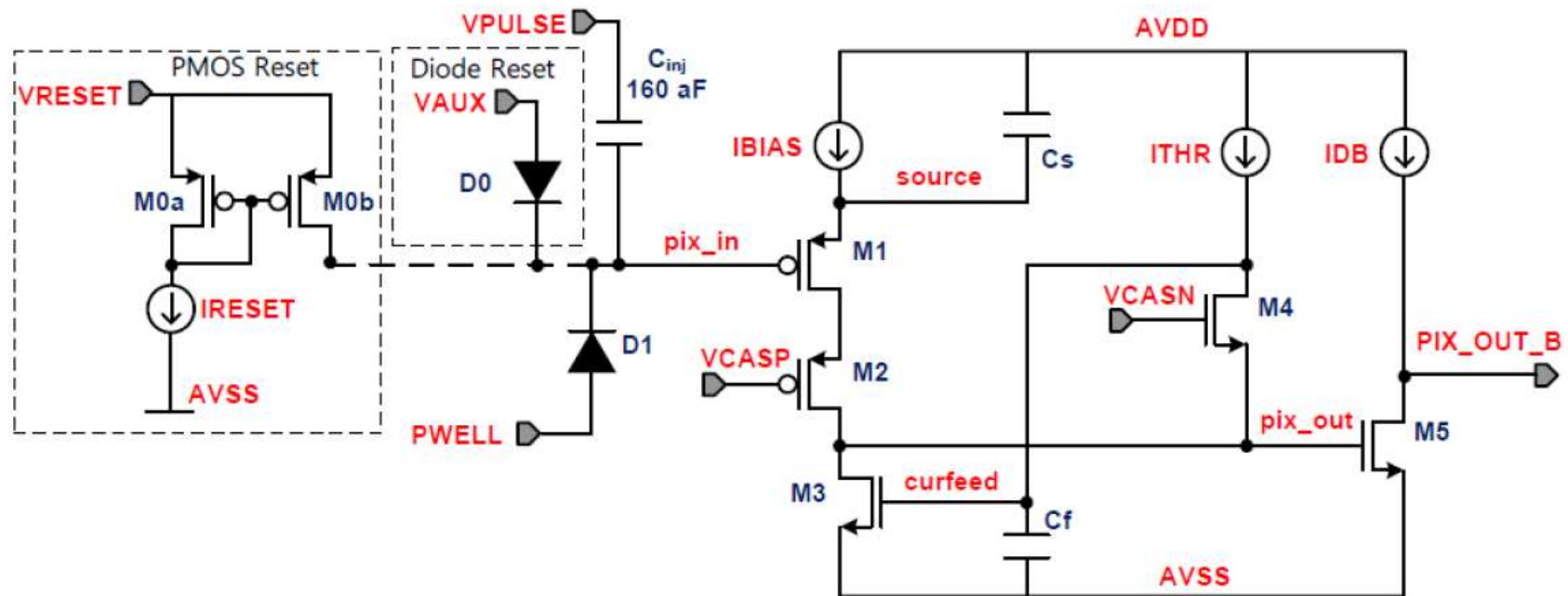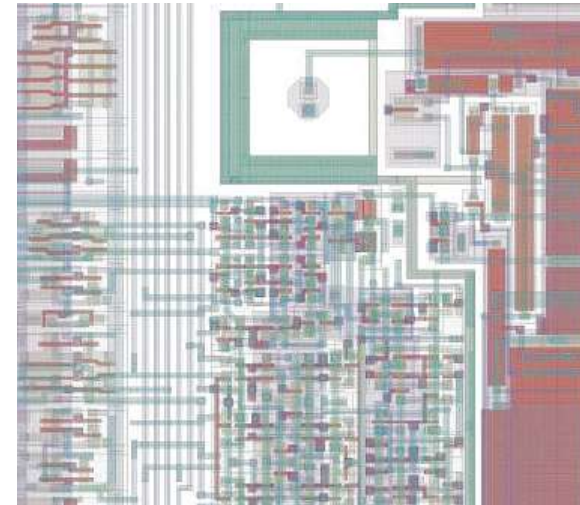

Evolution of MAPs

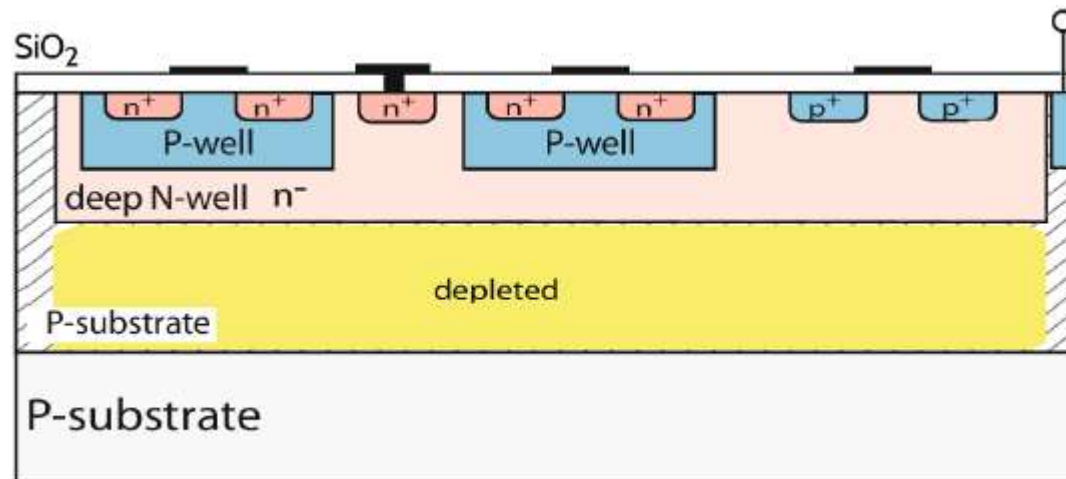- Going to HV-MAPS [I. Peric U. Bonn]
 - HV CMOS process => partial/full sensor depletion
 - Collection by drift and not diffusion => fast signal \sim ns
 - Better radiation tolerance
 - Nanosecond timing capability
 - Proposed for ATLAS upgrade and μ 3e




Ideal charge preamplifier

- ideal opamp in transimpedance ($C_f \ll C_d$)
 - Shunt-shunt feedback : low Z_{in} , low Z_{out}
 - $i_{in}(\omega) = j\omega C_d V_{in}(\omega) + j\omega C_f (V_{in}(\omega) - V_{out}(\omega))$
 - $V_{out}(\omega) = -G V_{in}(\omega)$ (opamp gain)
 - $\Rightarrow V_{out}(\omega)/i_{in}(\omega) = -1/j\omega C_f (1 + C_d / GC_f)$
 - Ideal opamp : $G \rightarrow \infty$
 - $V_{out}(\omega)/i_{in}(\omega) = -1/j\omega C_f$
 - Integrator : $v_{out}(t) = -1/C_f \int i_{in}(t) dt$


$$v_{out}(t) = -Q/C_f$$

- « Gain » : $1/C_f$: 0.1 pF \rightarrow 10 mV/fC
- C_f determined by maximum signal

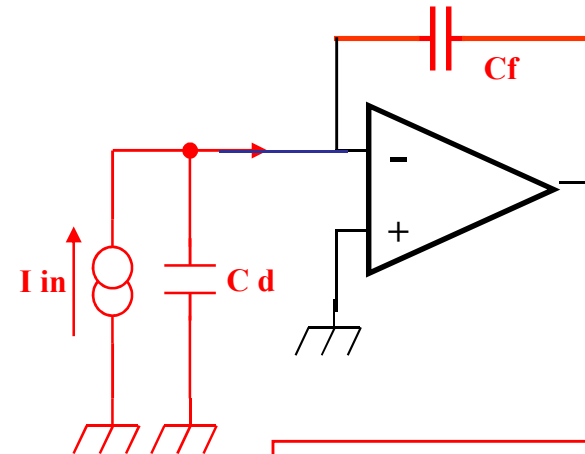- Integration on C_f
 - Simple : $V = -Q/C_f$
 - Unsensitive to preamp capacitance C_p
 - Turns a short signal into a long one
 - The front-end of 90% of particle physic:
 - But always built with custom circuits...




Charge sensitive preamp

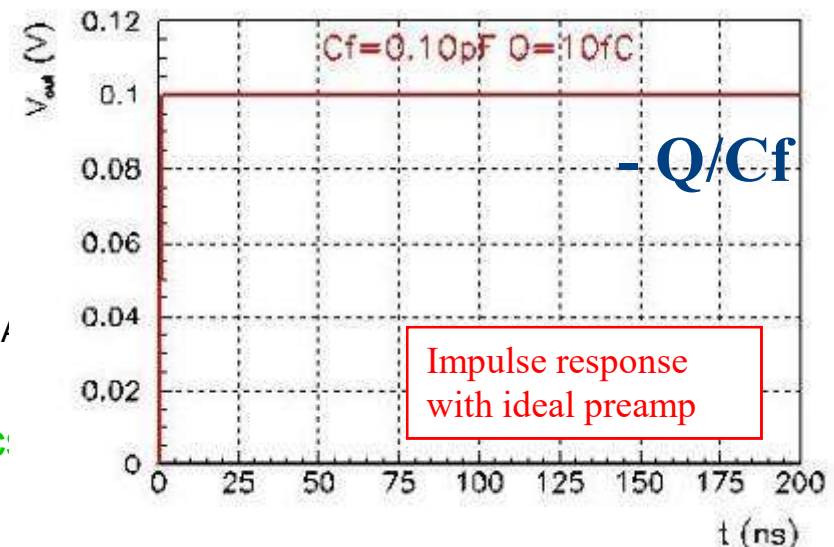

Preamp speed

- Finite opamp gain
 - $V_{out}(\omega)/i_{in}(\omega) = -Z_f / (1 + C_d / G_0 C_f)$
 - Small signal loss in $C_d/G_0 C_f \ll 1$
(ballistic deficit)
- Finite opamp bandwidth
 - First order open-loop gain
 - $G(\omega) = G_0/(1 + j \omega/\omega_0)$
 - G_0 : low frequency gain
 - $G_0\omega_0$: gain bandwidth product
 - $V_{out}(\omega)/i_{in}(\omega) = - 1/j\omega C_f (1+j\omega C_d/G_0\omega_0 C_f)$
- Preamp risetime
 - Time constant : τ (*tau*)
 - $\tau = C_d/G_0\omega_0 C_f$
 - Rise-time : $t_{10-90\%} = 2.2 \tau$
 - Rise-time optimised with w_C or C_f


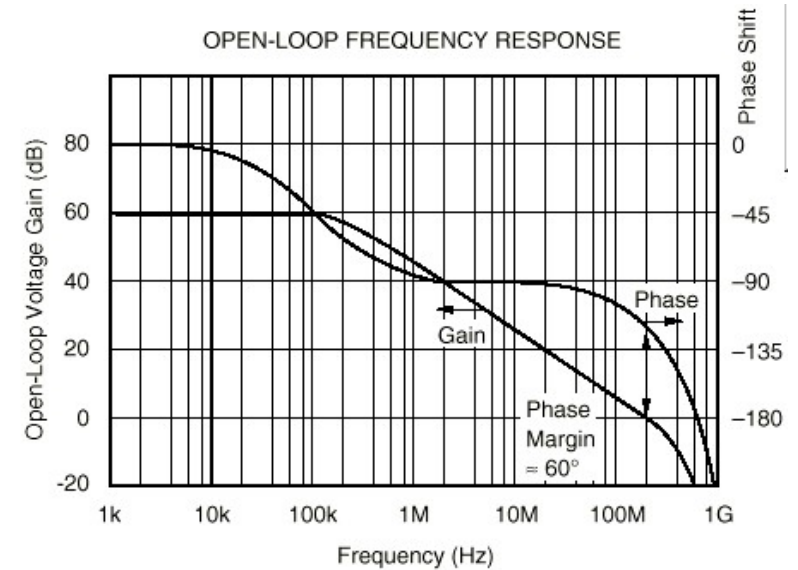


Impulse response with non-ideal preamp

Charge preamp seen from the input

- Input impedance with ideal opamp
 - $Z_{in} = Z_f / G+1$
 - $Z_{in} \rightarrow 0$ for ideal opamp
 - « Virtual ground » : $V_{in} = 0$
 - Minimizes sensitivity to detector impedance
 - Minimizes crosstalk

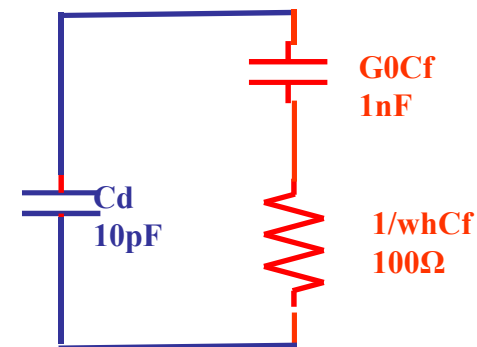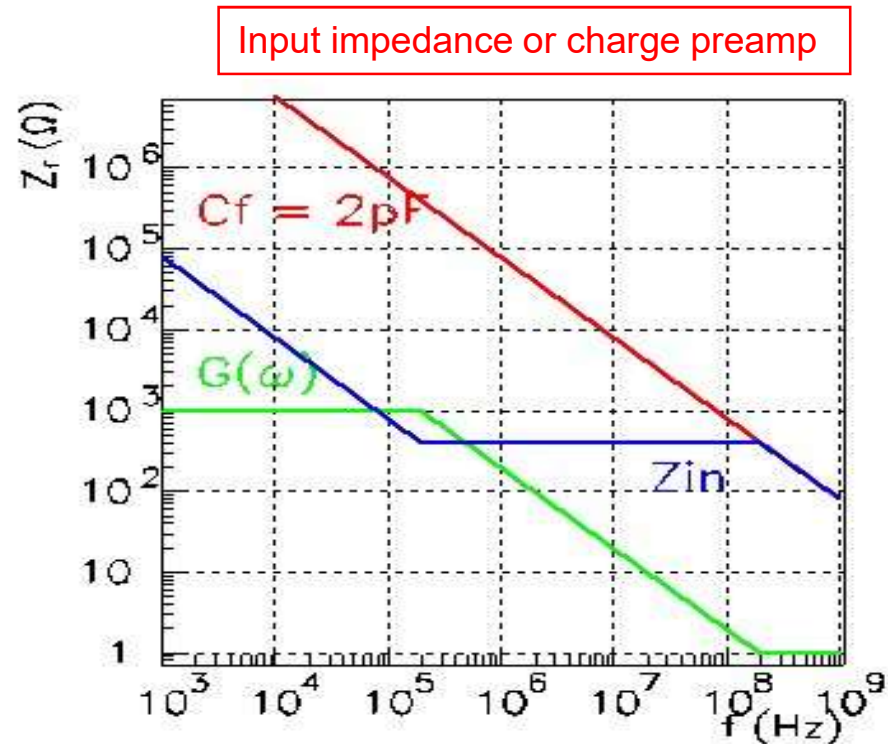- Input impedance with real opamp
 - $Z_{in} = 1/j\omega G_0 C_f + 1/ G_0 \omega_0 C_f$
 - Resistive term : $R_{in} = 1/ G_0 \omega_0 C_f$
 - Exemple : $\omega_C = 10^{10}$ rad/s $C_f = 1$ pF $\Rightarrow R_{in} = 100 \Omega$
 - Determines the input time constant : $t = R_{eq} C_d$
 - Good stability= (...!)
 - Equivalent circuit :




Electronically cooled resistors [TNS 73]

SIGNAL, NOISE AND RESOLUTION IN POSITION-SENSITIVE DETECTORS*

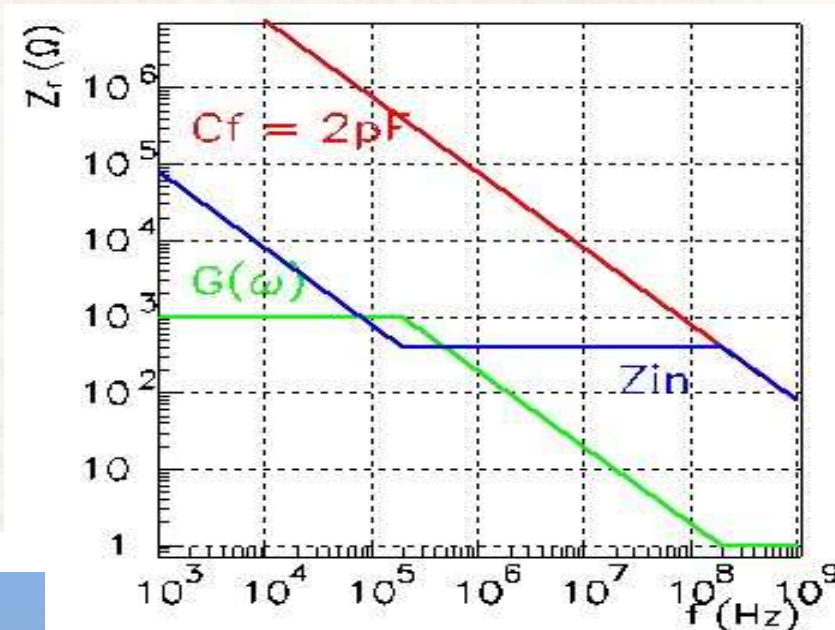
V. Radeka
Brookhaven National Laboratory
Upton, N. Y. 11973

ABSTRACT


An analysis is presented of signal, noise and position resolution relations for some of the most interesting position-sensing methods. "Electronic cooling" of delay line terminations is introduced in order to reduce noise in the position-sensing with delay lines. A new method for terminating transmission lines and for "noiseless" damping which employs a capacitance in feedback is presented. It is shown that the position resolution for the charge division method with resistive electrodes is determined only by the electrode capacitance and not by the electrode resistance, if optimum filtering is used.


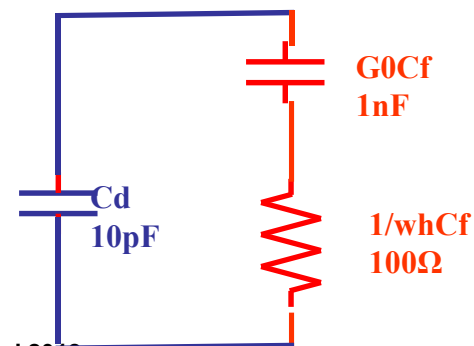
$$Z_{in} = 1/j\omega G_0 C_F + 1/ G_0 \omega_0 C_F$$




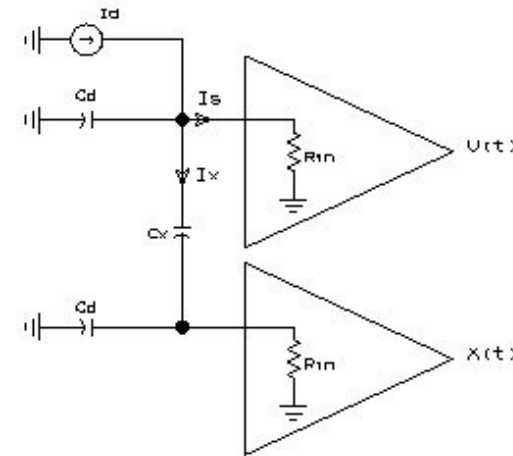- Capacitive coupling between neighbours
 - Crosstalk signal is **differentiated and with same polarity**
 - Small contribution at signal peak
 - Proportionnal to C_x/C_d and preamp input impedance
 - Slowed derivative if $R_{in}C_d \sim t_p \Rightarrow$ non-zero at peak




Crosstalk electrical modelization

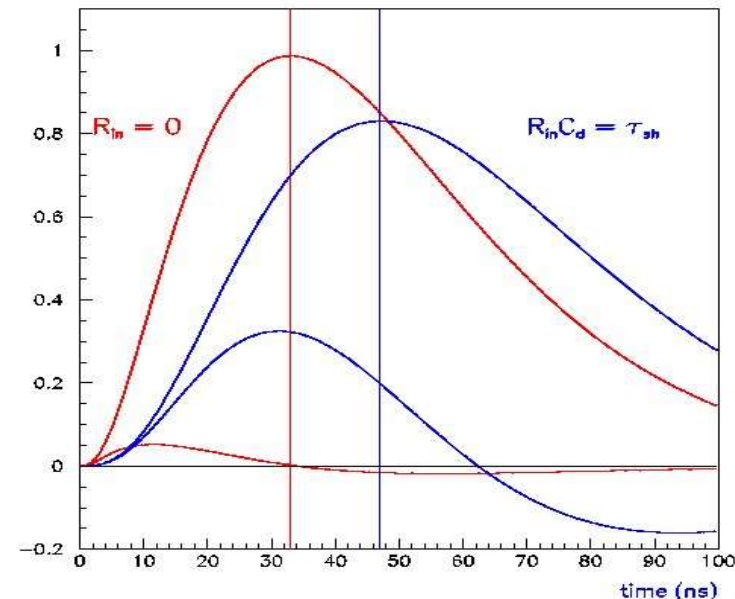- Long distance crosstalk
 - Inductive/resistive common ground return
 - References impedance
 - Connectors : mutual inductance




Charge preamplifier schematics

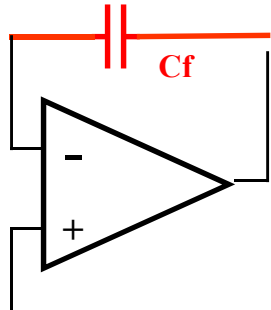
- More details after the section on noise




Charge preamp

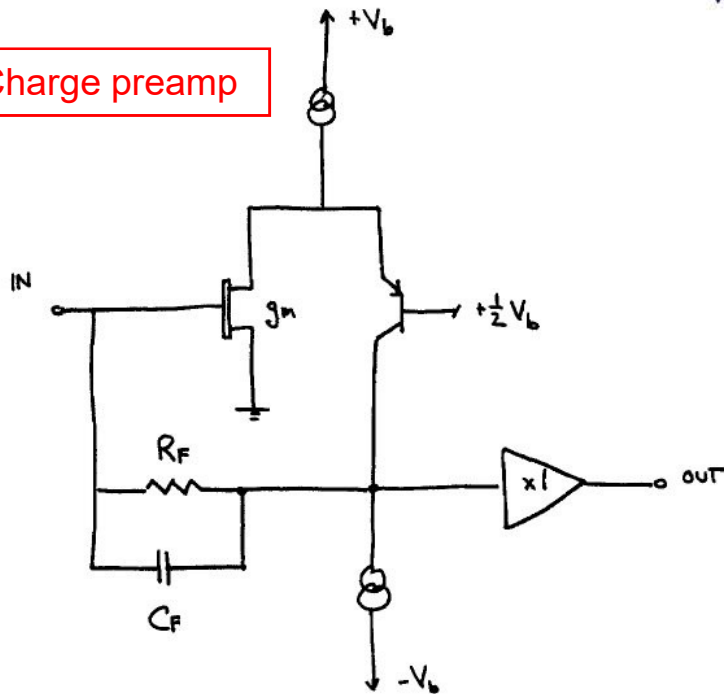

Charge preamp ©Radeka 68

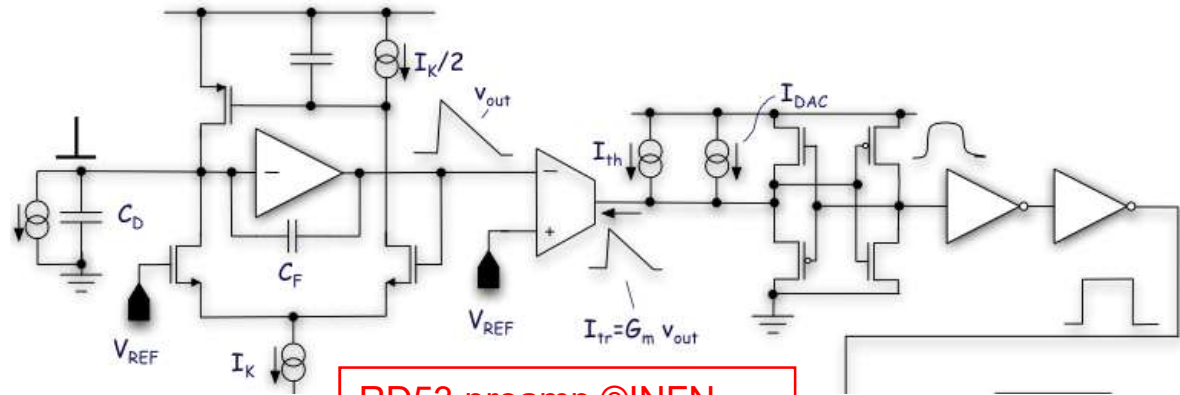


RD53 preamp ©INFN

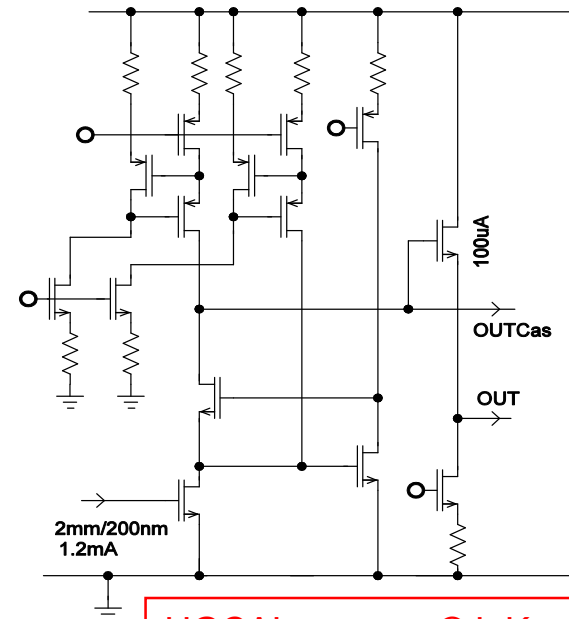

HGCal preamp ©J. Kaplon




Electronics noise

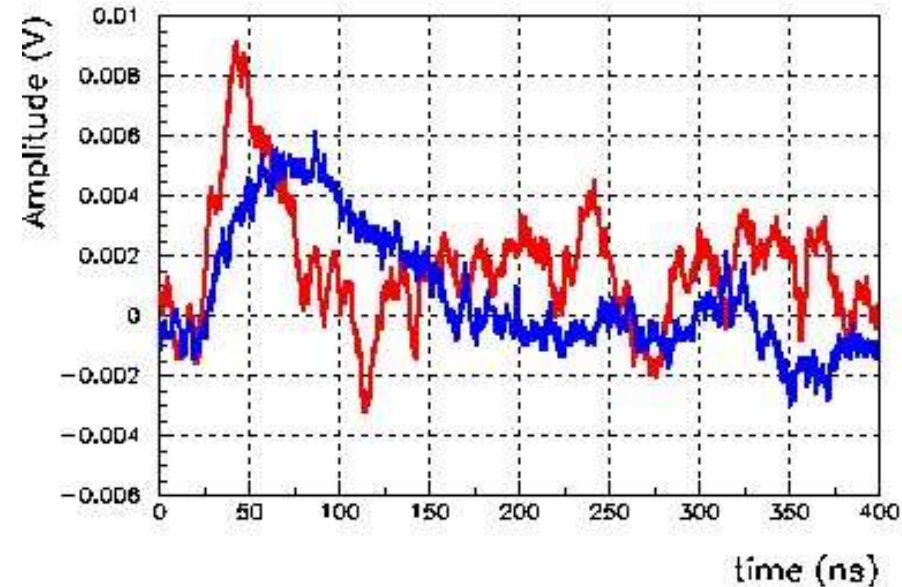- Definition of Noise
 - Random fluctuation superposed to interesting signal
 - Statistical treatment
- Three types of noise
 - Fundamental noise (Thermal noise, shot noise)
 - Excess noise ($1/f$...)
 - Parasitics -> EMC/EMI (pickup noise, ground loops...)




Electronics noise

- Modelization
 - Noise generators : $e_n, i_n,$
 - Noise spectral density of e_n & i_n : $S_v(f)$
 - $S_v(f) = | \mathcal{F}(e_n) |^2$ (V^2/Hz)
- Rms noise V_n
 - $V_n^2 = \int e_n^2(t) dt = \int S_v(f) df$
 - White noise (e_n) : $v_n = e_n \sqrt{\frac{1}{2}\pi f_{-3dB}}$

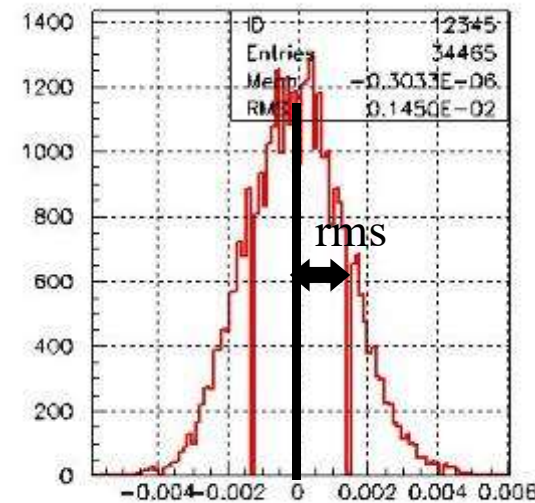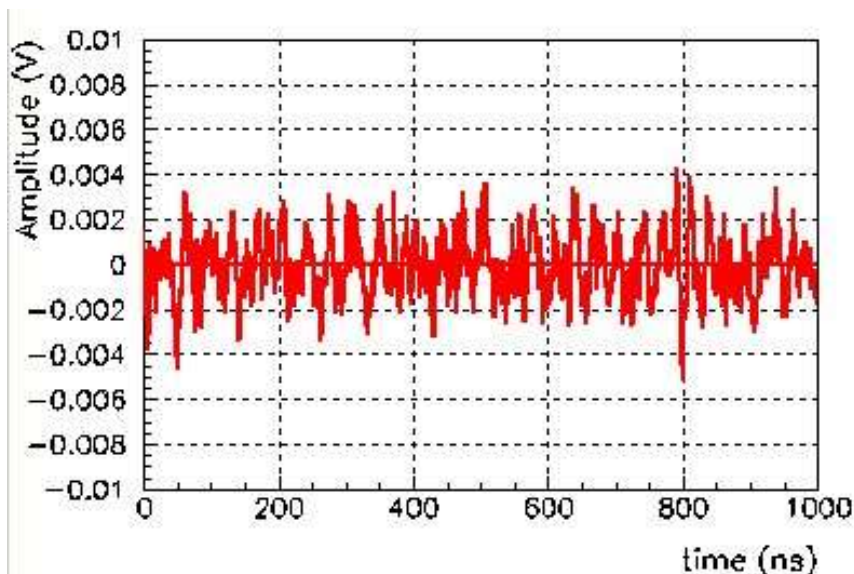
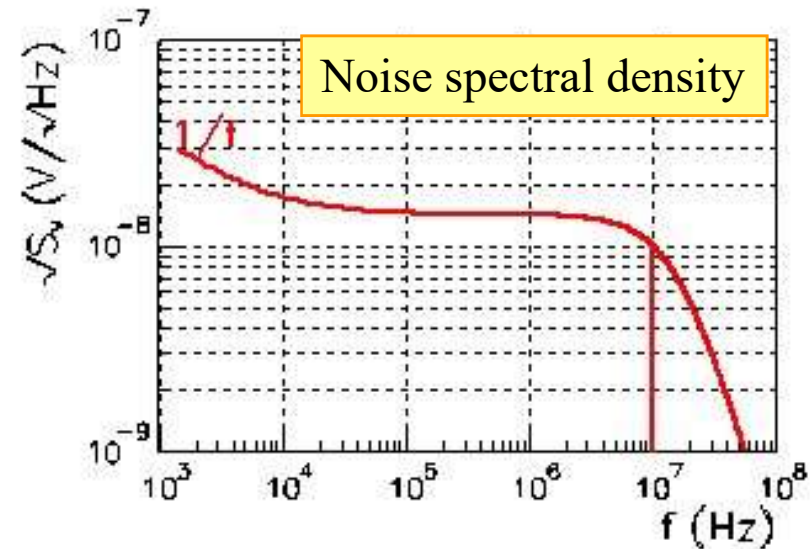


Calculating electronics noise

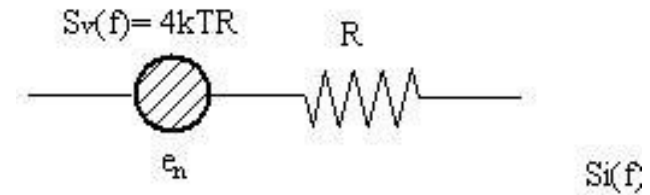- Fundamental noise
 - Thermal noise (**resistors**) : $S_v(f) = 4kTR$
 - Shot noise (**junctions**) : $S_i(f) = 2qI$



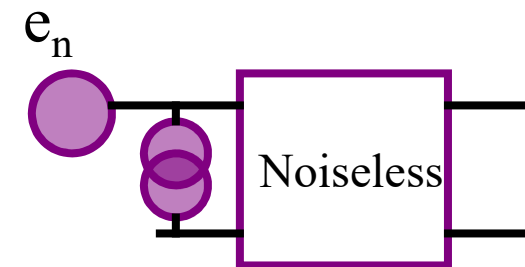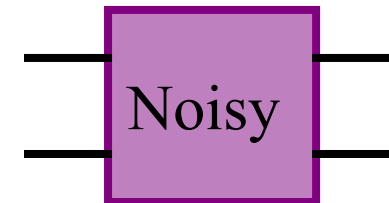- Noise referred to the input
 - All noise generators can be referred to the input as **2** noise generators :
 - A voltage one e_n in series : **series noise**
 - A current one i_n in parallel : **parallel noise**
 - Two generators : no more, no less...



■ **To take into account the Source impedance**

■ **Golden rule :**

■ **Always calculate the signal before the noise**
what counts is the signal to noise ratio

Noise generators referred to the input

Noise in transimpedance amplifiers




- 2 noise generators at the input
 - Parallel noise : (i_n^2) (leakage)
 - Series noise : (e_n^2) (preamp)


- Output noise spectral density :
 - $S_v(\omega) = (i_n^2 + e_n^2/|Z_d|^2) * |Z_f|^2$

- For charge preamps
 - $S_v(\omega) = i_n^2 / \omega^2 C_f^2 + e_n^2 C_d^2 / C_f^2$
 - Parallel noise in $1/\omega^2$
 - Series noise is flat, with a « noise gain » of C_d/C_f

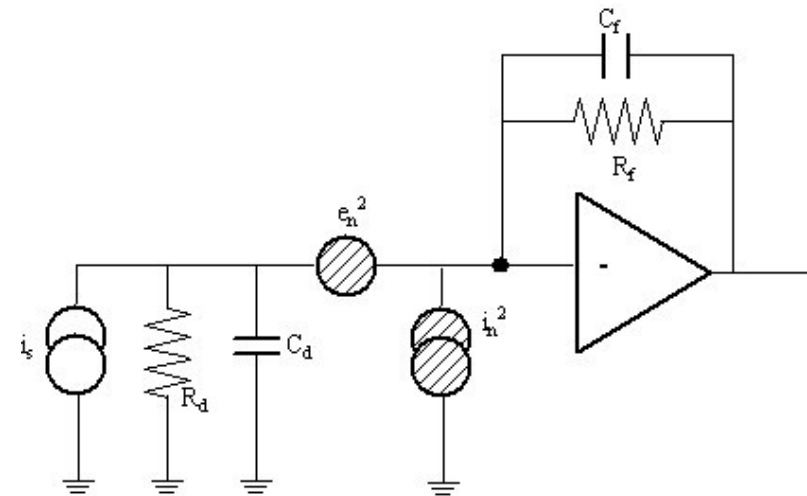- rms noise V_n
 - $V_n^2 = \int S_v(\omega) d\omega / 2\pi \rightarrow \infty$
 - Benefit of shaping ...





Noise generators in charge preamp

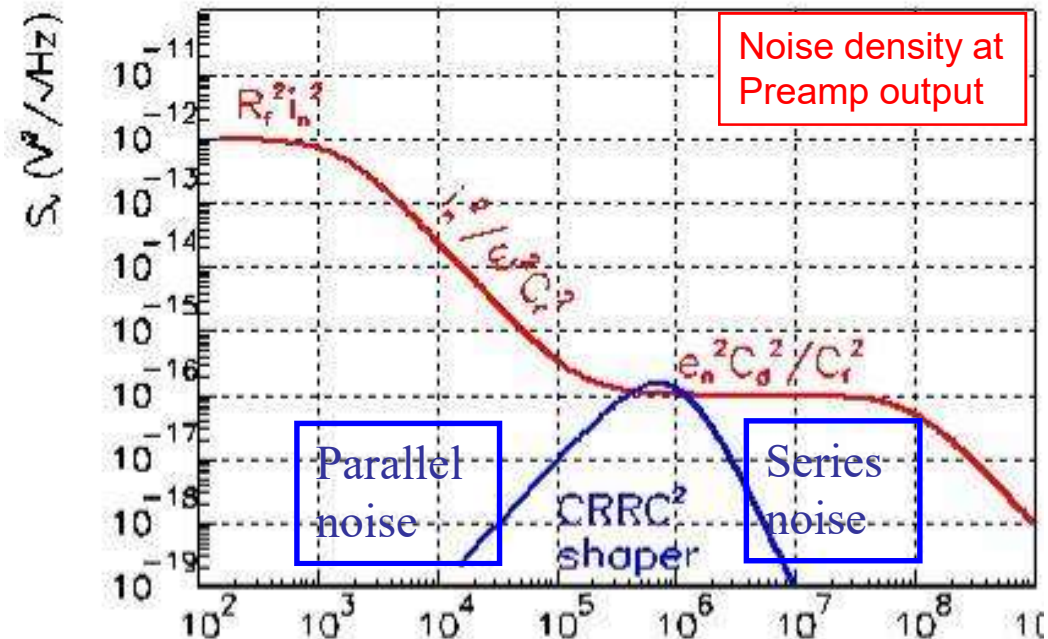

Equivalent Noise Charge (ENC) after CRRCⁿ


- Noise reduction by optimising useful bandwidth
 - Low-pass filters (**RCⁿ**) to cut-off high frequency noise
 - High-pass filter (**CR**) to cut-off parallel noise
 - -> pass-band filter CRRCⁿ
- Equivalent Noise Charge : **ENC**
 - Noise referred to the input in electrons
 - $ENC = I_a(n) e_n C_t / \sqrt{T} \oplus I_b(n) i_n^* \sqrt{T}$
 - Series noise in $1/\sqrt{T}$
 - Parallel noise in \sqrt{T}
 - 1/f noise independant of T
 - Optimum shaping time $T_{opt} = \tau_c / \sqrt{2n-1}$

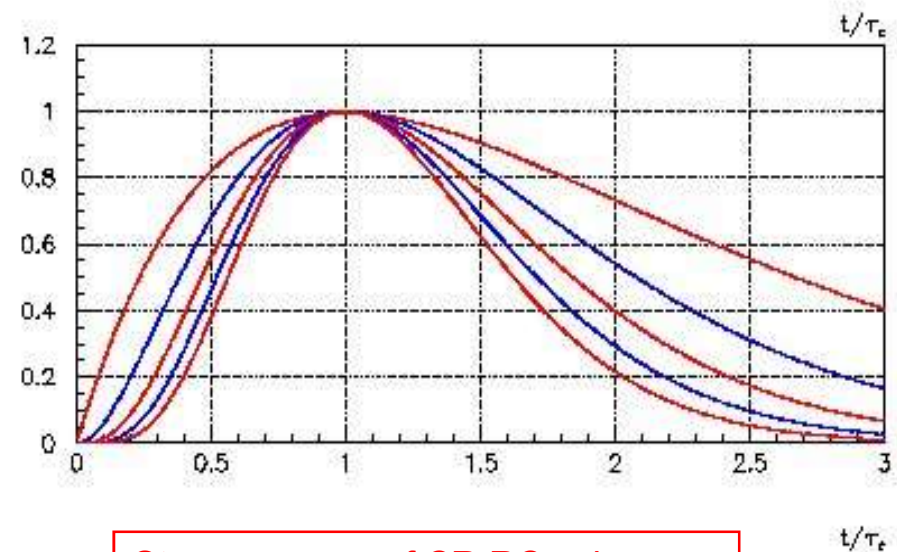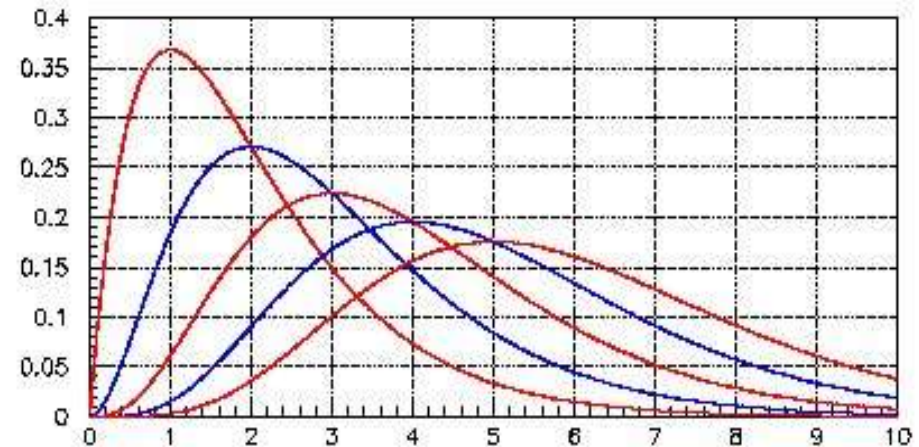

Step response of CR RCⁿ shapers

Equivalent Noise Charge (ENC) after CRRCⁿ

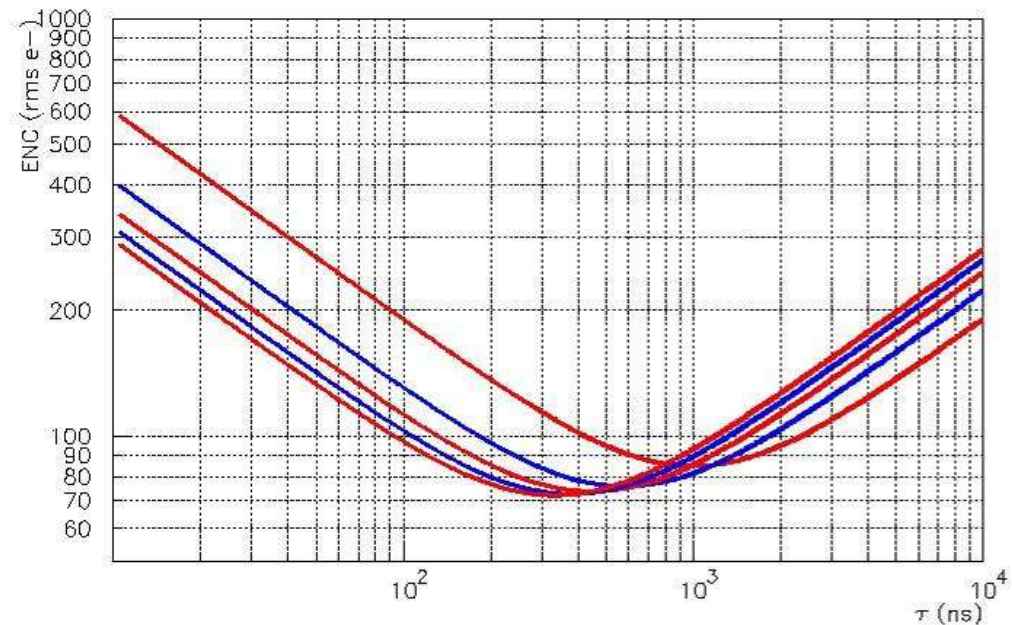- Peaking time t_p (5-100%)
 - ENC(**tp**) independent of n
 - Also includes preamp risetime
- Complex shapers are getting **obsolete** :
 - Power of **digital filtering**
 - Analog filter = CRRC ou CRRC²
 - antialiasing



ENC vs tau for CR RCn shapers

Equivalent Noise Charge (ENC) after CRRCⁿ


- A useful formula : **ENC (e- rms) after a CRRC² shaper :**

$$ENC = 174 e_n C_{tot} / \sqrt{t_p} (\delta) \oplus 166 i_n \sqrt{t_p} (\delta)$$

- e_n in nV/ $\sqrt{\text{Hz}}$, i_n in pA/ $\sqrt{\text{Hz}}$ are the **preamp** noise spectral densities
- C_{tot} (in pF) is dominated by the detector (C_d) + input preamp capacitance (C_{PA})
- t_p (in ns) is the shaper peaking time (5-100%)


■ Noise minimization

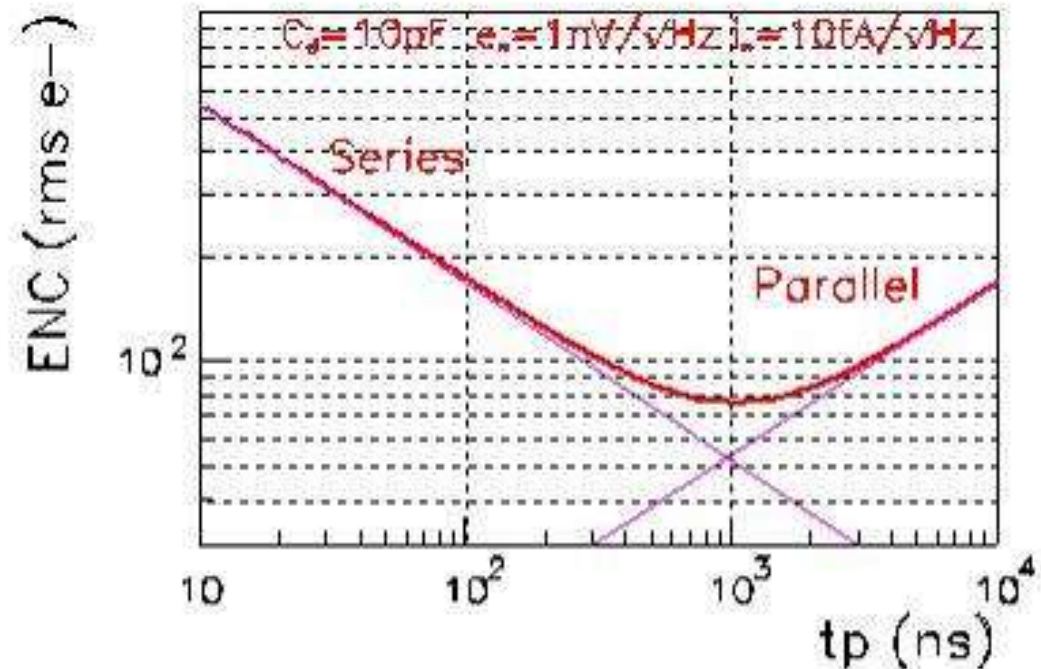- Minimize source capacitance
- Operate at optimum shaping time
- Preamp series noise (e_n) best with high trans-conductance (g_m) in input transistor
=> large current, optimal size




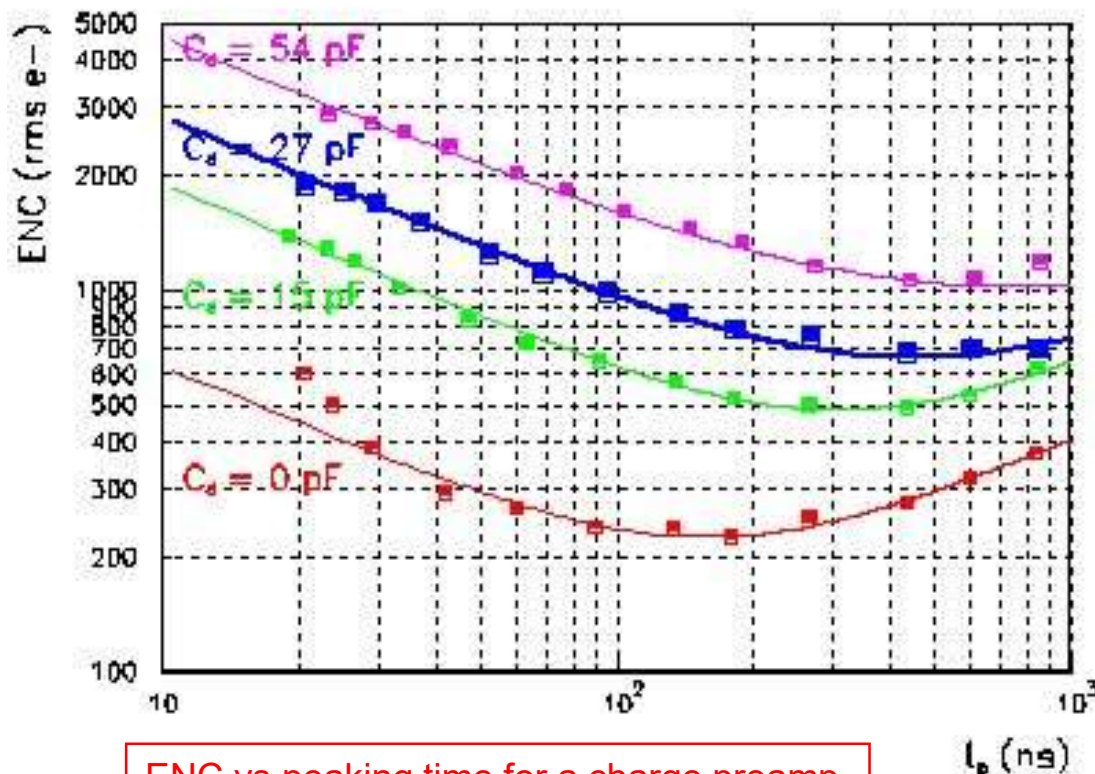Example of ENC measurement

- 2000/0.35 PMOS 0.35 μ m SiGe $I_d=500 \mu$ A
 - Series : $e_n = 1.4 \text{ nV}/\sqrt{\text{Hz}}$, $C_{PA} = 7 \text{ pF}$, $1/f \text{ noise} : 12 \text{ e-}/\text{pF}$, Parallel : $i_n = 40 \text{ fA}/\sqrt{\text{Hz}}$
 - Series noise e_n and Preamp capacitance extraction fitting $\text{ENC}(C_d)$
 - NB : linear fit wrong for e_n and C_{PA} , use quadratic fit :
 - $\text{ENC}^2(C_d) = A e_n^2(C_d+C_{pa})^2/t_p + B i_n^2 t_p + 2^{\text{nd}} \text{ stage}$
 - $\text{ENC}^2(C_d) - \text{ENC}^2(0) = A e_n^2 C_d^2 + 2A e_n^2(C_d+C_{pa})$





ENC vs peaking time for a charge preamp

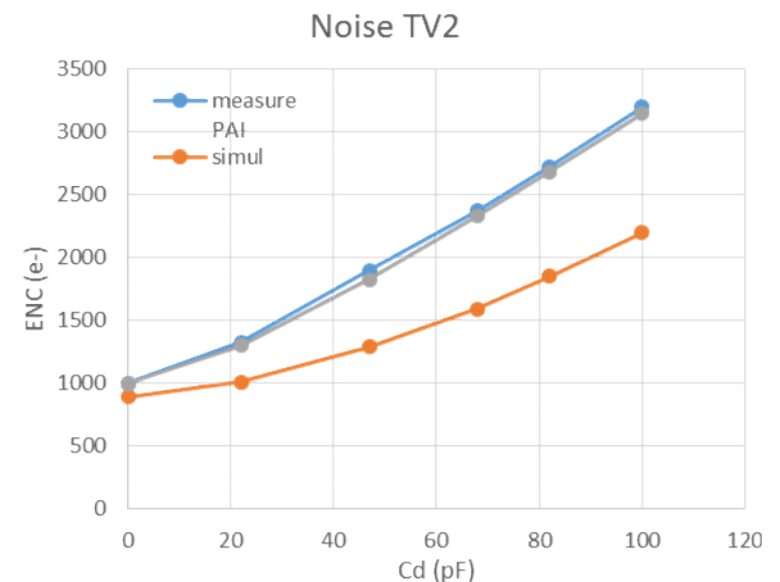



ENC vs Capacitance (other preamp)

Trigger efficiency

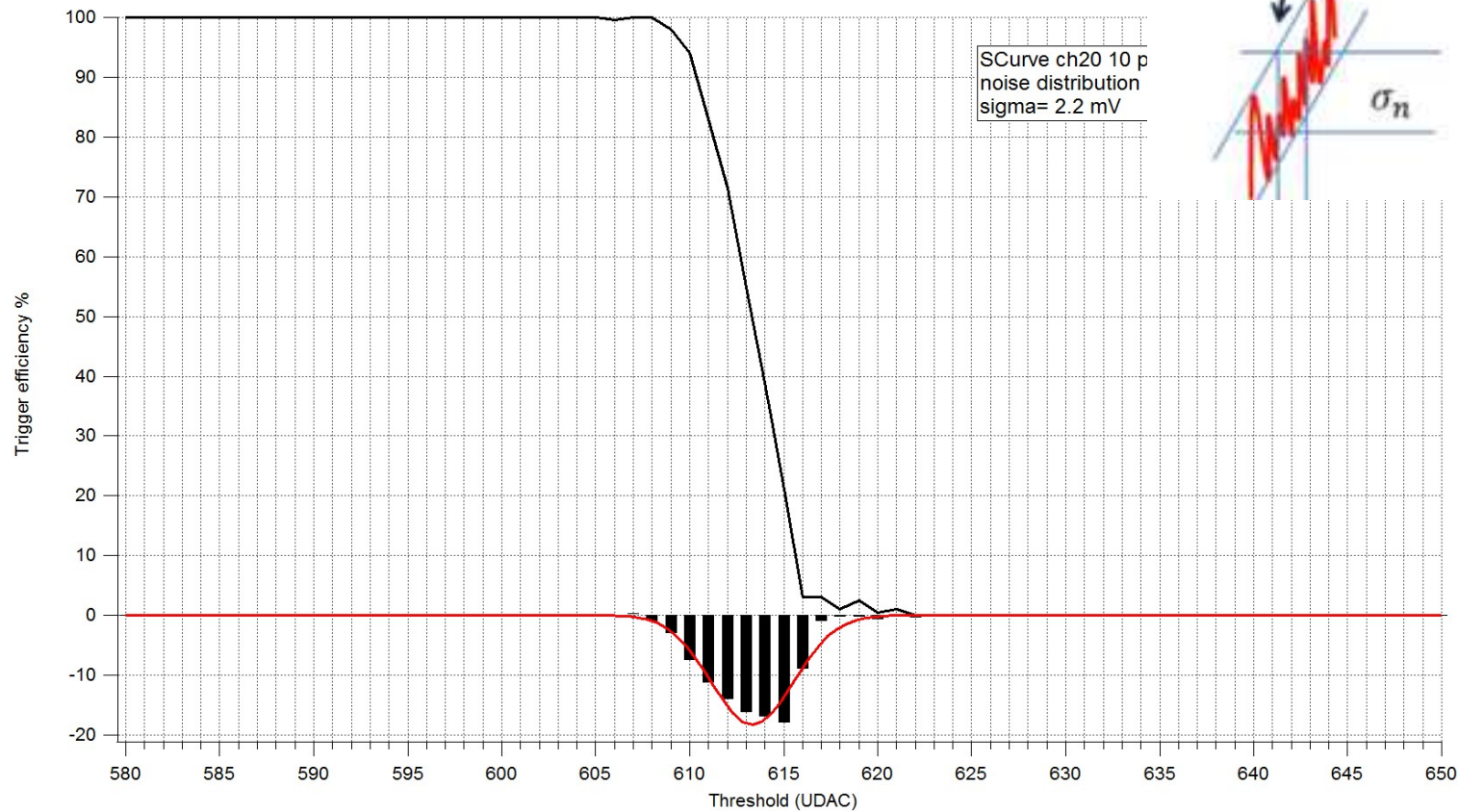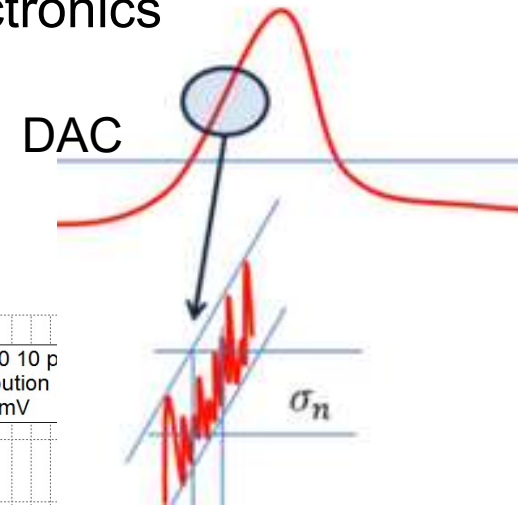- Preamp + discriminator front-end = tracker electronics
- scanning the DAC produces « s-curves »
- Derivative gives the noise




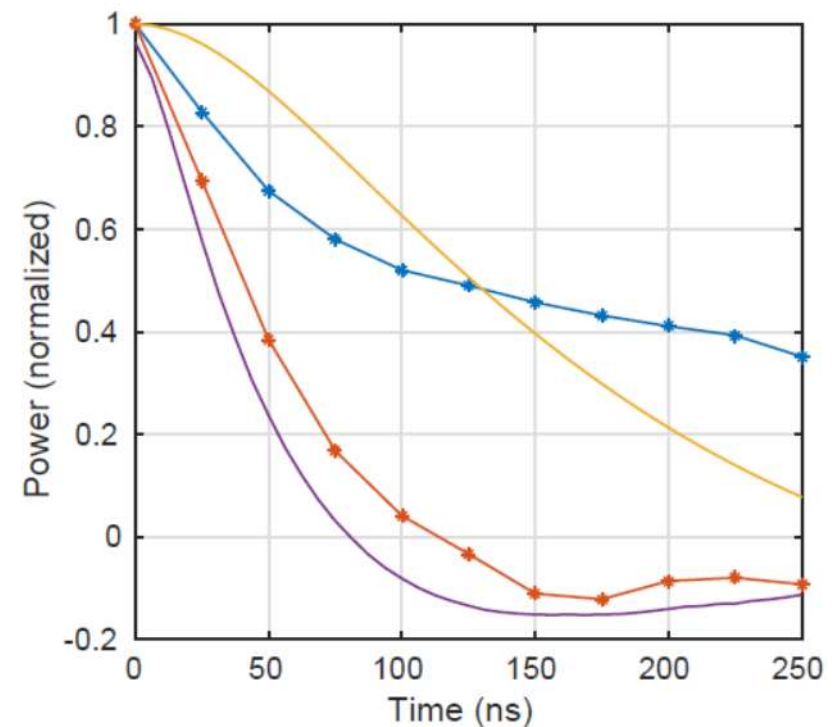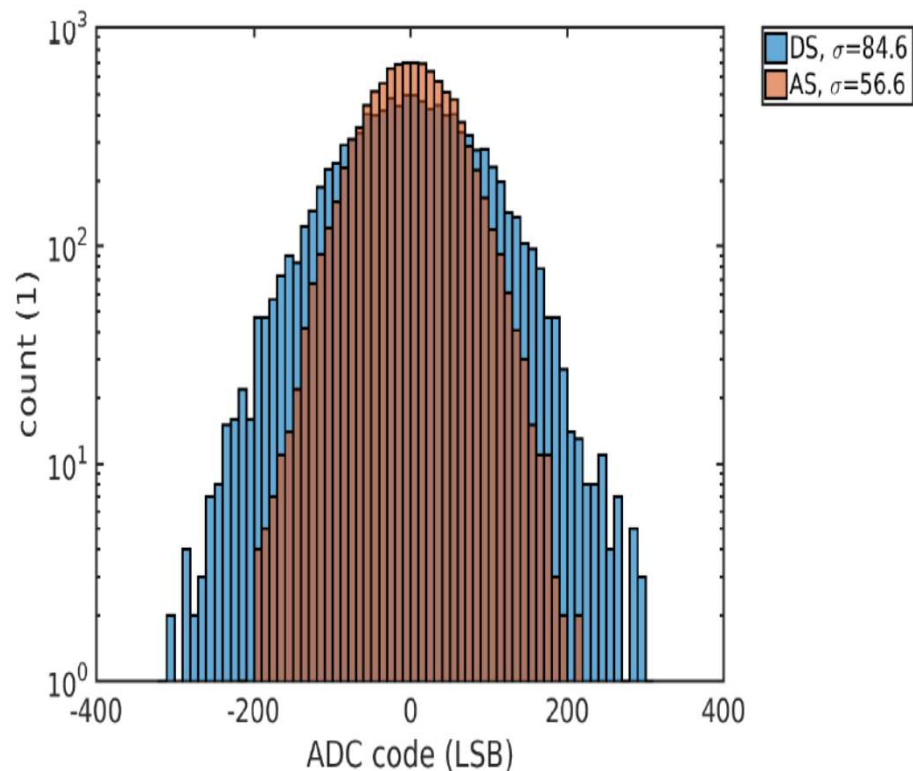- A constant concern in calorimetry
 - Coherent noise extracted by comparing direct and alternate sums on n channels (n=64) : $DS = \sum ped[i]$; $AS = \sum (-1)^i ped[i]$
 - Incoherent noise $IN = rms(AS) / \sqrt{n}$
 - Coherent noise : $CN = \sqrt{var(DS) - var(AS)} / n$
- Need to show that $CN / IN \sim 10\%$ can be obtained at system level




Summary of lecture 1

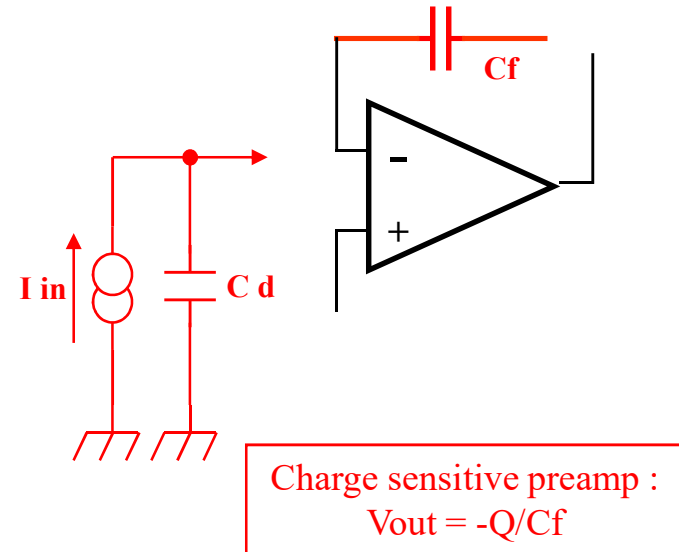- Importance of front-end on electronics on physics performance
- Benefits of charge preamplifiers :
low noise, low crosstalk
 - The front-end of 90% of particle physics detectors...
 - But always built with custom circuits...




Summary of transistor level design

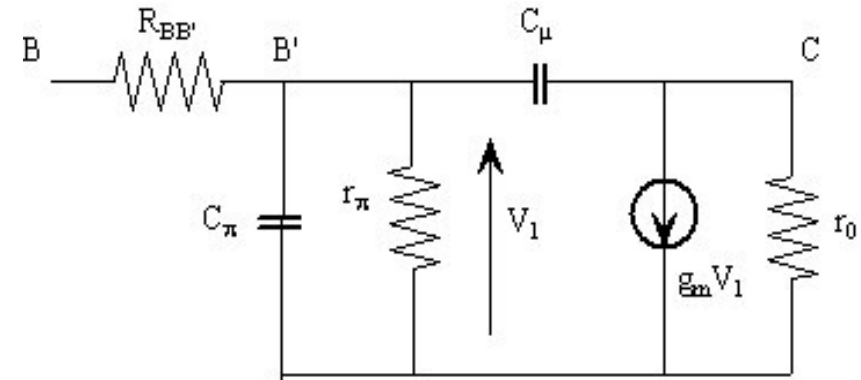- Performant design is at transistor level
- Simple models
 - hybrid π model
 - Similar for bipolar and MOS
 - Essential for design



High frequency hybrid model of bipolar

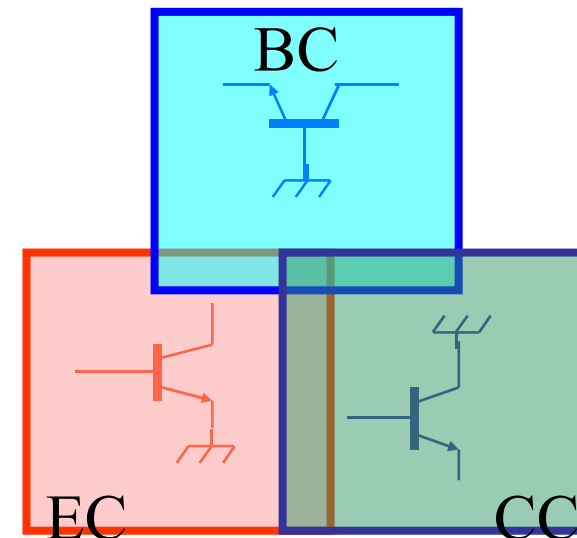- **Three basic configurations**
 - **Common emitter (CE) = V to I** (transconductance)
 - **Common collector (CC) = V to V** (voltage buffer)
 - **Common base (BC) = I to I** (current conveyor)
- **See backup slides**




The *Art* of electronics design


- Numerous « composites »
 - Darlington, Paraphase, Cascode, Mirrors...

Designing a charge preamp...

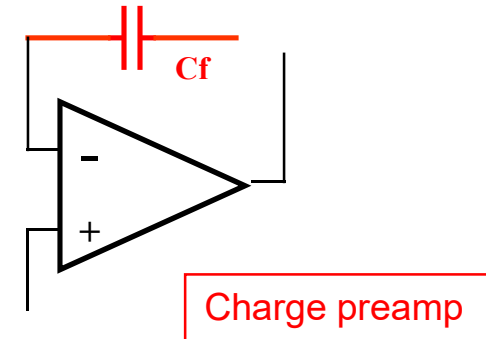
- From the schematic of principle
 - Using of a fast opamp (OP620)
 - Removing unnecessary components...
 - Similar to the traditionnal schematic «Radeka 68 »
 - Optimising transistors and currents



Charge preamp

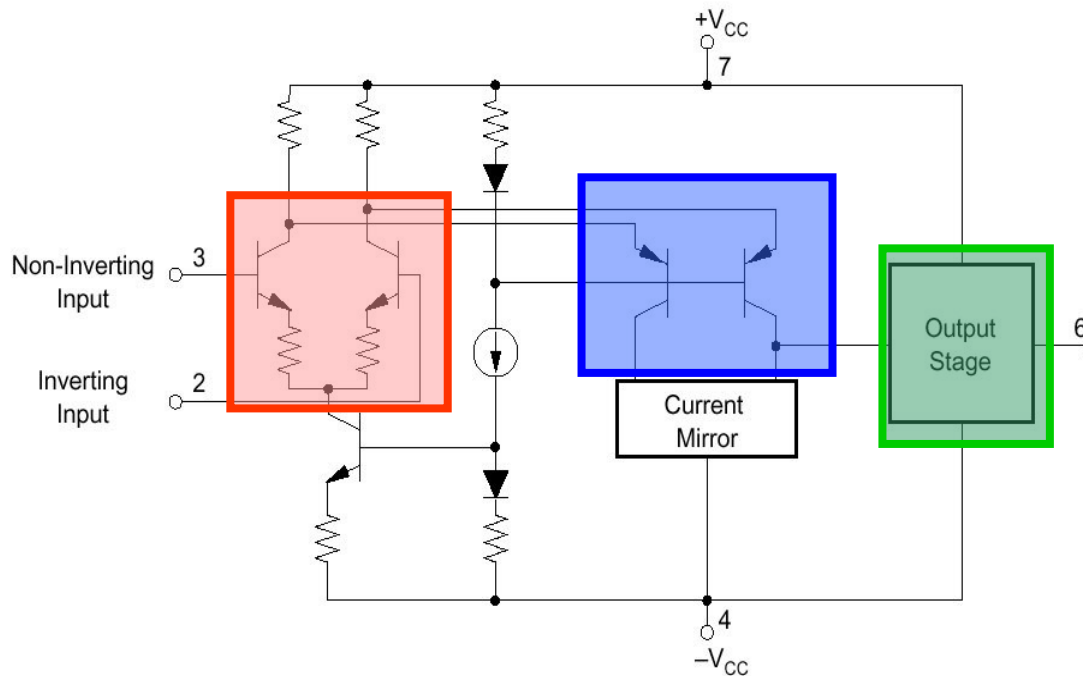


Schematic of a OP620 opamp ©BurrBrown

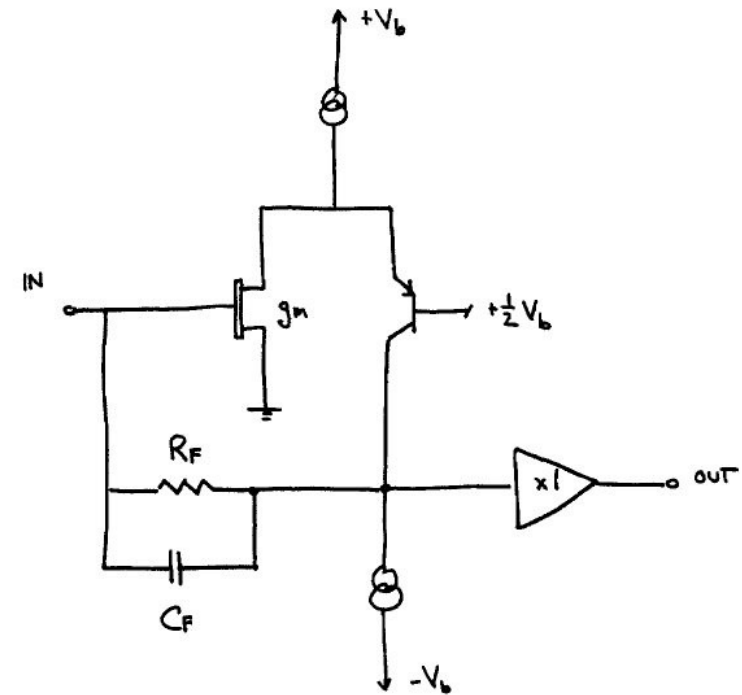

Charge preamp ©Radeka 68

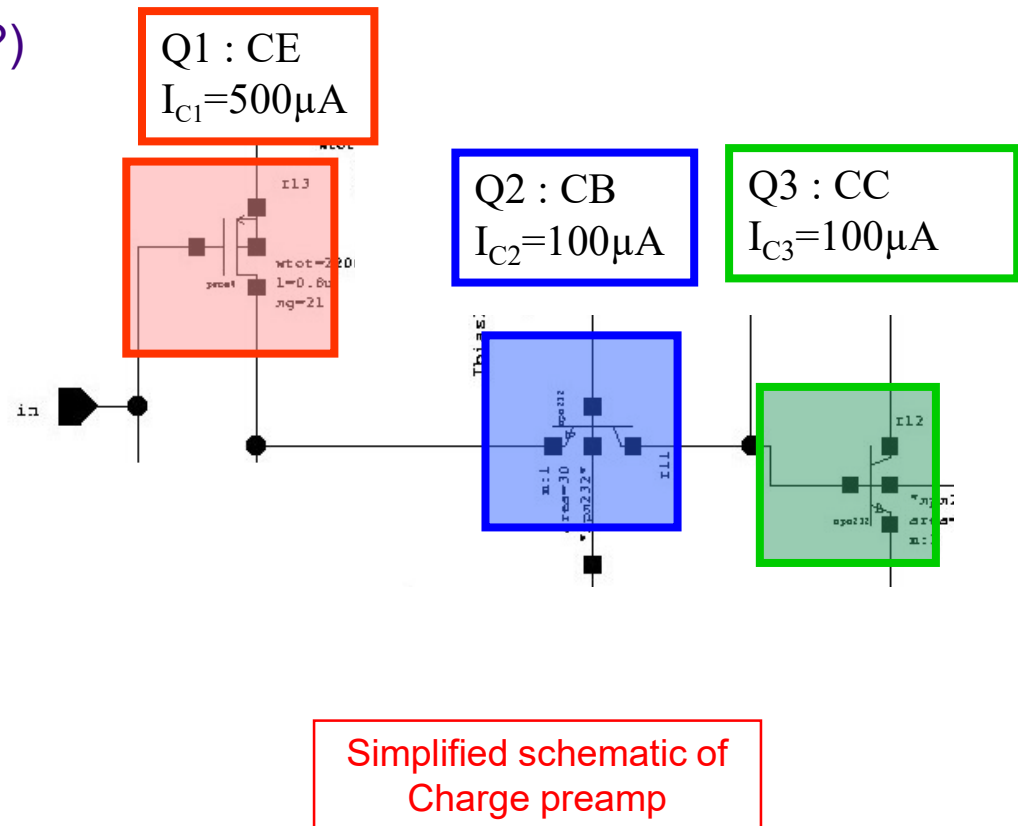Example : designing a charge preamp (2)


- Simplified schematic
- Optimising components
 - What transistors (PMOS, NPN ?)
 - What bias current ?
 - What transistor size ?
 - What is the noise contribution of each component ?
 - how to minimize it ?
 - What parameters determine the stability ?
 - What is the saturation behaviour
 - How vary signal and noise with input capacitance ?
 - How to maximise the output voltage swing ?
 - What is the sensitivity to power supplies, temperature...



MOS input transistor sizing




- Capacitive matching : strong inversion
 - g_m proportionnal to $W/L \sqrt{I_D}$
 - C_{GS} proportionnal to $W \cdot L$
 - ENC propotionnal to $(C_{det} + C_{GS}) / \sqrt{g_m}$
 - Optimum W/L : $C_{GS} = 1/3 C_{det}$
 - Large transistors are easily in moderate or weak inversion at small current

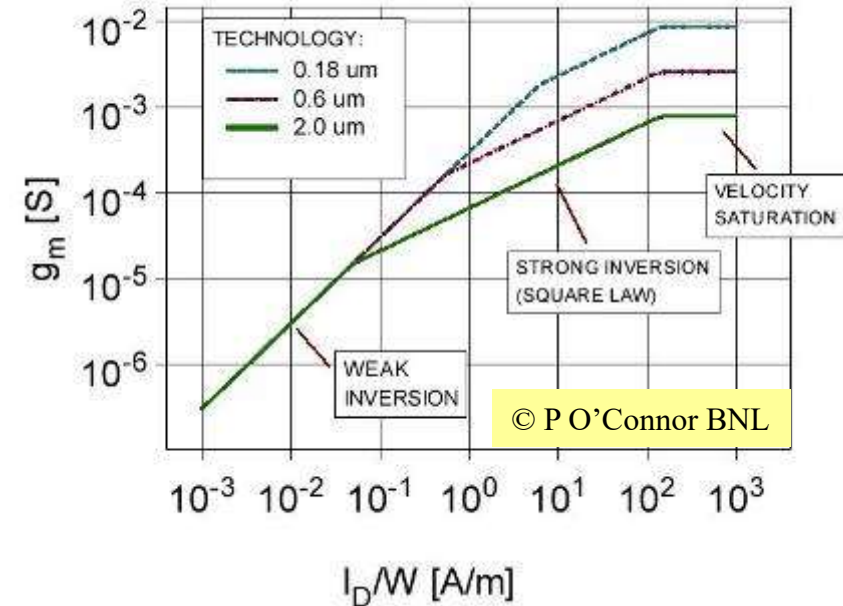- Optimum size in weak inversion
 - g_m proportionnal to I_D (indep of W, L)
 - ENC minimal for C_{GS} minimal, provided the transistor remains in weak inversion




PMOS vs NMOS [Paul O'Connor BNL]

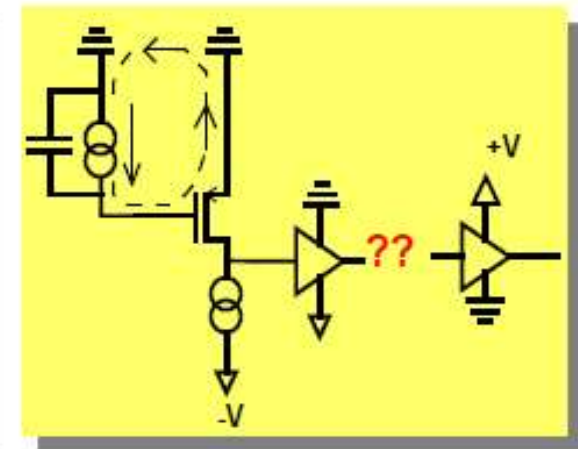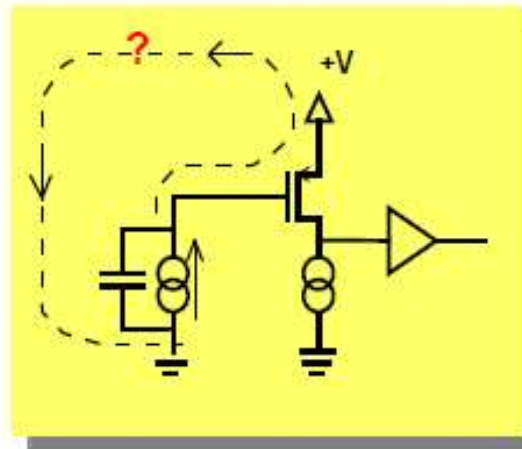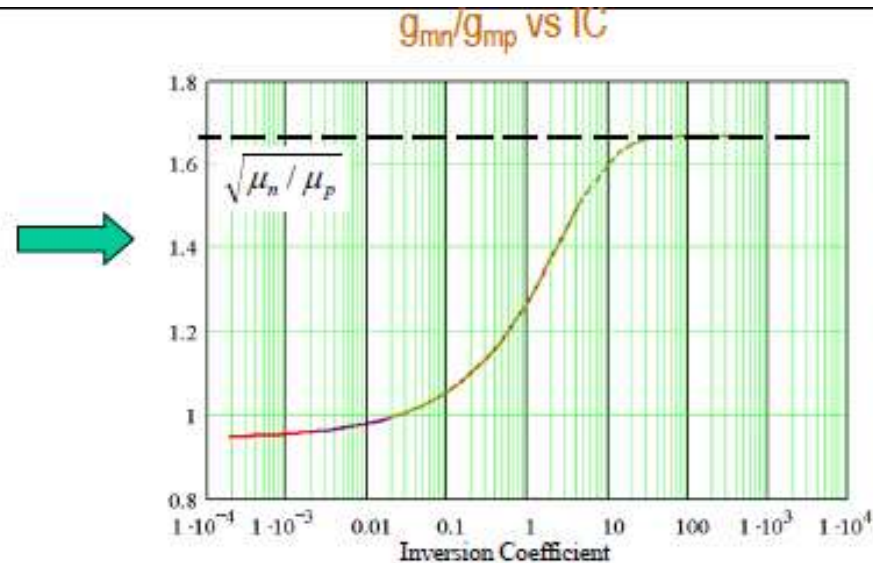- PMOS lower 1/f noise
- NMOS white series noise advantage over PMOS diminishes each generation
- PMOS can be operated at reverse V_{BS} to reduce bulk resistance noise
- PMOS lower tunneling current at ultra-thin t_{ox}
- Single-supply operation of PMOS-input preamp awkward:



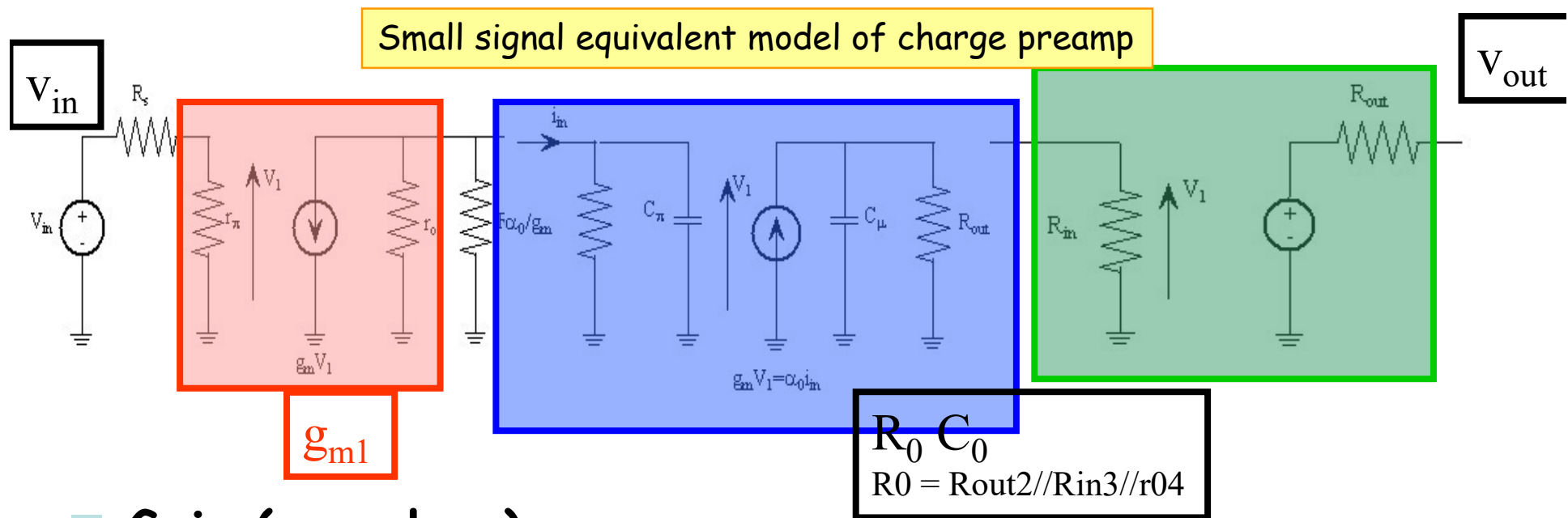Example : designing a charge preamp (3)

- Small signal equivalent model
 - Transistors are replaced by hybrid π model
 - Allows to calculate open loop gain




■ Gain (open loop) :

$$v_{out}/v_{in} = -g_{m1} R_0 / (1 + j\omega R_0 C_0)$$

- Ex : $g_{m1}=20\text{mA/V}$, $R_0=500\text{k}\Omega$, $C_0=1\text{pF} \Rightarrow G_0=10^4$ $\omega_0=210^6$ $G_0\omega_0=2 \cdot 10^{10} = 3 \text{ GHz}!$

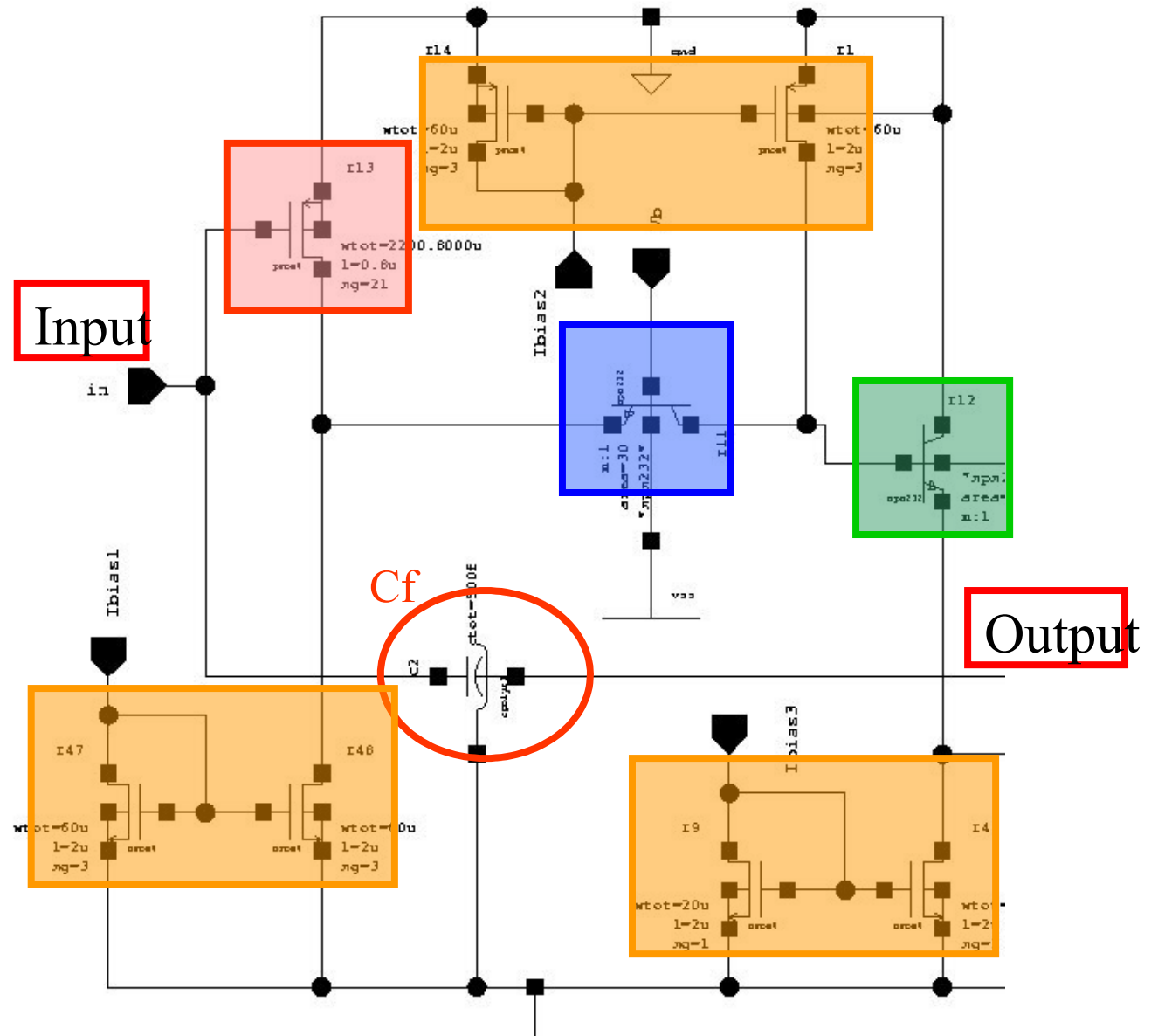
Example : designing a charge preamp (4)

- Complete schematic
 - Adding bias elements




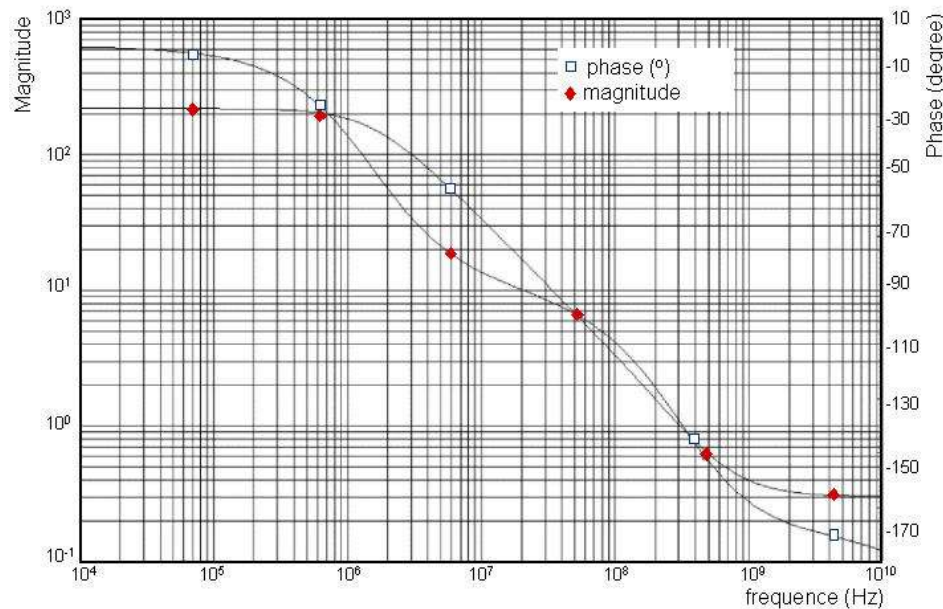Example : designing a charge preamp (5)

- Complete simulation
 - Checking hand calculations against 2nd order effects
 - Testing extreme process parameters (« corner simulations »)
 - Testing robustness (to power supplies, temperature...)




Simulated open loop gain

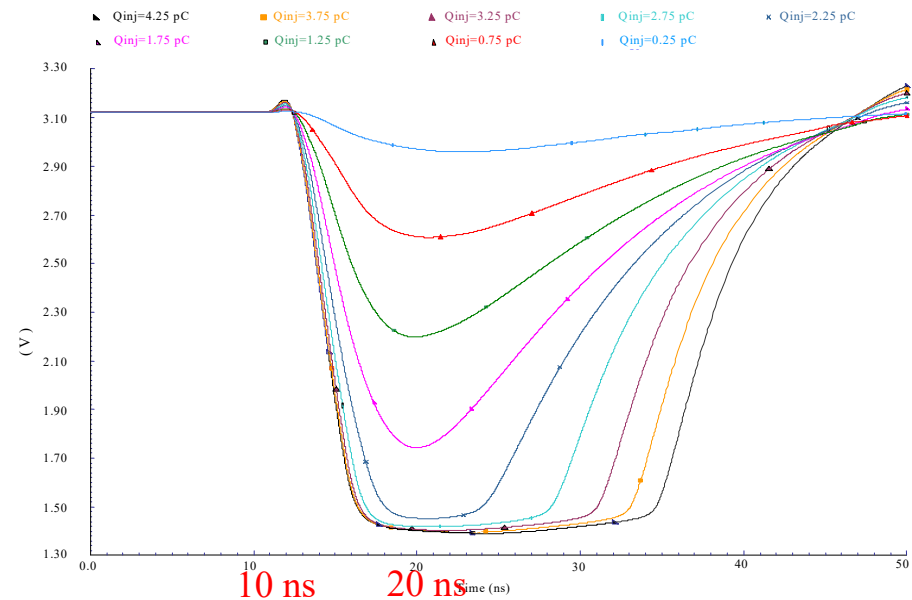


Saturation behaviour

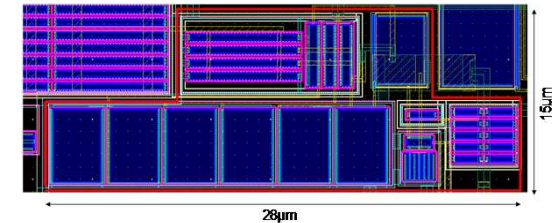Example : designing a charge preamp (6)


- Layout
 - Each component is drawn
 - They are interconnected by metal layers
- Checks
 - DRC : checking drawing rules (isolation, minimal dimensions...)
 - ERC : extracting the corresponding electrical schematic
 - LVS (layout vs schematic) : comparing extracted schematic and original design
 - Simulating extracted schematic with parasitic elements
- Generating GDS2 file
 - Fabrication masks : « reticule »



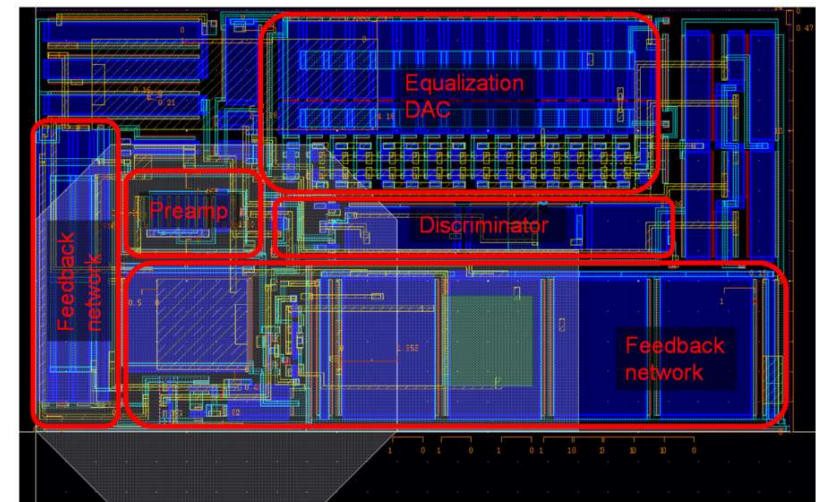Charge preamp in 65nm
Clicpix P. Valerio (CERN 2013)






From preamp to chip : Timepix 3...

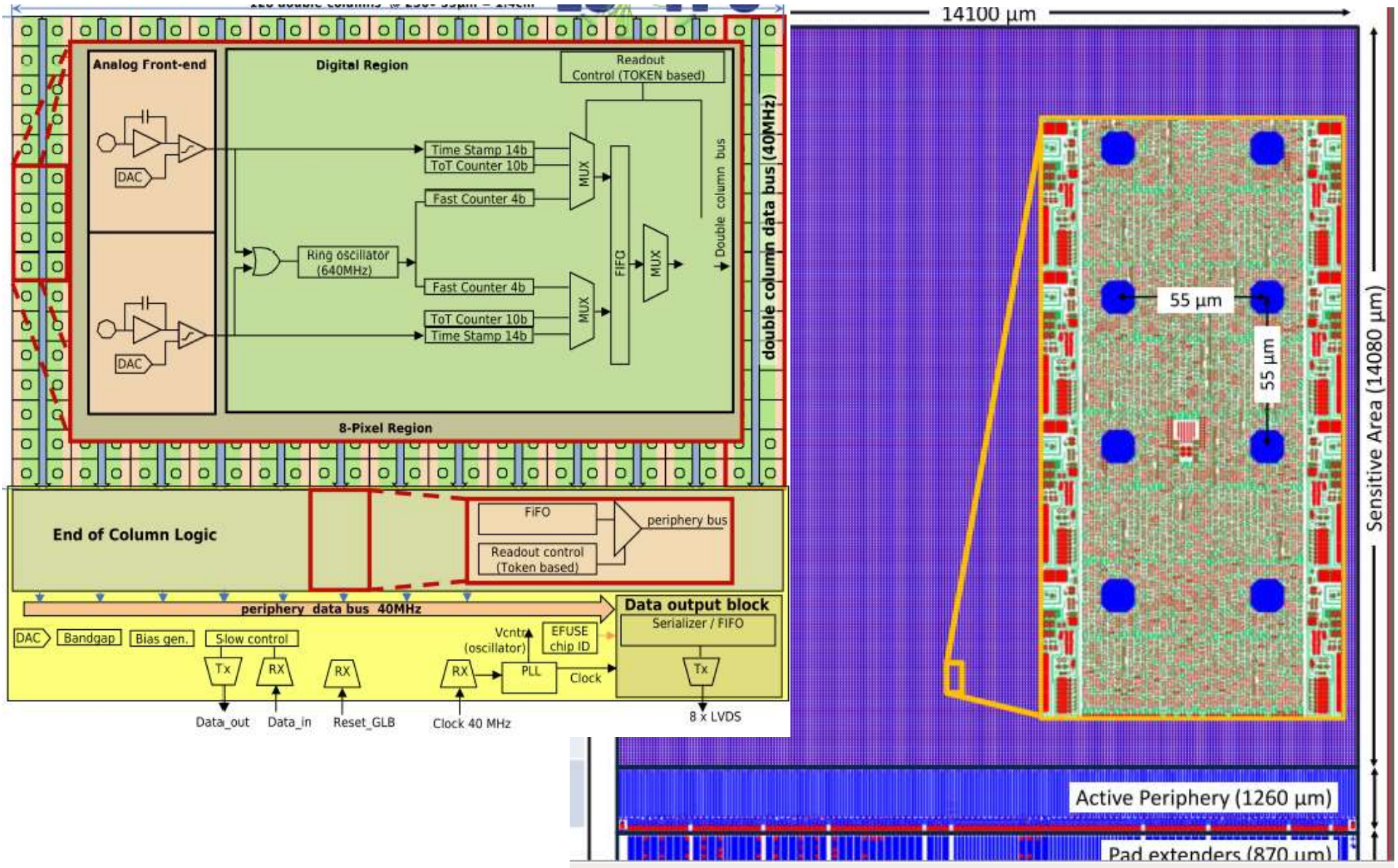


Digital implementation global Flow
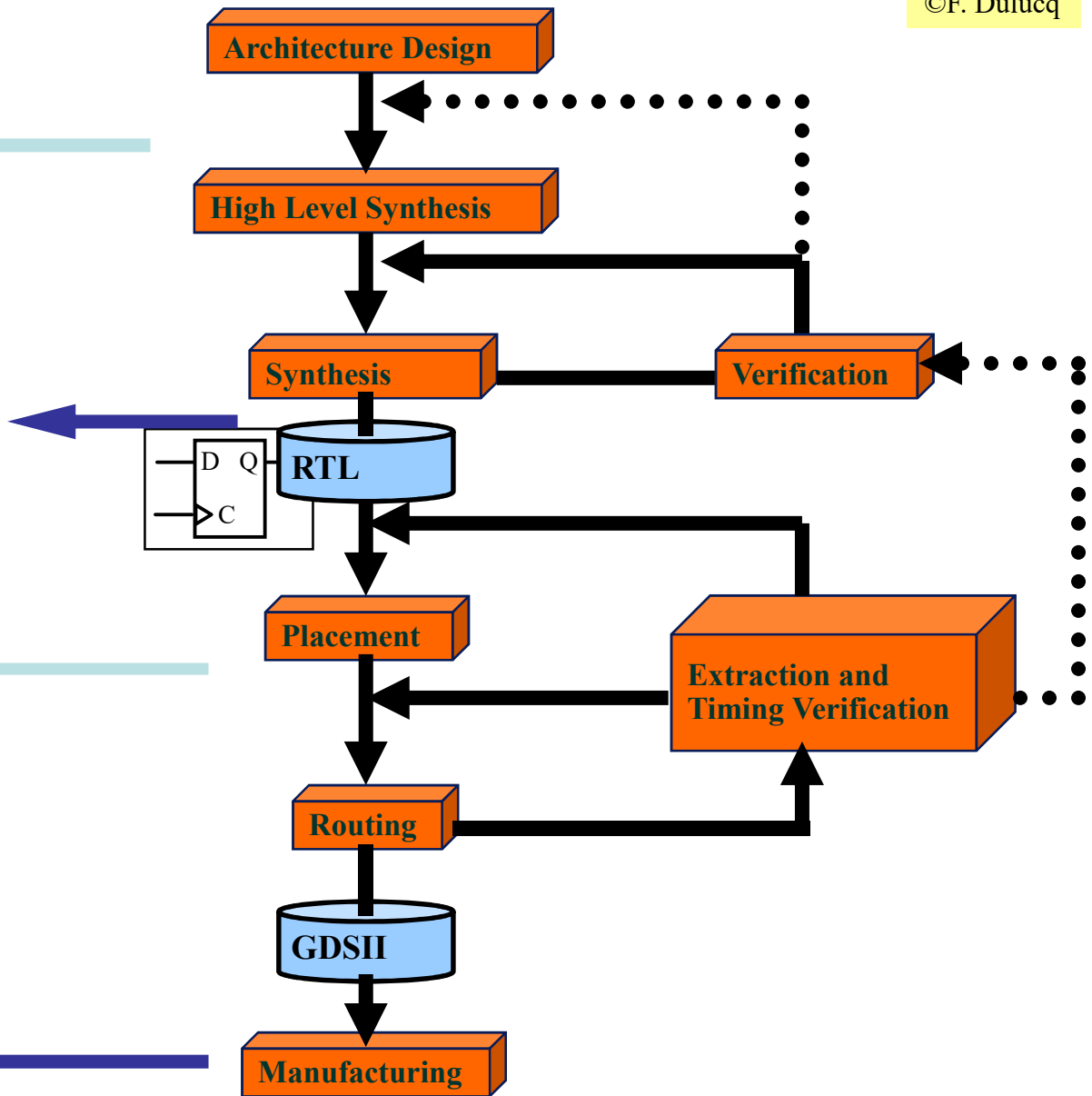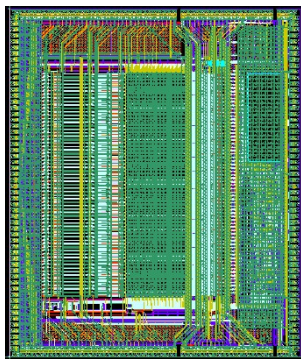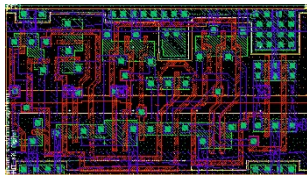
```
process(Rstb, Clk)
begin
  if Rstb = '0' then
    Q <= '0';
  elsif rising_edge Clk then
    Q <= D;
  end if;
end process;
```




ASIC specific flow for digital routing

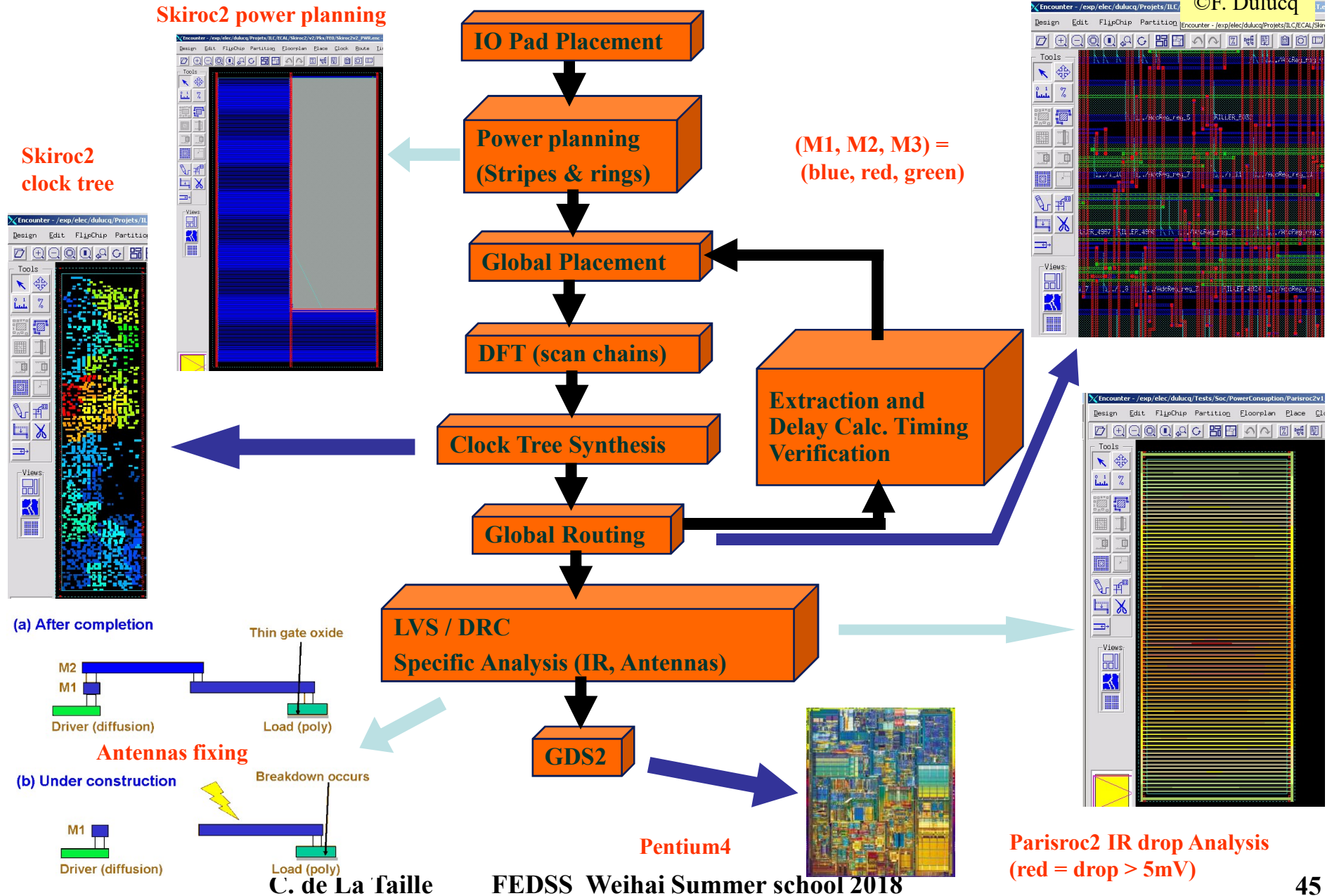

Post layout simulation (extracted RC)

MIN PVT (1.6 ; 3.6V ; -50°C)

MAX PVT (1.4 ; 3V ; 125°C)

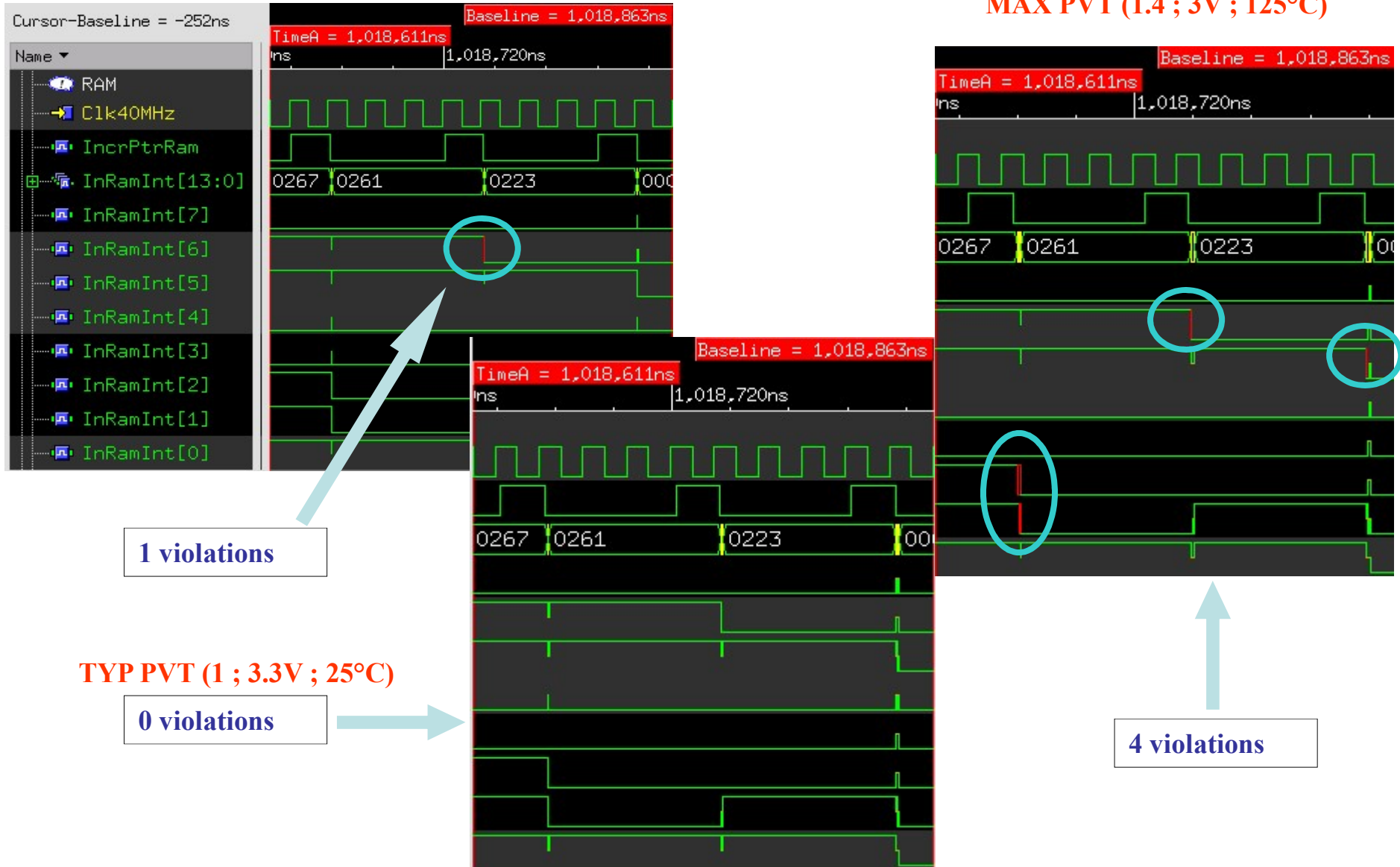

1 violations

TYP PVT (1 ; 3.3V ; 25°C)

0 violations

4 violations


- Coexistence analog-digital
 - Capacitive, inductive and common-impedance couplings
 - A full lecture !
 - A good summary : there is no such thing as « ground », pay attention to current return



C. de La Taille FEDSS Weihai Summer school 2018




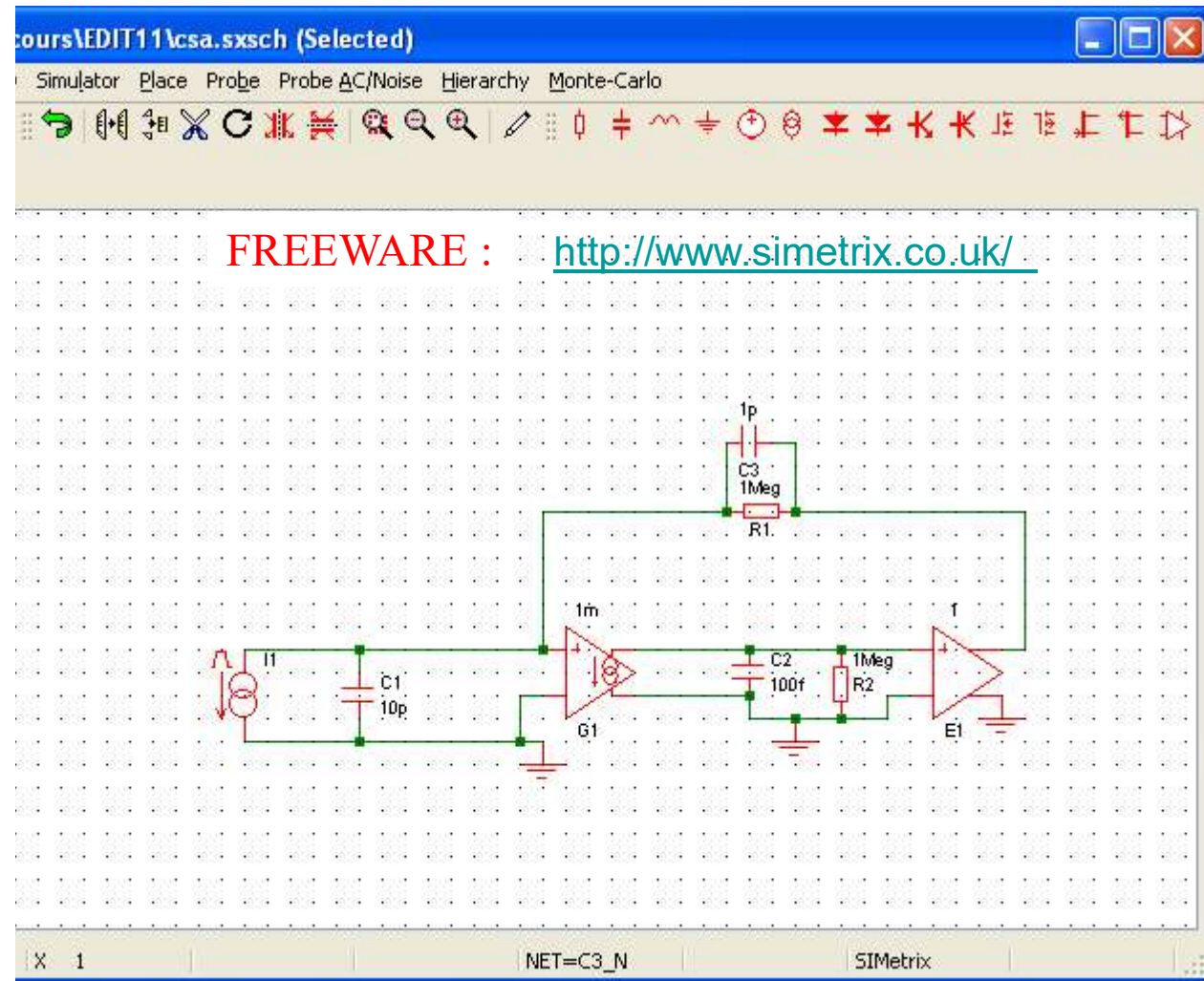
Example : bandwidth and EMC of simple charge preamp

- Simulate impulse response
- Frequency response
- Input impedance
- Ballistic deficit
- Effect of amplifier gain
- Effect of resistive feedback
- Test pulse injection
- Effect of input capacitance
- **Parasitic inductance**
- Capacitive crosstalk
- Resistive/Inductive ground return




Evolution of calorimetry



- 3D calorimetry : eta, phi, Energy
- 4D calorimetry : x,y,z,E
- 5D calorimetry : x,y,z,E,t
 - High granularity=> Millions of channels => **Low power !**
 - Power pulsing ~1% for ILC
 - Low power + CO2 cooling for HL-LHC
 - Energy measurement : Large dynamic range
 - MIP sensitivity => low noise (~0.1 fC)
 - Up to thousands of MIPs (~10 pC)
 - Timing information
 - Nice addition for ILC for PID : few ns is enough
 - Crucial for HL-LHC : pileup mitigation, need **few tens of ps**
 - Embedded electronics vs data out
 - Daisy chain and low power busses for ILC
 - High speed e/optical links for HL-LHC
 - Radiation levels
 - Negligible at an ILC
 - Daunting at HL-LHC : >100 Mrad 1^{E16}N

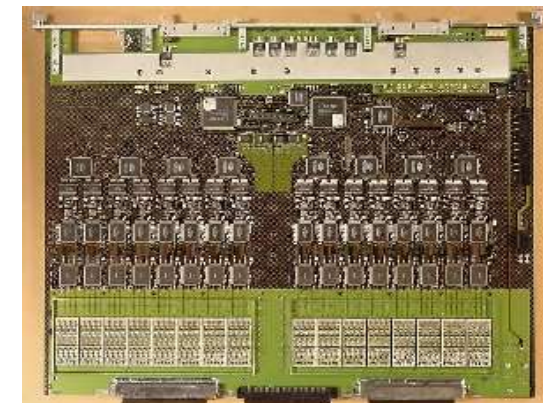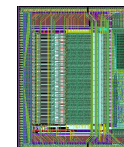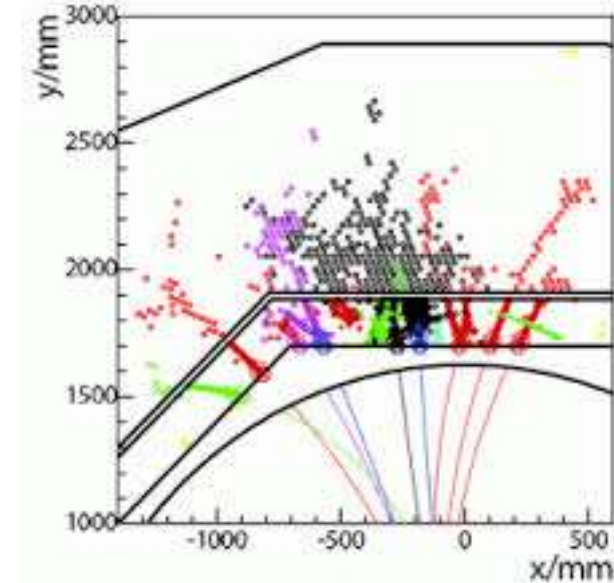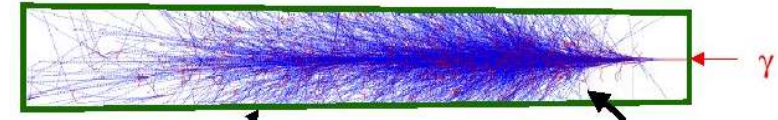



- R&D on imaging calorimetry
 - Particle Flow Algorithms [
 - Electronics crucial (low noise, low power, fully integrated)
 - Several innovative features (power pulsing, SiPM...)
 - Validation of technological prototypes
 - **Common R/O features**
 - Worldwide collaboration

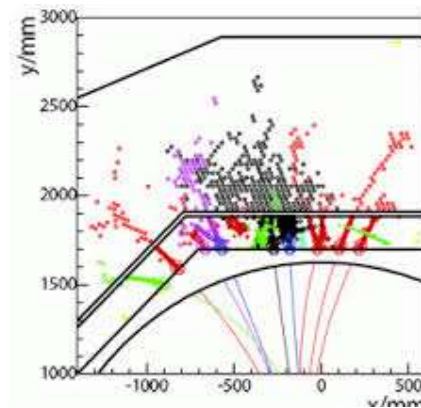


SKIROC2

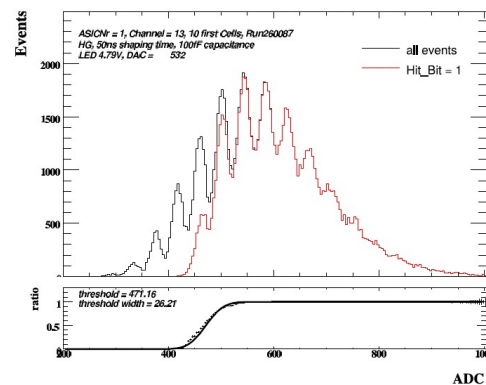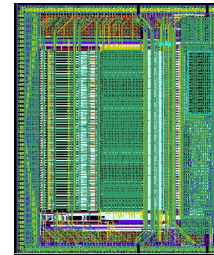


SPIROC2

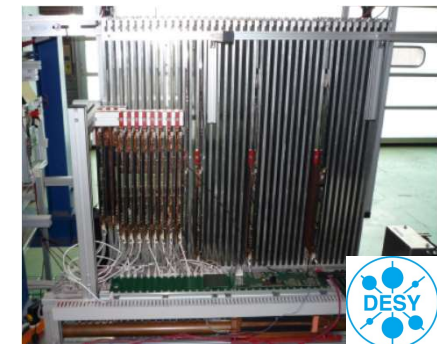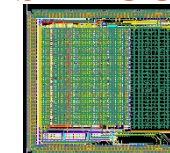


AIDA

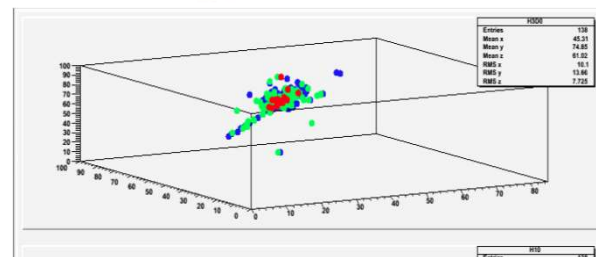


HARDROC2


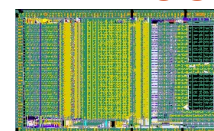


MICROROC

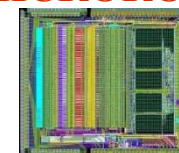

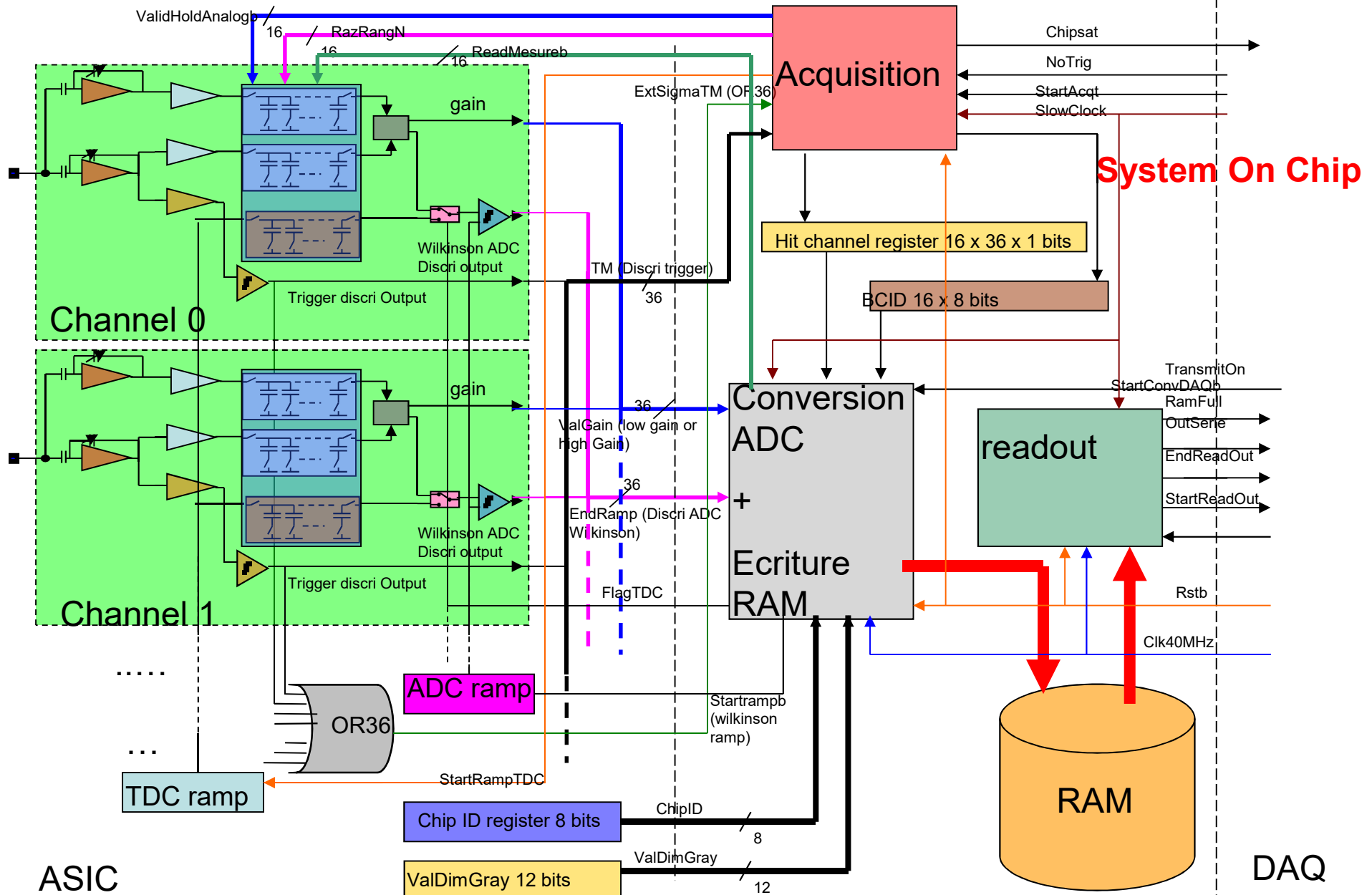

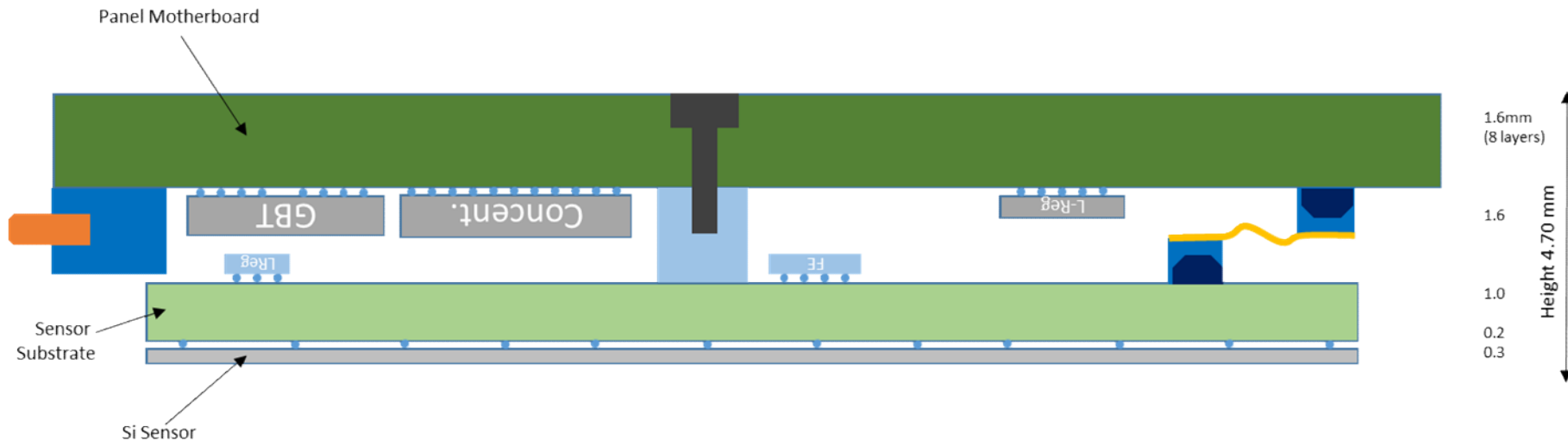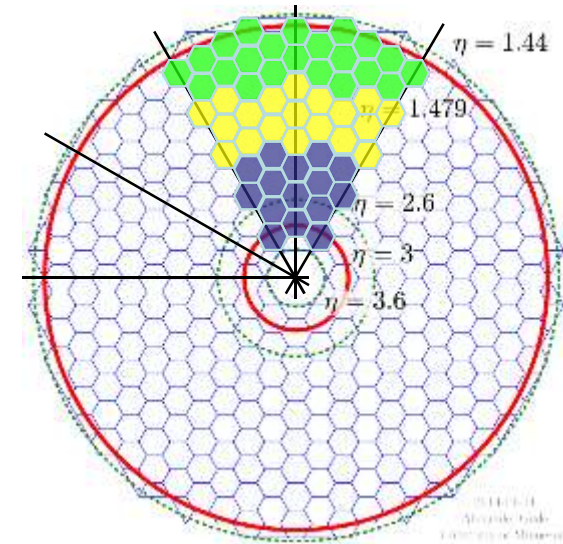- Stringent requirements for Front-End Electronics
 - Low power (< 10 mW),
 - low noise (< 2000 e⁻) MIP ~ 1 -4 fC
 - High radiation (200 Mrad, 10^{16} N)
 - System on chip (digitization, processing...)
 - High speed readout (5-10 Gb/s)
 - ~ 10 million channels







HGCAL readout ASIC : HGCROC




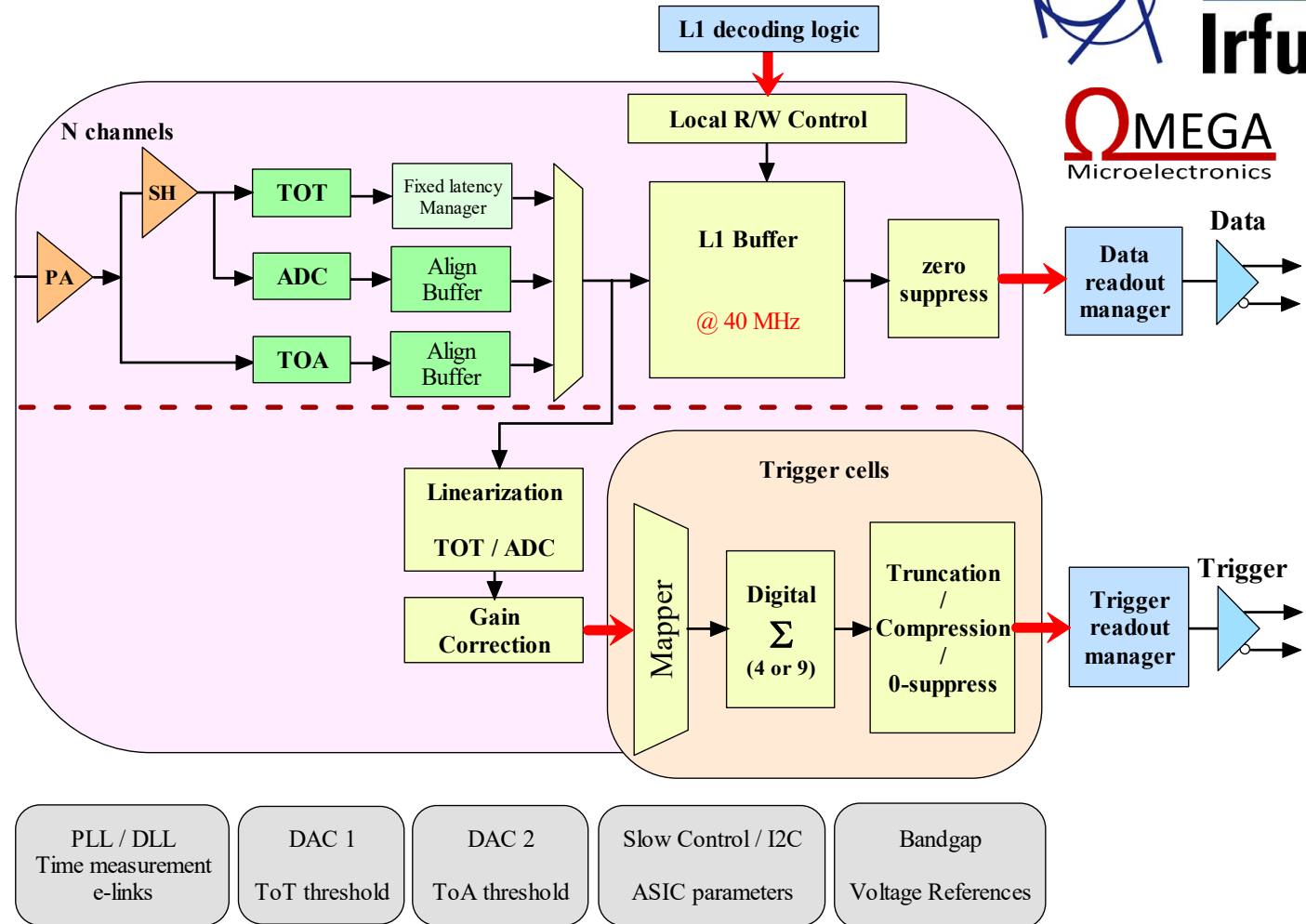
- 72 channels dual polarity
- 10bit 40 MHz ADC 0-100 MIPs
- TOT above with 60 ps TDC
- Timing down to 25 ps
- Trigger sums at 40 MHz
- 1.28 Gb/s elink outputs



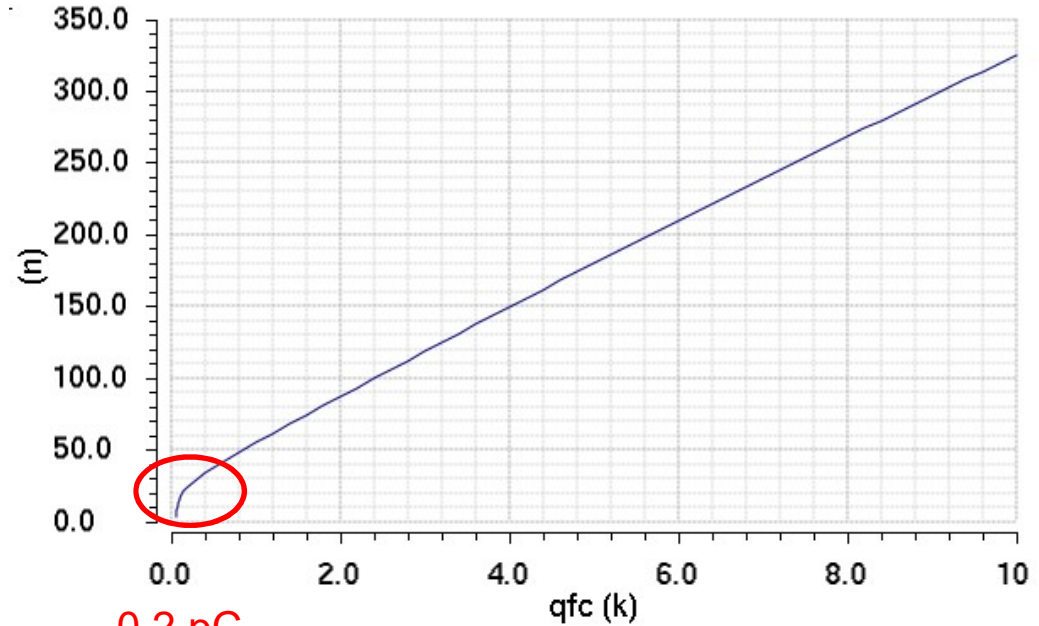
- key issues to be studied :
 - Noise
 - Resolution
 - Stability
 - Linearity
 - Accuracy
 - Calibration
 - crosstalk
 - Radiation
 - Timing
 - Systematic effects




0.2 pC
~100 MIPS

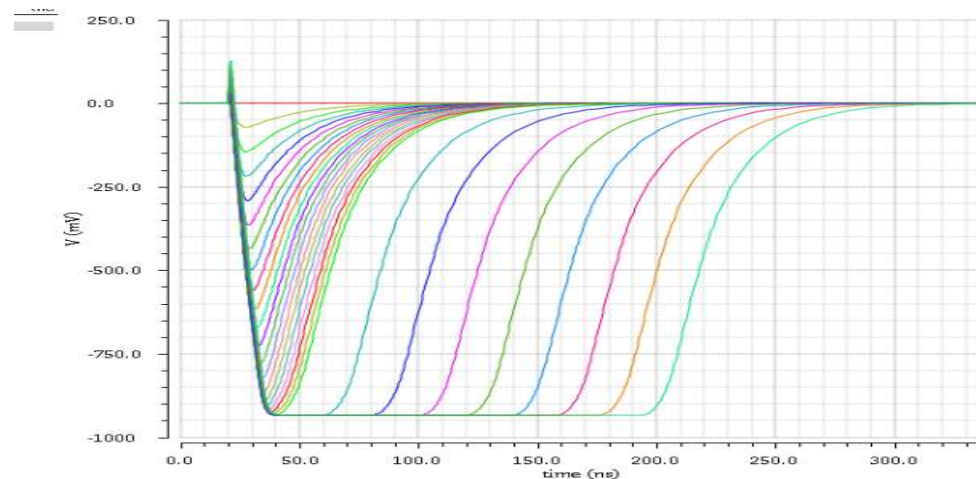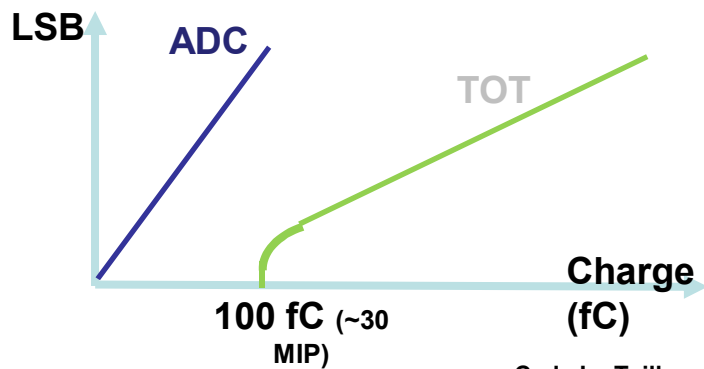


Test Vehicles 1 & 2 (2016)

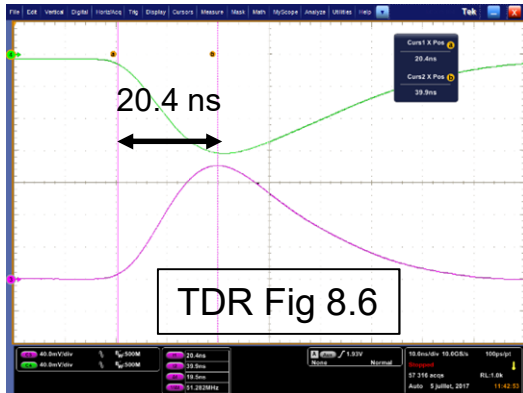

✓ Peaking time 20 ns

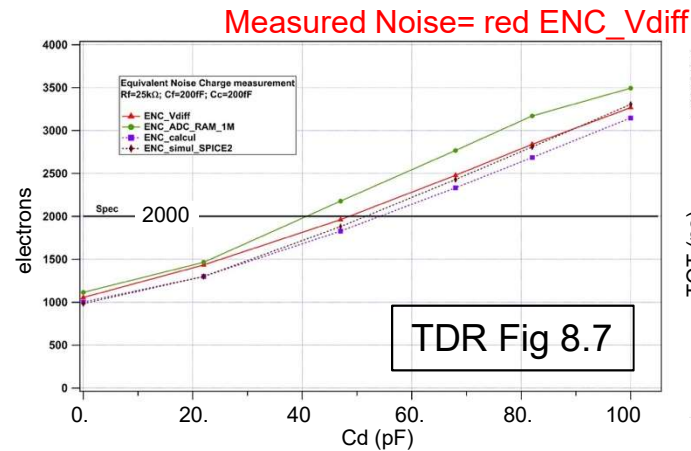


✓ Noise in agreement with simulation

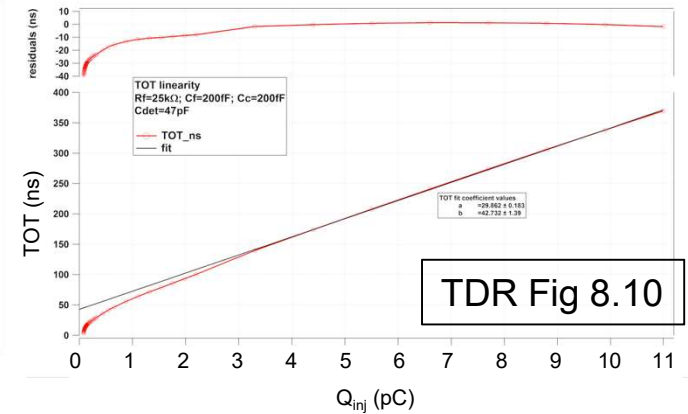

✓ ToT linearity

HGCROC1 (submitted July 2017)

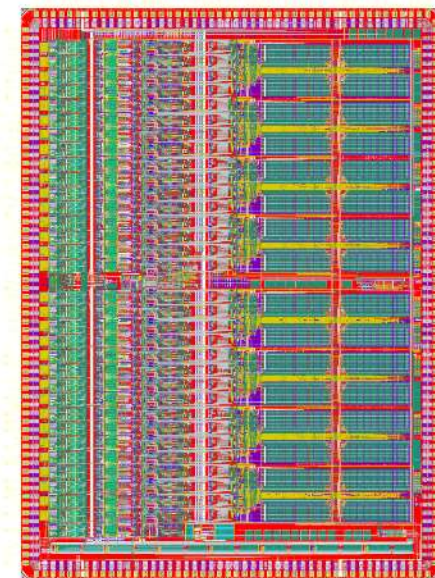- Missing some digital functionalities
- 32 channels instead of 78
- 2 variants for ToT TDCs
- SAR Omega ADC
- 1.28 Gb/s E-links
- L1 Buffer: provisional SRAM (too high power, new one being designed)
- Now under test



OMEGA
Microelectronics



Irfu



Imperial College
London




Need for timing

- Time resolution $< 50\text{ps}$ required by many experiments/applications keeping low power, large dynamic range


- **PET/ Time of Flight measurements (SiPM)**

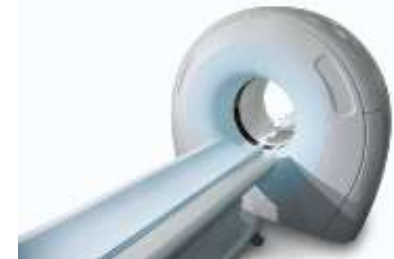- Dynamic range : 1 pe (100fC) up to 3000 pe (300 pC)
- Time resolution $< 100\text{ps}$



- **CMS High Granularity CALorimeter: (Si pin diodes)**

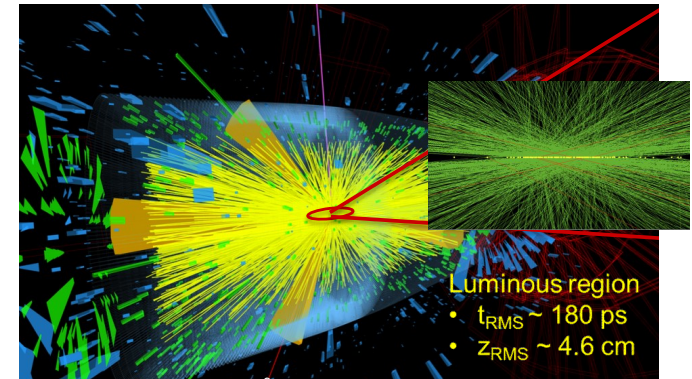- Large dynamic range : few fC up to $\sim 10\text{ pC}$
- Calorimetry => Precision /linearity $< 1\%$
- Fast timing ability $\sim 50\text{ps}$ (for $> 10\text{ mips}$ desirable)
- Peaking time 15-20 ns (minimize noise, minimise Out of Time pileup)
- Power on detector $< \sim 10\text{ mW/channel}$ all included



- **ATLAS High Granularity Timing Detector (LGAD)**



- Time performance $\sim 30\text{ ps}$: To reject Time Pile up events => better particle identification



Time walk and time jitter (see talk by A. Rivetti)

Time walk: the voltage value V_0 is reached at different time for signal of different

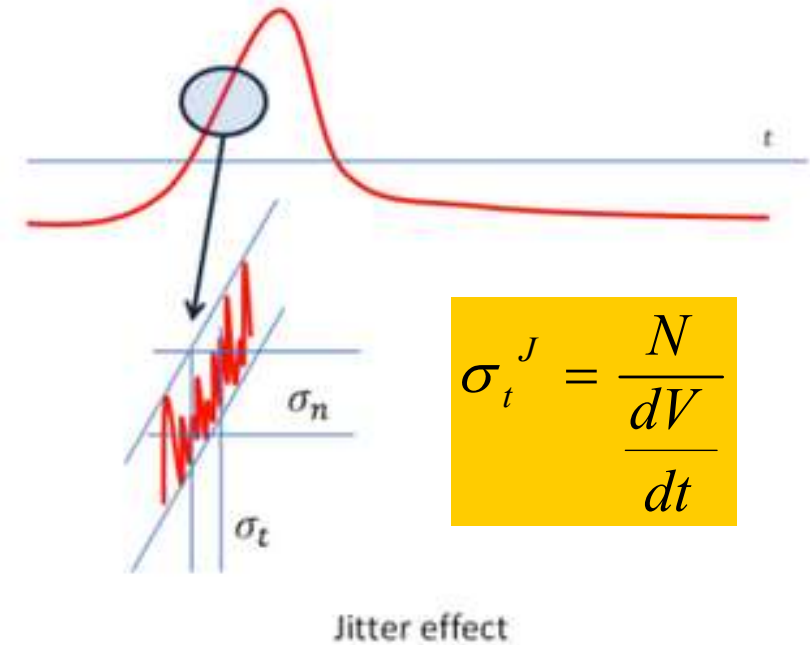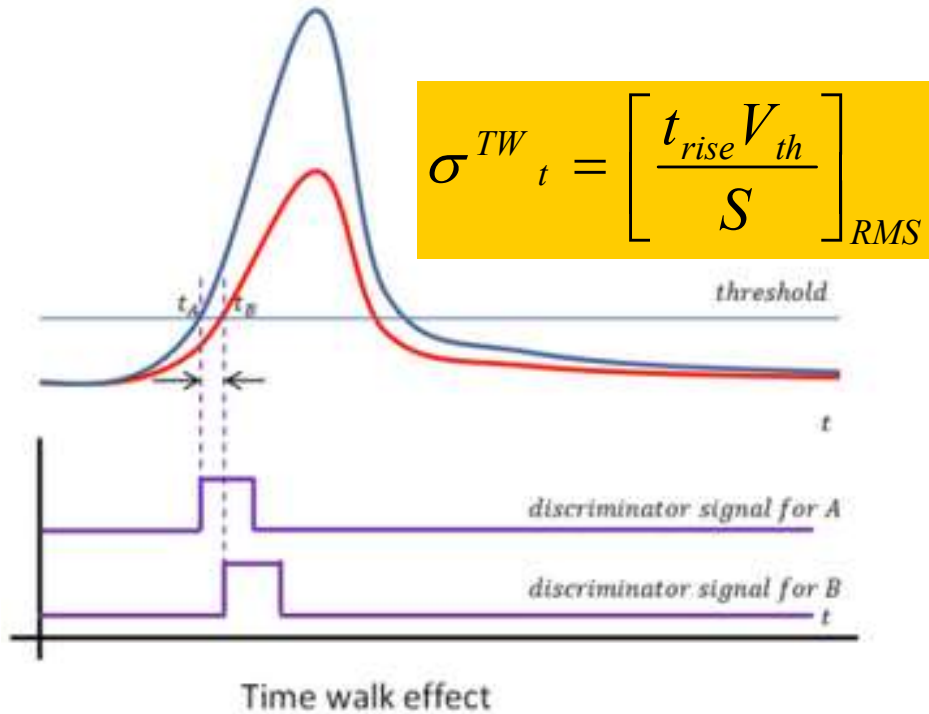Jitter: the noise is summed to the signal, causing amplitude variations



Due to the physics of signal formation

Mostly due to electronic noise




$$\sigma_t^2 = \left(\frac{t_{rise}}{S/N} \right)^2 + \left(\left[\frac{t_{rise} V_{th}}{S} \right]_{RMS} \right)^2 + \left(\frac{TDC_{bin}}{\sqrt{12}} \right)^2$$

Jitter

Time Walk

TDC

High speed preamps...

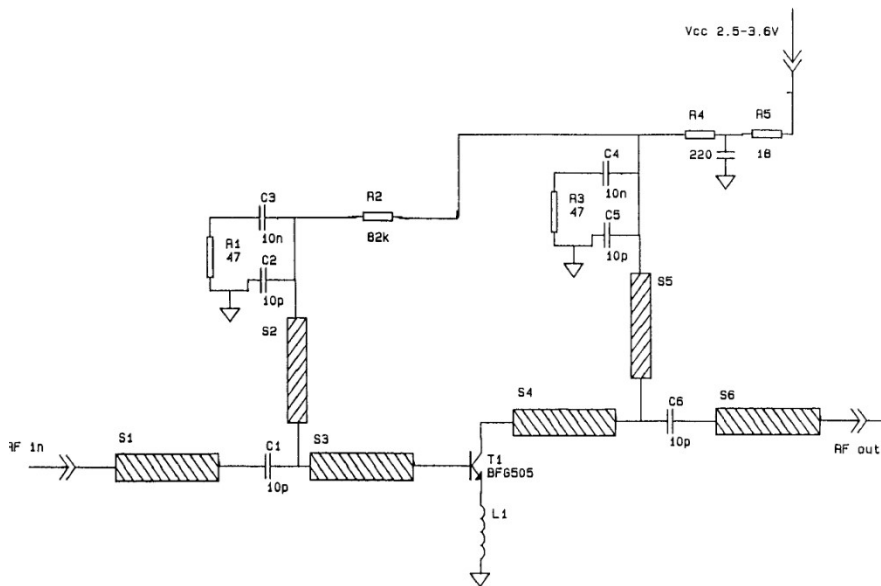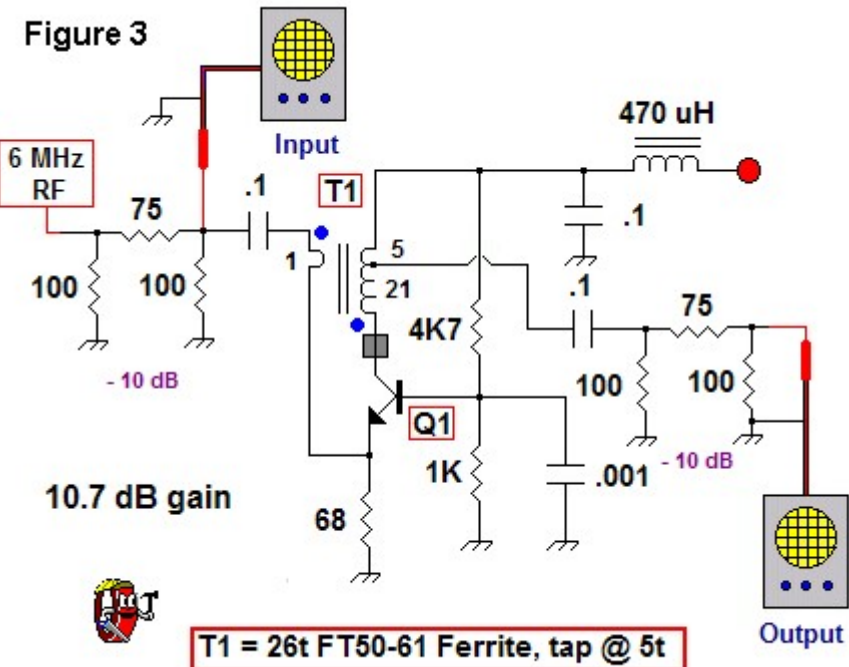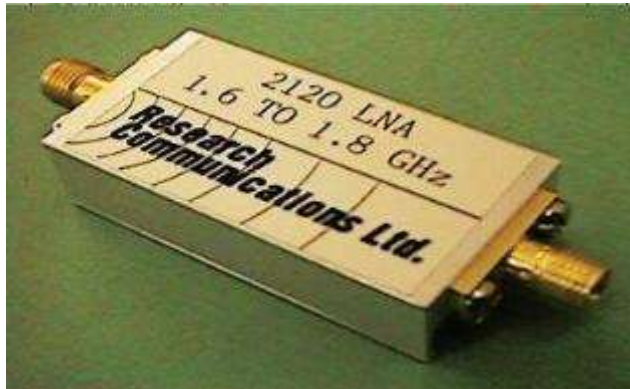

Timing optimization : common view

- Jitter due to electronics noise:


$$\sigma_t^J = \frac{N}{\frac{dV}{dt}}$$

- also presented as $j = tr / (S/N)$
- dV/dt prop to BW, N prop to \sqrt{BW} => jitter prop to $1/\sqrt{BW}$




⇒ « the faster the amplifier the better the jitter ? »

⇒ « High speed preamps need to be low impedance (50 Ω or less) »

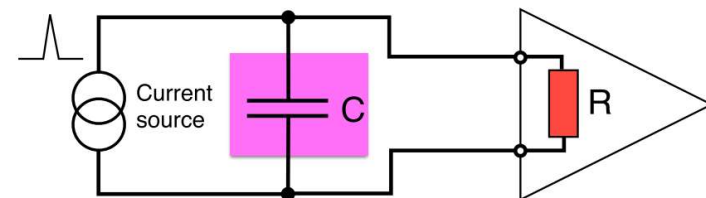NB : $tr = t_{10-90\%} = 2.2 \tau$.
 $f_{-3dB} = 1/2\pi\tau = 0.35 / t_{10-90}$
 $f_{-3dB} = 1 \text{ GHz} \leftrightarrow t_{10-90\%} = 300 \text{ ps}$
 $1 \text{ ps} = 300 \mu\text{m in vacuum}$




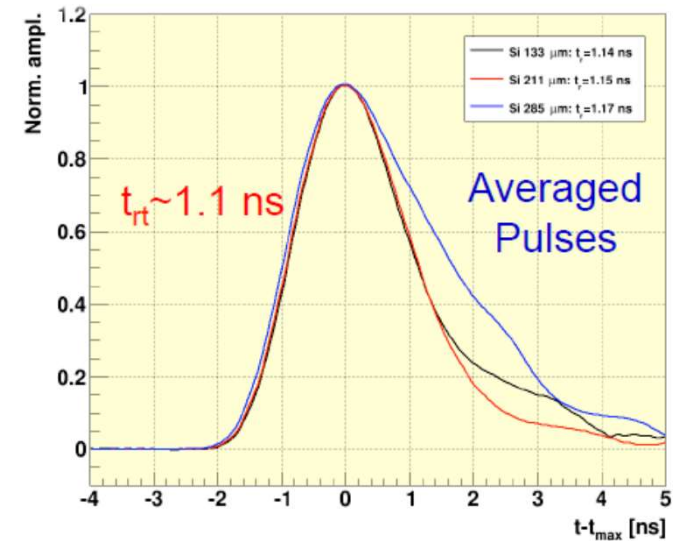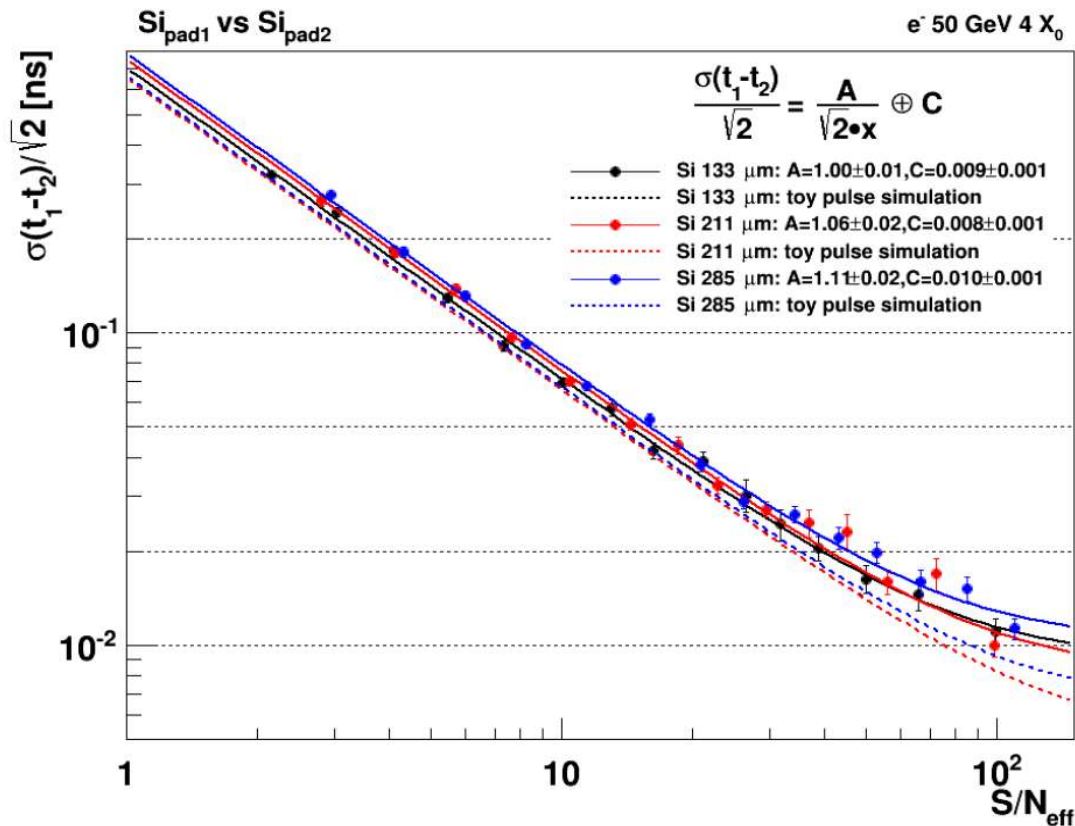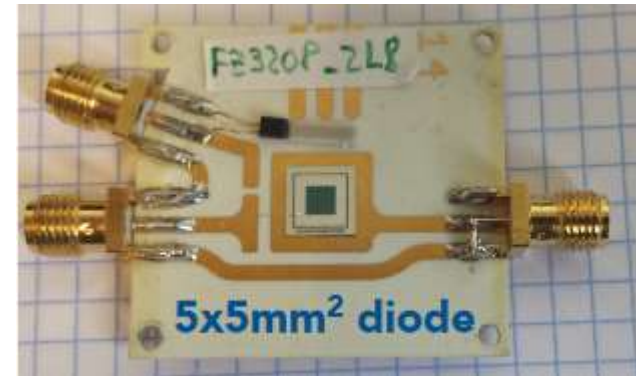- CMS HGCAL testbeam measurements
- Jitter : $j \sim 1 \text{ ns} / \text{S/N}$
 - But S and N depend on BW...
 - Parts come from detector and from electronics




© M. Mannelli et al. ACES 2016
<https://indico.cern.ch/event/468486>

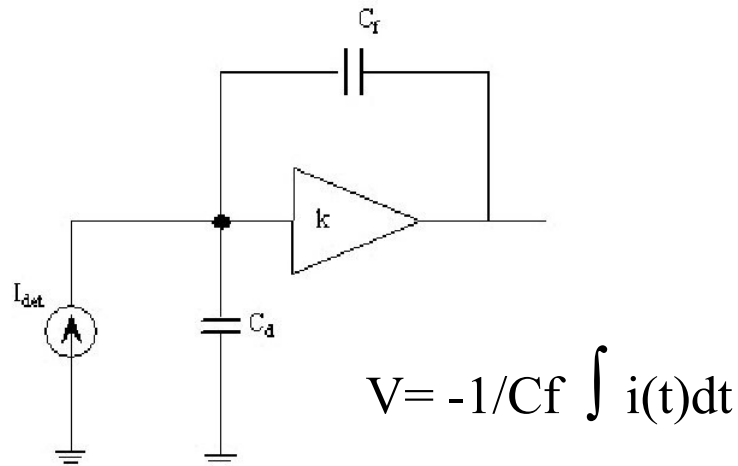- Charge preamp
- Capacitive feedback C_f
- $V_{out}/I_{in} = -1/j\omega C_f$
- Perfect integrator : $v_{out} = -Q/C_f$
- Difficult to accommodate large SiPM signals (200 pC)
- Lowest noise configuration
- Need R_f to empty C_f




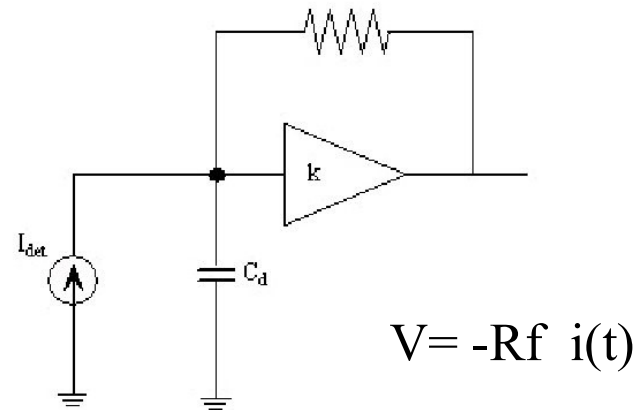- Current preamp
- Resistive feedback R_f
- $V_{out}/I_{in} = -R_f$
- Keeps signal shape
- Need C_f for stability




Transimpedance configuration

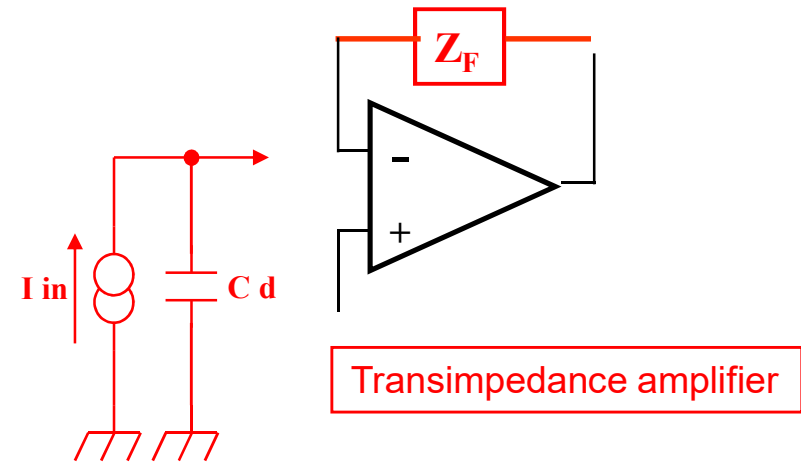- Transfer function
 - Using a VFOA with gain G
 - $V_{out} - v_{in} = -Z_f i_f$
 - $V_{in} = Z_d (i_{in} - i_f) = -v_{out}/G$
 - $V_{out}(\omega)/i_{in}(\omega) = -Z_f / (1 + Z_f/GZ_d)$



- $Z_f = R_f / (1 + j\omega R_f C_f)$
 - At $f \ll 1/2\pi R_f C_f$:
 - $V_{out}(\omega)/i_{in}(\omega) = -R_f$
 - current preamp**
 - At $f \gg 1/2\pi R_f C_f$:
 - $V_{out}(\omega)/i_{in}(\omega) = -1/j\omega C_f$
 - charge preamp**

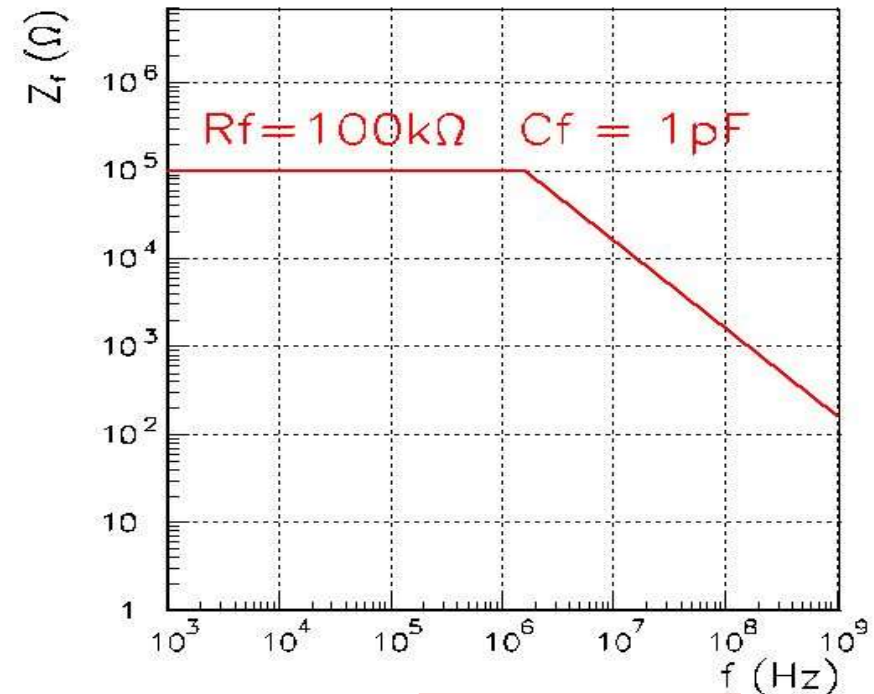
- Ballistic deficit with charge preamp
 - Effect of finite gain : G_0
 - Output voltage «only» $Q C_d/G_0 C_f$



Transfer function


Charge vs Current preamps

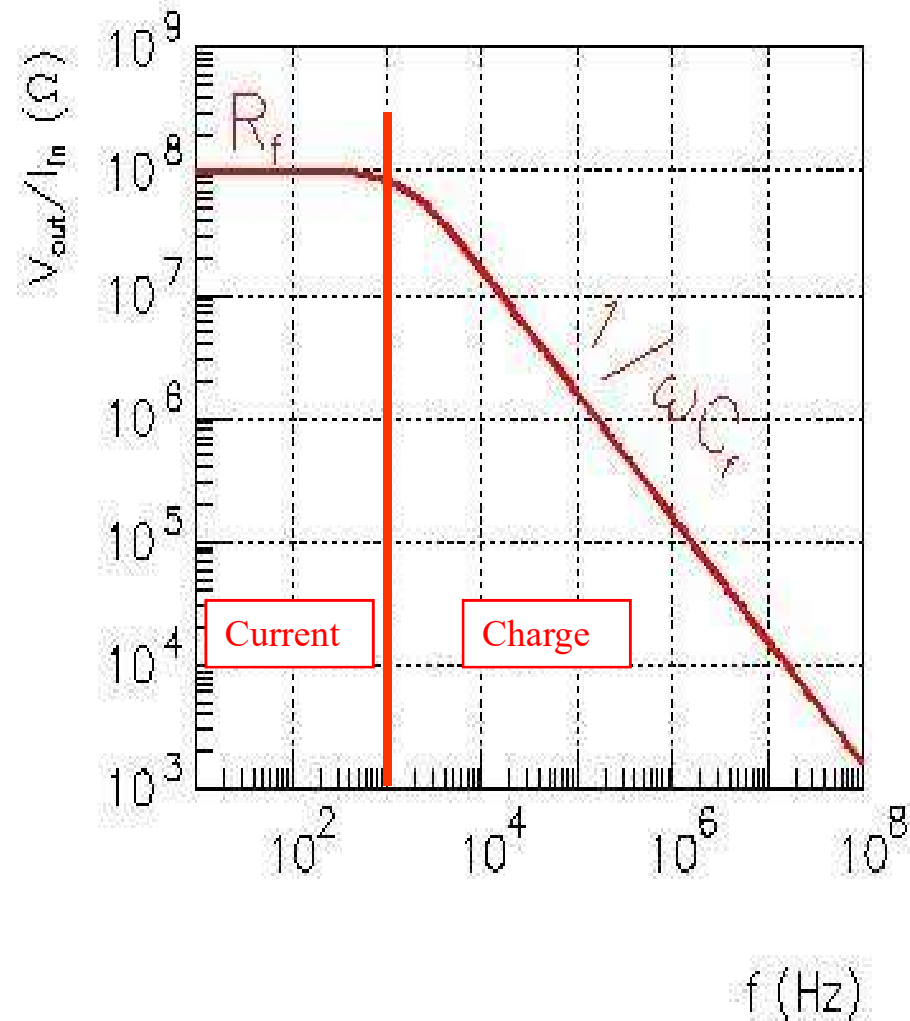- Charge preamps
 - Best noise performance
 - Best with short signals
 - Best with small capacitance
- Current preamps
 - Best for long signals
 - Best for high counting rate
 - Significant parallel noise
- Charge preamps are not slow, they are long
- Current preamps are not faster, they are shorter (but easily unstable)




Input impedance

- Input impedance
 - $Z_{in} = Z_f / G + 1$
 - $Z_{in} \rightarrow 0$ **virtual ground**
 - Minimizes sensitivity to detector impedance
 - Minimizes crosstalk
- Equivalent model
 - $G(\omega) = G_0 / (1 + j \omega / \omega_0)$
- Terms due to C_f
 - $Z_{in} = 1 / j\omega G_0 C_f + 1 / G_0 \omega_0 C_f$
 - **Virtual resistance** : $R_{eq} = 1 / G_0 \omega_0 C_f$
- Terms due to R_f
 - $Z_{in} = R_f / G_0 + j \omega R_f / G_0 \omega_0$
 - **Virtual inductance** : $L_{eq} = R_f / G_0 \omega_0$
- Possible oscillatory behaviour with capacitive source

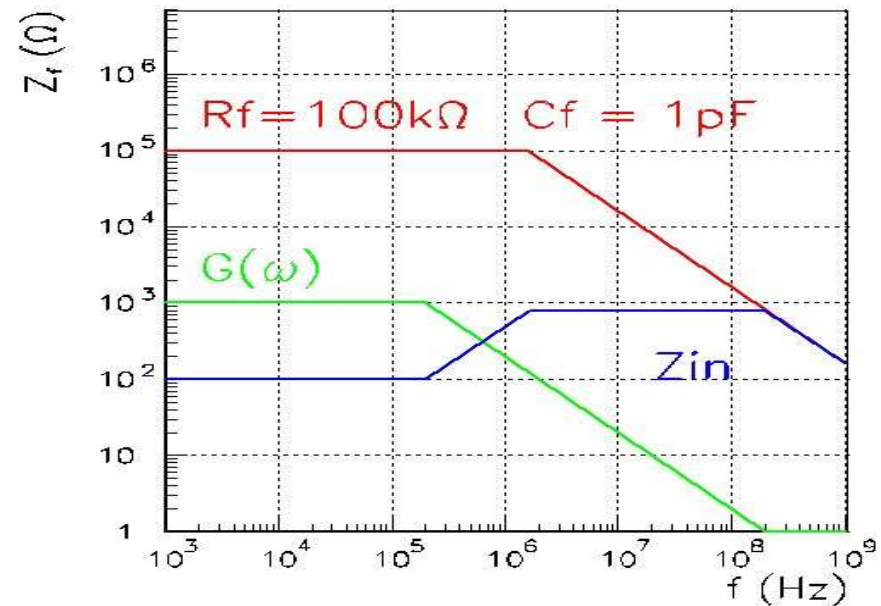

Input impedance or TZA

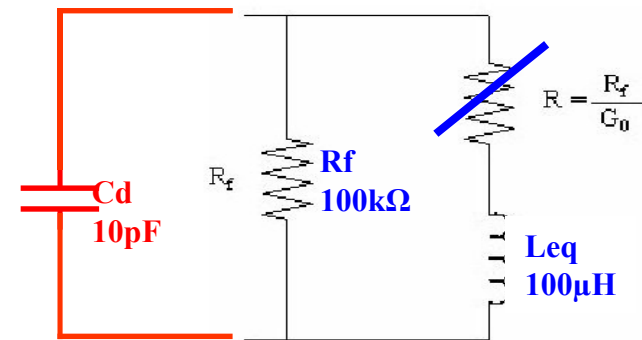


Equivalent circuit at the input


Current preamplifiers :

- Easily oscillatory
 - Unstable with capacitive detector
 - Inductive input impedance : $= R_f / \omega C$
 - Resonance at : $f_{res} = 1/2\pi \sqrt{L_{eq} C_d}$
 - Quality factor : $Q = R / \sqrt{L_{eq}/C_d}$
 - $Q > 1/2 \rightarrow$ ringing
 - Damping with capacitance C_f
 - $C_f = 2 \sqrt{C_d/R_f G_0 \omega_0}$
 - Easier with fast amplifiers

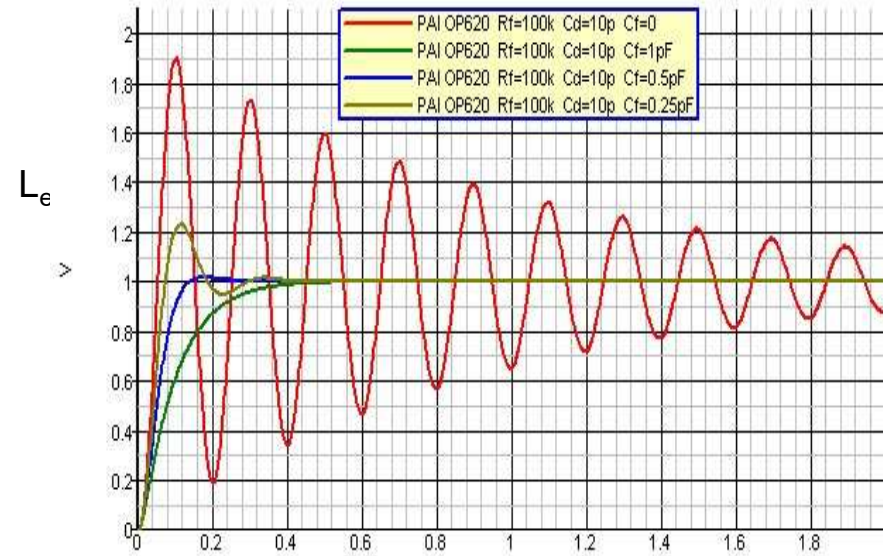- In frequency domain
 - $H(j\omega) = -R_f / (1 + j\omega R_f C_d / G_0)$
 - $G(\omega) = G_0 / (1 + j\omega / \omega_0)$
 - $H = -R_f / (1 + j\omega R_f C_d / G_0 - \omega^2 R_f C_d / G_0 \omega_0)$



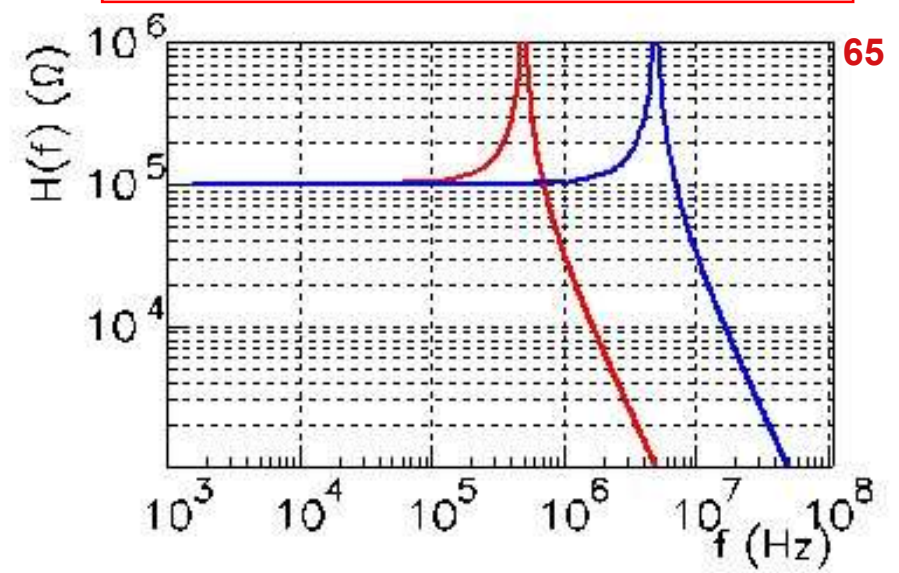
Step response of current sensitive preamp



- Open loop configurations : current conveyors, RF amplifiers
- Usually designed at transistor level MOS or SiGe


- **Current conveyors**

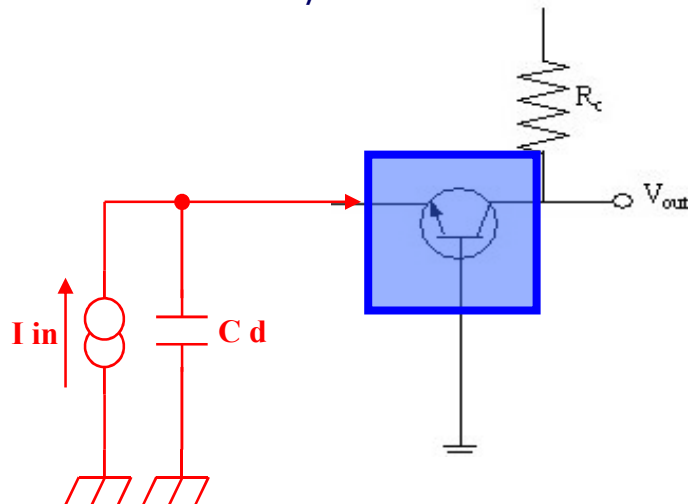- Small Z_{in} : current sensitive input
- Large Z_{out} : current driven output
- Unity gain current conveyor
- E.g. : (super) common-base configuration
- Low input impedance : $R_{in} = 1/g_m$
- Transimpedance : R_c
- Bandwidth : $1/2\pi R_c C_u > 1 \text{ GHz}$






- **RF amplifiers**

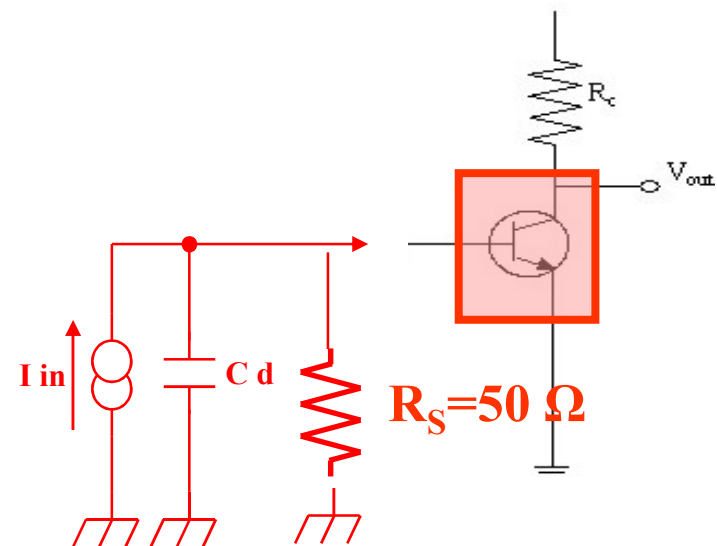- Large Z_{in} : voltage sensitive input
- Large Z_{out} : current driven output
- Current conversion with resistor R_S
- E.g. common-emitter configuration
- Transimpedance : $-g_m R_c R_S$
- Bandwidth : $1/2\pi R_S C_t$



Signal : detector current

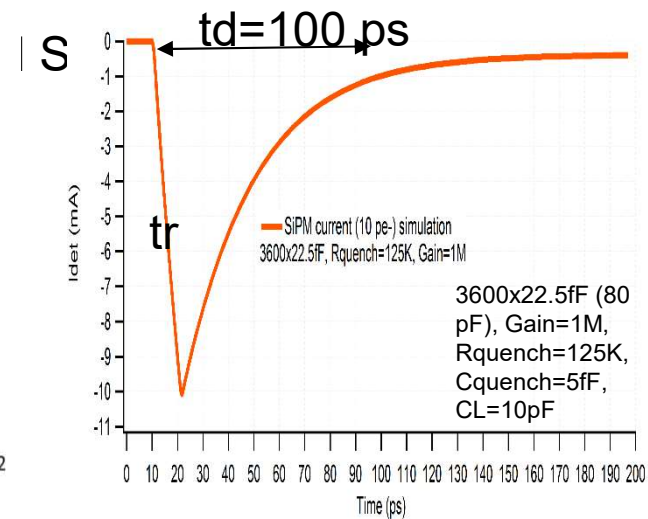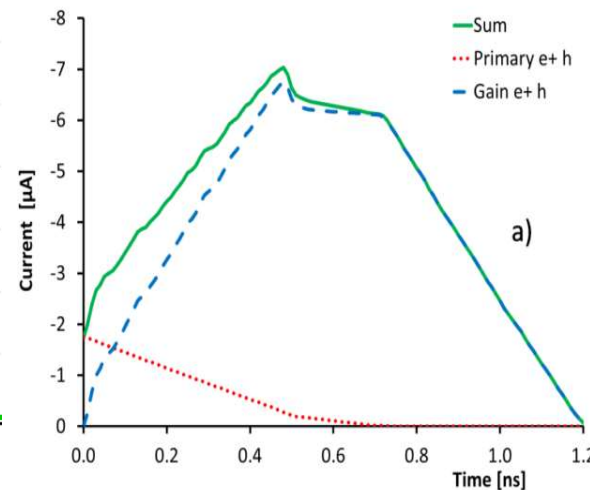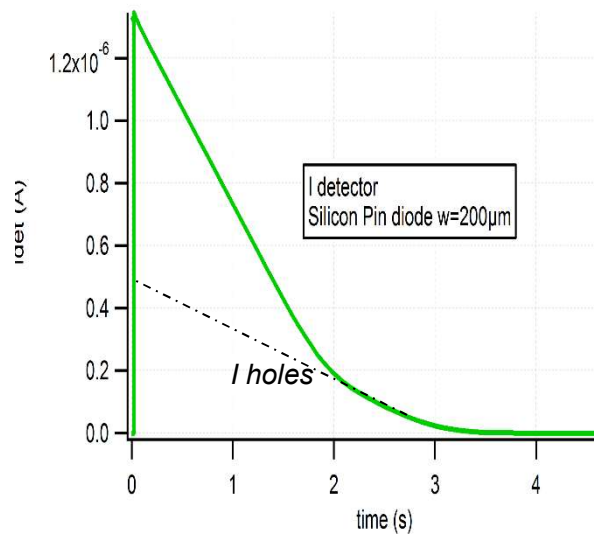
- PN diode $w = 200\mu\text{m}$
- Very short rise time : $t_r \sim 10\text{ps}$
- Relatively long «drift time» : $t_d \sim 2\text{ns}$
- LGAD sensor $w = 50\mu\text{m}$
- rise time : $t_r \sim 500\text{ps}$
- Decay time» : $t_d \sim 700\text{ps}$
- SiPM detector (10pe-)
- very short rise time : $t_r \sim 10\text{ps}$
- Short duration : $t_d \sim 100\text{ps}$,






© *Harmut Sadrozinski (Santa Cruz) “the beautiful risetime of the detector is spoilt by the electronics”*

Detector impedance and input voltage

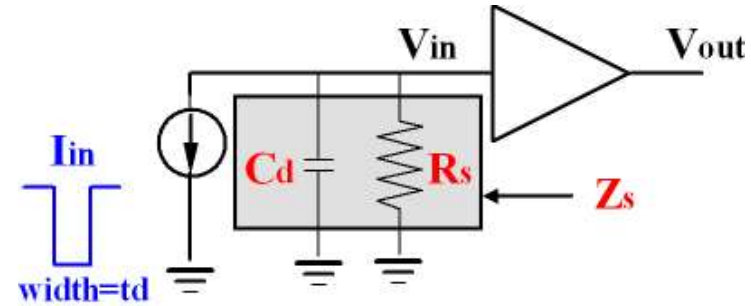- 1 GHz, C_d =few tens of pF, input signal width < 1 ns
- $C_d > 1$ pF, Z_s @1GHz dominated by C_d
- Rise time: $t_r = t_d$ when $t_d \ll R_s C_d$ and $t_r = R_s C_d$ when $t_d \gg R_s C_d$







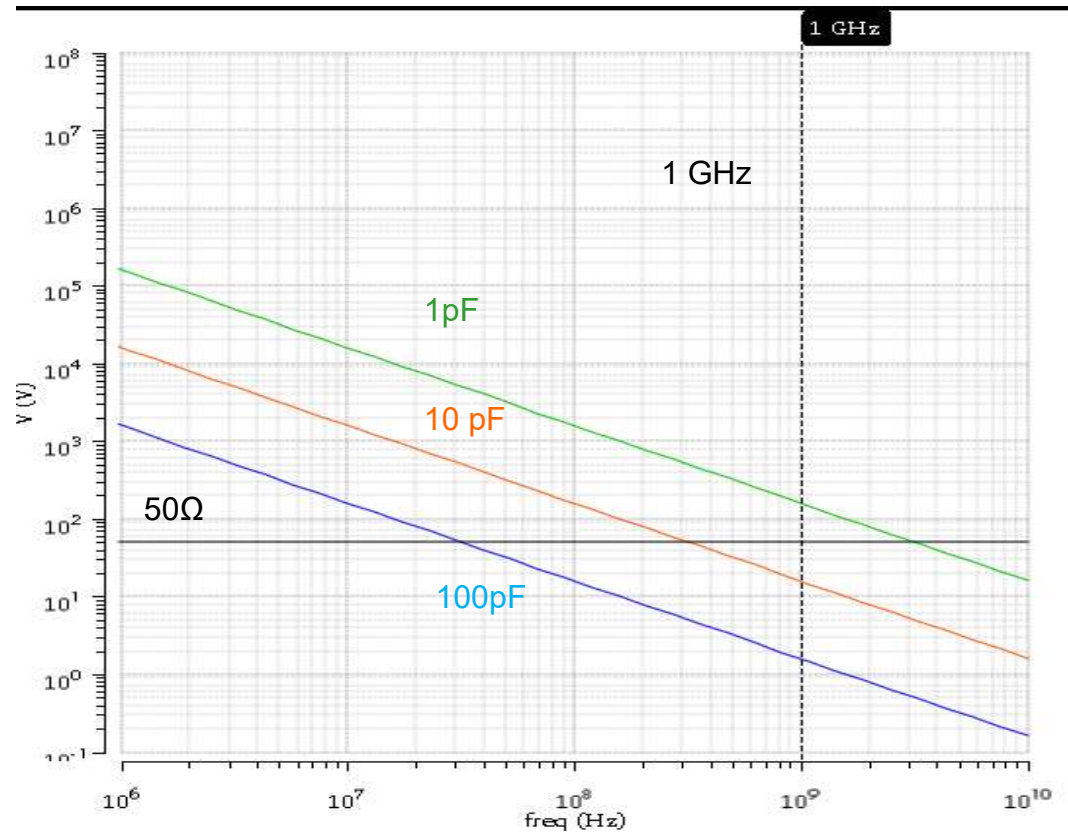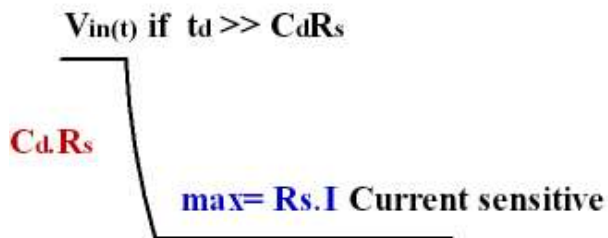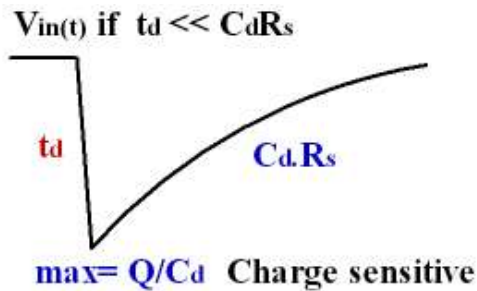At HF : difficult to beat the capacitance
=> signal integrated on C_d






voltage vs current sensitive

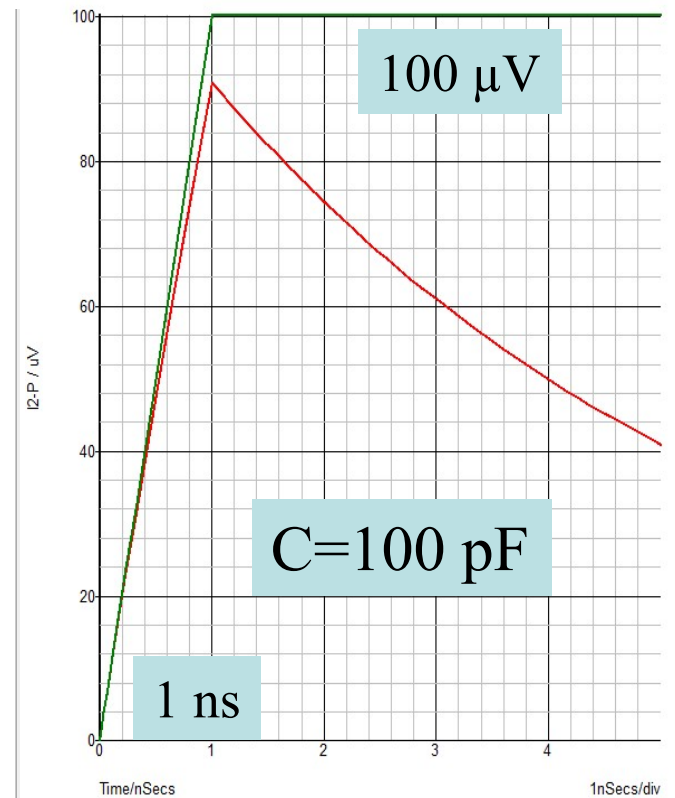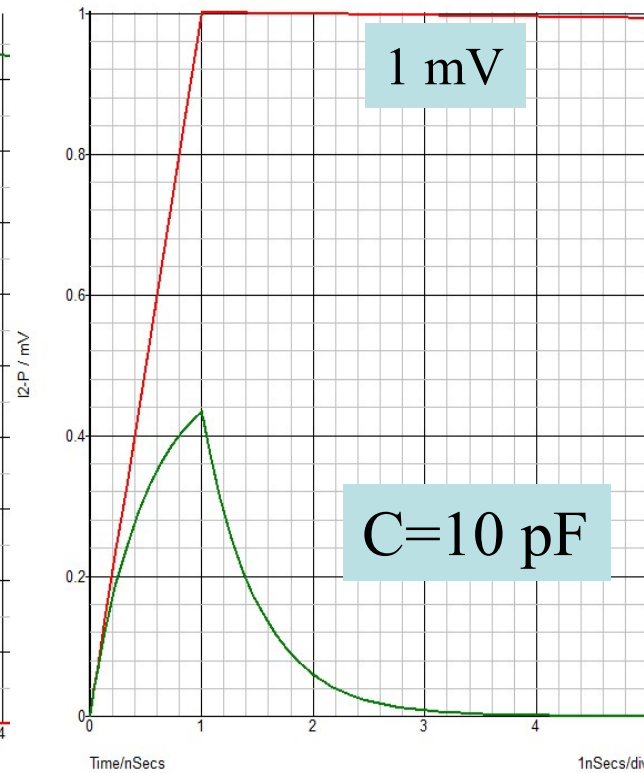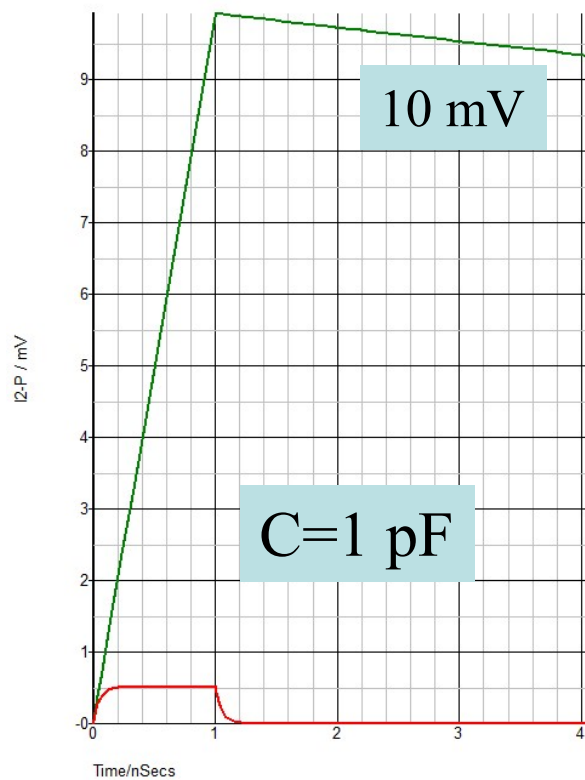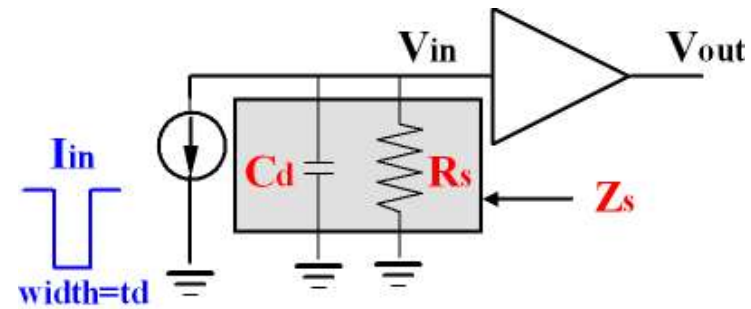- Example : 10 fC – 1 ns signal from 1-10-100 pF sensors into 50 Ω (current) or 50k (voltage) preamp



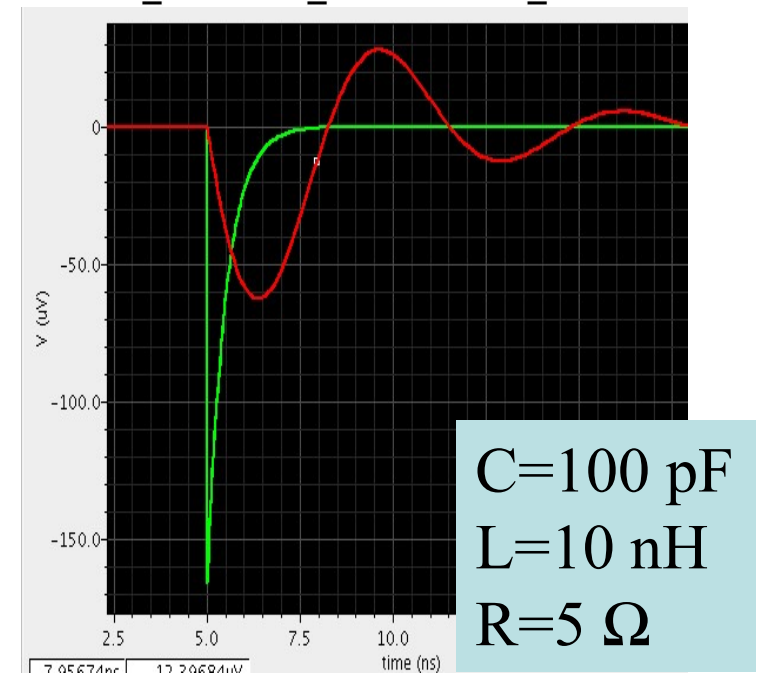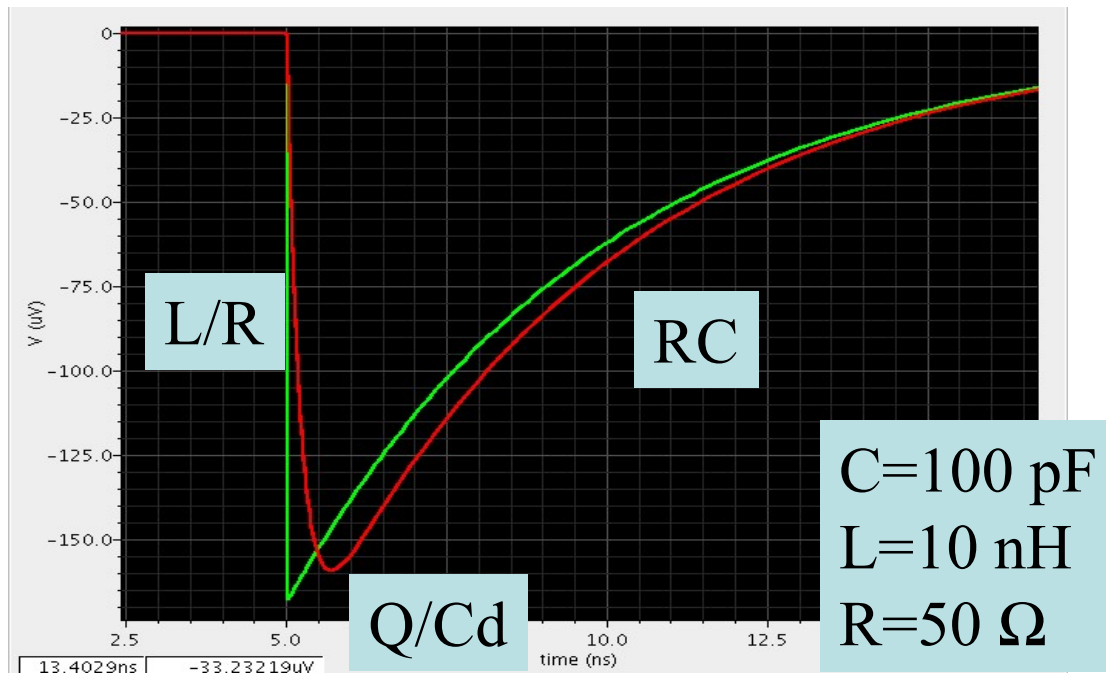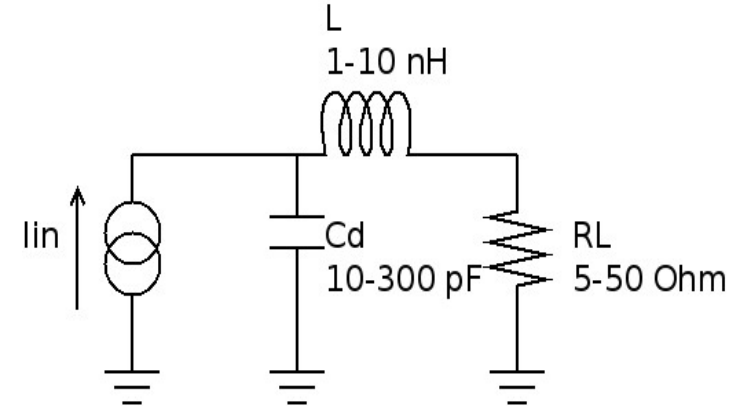Examples of pulse shapes

- SiPM pulse : $Q=160$ fC, $C_d=100$ pF, $L=0-10$ nH, $R_{PA}=5-50 \Omega$
- Sensitivity to parasitic inductance
- Choice of R_{PA} : decay time, stability
- Small R_{PA} not necessarily the fastest
- Convolve with current shape... (here delta)




- Response to very short pulse

- Broadband

- $Z_{in} = R_s$ (50 Ohm)

- $V_{in} = Q/C_{in}$

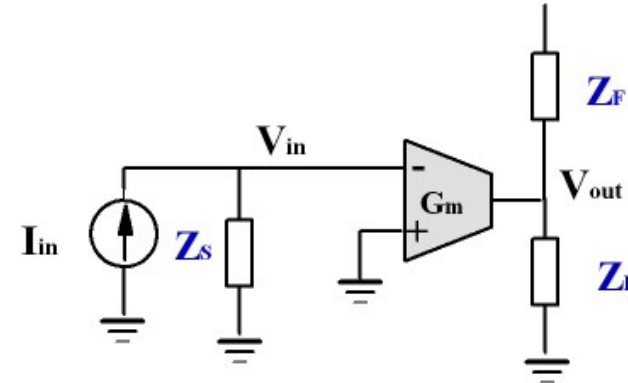
- $V_{OUT} = -G_m R_F \frac{Q_{IN}}{C_d}$



- Transimpedance

- $Z_{in} \sim Z_f/G \sim 1/g_m$

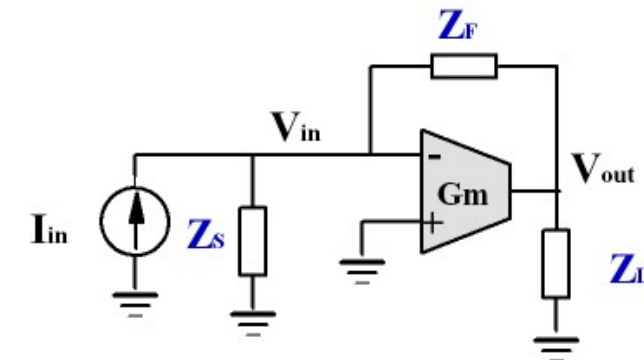- $V_{OUT} = \frac{1}{1 + j\omega \frac{C_d}{G_m}} \frac{R_F}{G_m} I_{IN} \approx -G_m R_F \frac{Q_{IN}}{C_d}$




- Same response at High Frequency

- For highest speed : go to broadband. Faster, less stability issues

- Jitter is given by [details in backup] :
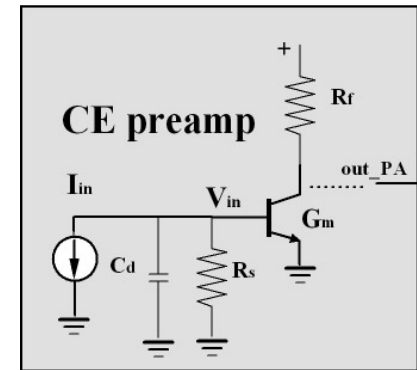
$$\sigma_t^J = \frac{N}{dV/dt} = \frac{e_n}{\sqrt{2t_{10-90_PA}}} \frac{C_d \sqrt{t_{10-90_PA}^2 + t_d^2}}{Q_{in}} = \frac{e_n C_d}{Q_{in}} \sqrt{\frac{t_{10-90_PA}^2 + t_d^2}{2t_{10-90_PA}}}$$



- Optimum value: $t_{10-90_PA} = t_d$ (current duration)


$$\sigma_t^J = \frac{e_n C_d}{Q_{in}} \sqrt{t_d}$$

C_d : detector capacitance
 t_{10-90_PA} : rise time of the PA
 t_d : drift time of the detector
 e_n : preamp noise density

Dominated by sensor
 Electronics only gives
 the spectral density of
 the input transistor e_n

- Gives ps/fC as scales with $1/Q_{in}$
- Electronics noise e_n given by the input transistor transconductance g_m :

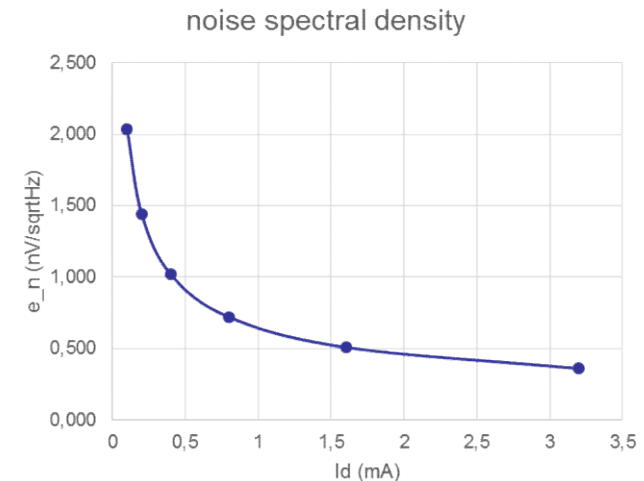
$$e_n = \sqrt{\frac{2kT}{g_m}} \approx \frac{2kT}{\sqrt{qI_D}}$$



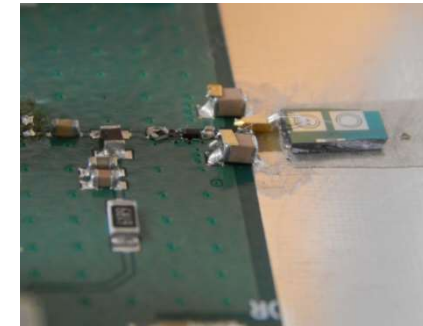
Examples [measurements from testbeam studies]


- NA62 tracker : PIN diode thickness 300 μm $A=0.09 \text{ mm}^2$
 - $C_d = 0.1 \text{ pF}$ $e_n = 11 \text{ nV}/\sqrt{\text{Hz}}$ $t_d = 3 \text{ ns}$ $\sigma = 60 \text{ ps/Q(fC)}$
 - 1 MIP = 3 fC $\Rightarrow \sigma = 20 \text{ ps}/\text{\#MIP}$ ($\sim 60\text{-}200 \text{ ps}$ measured)
- CMS HGCAL : PIN diode thickness 300 μm $A=25 \text{ mm}^2$
 - $C_d = 8 \text{ pF}$ $e_n = 1 \text{ nV}/\sqrt{\text{Hz}}$ $t_d = 3 \text{ ns}$ $\sigma = 420 \text{ ps/Q(fC)}$
 - 1 MIP = 3.8 fC $\Rightarrow \sigma = 110 \text{ ps}/\text{\#MIP}$ ($\sim 200 \text{ ps}$ measured)
- ATLAS HGTD : LGAD diode thickness 50 μm $A= 2 \text{ mm}^2$
 $G = 10$
 - $C_d = 2 \text{ pF}$ $e_n = 2 \text{ nV}/\sqrt{\text{Hz}}$ $t_d = 0.5 \text{ ns}$ $\sigma = 50 \text{ ps/Q(fC)}$
 - 1 MIP = 5 fC ($G=10$) $\Rightarrow \sigma = 10 \text{ ps}/\text{\#MIP}$ ($\sim 40 \text{ ps}$ measured)
- SiPM $G = 1^{\text{E}6}$
 - $C_d = 300 \text{ pF}$ $e_n = 1 \text{ nV}/\sqrt{\text{Hz}}$ $t_d = 100 \text{ ps}$ $\sigma = 3 \text{ ns/Q(fC)}$
 - 1 pe = 160 fC $\Rightarrow \sigma = 20 \text{ ps}/\text{\#pe}$ ($\sim 60 \text{ ps}$ measured)

$$\sigma_t^J = \frac{e_n C_d}{Q_{in}} \sqrt{t_d}$$






SiGe preamp © N. Spencer (UCSC)

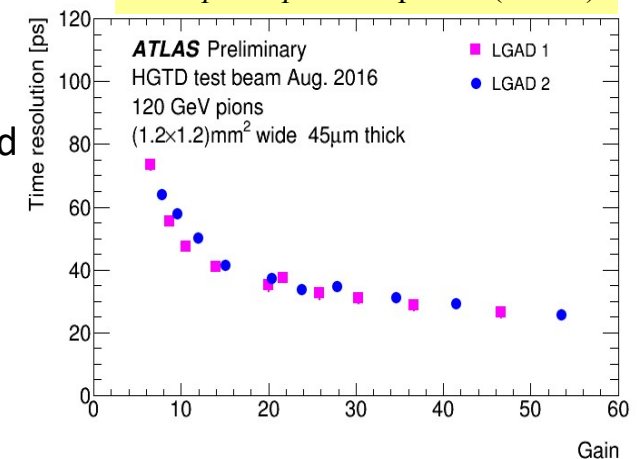


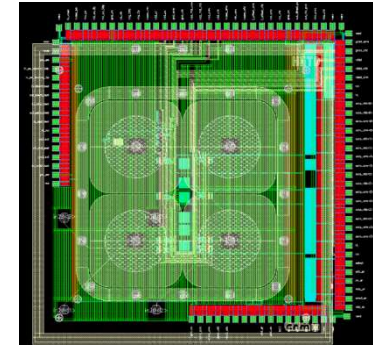


- ALTIROC ASIC designed for HGTD (Atlas LGAD Timing Read-Out Chip)
 - Broadband amplifier + high speed discriminator $P_d = 1 \text{ mW}$
 - Optimized for $1 \text{ mm}^2 \text{ } 50 \text{ }\mu\text{m}$ LGAD ($C_d=2 \text{ pF}$)
- TOA and TOT vs injected charge with additional $C_d= 2 \text{ pF}$
- Preamp and testboard capacitance : $\sim 1.3 \text{ pF}$
- **Jitter = 27 ps @ 10 fC**
- Time walk = 800 ps

© C. Agapopoulou LAL

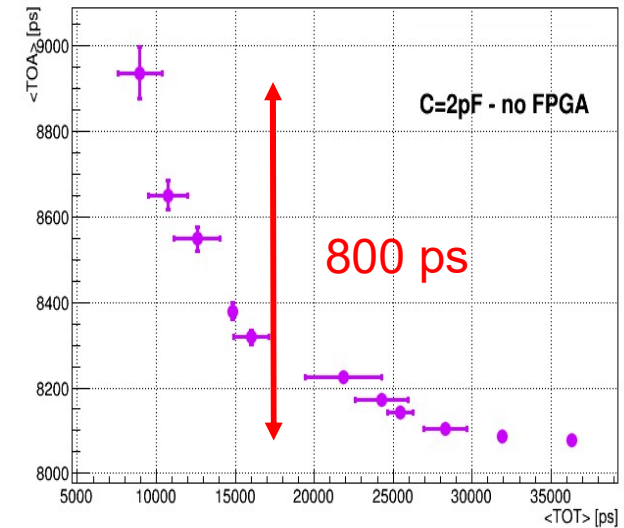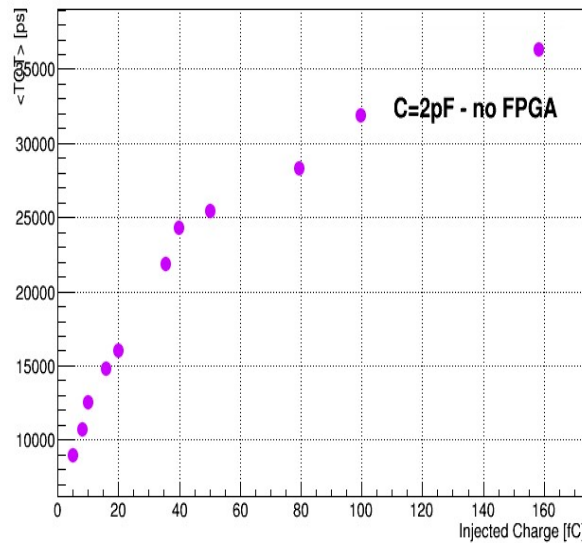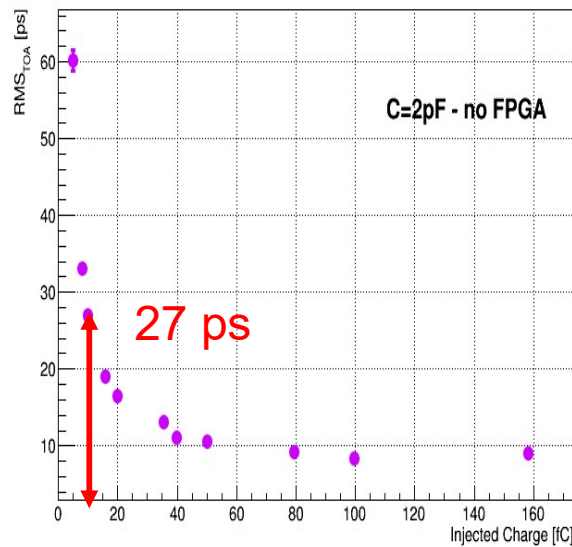

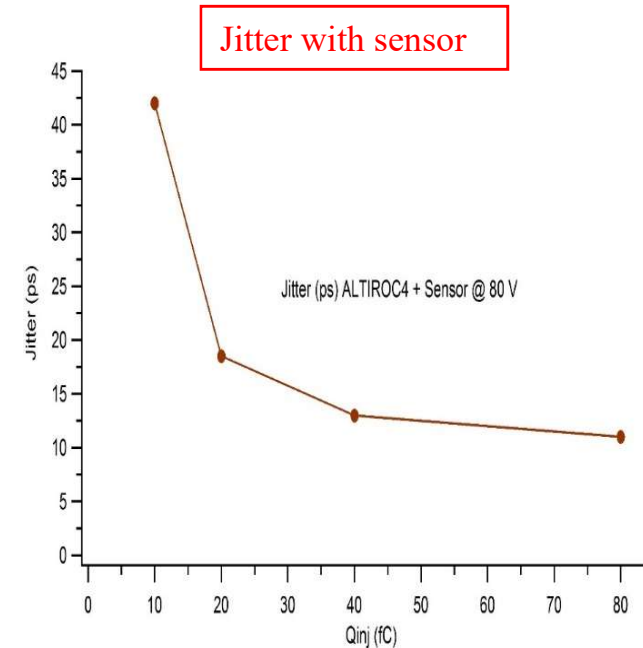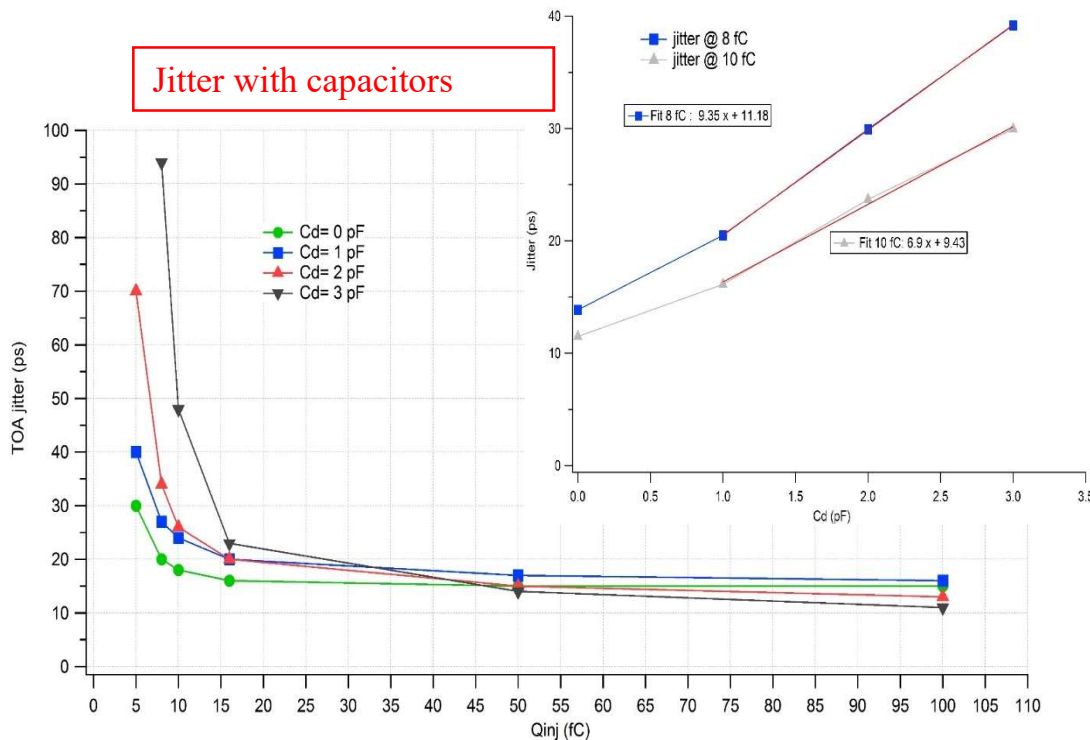- 1x1 mm² sensors fabricated by CNM/IFAE Barcelona
- Bump-bonded to ALTIROC0 at Barcelona
- Sensor connected, biased at 80 V to have the actual capacitance
- Testpulse injection with $C_{inj}=0.1$ pF
- **Jitter = 40 ps @ 10 fC**
- Corresponds to $C_d \sim 3$ pF




- SPTR
 - FWHM ~ 200 ps
 - Rms ~ 80 ps

Single photon time resolution of state of the art SiPMs




M.V. Nemallapudi,¹ S. Gundacker, P. Lecoq and E. Auffray

CERN,
23 Rue de Meyrin, Geneva, 1211-CH

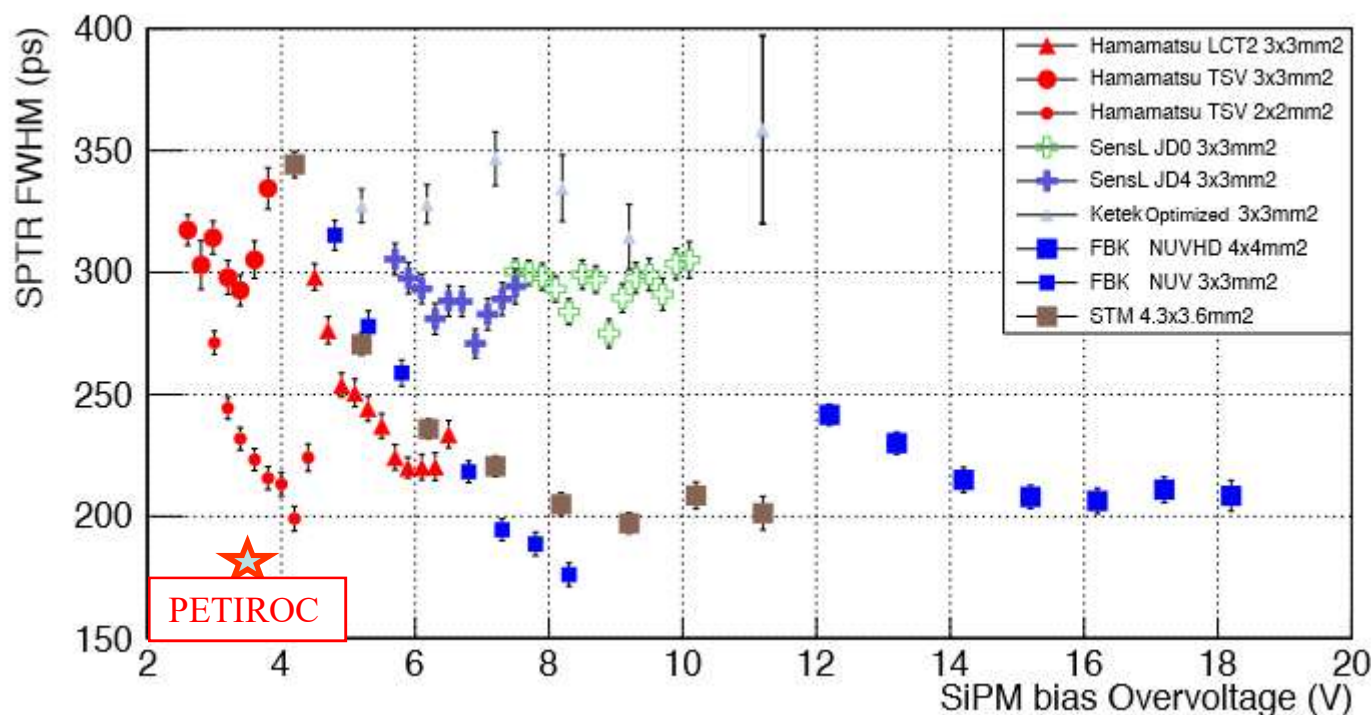

Going to lower SPTR

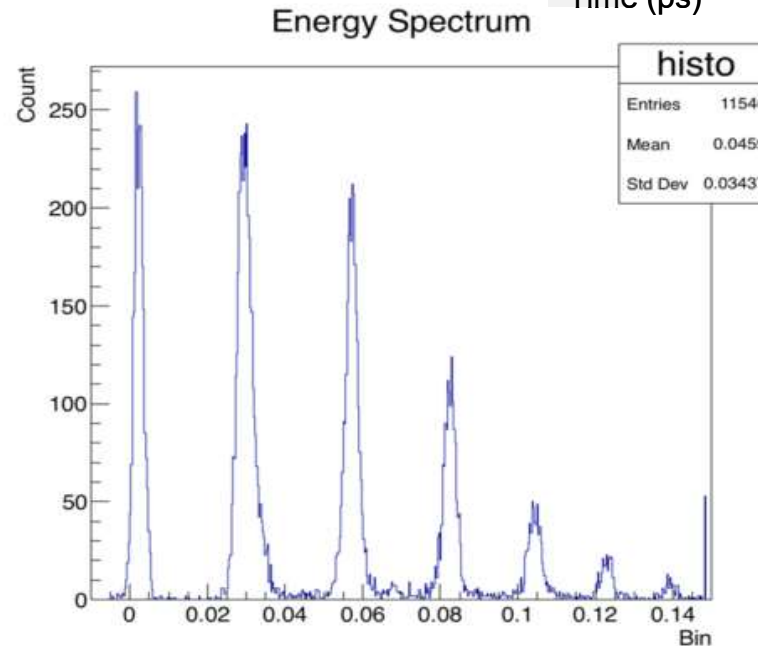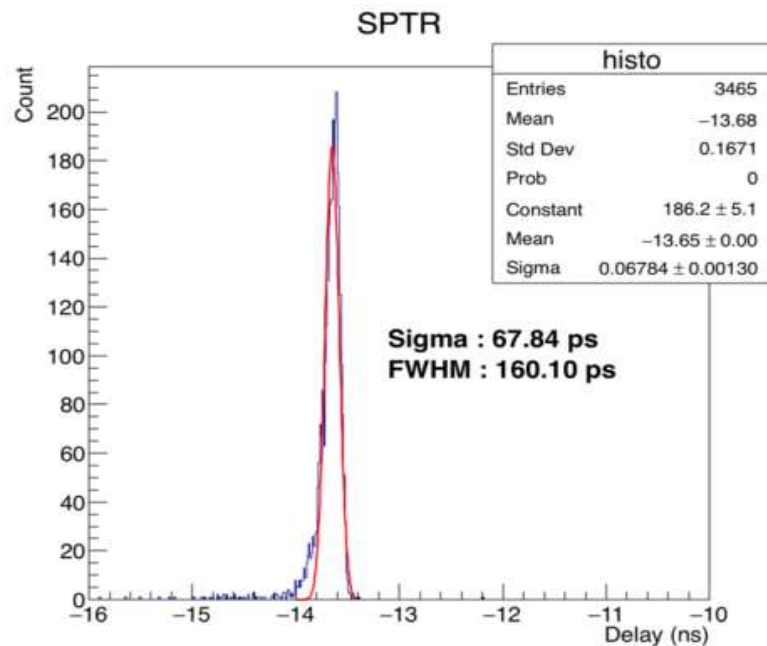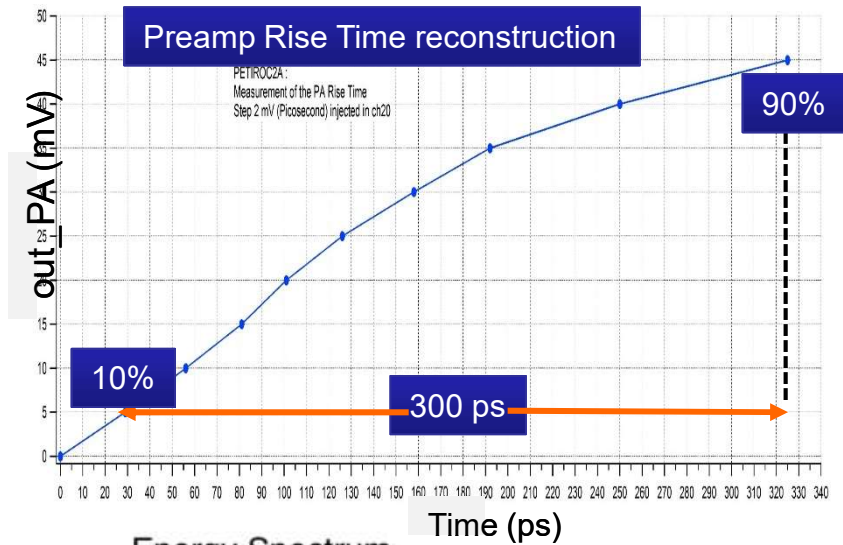- Expect ~ 20 ps/pe
- NINO risetime ~1 ns
- Test with PETIROC2 ($t_r = 300$ ps)
 - SPTR = 67 ps rms (180 ps FWHM)
- Possible effect of stray inductance
- Further studies in FAST framework




- Imaging calorimeters ramping up !
 - Require highly integrated R/O electronics : System On Chip
 - Low power, low noise, high speed, large dynamic range
 - Timing capability down to a few tens of ps
 - Lots of system issues
- Timing performance dominated by sensor characteristics
 - Capacitance, duration, MIP charge
 - Theory predicts :
 - Electronics affects only $g_m \sim I_d/2U_T$
- Work getting organized towards 10 ps (1 ps ?) timing

$$\sigma_t^J = \frac{e_n C_d}{Q_{in}} \sqrt{t_d}$$


A few (personal) comments

- Strong push for high speed front-end > GHz
 - Essential for timing measurements
 - Several configurations to get GBW > 10 GHz
 - Optimum use of SiGe bipolar transistors
- Voltage sensitive front-end
 - Easiest : 50 Ω termination, many commercial amplifiers (mini circuit...)
 - Beware of power dissipation
 - Easy multi-gain (time and charge)
- Current sensitive front-end
 - Potentially lower noise, lower input impedance
 - Largest GBW product
- In all cases, importance of reducing stray inductance


Electronics moves onto detectors

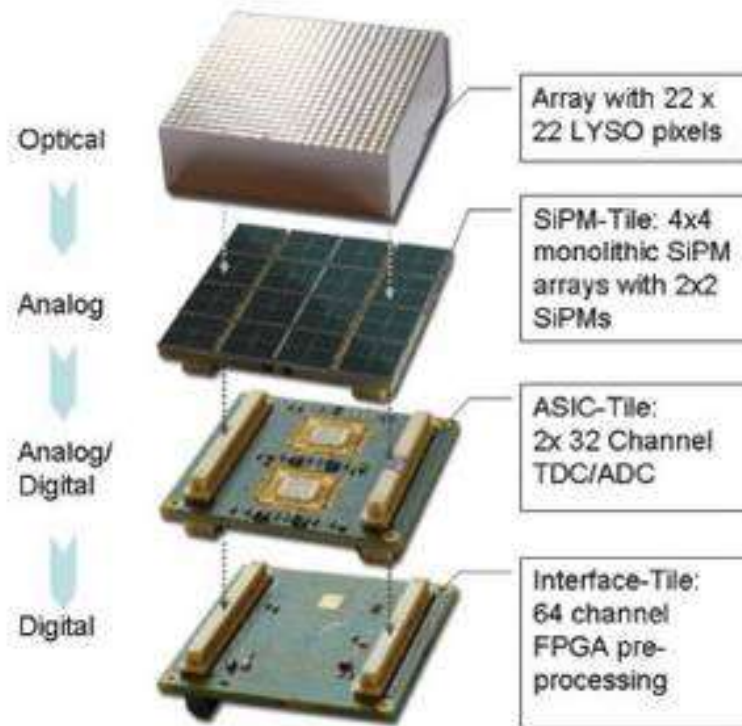


PET hyperimage project [P. Fisher]

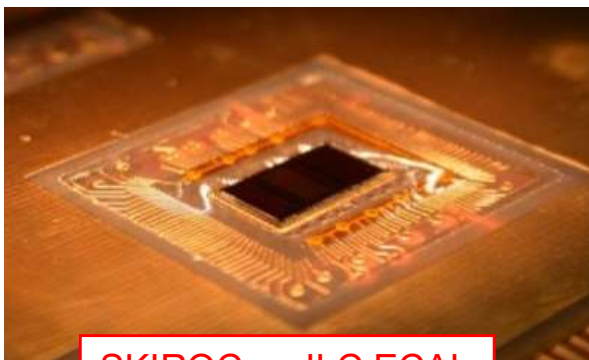

SKIROC on ILC ECAL

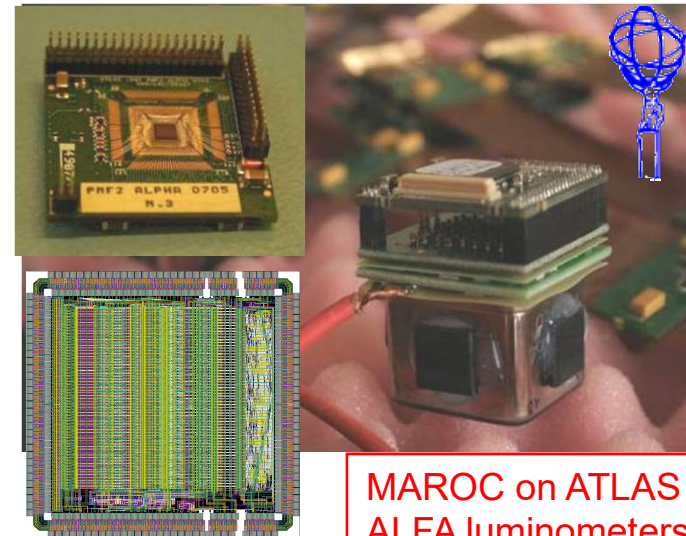


MAROC on ATLAS
ALFA luminometers

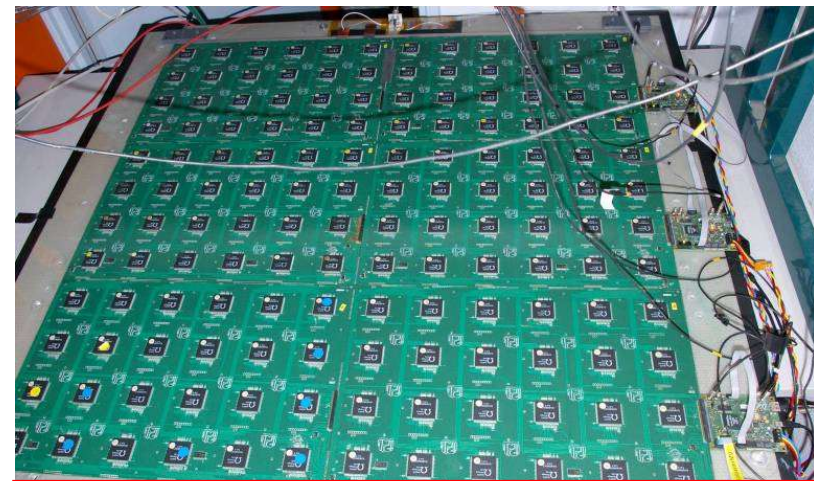

1m² RPC detector for ILC DHCAL [I. Laktineh]


Evolution of technologies

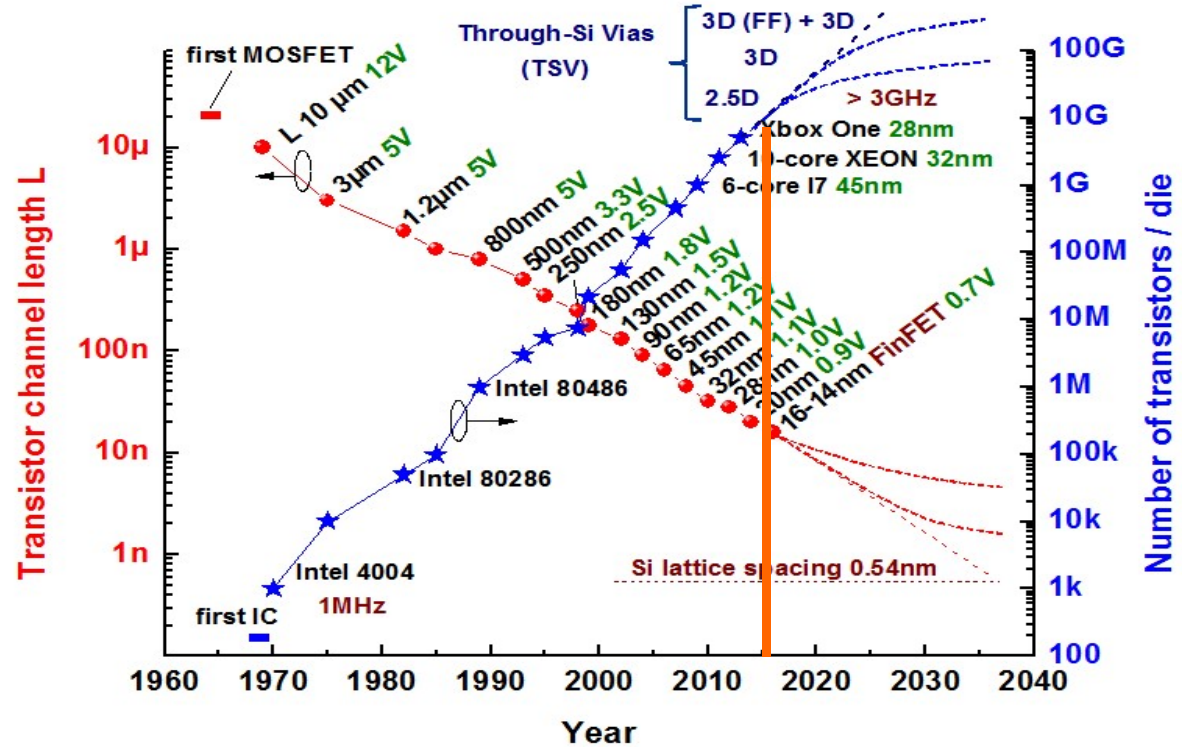- Performant design is at transistor level
- More and more functions are integrated inside chips (ASICs)
- Evolution of technologies make them more and more performant but more and more complex
- Cost increases ...
 - MPW costs :
 - 350 nm : 1 k€/mm²
 - 130 nm : 2 k€/mm²
 - 65 nm : 6 k€/mm²
- Chip size also...
- PP a few M\$/400G\$



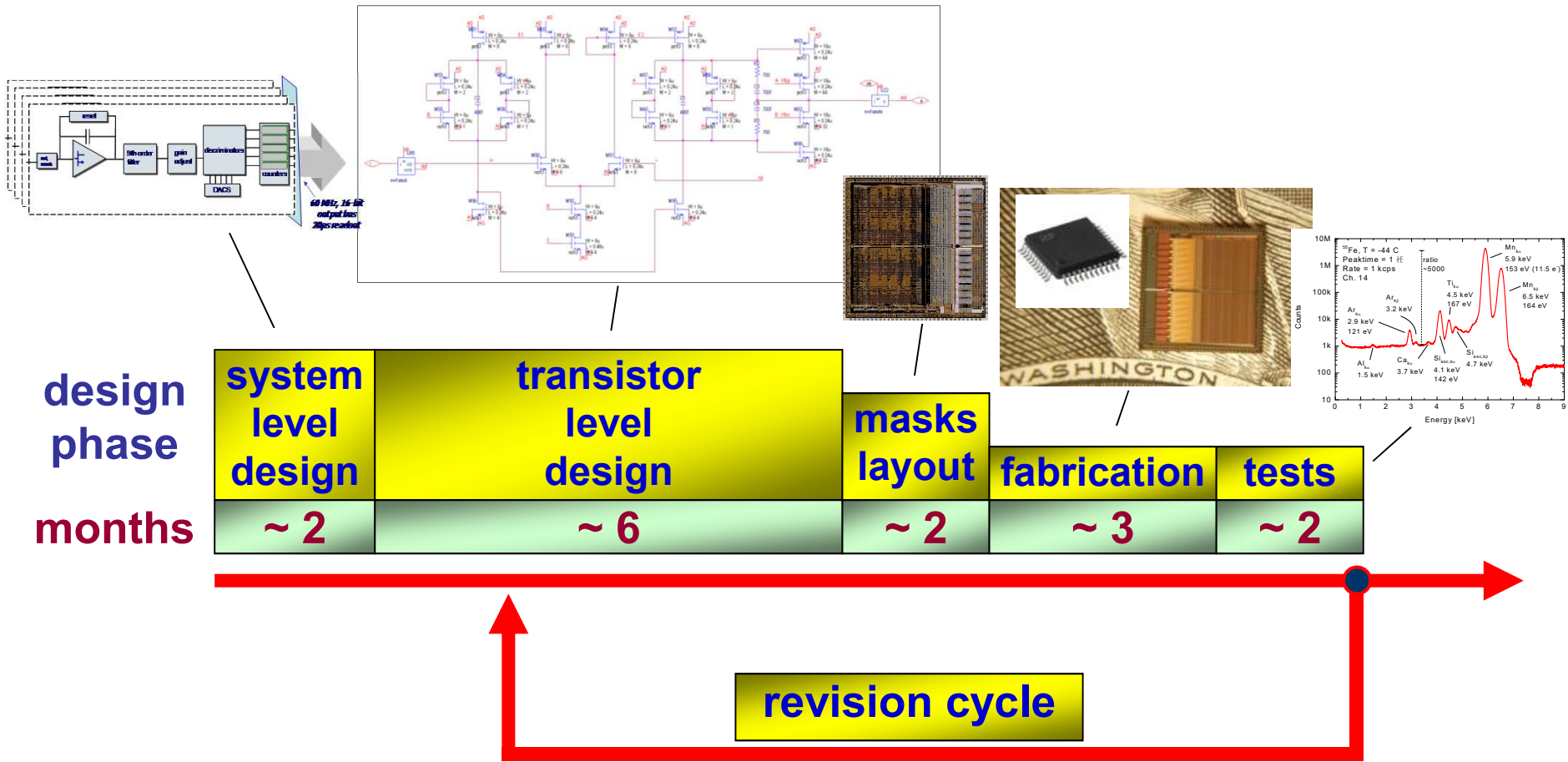10 ans d'évolution des spécifications techniques pour la réalisation d' ASIC






From concept to ready-for-production:

1 - 2 cycles, 2 - 3 years, 3-6 FTE (depending on complexity)

Higher functionality and complexity means more resources and expertise , higher risk, longer development time


- Low-noise, low-power **charge amplifiers**
 - gas, liquid, solid state detectors
 - capacitances from 10^{-14} to 10^{-8} F
- Switched and continuous **adaptive reset**
- **High-order filters**, stabilizers, drivers
 - peak time / gain adjustment
- Single- and multi-level **discriminators**
- **Peak and time detectors**, derandomizers
- **Analog memories and multiplexers**
- **Counters** and digital memories
- Configuration registers
- **ESD protections**
- **Calibration pulse generators**
- **Analog-to-digital** converters
- **Digital-to-analog** converters
- Precision **band-gap references**
- **Temperature sensors**
- Readout control logic
- Low-voltage **differential signaling**
- **Current-mode** analog and digital interface

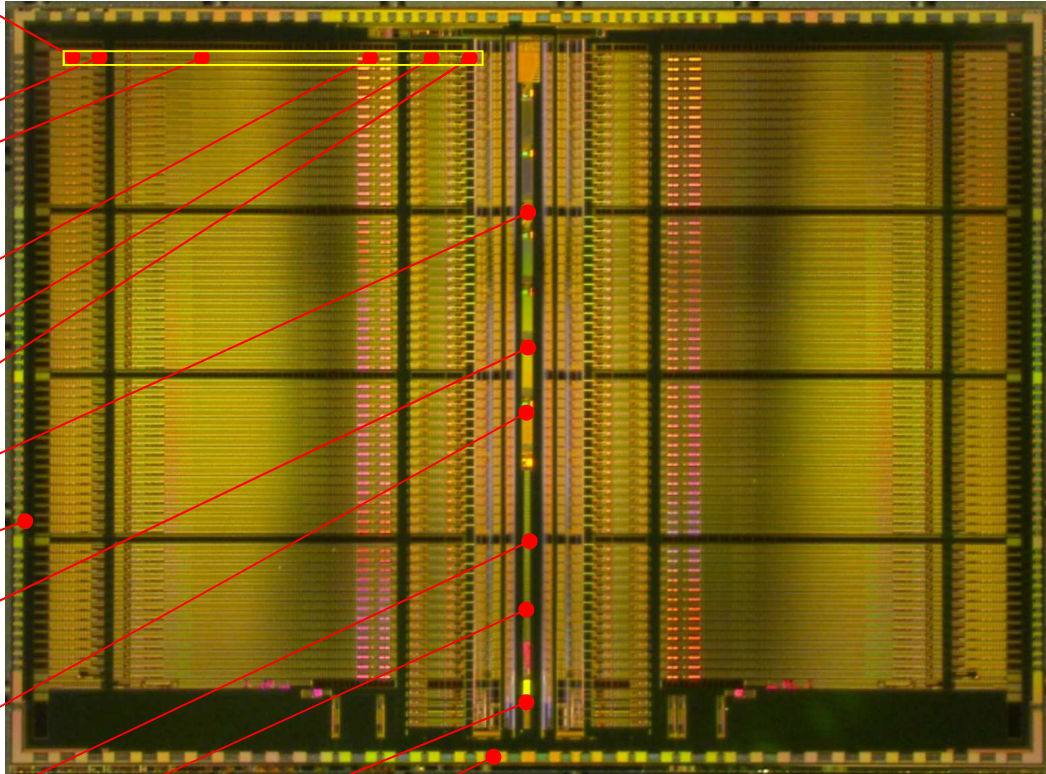

**ASIC for 3D CZT 3D CZT
Position Sensitive Detectors**

- **128 channels**
- **2 mW/channel**
- **13 x 10 mm²**
- **300,000 transistors**
- **CMOS 250 nm**

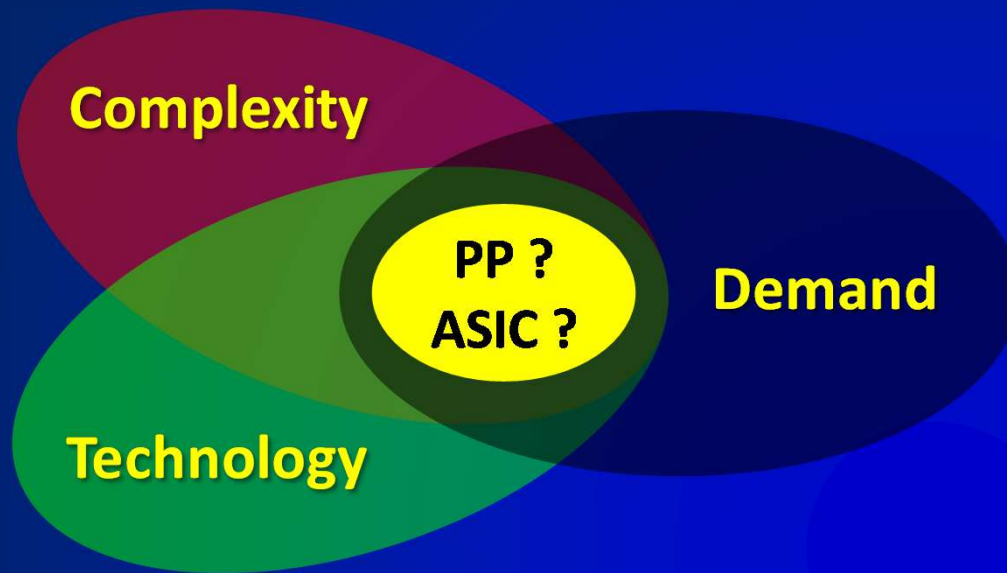
Functionality and complexity increase by the years



Collaborations ?

- only part of the solution
- communication
- overhead
- lead of large group

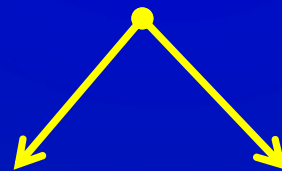The number of ASIC designers has to increase !



**involve
non-PP ASIC groups**

**increase size
of PP ASIC groups**


A note on ASICs in detectors:

ASIC developments are complex and require concentration of expertise and resources. For an ASIC to be successful, adequate infrastructure and collaboration on integral design of detectors and signal processing electronics is critical.

.

Microelectronics design teams

- Importance of team building

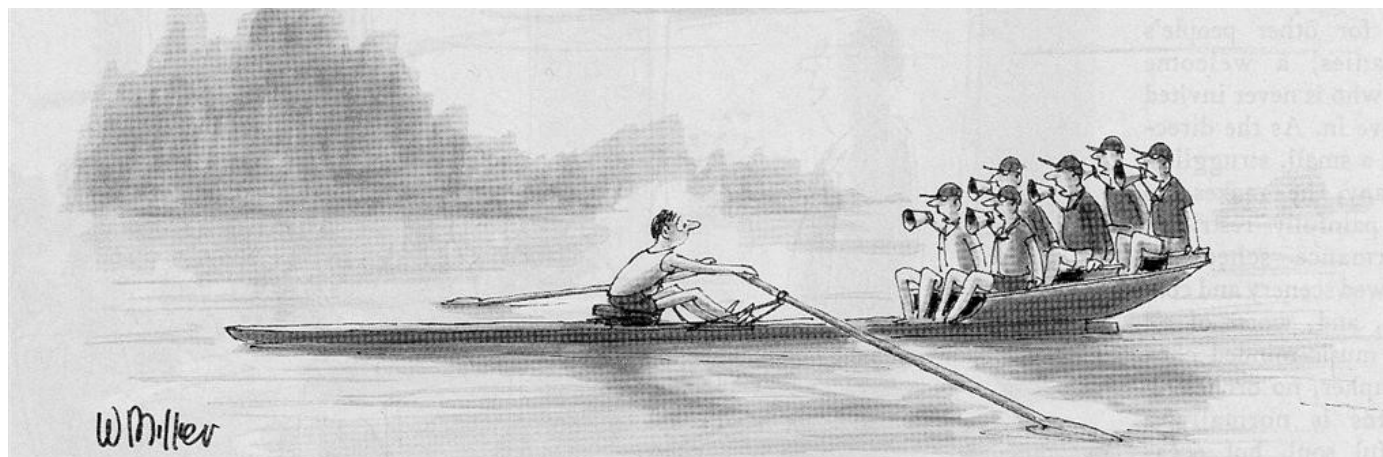

- enjoy designing electronics for future detectors !
- Profit from the nice location to foster collaborations
- 谢谢大家倾听我的报告








backup


Ωmega

NINO architecture

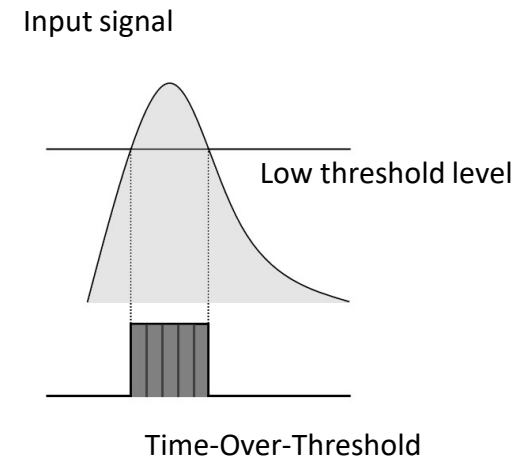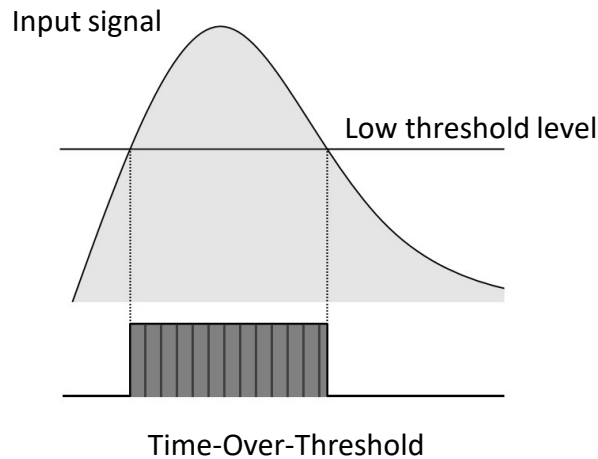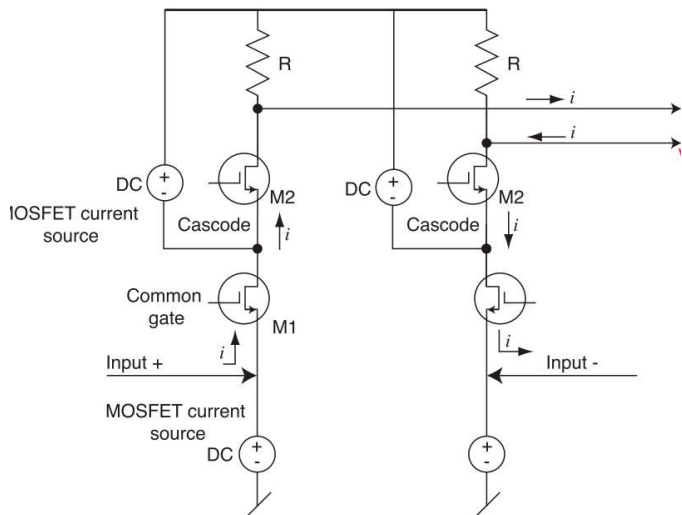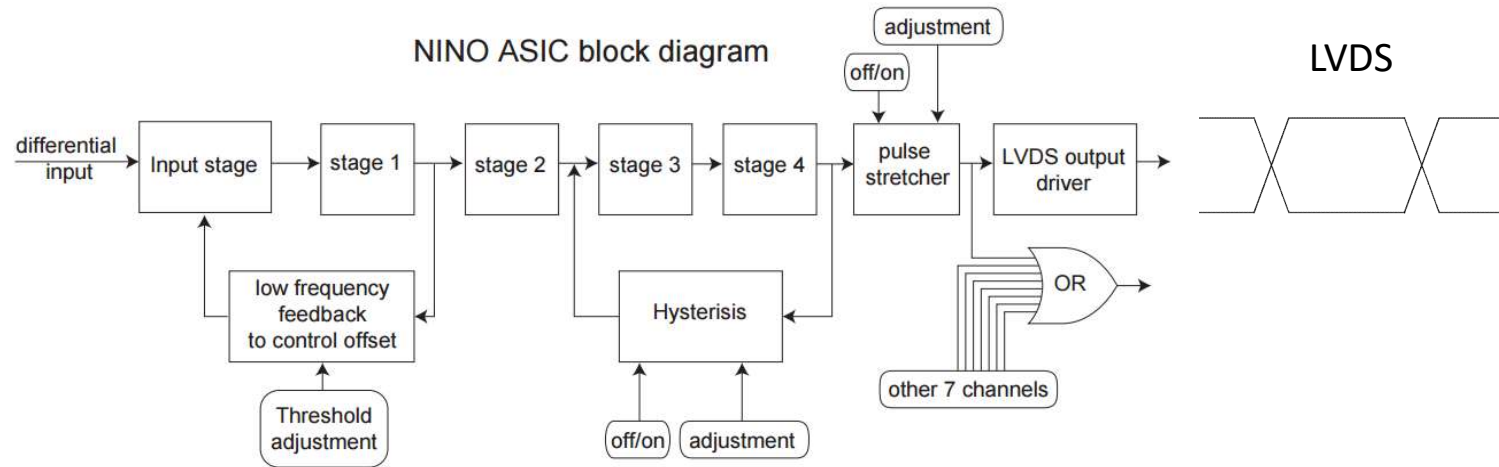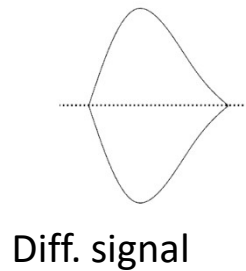- Current conveyor and discriminator
- Time over threshold for time walk correction




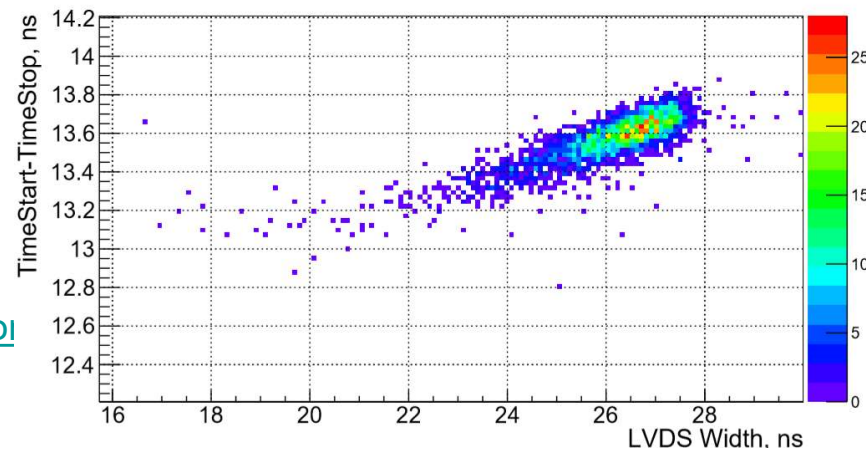- 60 ps jitter on detector
- Evolving to SUPER-NINO
 - Lower input impedance (5 ohm)
 - Targetting SiPM readout
 - Coupled to pico-TDC
 - <https://indico.cern.ch/event/609917/contribution/ernino-status.pdf>




Time-width distribution without correction.

Distribution of the LVDS widths.

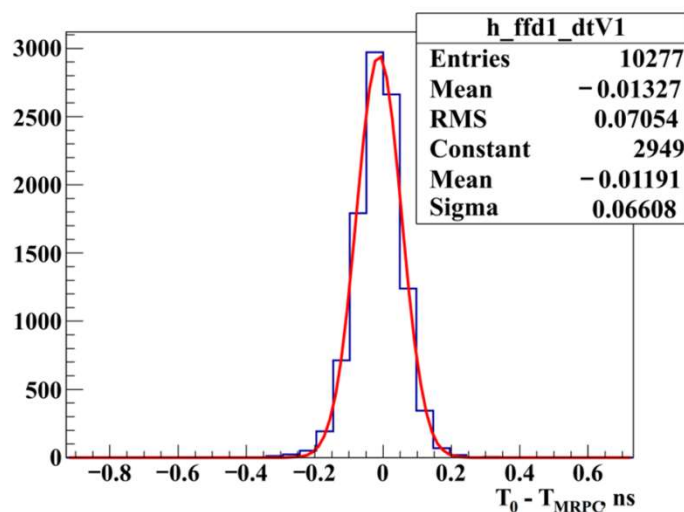



Distribution of the LVDS widths.

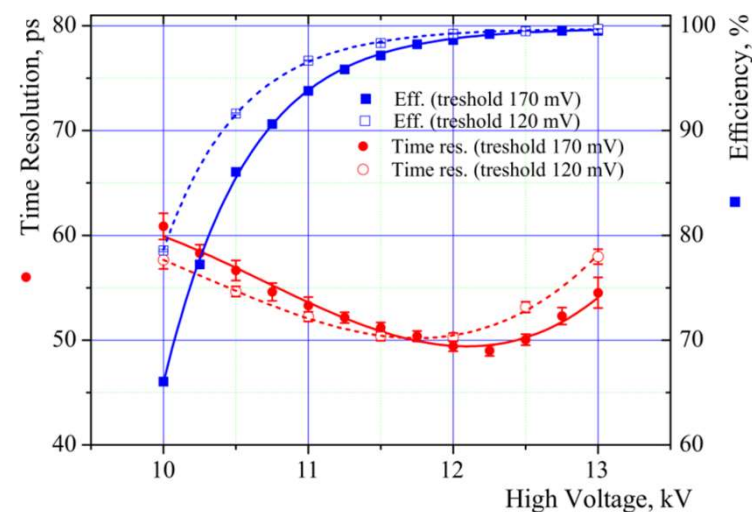

PETIROC2 DESCRIPTION

- Time of Flight read-out chip with embedded TDC (25 ps bin) and ADC
- Dynamic range: 160 fC up to 400 pC
- 32 channels (negative input)
 - 32 trigger outputs
 - NOR32_chrage
 - NOR32 time
 - Charge measurement over 10 bits
 - Time measurement over 10 bits
 - One multiplexed charge output
- Common trigger threshold adjustment and 6bit-dac/channel for individual adjustment
- Variable shaping time of the charge shaper
- 32 8bit-input dac for SiPM HV adjustment
- Power consumption 6 mW/ch
- Front-end
 - Broad Band SiGe fast amplifier
 - Fast SiGe discriminator
 - 1 GHz overall bandwidth, gain = 25

AMS 0,35 μ m SiGe

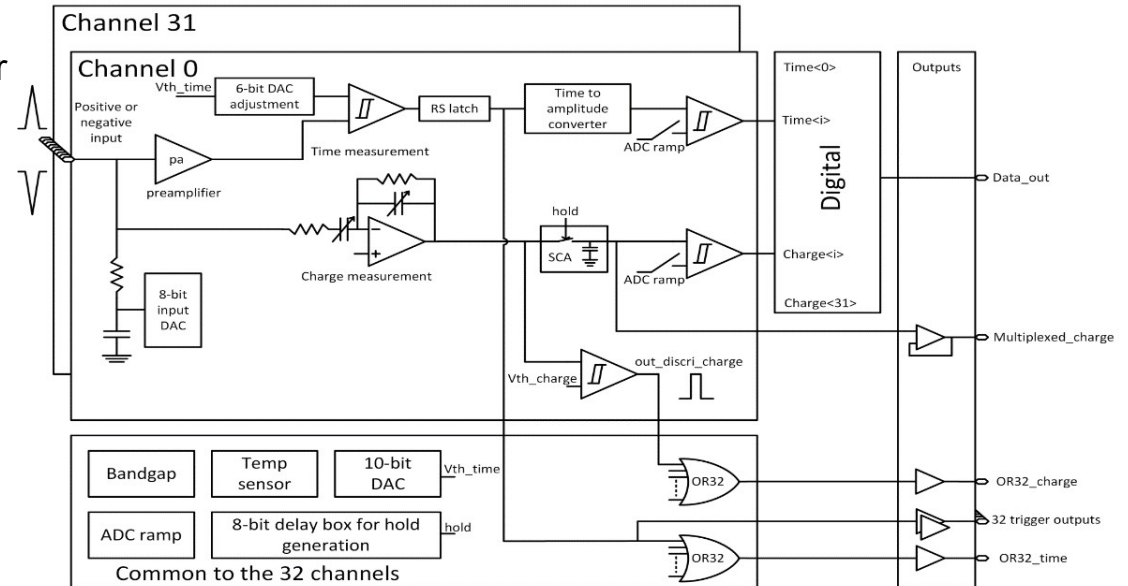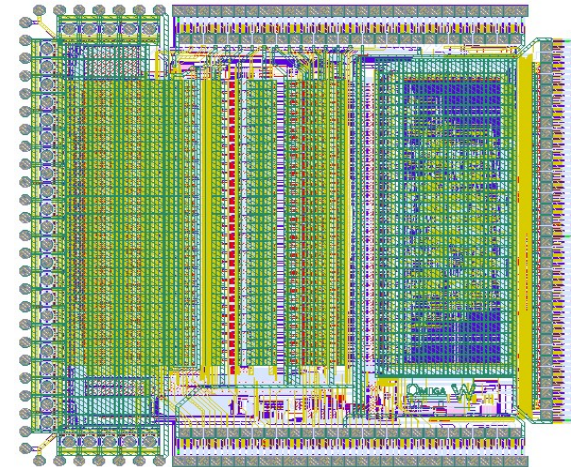

PETIROC2A: performance

