

Status of Digital Pixel

Tianya Wu

CEPC MOST2 Chips Meeting

twu@ifae.es

04-03-2019



華中師範大學
CENTRAL CHINA NORMAL UNIVERSITY

- ALPIDE logic block
- FE_I3 logic block
- Outlook




ALPIDE Digital Cell



2 Configuration bits:

- Pixel pulsing
- Pixel masking

It will cost around 60 transistors.

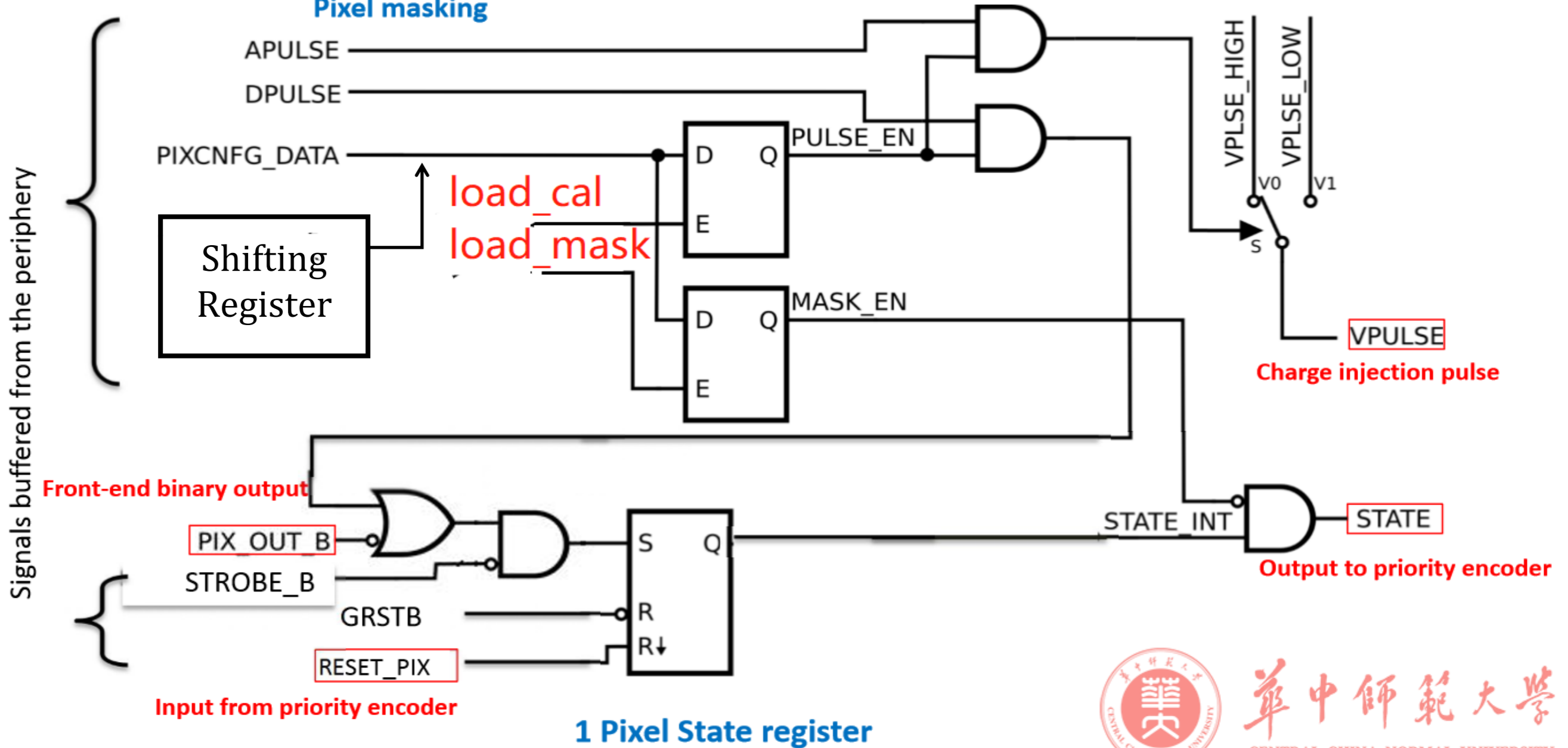


Optional Digital Cell

 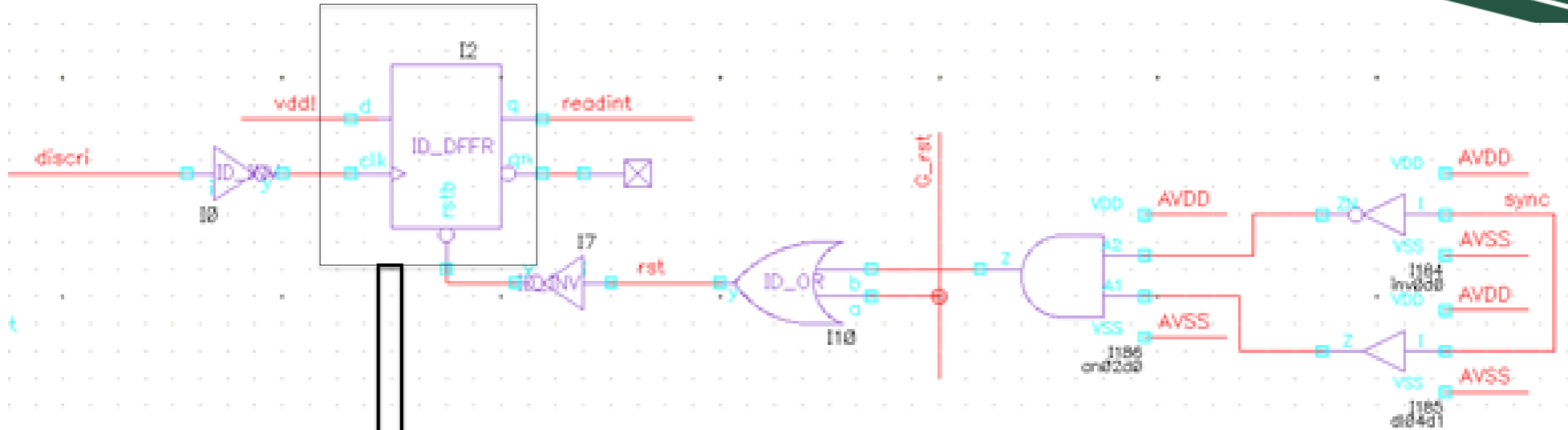

It will cost around 96 transistors.
Including Masking and Analog
Calibration circuits.
This is not the best choice.



FE-I3 Digital Cell

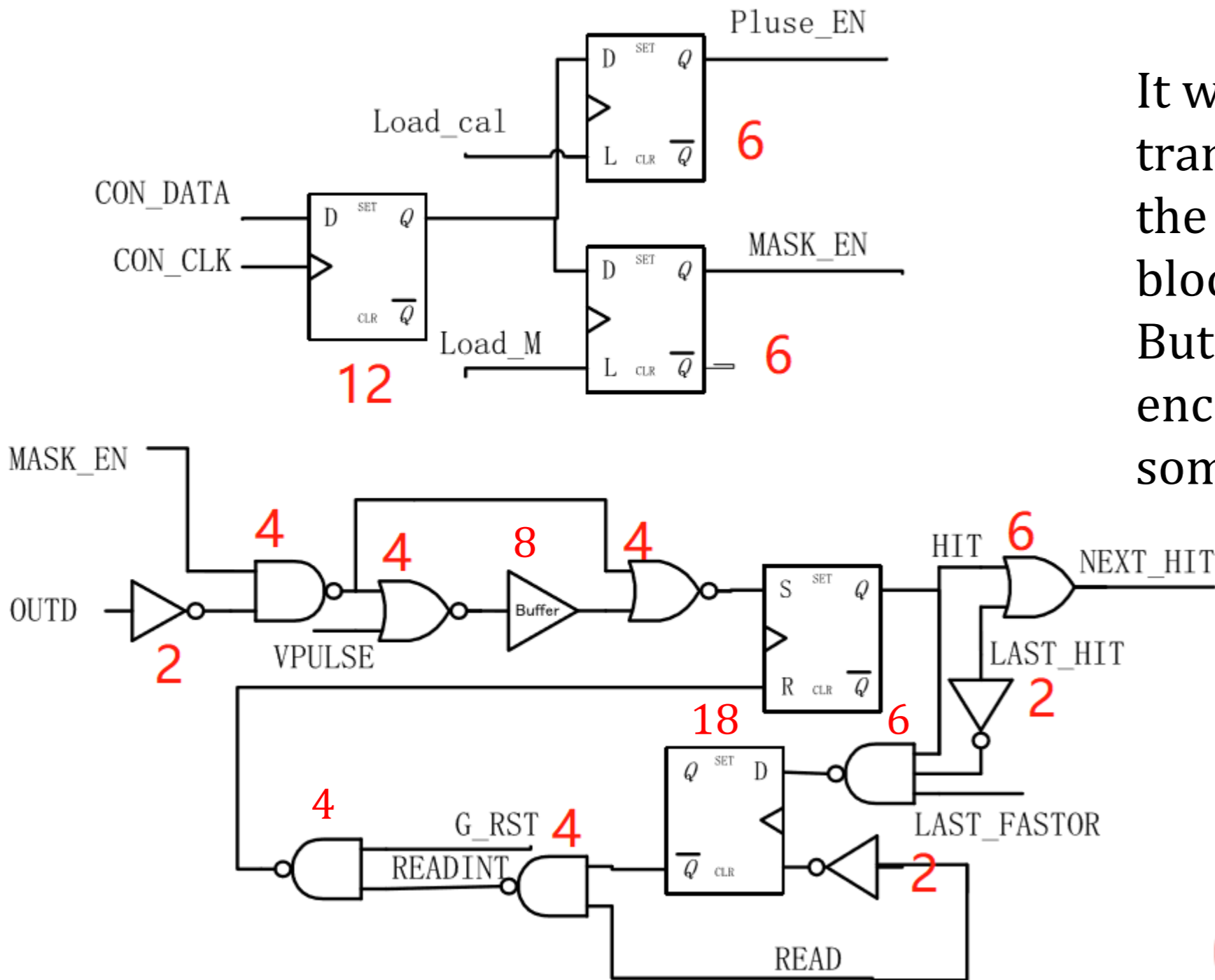

It will cost around 104 transistors, including the Analog calibration block.
But the address encoder part will save some area than ALPIDE



Conclusion:

- From my simulation result, the ALPIDE structure will need a trigger latency signal (Strobe) more to reduce the effect of analogue pulse duration.
- Both of them are working fine with the external configuration bits.

Next tasks to do:

- Do the standard cell layout.
- Simulate the full column and submit it.



Thanks for your attention.

