

# Design of on-chip LDO for CMOS pixel sensor

Jia Wang

School of computer science  
Northwestern Polytechnical University  
2019.4.30



# Outline

- Design requirement
- Circuit design
  - Bandgap
  - LDO
- Summary



# Design requirement


Parameters	Value
Input voltage	<2 V
Output voltage	1.8 V
Maximum output current	200 mA
Load capacitance	~200 nF
TID	> 1 Mrad.
Maximum dropout voltage	0.2 V
Fully integrated on-chip	
Low noise, High PSR	



# Circuit design


- Two blocks
  - Bandgap
    - supplying reference voltage

– LDO

 




# Schematic of Bandgap

 




# Simulation Results

 

$V_{bg}=0.976 \text{ V @ } V_{dd} \geq 1.8 \text{ V}$




# VBG VS Temperature

 




# Start-up

 




# LDO

 




 $V_{out}$  VS  $I_{load}$  @  $V_{in} = 2 V$





 $V_{in}$  VS  $V_{out}$  @  $I_{load}=0.2A$





## Summary and next work

- Bandgap circuit design has been finished.
- LDO circuit design is under going.
- Layout will be finished in 7 days.
- IO PAD?
- 1.8 V or 3.3 V MOS?